


EE 420 / EEL 620

Lecture 23


Analog IC Design

April 19, 2017

$$i = qNv_i^2$$

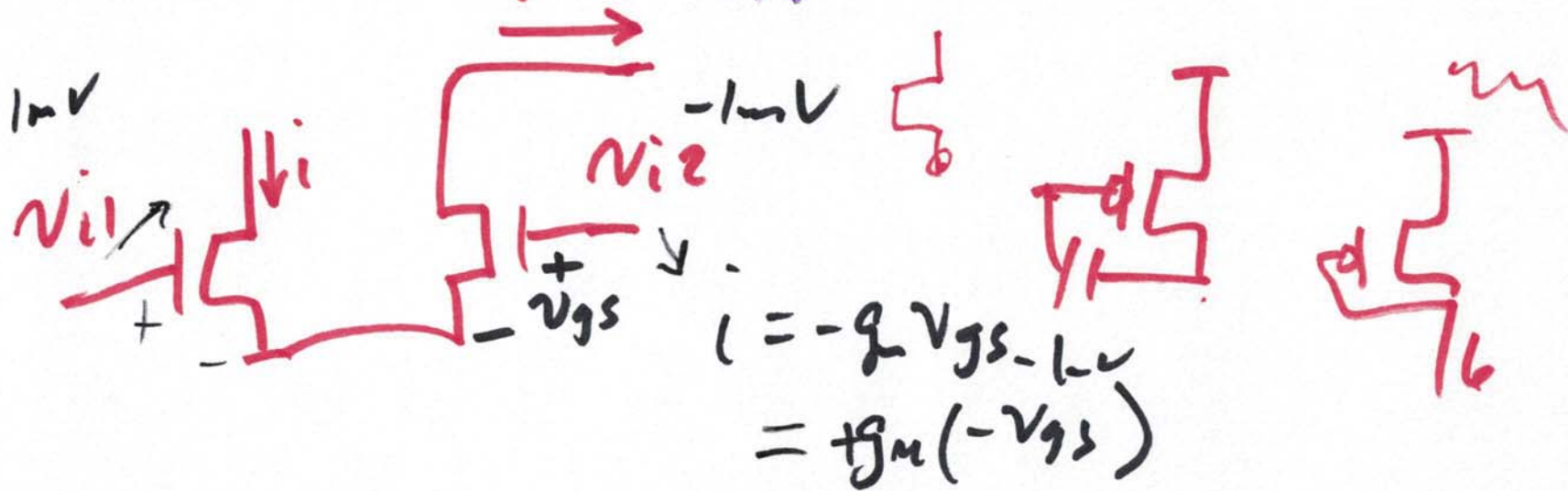

11

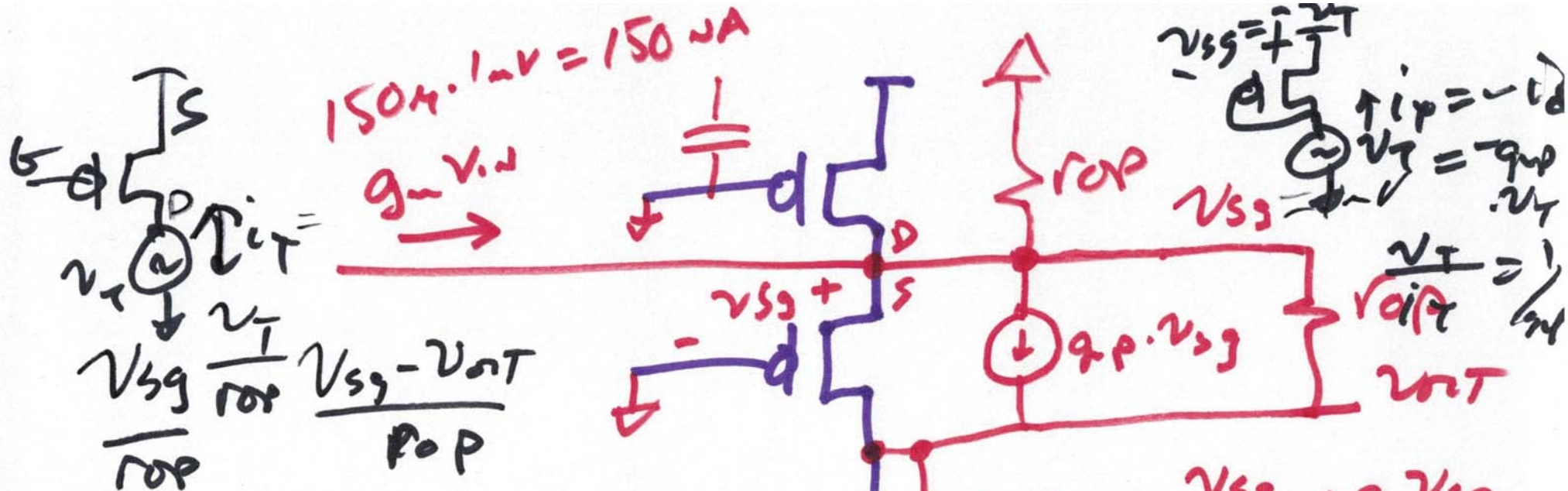

$$\frac{v_{sg}}{r_{op}} = \frac{v_{sg} - V_T}{r_{op}}$$

$$g_m v_{in} = \frac{v_{sg}}{1/g_{mp}}$$

If  $1/g_{mp} \ll r_{op}$  then  $g_p r_{op} \gg 1$

$$v_{sg} = \frac{g_m v_{in}}{g_p}$$


$$g_p v_{sg} + \frac{v_{sg} - V_T}{r_{op}} = 0$$

$$\frac{v_{sg}}{r_{op}} = g_p v_{sg} + \frac{v_{sg} - V_T}{r_{op}}$$



$$\frac{v_T}{i_T} = \frac{1}{g_p}$$


UNLV ELECTRICAL & COMPUTER ENGINEERING

CMOSedu.com

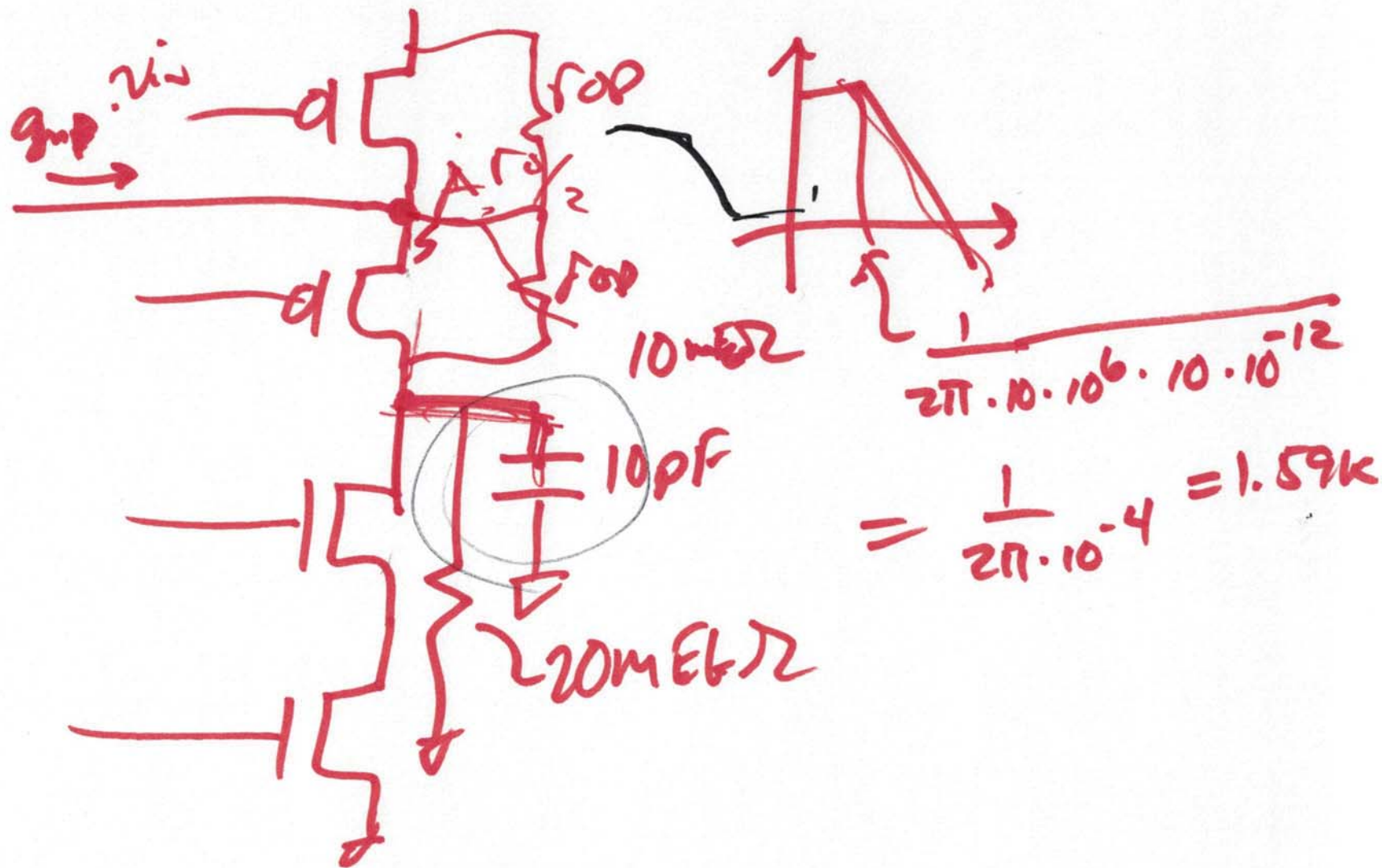

5)

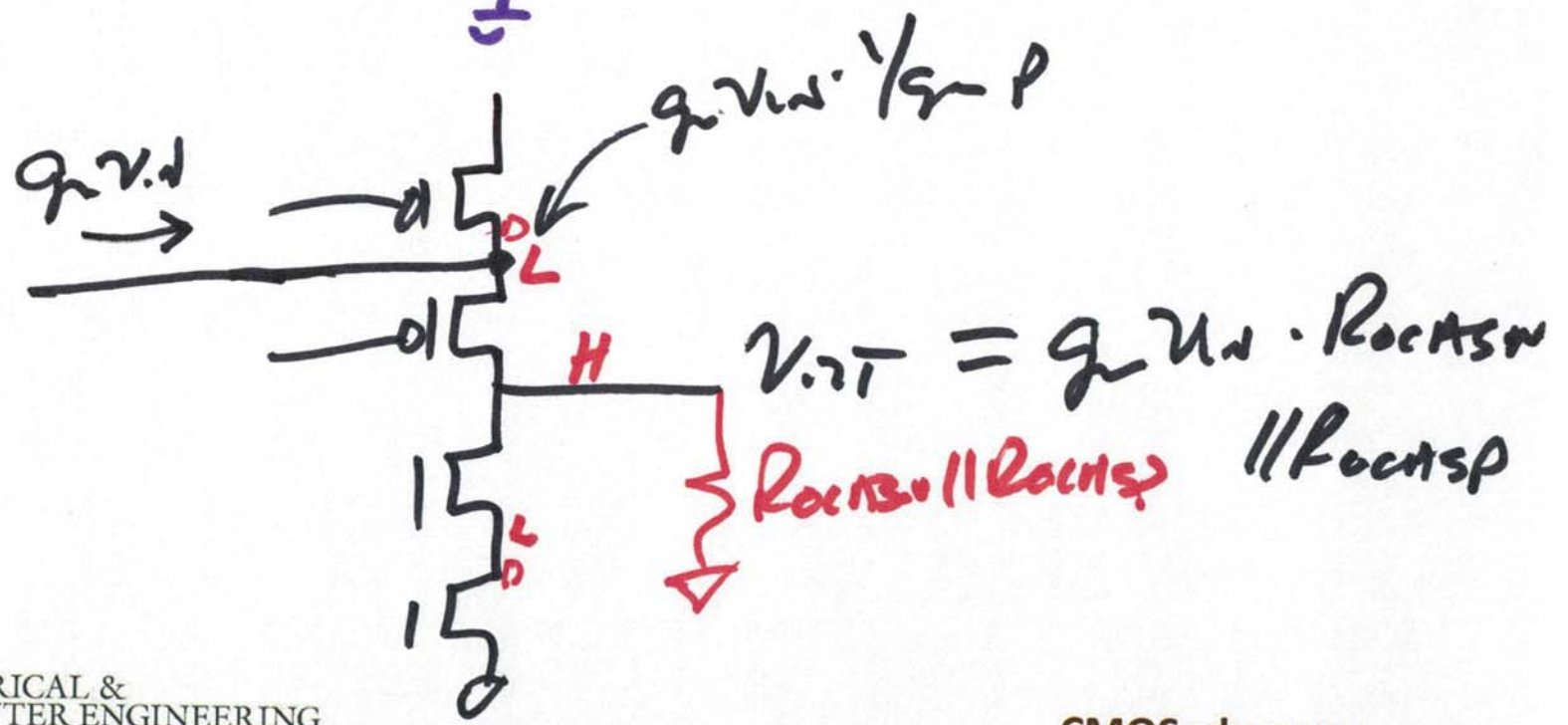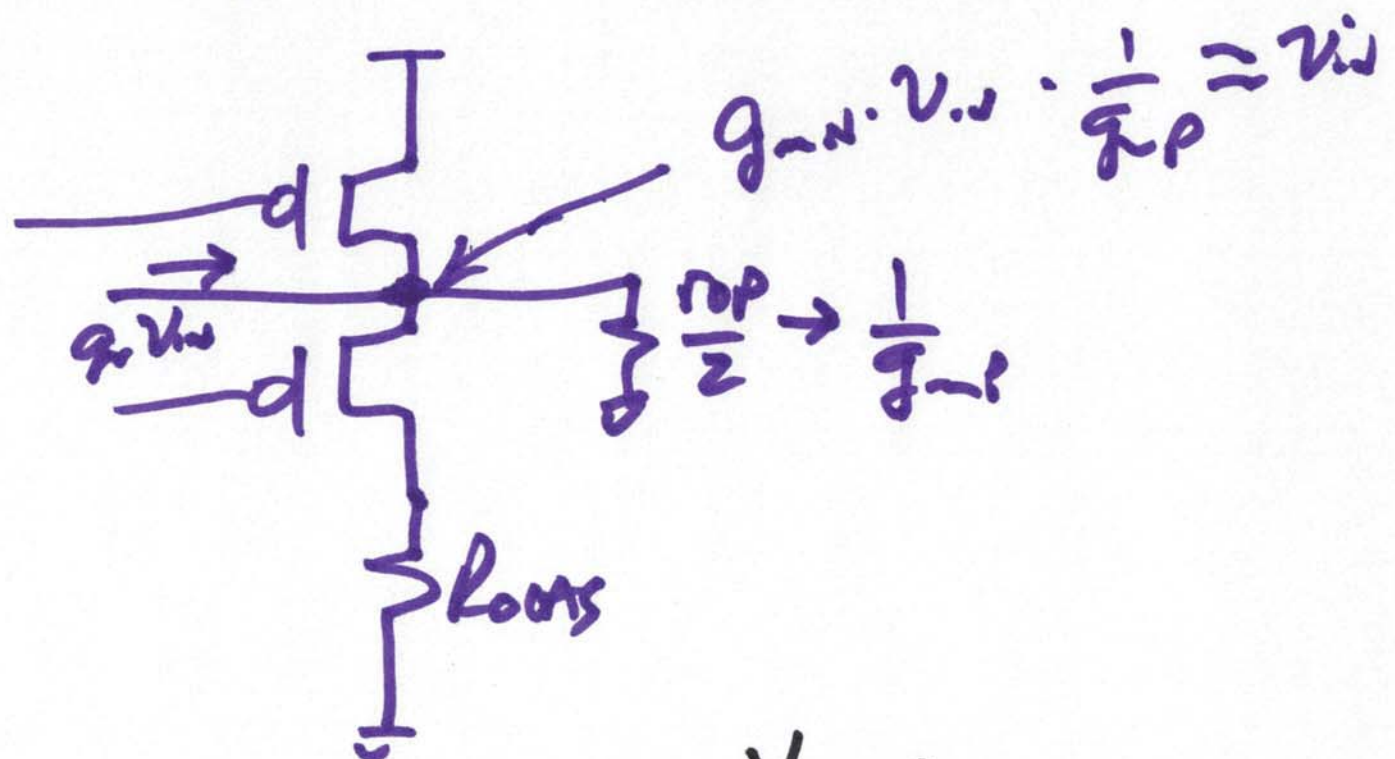


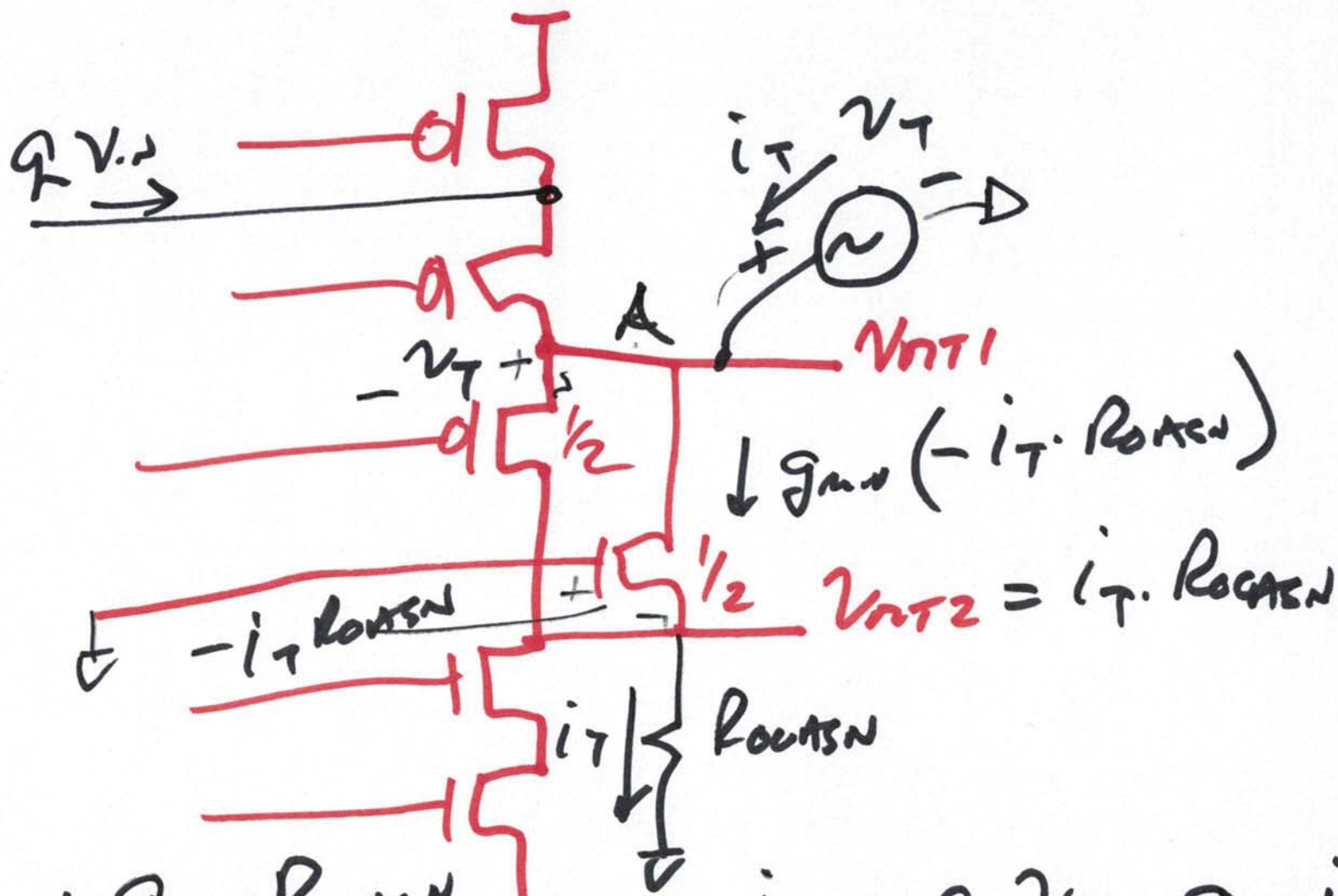

$$\frac{v_T}{i_T} = \frac{1 + g_{mD} \cdot R_{OCSN}}{g_{mD}} \approx R_{OCSN} \quad i_T = g_{mD} v_T - g_{mN} i_T R_{OCSN}$$

$$i_T (1 + g_{mD} \cdot R_{OCSN}) = g_{mD} \cdot v_T$$

5)

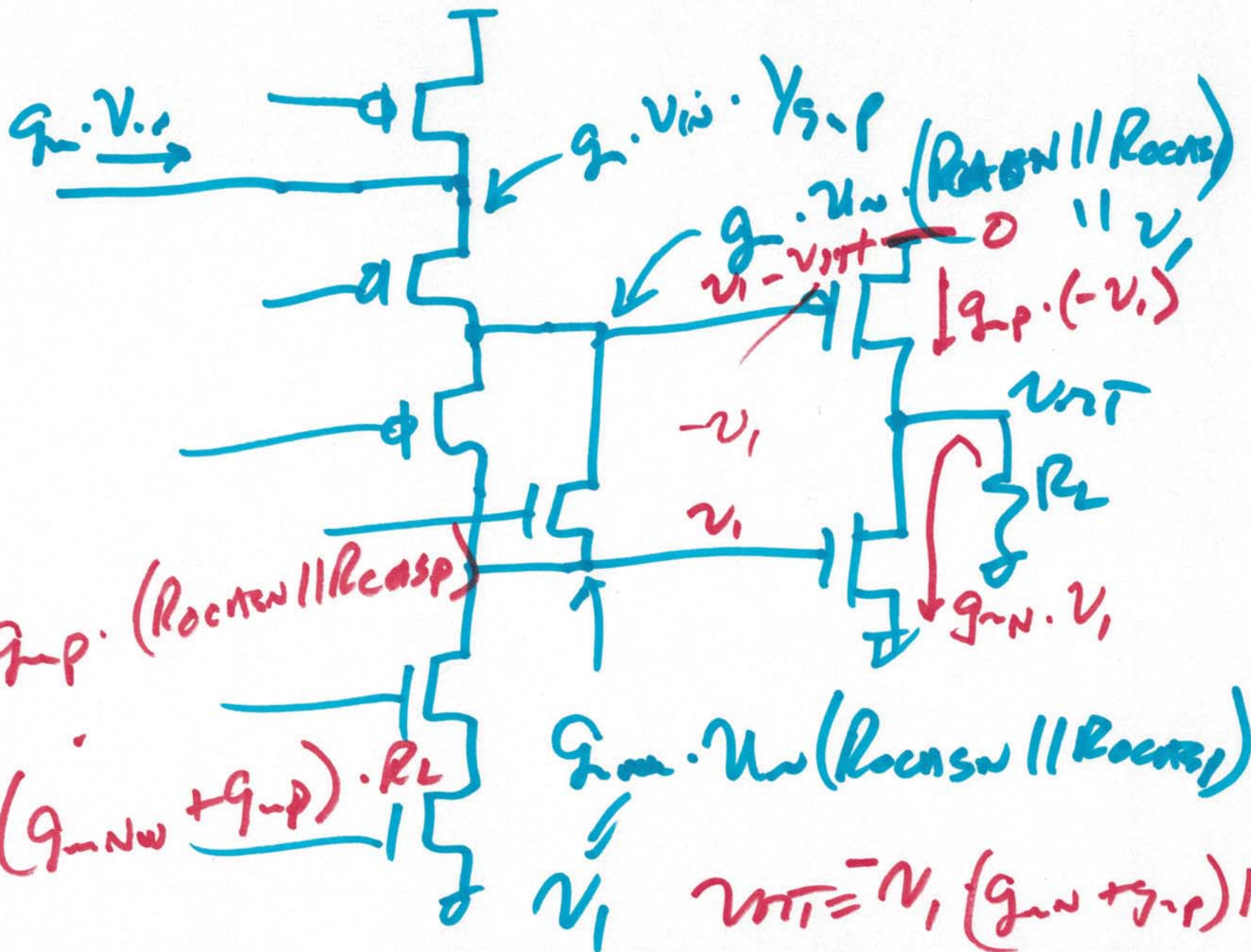

$$\frac{v_{out}}{v_{id}} = g_{mP} \cdot (R_{outN} \parallel R_{outP})$$


$$(g_{mN} + g_{mP}) \cdot R_L$$

$$g_{mN} \cdot v_{id} \cdot (R_{outN} \parallel R_{outP})$$

$$v_{out} = v_{id} \cdot (g_{mN} + g_{mP}) \cdot R_L$$

$$\frac{v_{out}}{v_{id}} = (g_{mN} + g_{mP}) \cdot R_L$$

b)

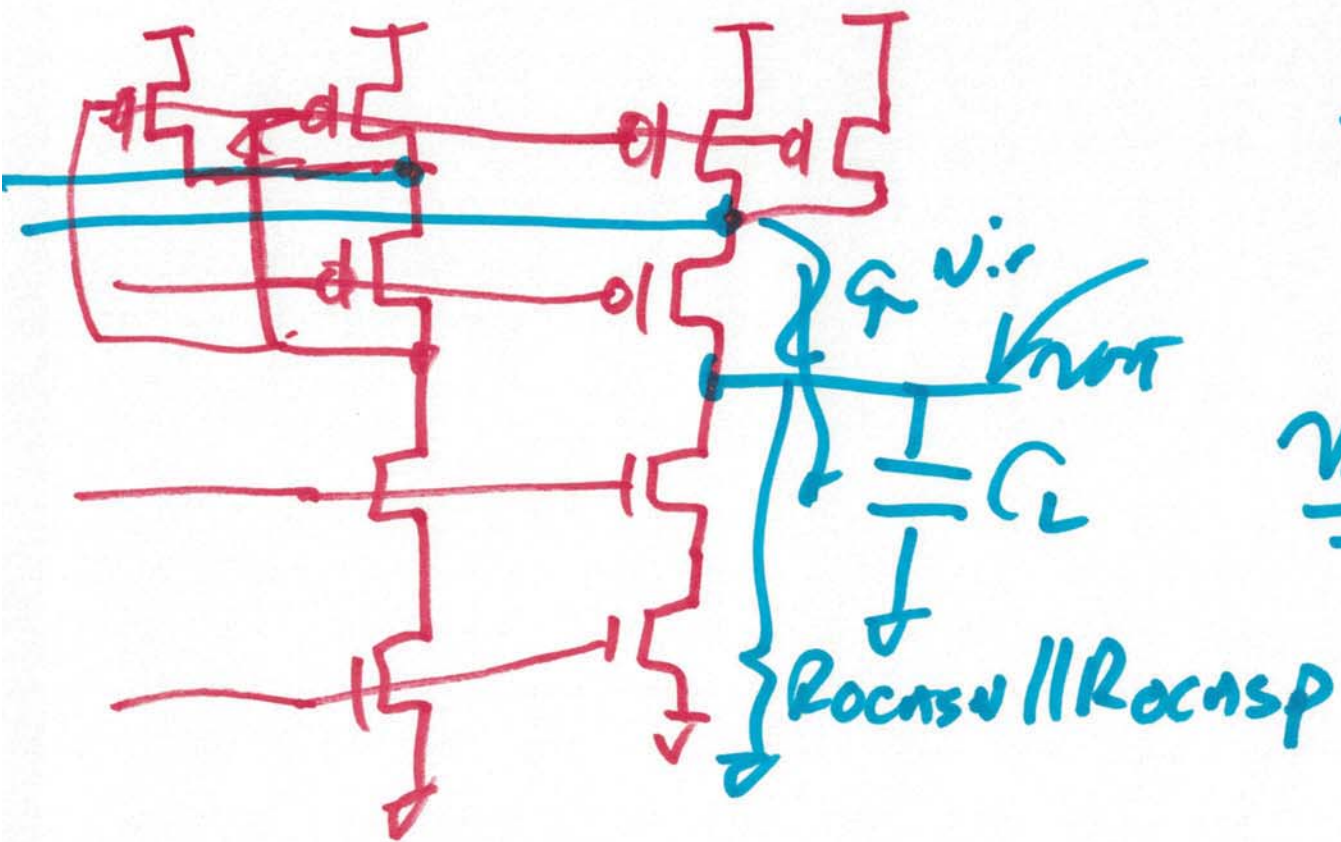


$$f_{3dB} = \frac{1}{2\pi C_L \cdot R_{outN} || R_{outP}}$$

$$\frac{V_{VT}}{v_i} = g_{mN} \cdot R_{outN} || R_{outP}$$

folded  
cascode

11


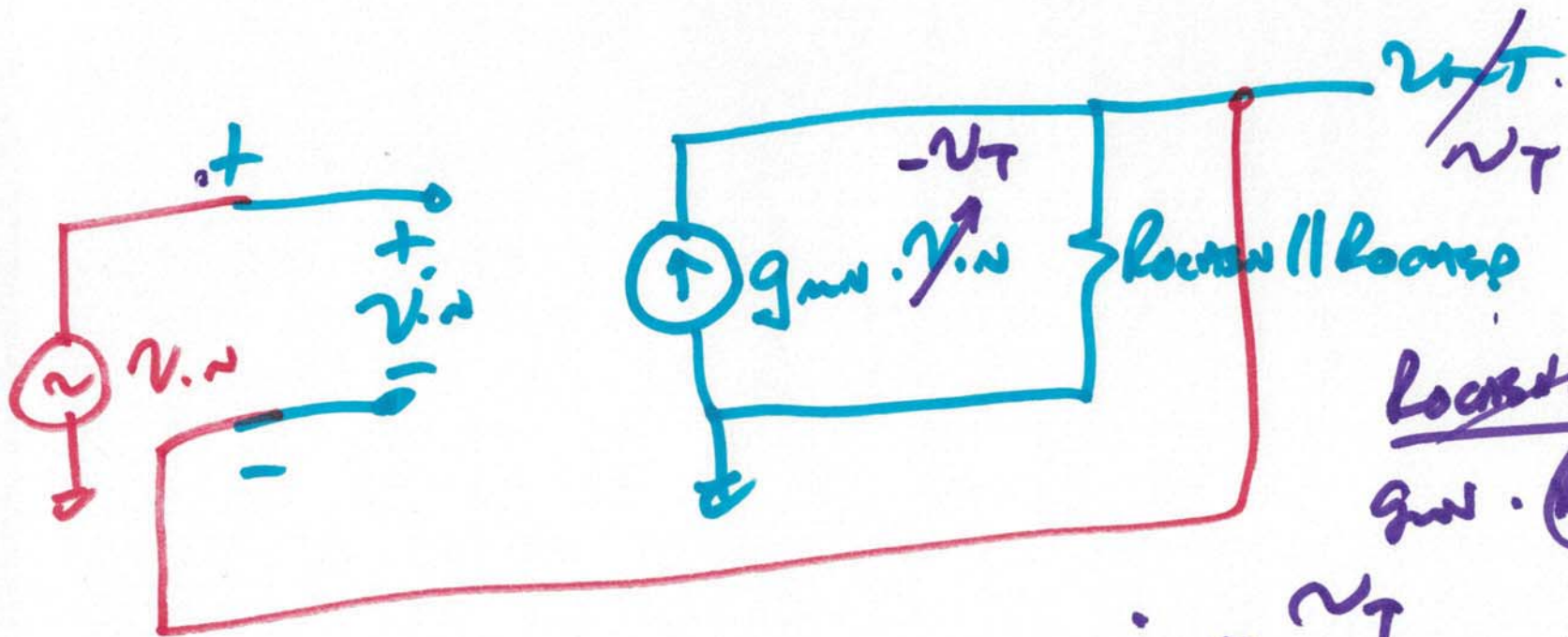


$$\frac{R_{out} || R_{load}}{g_m \cdot (R_{out} || R_{load})}$$

$$i_T = \frac{v_T}{R_{out} || R_{load}} + g_m \cdot v_T$$

$$i_T = v_T \cdot \left( \frac{g_m \cdot R_{out} || R_{load}}{R_{out} || R_{load}} \right)$$

$g_m$

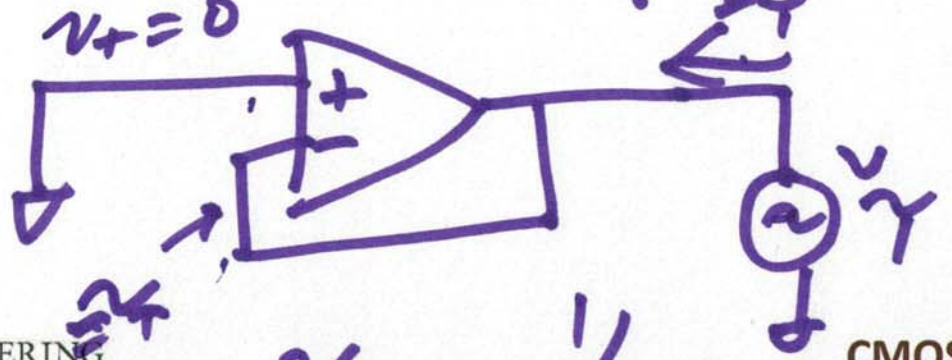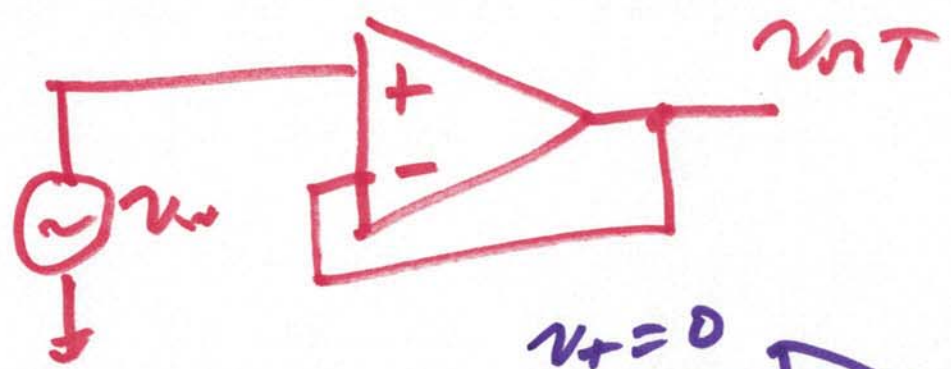

$$\frac{v_T}{i_T} = \frac{1}{g_m}$$

8)