

EE 4220

Analog Circuits I

Lecture 5

$$q = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH})$$

$$q = \sqrt{2 I_D K_P \cdot \frac{W}{L}}$$

$$I_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{TH})^2$$


$$V_{GS} > V_{TH}$$

$$V_{GS} \geq V_{GS} - V_{TH}$$

$$V_{GS} = \sqrt{\frac{2 I_D}{K_P \cdot \frac{W}{L}}} + V_{TH}$$

$$V_{GS} = 2.5 - V_{S1,2}$$

Ex. 9.5

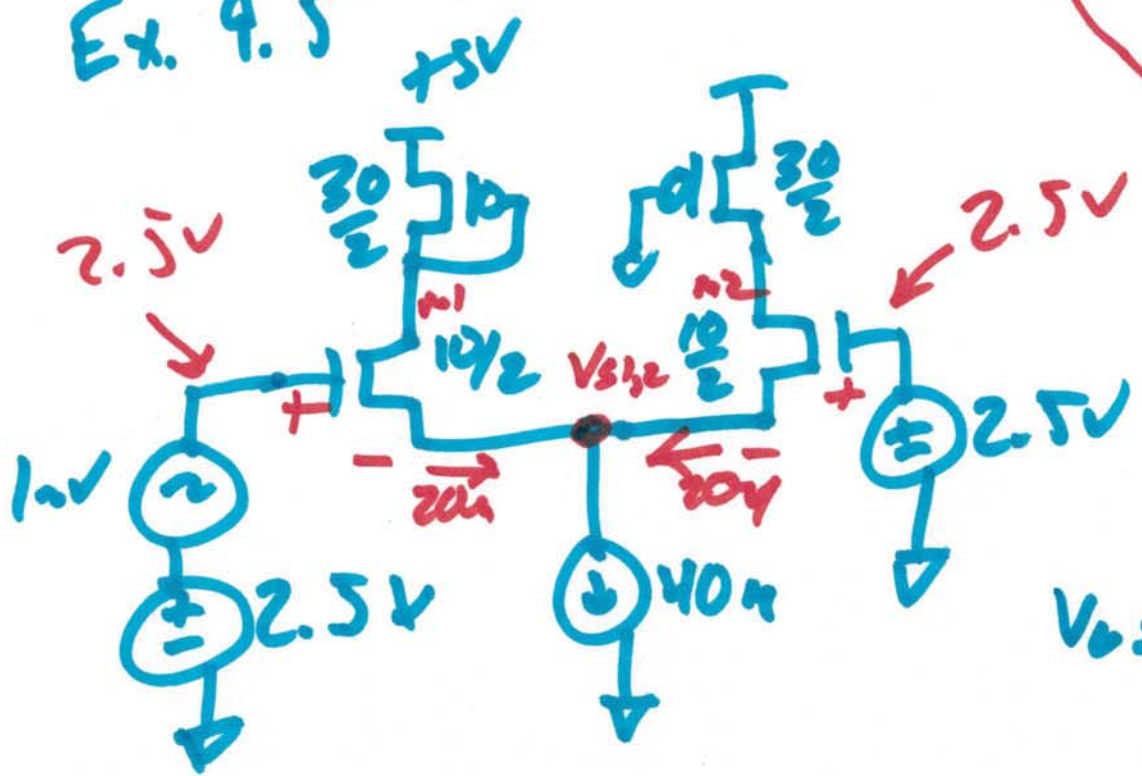

)

$$2.5 - V_{s1,2} = \sqrt{\frac{20\mu\text{A} \cdot 2^1}{120\mu\text{A} \cdot 5}} + .8$$


//
1.05

$$V_{s1,5} = \underline{\underline{1.45\text{V}}} = \sqrt{\frac{40}{600}} + .8$$

$$= \sqrt{\frac{1}{15}} + .8$$

$$= \frac{1}{\sqrt{15}} + .8 = \underline{\underline{1.05 = V_{cs}}}$$

AC CKT

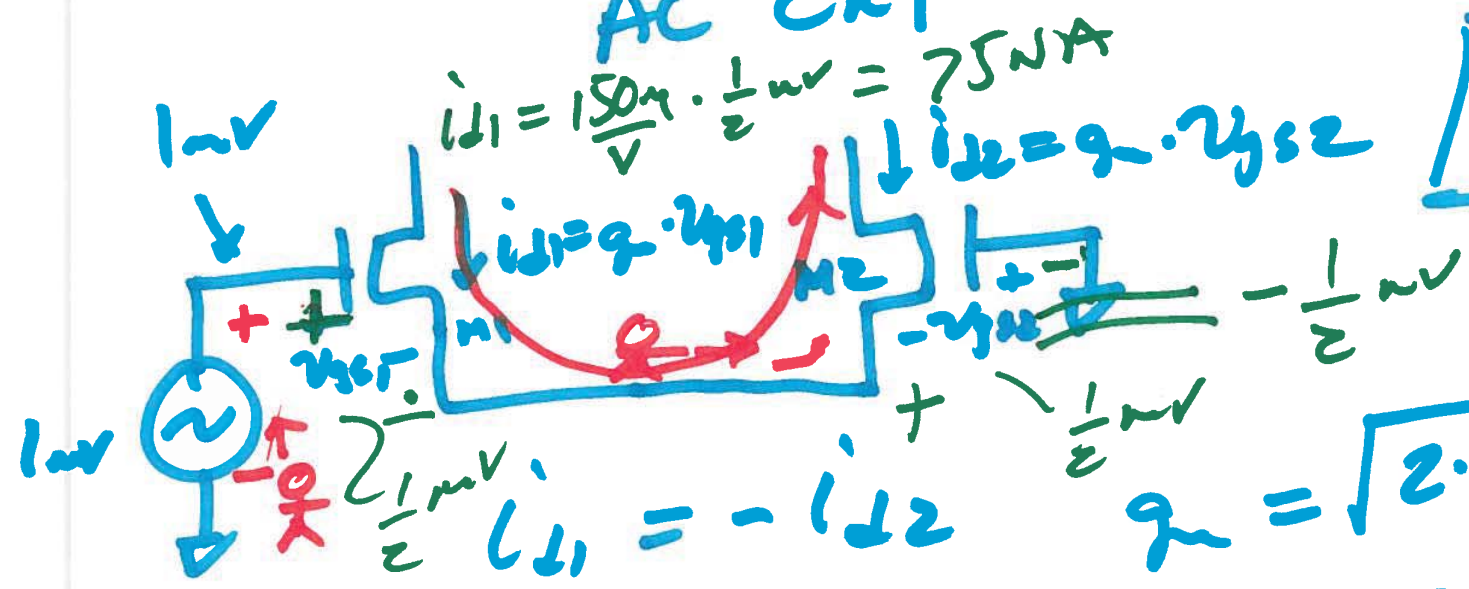

$$i_d = g_m v_{gs}$$

$$v_{gs1} = -v_{gs2}$$

$$1 \mu V - v_{gs1} + v_{gs2} = 0$$

$$1 \mu V - 2v_{gs1} = 0$$

$$v_{gs1} = \frac{1}{2} \mu V$$

3)




$$V_{GS} = \sqrt{\frac{2 I_D}{K_P \cdot \frac{W}{L}}} + 0.9$$



.25

$$V_{GS} = 1.13V$$

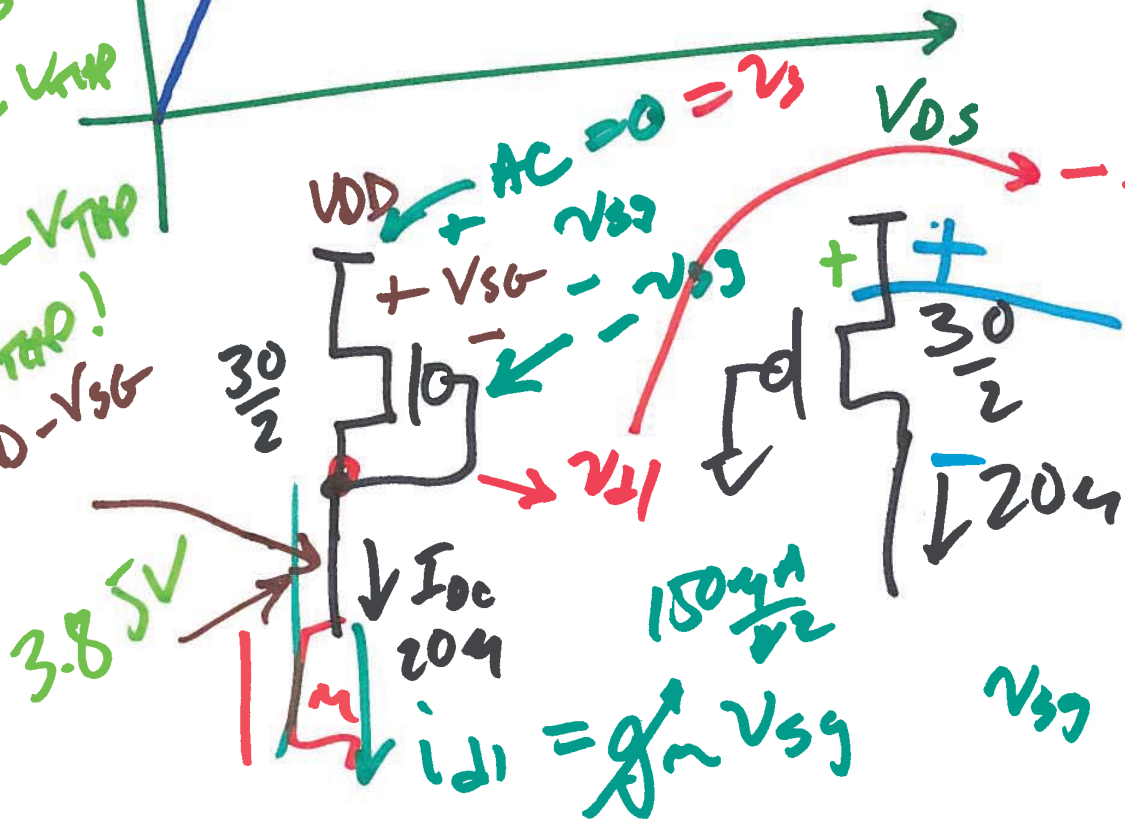$V_{GS} > V_{THP}$
 $V_{SD} \geq V_{GS} - V_{THP}$
 $\frac{V_{SD}}{2} \geq \frac{V_{GS}}{2} - \frac{V_{THP}}{2}$
 $V_{SD} - V_{GS}$



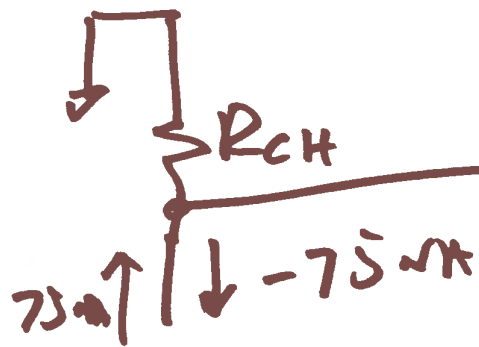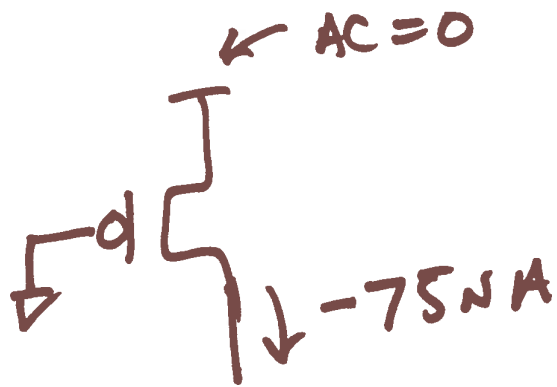$V_{SD} = 5V$
 $V_{SD} \geq V_{GS} - V_{THP}$
 $\geq 5 - .9$
 $\frac{75\mu}{150\mu} = 4.1$
 $V_{SG} = \frac{1}{2} mV$



$$V_{d24} = 75 \text{ nA} \cdot 407 \Omega$$

$$= \underline{\underline{30.5 \text{ mV}}}$$


$$V_{d24} = 75 \text{ nA} \cdot R_{CH}$$

$$R_{CH} = \frac{1}{k_p \cdot \frac{W}{L} (V_{SG} - V_{TP})}$$

$$= \frac{1}{40 \mu\text{A/V} \cdot \frac{30}{2} (\cancel{1.5} - .9)}$$

$$= 407 \Omega$$

5)

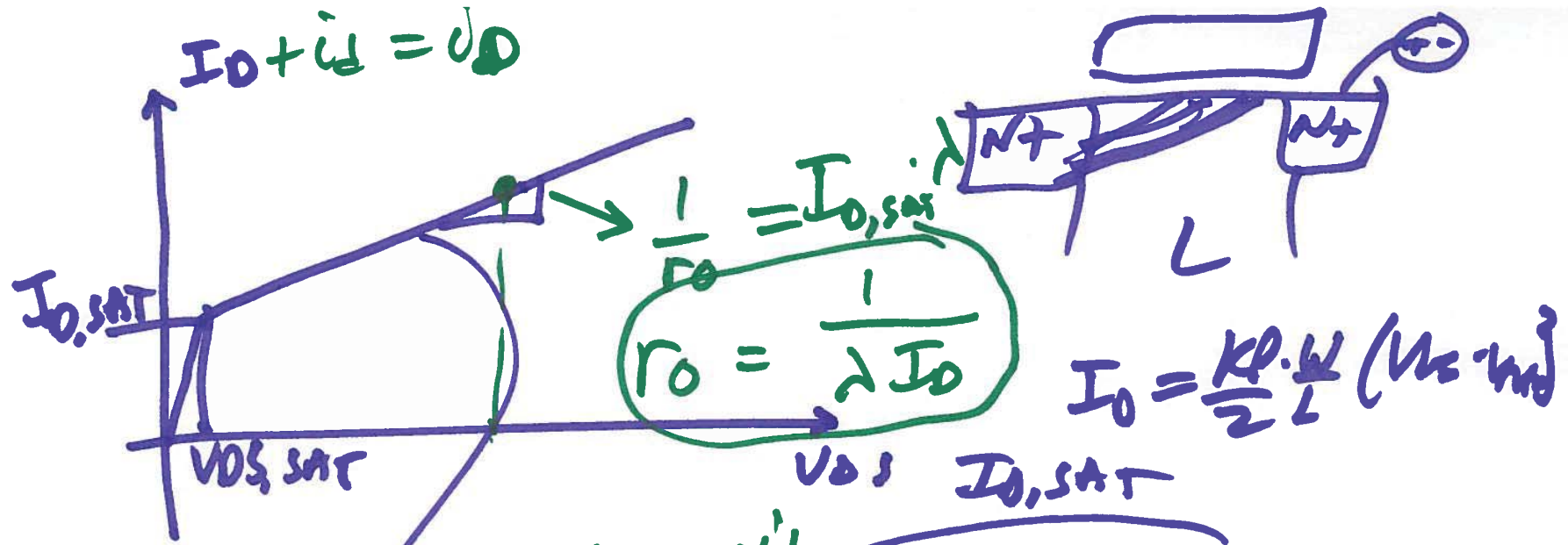

$i_d = I_D + i_d$

$I_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{th})^2$

$(1 + (V_{GS} - V_{GS,sat}) \lambda)$

$V_{GS} > V_{GS,sat}$ $V_{GS,sat} = V_{GS} - V_{th}$

$\frac{\delta i_d}{\delta V_{GS}} \Big|_{\substack{I_D = \text{const} \\ V_{GS} = \text{const}}} = I_{D,sat} \cdot \lambda \cdot \frac{\delta V_{GS}}{\delta V_{GS}}$

