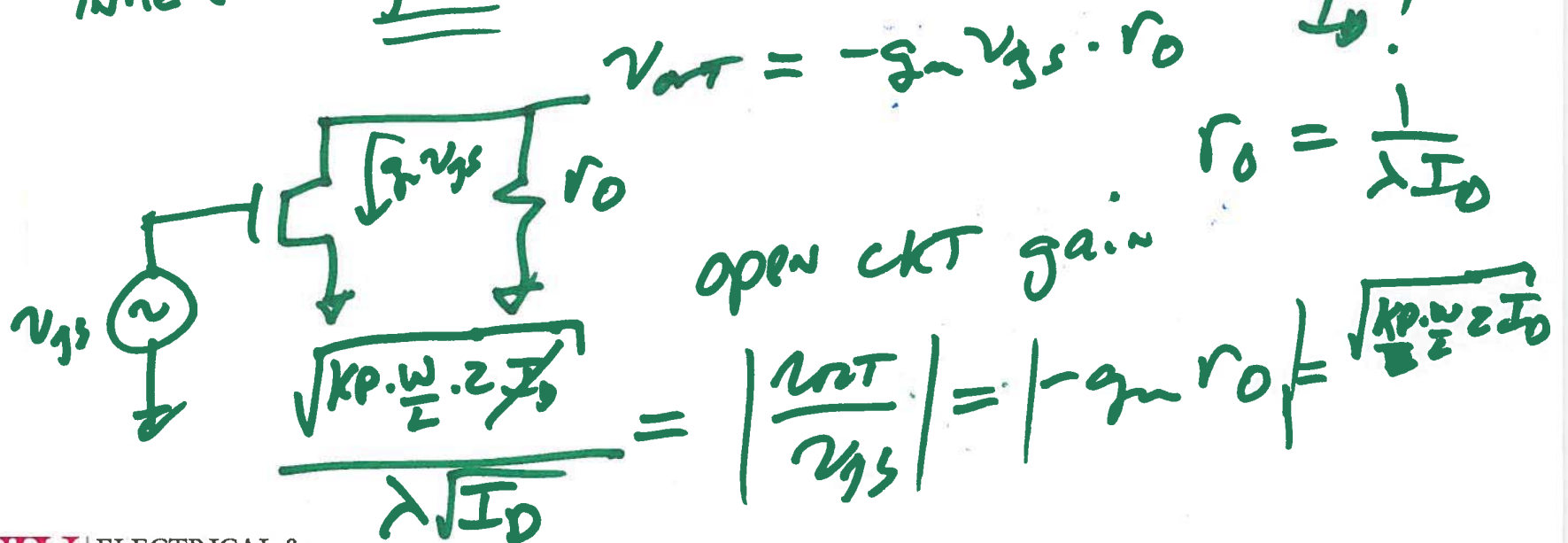


Lecture 6

EE 420 / ECG 620

Analog IC Design

How do we select W/L & V_{GS} where $\underbrace{\text{gain}}$ of transistor and thus I_D !




Open book and closed notes.

Show your work for credit.

For the following assume: $V_{THN} = 800\text{ mV}$, $V_{THP} = 900\text{ mV}$, $KP_n = 120\text{ }\mu\text{A/V}^2$, and $KP_p = 40\text{ }\mu\text{A/V}^2$.

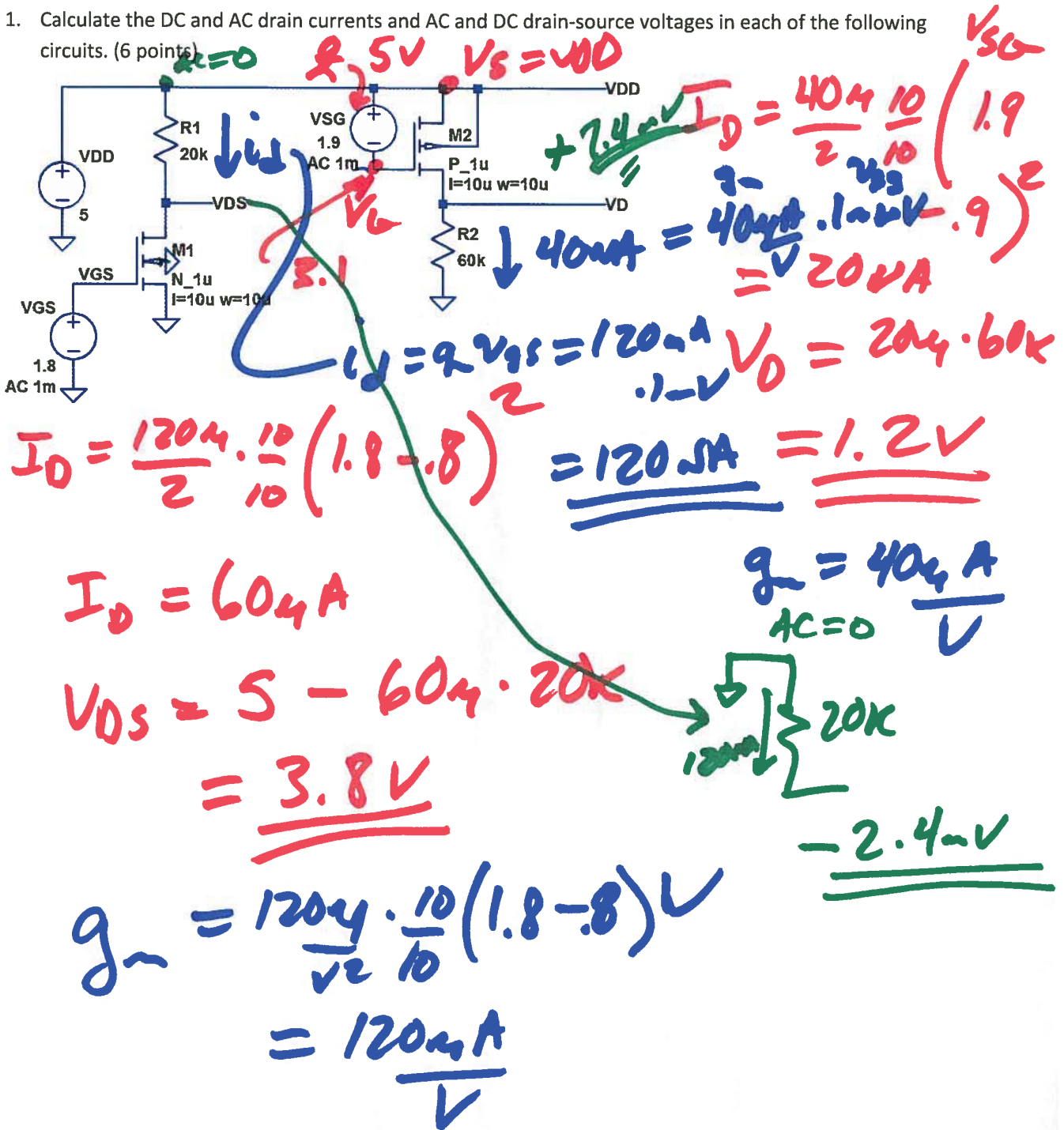1. Calculate the DC and AC drain currents and AC and DC drain-source voltages in each of the following circuits. (6 points)



2)

$$\left| \frac{v_{IT}}{v_{OV}} \right| = g_m r_o = \frac{\sqrt{k_p \frac{W}{L} \cdot 2 I_D}}{\lambda I_D} = \frac{\sqrt{k_p \frac{W}{L} \cdot 2}}{\lambda \sqrt{I_D}}$$

$$\sqrt{I_D} = \sqrt{\frac{k_p W}{2 L}} \cdot (V_{GS} - V_{THN}) \quad \lambda \propto \frac{1}{L}$$

$$C_{IH} = \frac{dv}{dt}$$

$$\left| \frac{v_{IT}}{v_{OV}} \right| = g_m r_o = \frac{2}{(V_{GS} - V_{THN}) \lambda}$$


overdrive voltage
= V_{OVN}

General design

$$V_{OVN} = 5\% \text{ of } V_{DD}$$

$$\left| \frac{v_{IT}}{v_{OV}} \right| = g_m r_o \propto \frac{2L}{V_{GS} - V_{THN}}$$

Speed

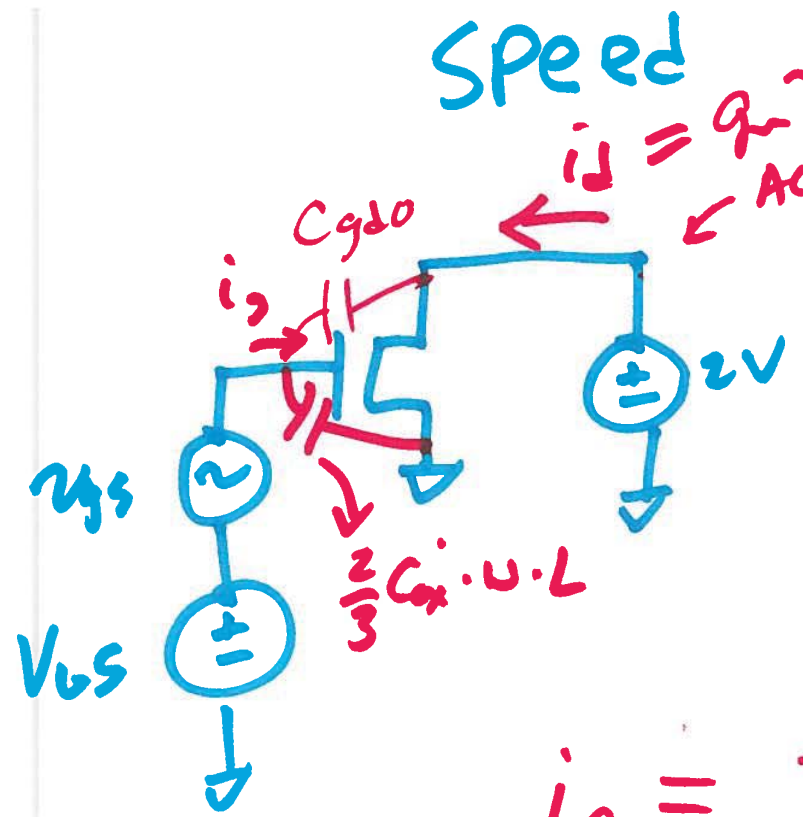


$$\frac{i_d}{i_g} = \frac{g_m}{j\omega(C_{gs} + C_{gd0})}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd0})}$$

$$= \frac{v_{gs}}{\sqrt{(j\omega C_{gs} + j\omega C_{gd0})}}$$
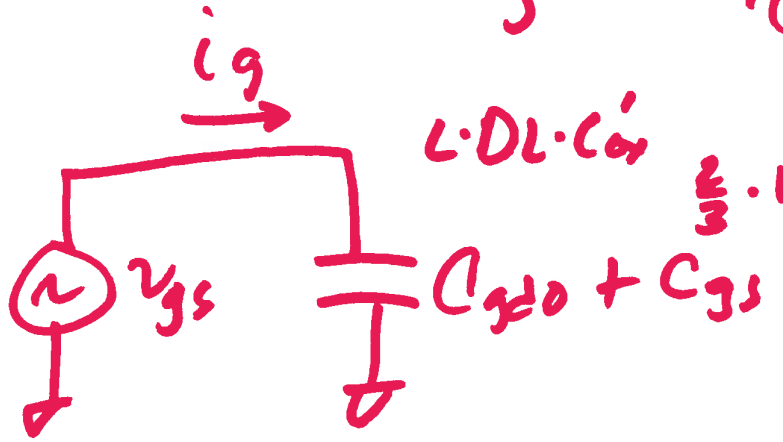
$$i_g = \frac{v_{gs}}{\sqrt{(j\omega C_{gs} + j\omega C_{gd0})}}$$



$$f_T = \frac{g_m}{2\pi (C_{gs} + C_{gdo})}$$

$$\Downarrow$$

$$C_{gs} \gg C_{gdo}$$

$$k_p \cdot \frac{W}{L} (V_{GS} - V_{THN})$$

$$\approx \frac{k_p \cdot \frac{W}{L} (V_{GS} - V_{THN})}{2\pi \cdot \frac{2}{3} W \cdot L \cdot C_{ox}'}$$

$$k_p = \mu_n C_{ox}' \cdot 4n$$

$$= \frac{k_p \cdot \frac{W}{L} \cdot 3}{C_{ox}' \cdot 2\pi \cdot 2} (V_{GS} - V_{THN})!$$

$$f_T = \frac{4n \cdot 3}{4\pi L^2} \cdot (V_{GS} - V_{THN})$$

↑ short-channel!

Figure of MERIT

$$G_{AV} \cdot f_T \text{ product} = G_{FT}$$


$$G_{FT} = \frac{2k \cdot \mu_n \cdot 3 \cdot (V_{GS} - V_{THN})}{(V_{GS} - V_{THN}) \cdot 4\pi \cdot L^2}$$

High-speed \rightarrow minimum L

general design $\rightarrow L = 2 \text{ to } 5$ times
Minimum L

Longer devices match better




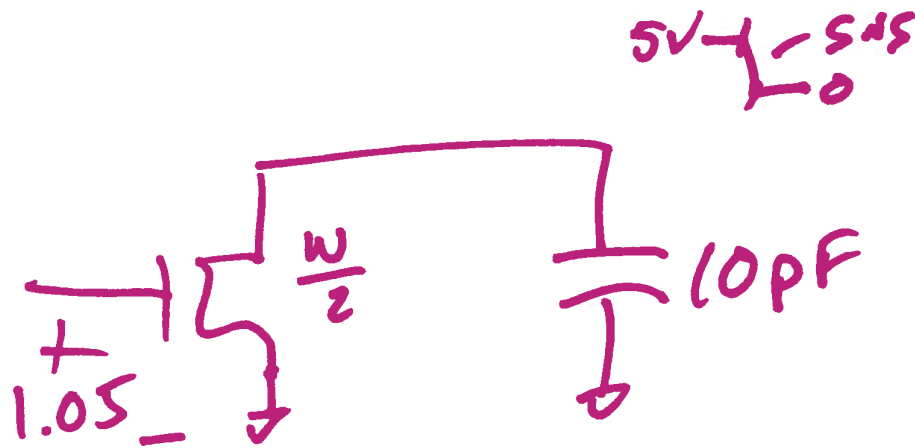


$$I = C \frac{dv}{dt}$$


$$I = 10\text{pF} \cdot \frac{5}{5\text{ns}}$$
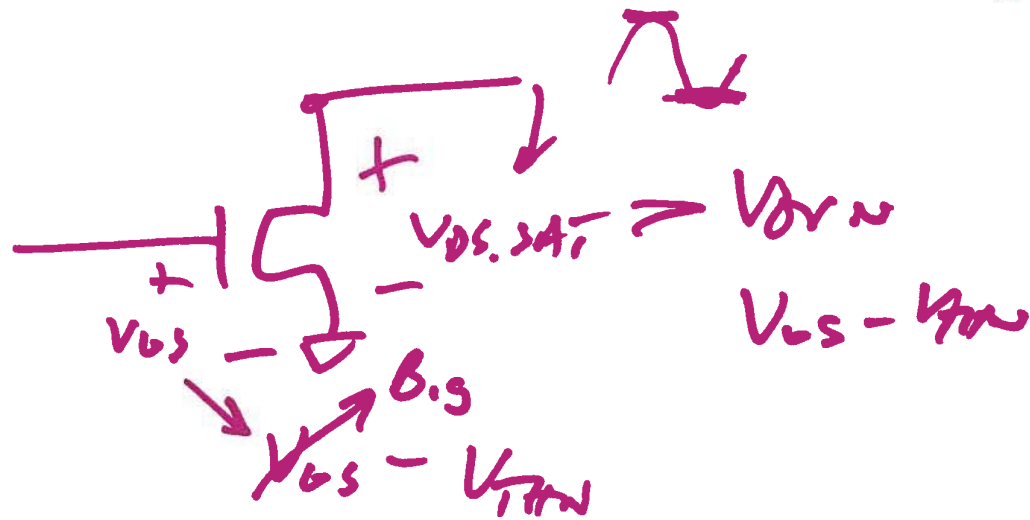
$$\underline{\underline{I = 10\text{mA}}}$$



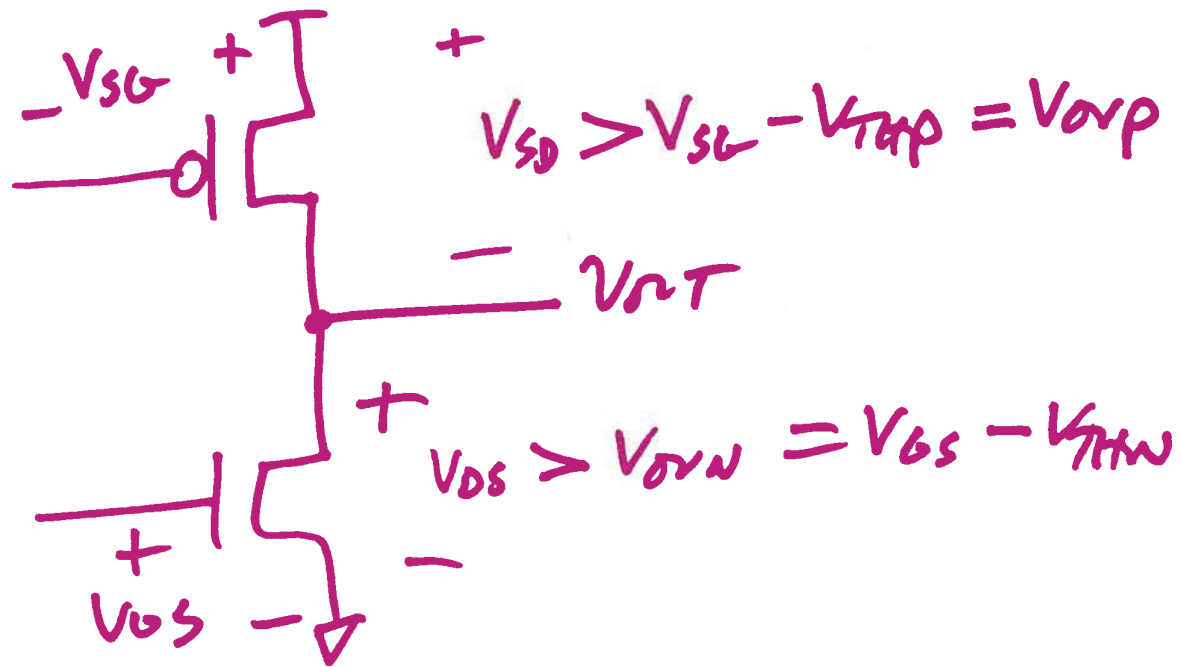
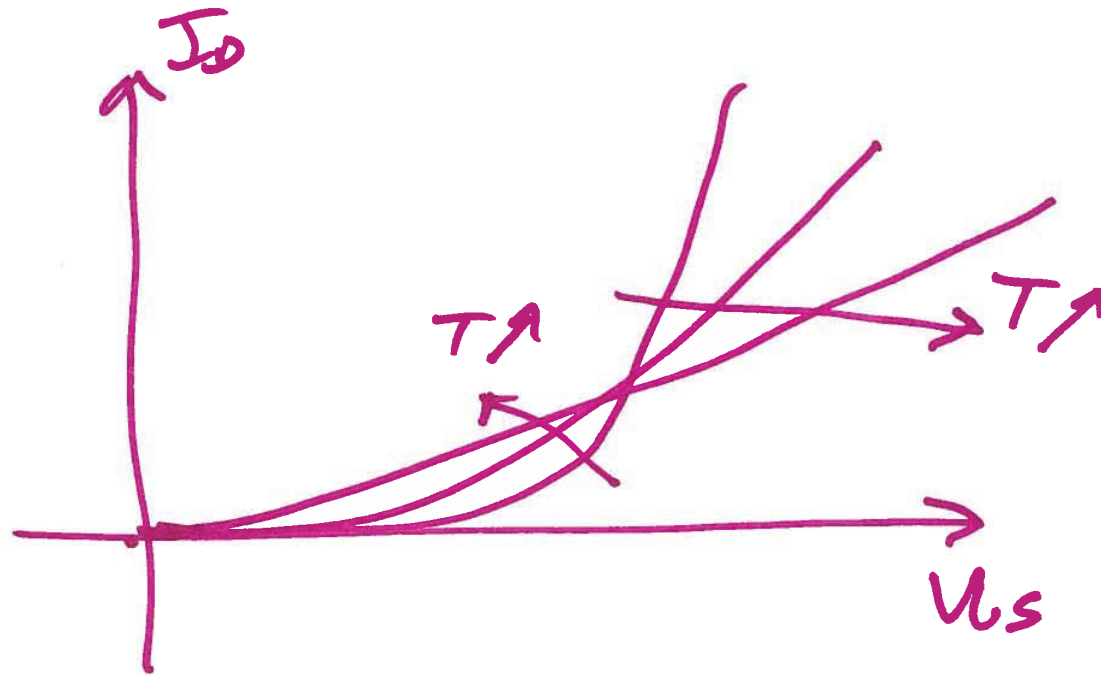
$$I_D = \frac{\mu_n \cdot C_{ox}}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2$$



9)