

EE 420 / ECG 620

Analog IC Design

Lecture 7

Feb. 8, 2017

$$g_m = k_p \cdot \frac{W}{L} (V_{GS} - V_{THN})$$

$$254 = \frac{k_p}{2} \cdot \frac{6}{1.2} (1.05 - .8)^2$$


$$k_p =$$


$$10 = k_p \cdot \left(\frac{1}{4}\right)^2$$

$$k_p = 160 \mu A/V^2$$

1)

CURRENT MIRRORS

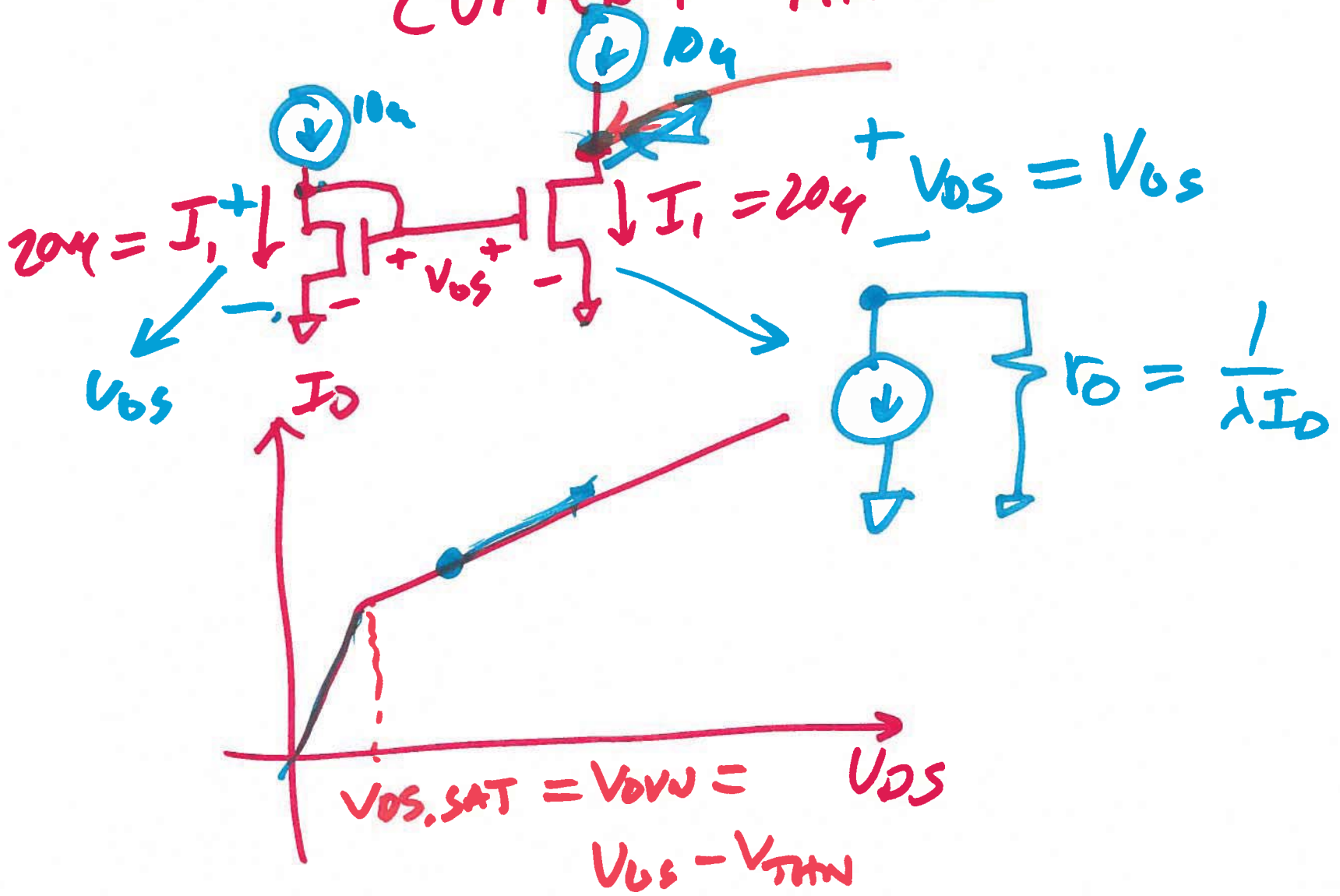

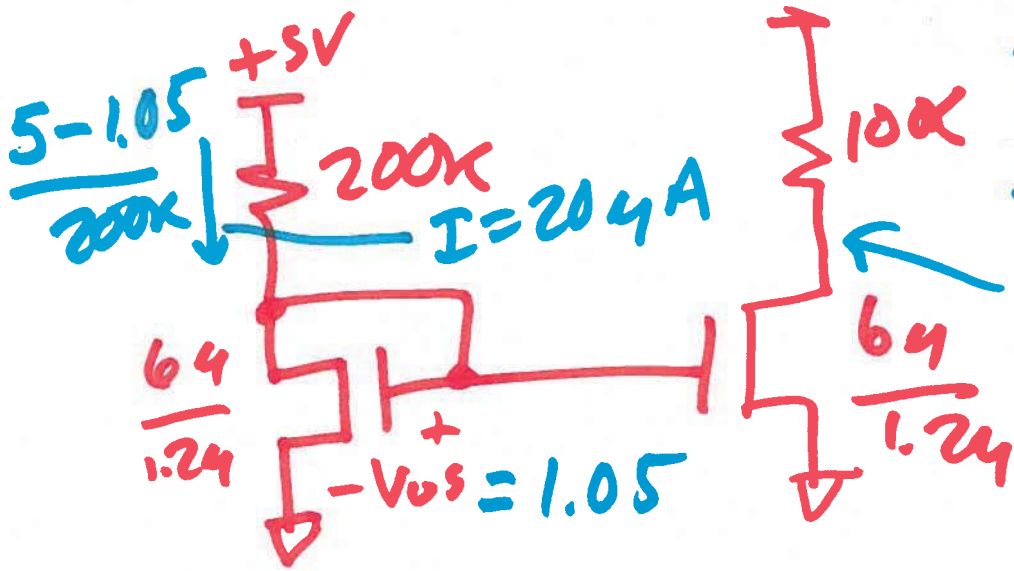

$$5 - 204A \cdot 100k = \underline{\underline{3V}}$$

$$20 \times 10^{-6} \times 10^5 = \underline{\underline{2V}}$$

$$\frac{5 - V_{bs}}{200k} = \frac{160 \mu A/V^2}{2} \cdot \frac{6}{1.2} (V_{bs} - 0.8)^2$$

$$5 - V_{bs} = 2 \times 10^5 \cdot 400 \times 10^{-6} \cdot (V_{bs} - 0.8)^2$$

$$= 80(V_{bs}^2 - 1.6V_{bs} + 0.64)$$


$$0 = 80V_{bs}^2 - 127V_{bs} + \cancel{46.2}$$

$$+ 127 \pm \sqrt{127^2 - 4 \cdot 80 \cdot \cancel{46.2}}$$

$$V_{bs} = \frac{127 \pm \sqrt{127^2 - 4 \cdot 80 \cdot 46.2}}{160}$$

$$\boxed{V_{bs} = 1.05}$$

3)

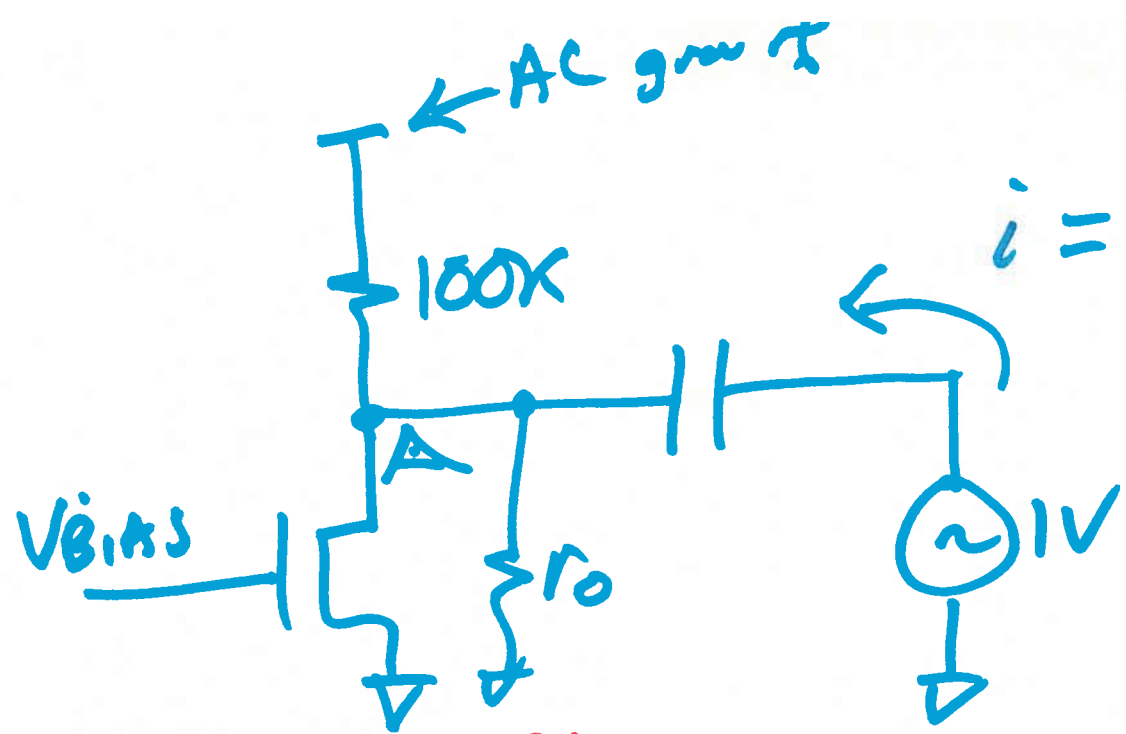

$$i = \frac{1}{100k \parallel r_o} \approx 10 \mu A$$

Assuming $r_o \gg 100k$



$$i = \frac{v_{AC}}{100k + r_o}$$