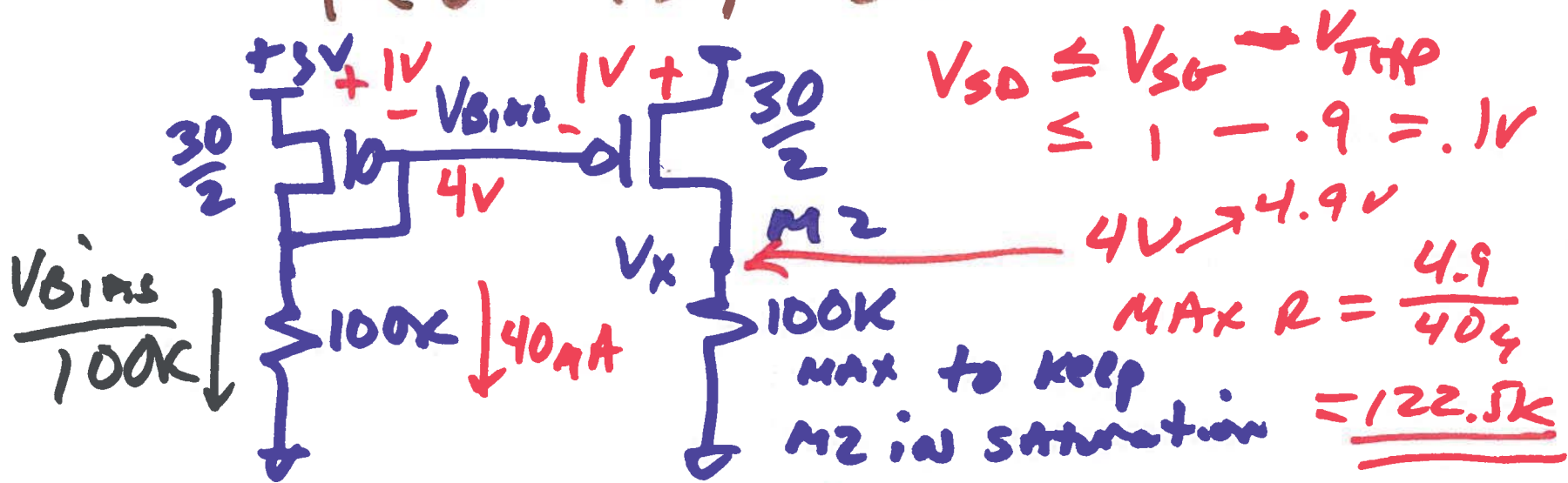


EE 420/ECG 620

# Analog IC Design

## Lecture 8

Feb. 13, 2017



$$\frac{V_{BIAS}}{100\mu} = \frac{40\mu A/\sqrt{2} \cdot 30}{2} \left(5 - V_{BIAS} - 0.9\right)^2$$

$$\frac{300\mu A}{\sqrt{2}}$$

$$4.1 - V_{BIAS}$$

$$\frac{10^5 \cdot 3 \times 10^{-4}}{30}$$

$$\begin{array}{r} 4.1 \\ \times 4.1 \\ \hline 41 \\ 164 \\ \hline 16.81 \end{array}$$

$$\frac{480}{24}$$

$$V_{BIAS} = 30 \left( 16.81 - 8.2 V_{BIAS} + V_{BIAS}^2 \right)$$


$$V_{BIAS} = 504 - 246 V_{BIAS} + 30 V_{BIAS}^2$$

$$0 = 504 - 247 V_{BIAS} + 30 V_{BIAS}^2$$

$$0 = 16.81 - 8.2 V_{BIAS} + V_{BIAS}^2$$

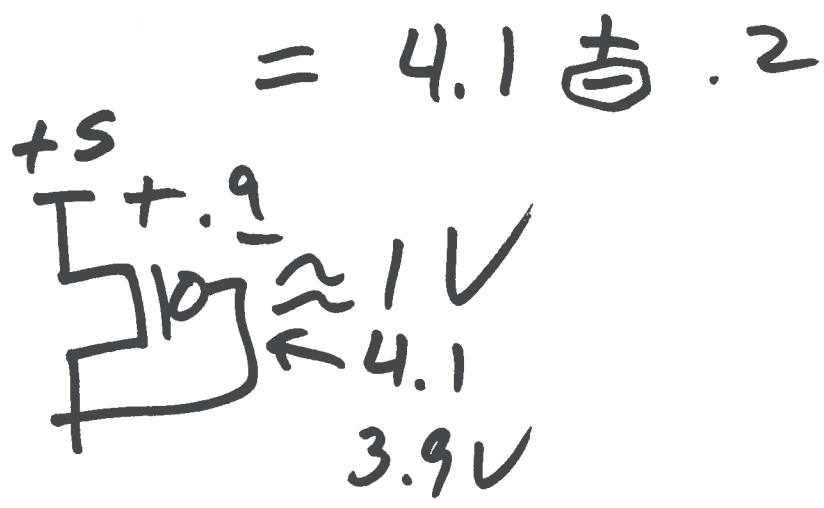2)


$$V_{BIAS} = \frac{8.2 \pm \sqrt{67.21 - 4 \cdot 16.81}}{2}$$




$$\frac{67.21 - 67.04}{.17} = .2$$

$$V_{BIAS} = 4V$$

3)

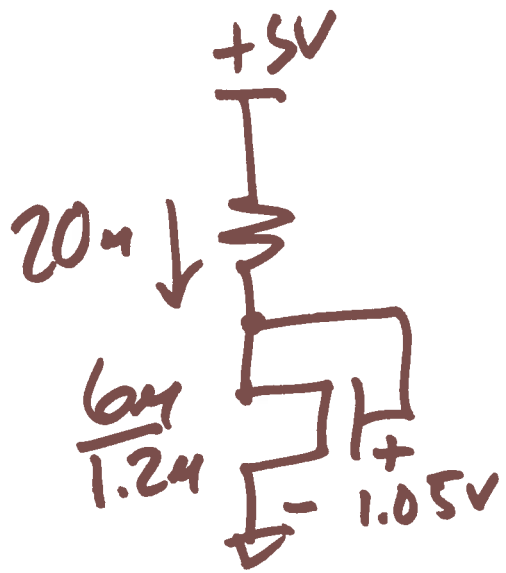
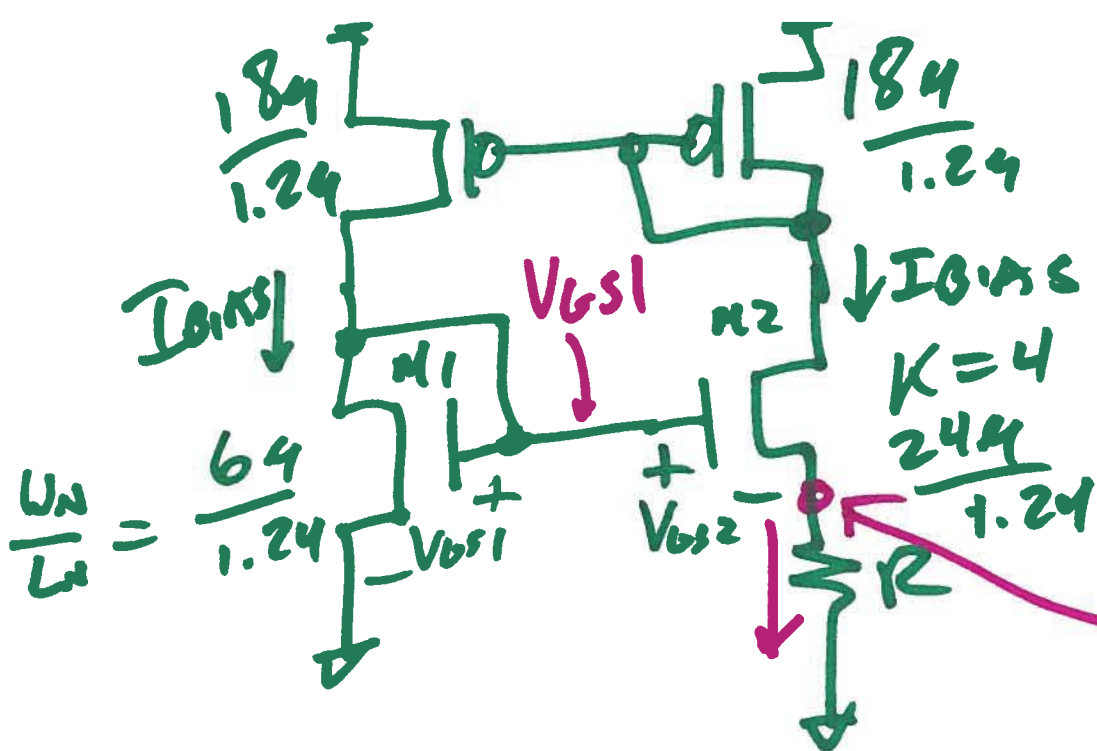
$$\frac{5 - 1.05}{20k} = R = \frac{3.95}{20k} = 200k$$



$$I_{BIAS} = \frac{V_{GS1} - V_{GS2}}{R}$$

$$= \left( V_{THN} + \sqrt{\frac{2I_{BIAS}}{K \mu_N \frac{W_N}{L_N}}} - V_{THN} - \sqrt{\frac{2I_{BIAS}}{K \mu_N \frac{W_N}{L_N}}} \right) \frac{1}{R}$$

$$V_{GS1} = V_{THN} + \sqrt{\frac{2I_{BIAS}}{K \mu_N \frac{W_N}{L_N}}}$$

$$I_{BIAS} = \sqrt{\frac{2I_{BIAS}}{R^2 \cdot K \mu_N \frac{W_N}{L_N}}} \left( 1 - \frac{1}{\sqrt{K}} \right)$$

$$V_{GS2} = V_{THN} + \sqrt{\frac{2I_{BIAS}}{K \cdot K \mu_N \cdot \frac{W_N}{L_N}}}$$

$$\sqrt{I_{BIAS}} = \sqrt{\frac{2}{R^2 \cdot K \mu_N \frac{W_N}{L_N}}} \left( 1 - \frac{1}{\sqrt{K}} \right)$$

$$I_{BIAS} = \frac{2}{R^2 \cdot K \mu_N \frac{W_N}{L_N}} \left( 1 - \frac{1}{\sqrt{K}} \right)^2$$

5)

$$I_{BIAS} = \frac{2}{R^2 \cdot K_P \cdot \frac{W_N}{L_N}} \cdot \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$g_m = \sqrt{2 I_{BIAS} \cdot K_P \frac{W_N}{L_N}}$$

---

SAY  $K = 4$

$$I_{BIAS} = \frac{1}{2R^2 \cdot K_P \cdot \frac{W_N}{L_N}}$$

$$g_m = \sqrt{\frac{2}{2R^2 \cdot K_P \cdot \frac{W_N}{L_N}} \cdot K_P \frac{W_N}{L_N}} = \frac{1}{R}$$

$$R = \frac{1}{1304} = \underline{\underline{7.7K}}$$