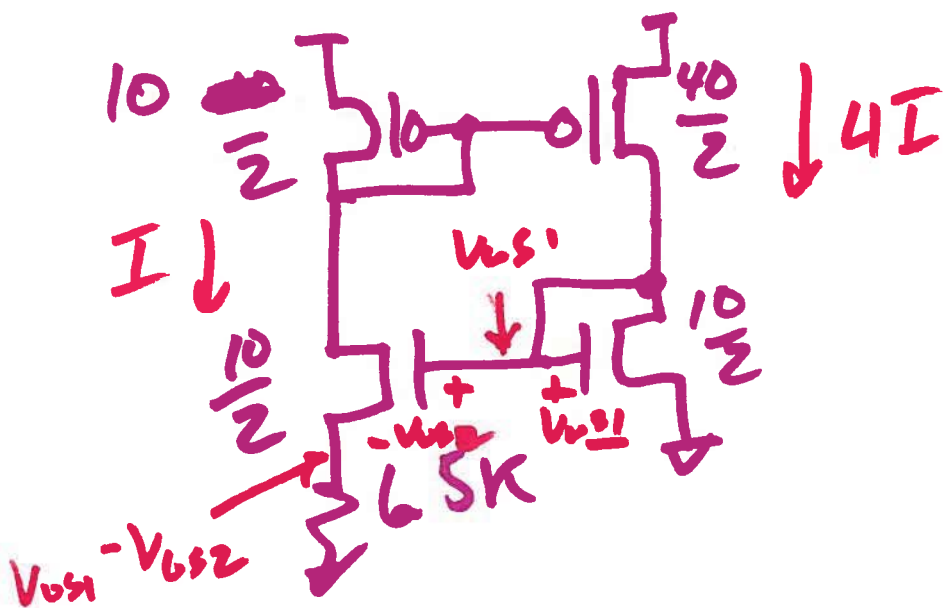


EE 420 / ECE 620

Analog IC Design

Lecture 9

2/15/2017



$$V_{oss1} = \sqrt{\frac{2 \cdot 4I}{k\mu_n \cdot \frac{10}{2}}} + V_{THW}$$

$$V_{oss2} = \sqrt{\frac{2I}{k\mu_n \cdot \frac{10}{2}}} + V_{THW}$$

$$I = \frac{V_{oss1} - V_{oss2}}{6.5k} = \sqrt{\frac{2 \cdot I}{R^2 k\mu_n \cdot \frac{10}{2}}} (\sqrt{4} - 1)$$

(R)

$$I = \frac{1}{R} \left( \sqrt{\frac{2 \cdot 4I}{k_n \cdot \frac{10}{2}}} - \sqrt{\frac{2I}{k_n \cdot \frac{10}{2}}} \right)$$

$$= \sqrt{\frac{2I}{R^2 k_n \cdot \frac{10}{2}}} (\sqrt{4} - 1)$$



$$I = \sqrt{\frac{2I}{R^2 \cdot k_n \cdot \frac{10}{2}}}$$

$$I = \frac{2}{R^2 \cdot k_n \cdot \frac{10}{2}} = \frac{2}{(6.5k)^2 \cdot 5 \cdot 120\mu}$$


$$= \underline{\underline{78\mu}}$$

2)

# CASCODING

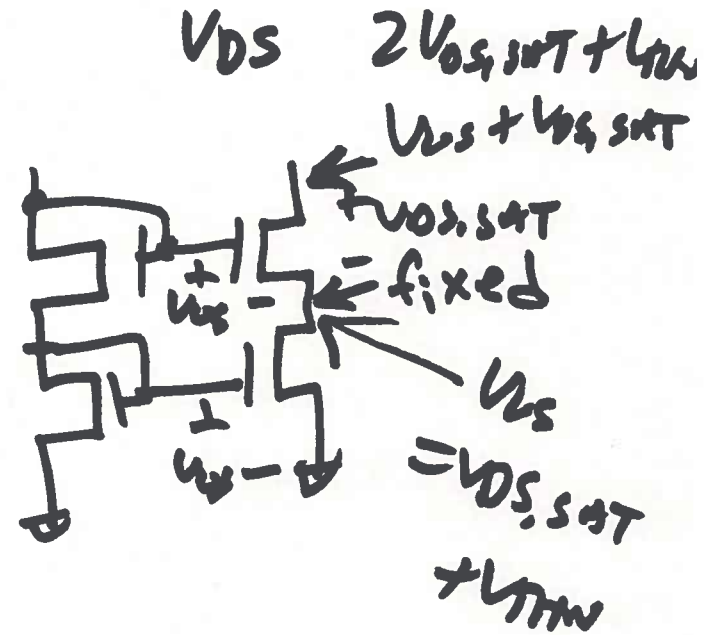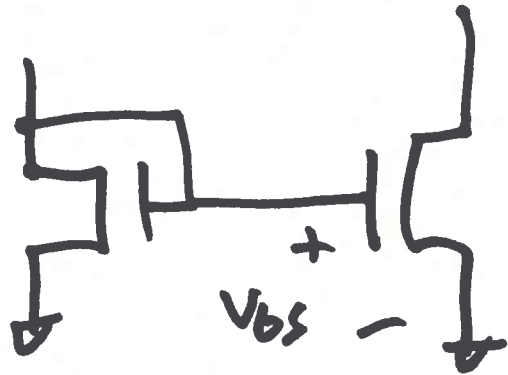

# AC CKT

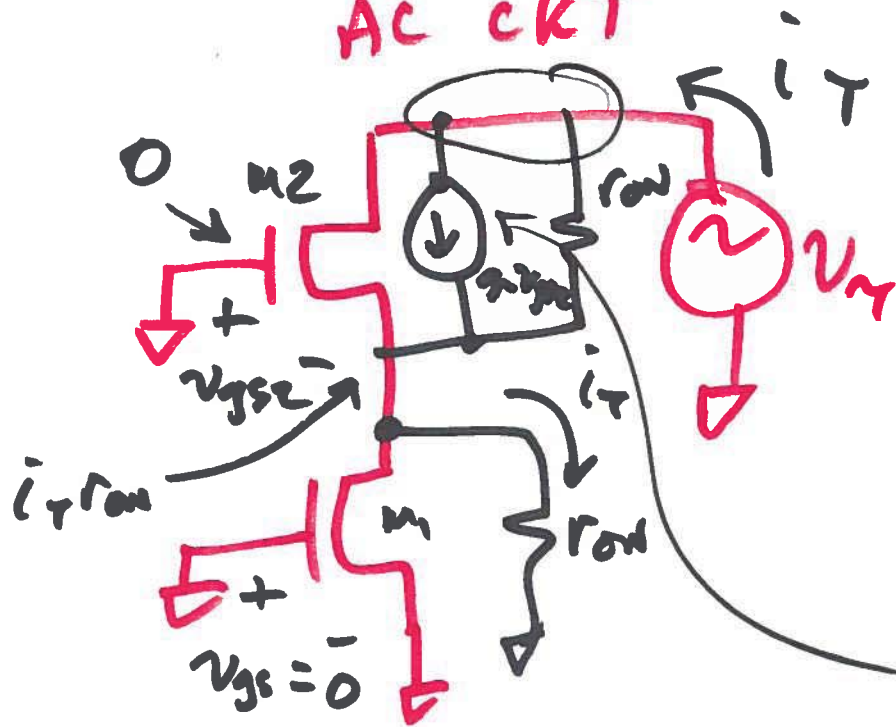

$$R_{out} = \frac{v_T}{i_T}$$

$$v_{gs2} = -i_T r_{DN}$$

$$g_{mN} v_{gs2} = g_{mN} (-i_T r_{DN})$$

$$130 \mu \cdot (2 \text{ M}\Omega)^2$$


$$130 \cdot 2 \cdot 2 \text{ M}\Omega$$

$$520 \text{ M}\Omega$$

$$i_T = -g_{mN} i_T r_{DN} + \frac{v_T - (i_T r_{DN})}{r_{DN}}$$

$$i_T (1 + g_{mN} r_{DN} + 1) = \frac{v_T}{r_{DN}}$$
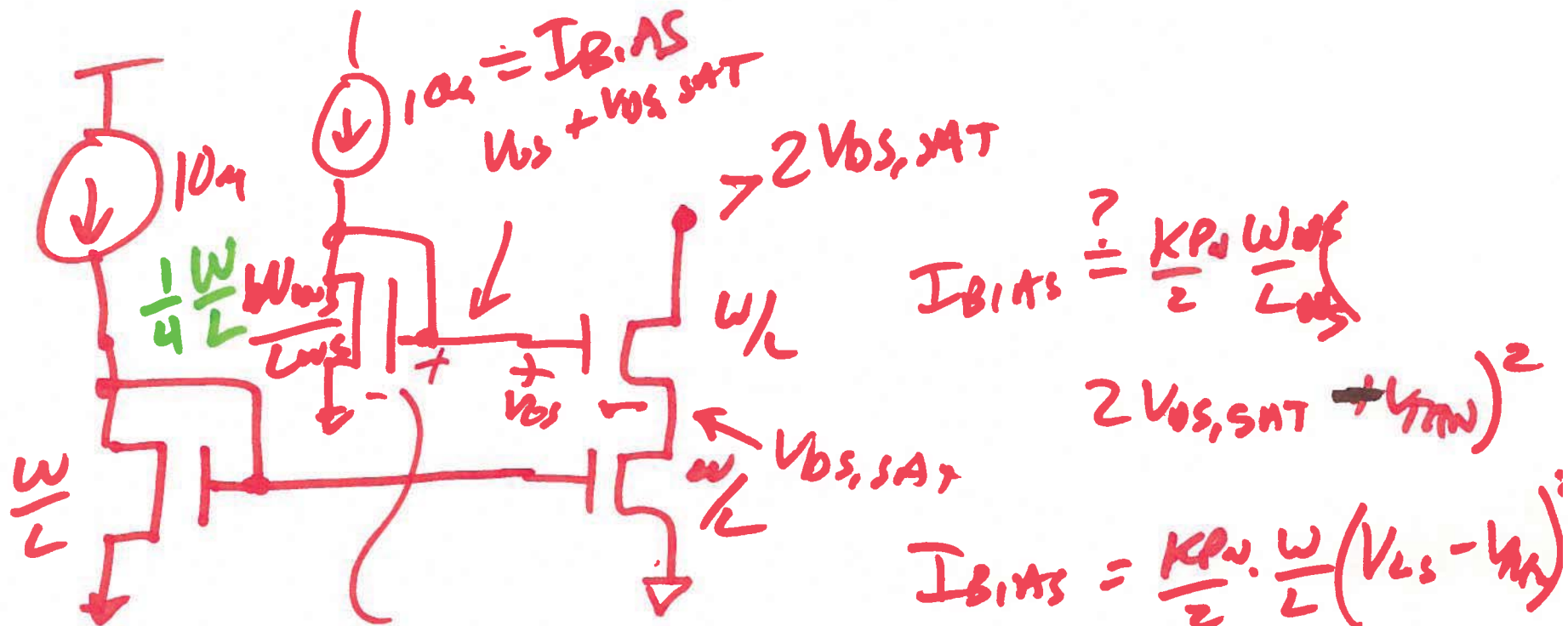
$$R_{out} = \frac{v_T}{i_T} = 2r_{DN} + g_{mN} r_{DN}^2 \approx g_{mN} r_{DN}^2$$



$$V_{GS} + V_{DS,SAT} = 2V_{DS,SAT} + V_{TN}$$

$$V_{GS} = \sqrt{\frac{2I_{BIAS}}{K_P \cdot \frac{W}{L}}} + V_{TN}$$


5)

$$\frac{KPN}{2} \frac{WWS}{LWS} \left( \overset{V_{DS,SAT} + V_{THN}}{V_{GS} - V_{THN} + V_{DS,SAT}} \right)^2 = \frac{KPN}{2} \frac{WWS}{LWS} (2 V_{DS,SAT})^2$$

$$= \frac{KPN}{2} \frac{W}{L} \left( \underbrace{V_{GS} - V_{THN}}_{V_{DS,SAT}} \right)^2 = \frac{KPN}{2} \cdot \frac{W}{L} V_{DS,SAT}^2$$

$$W = WWS$$

$$LWS = 4L$$

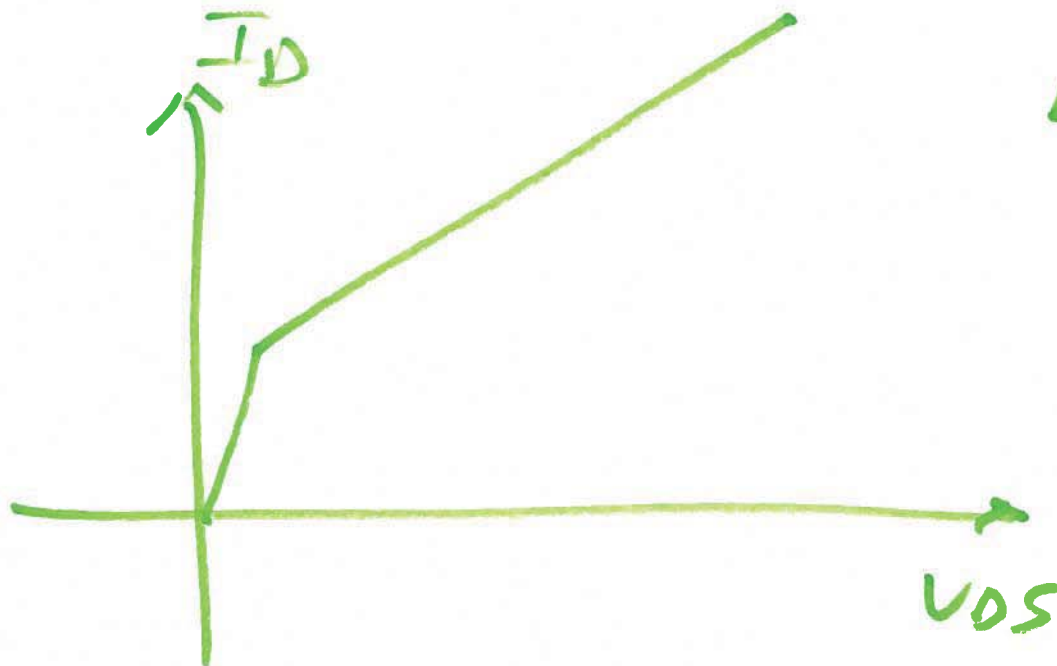

6)