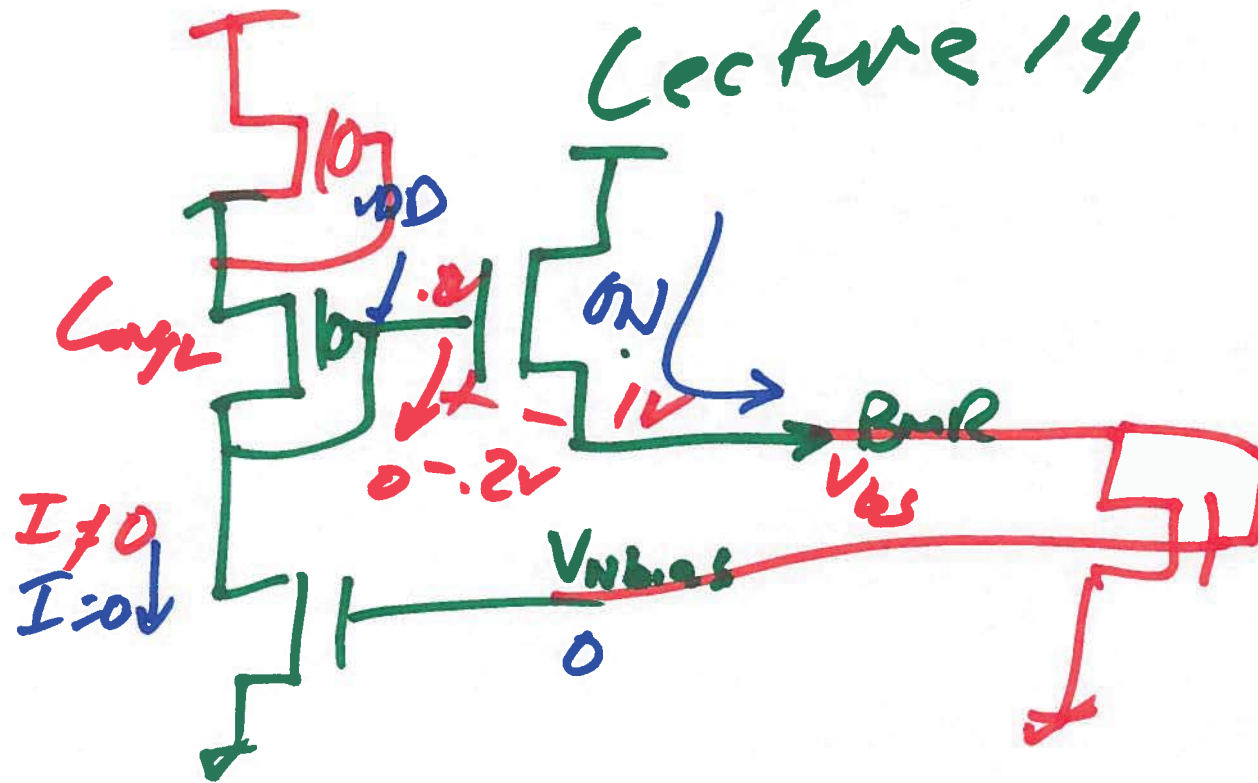



EE 420 / ECE 620
Analog IC Design
MARCH 25, 2019

Lecture 14



COMMON-SOURCE Amp


with current source load

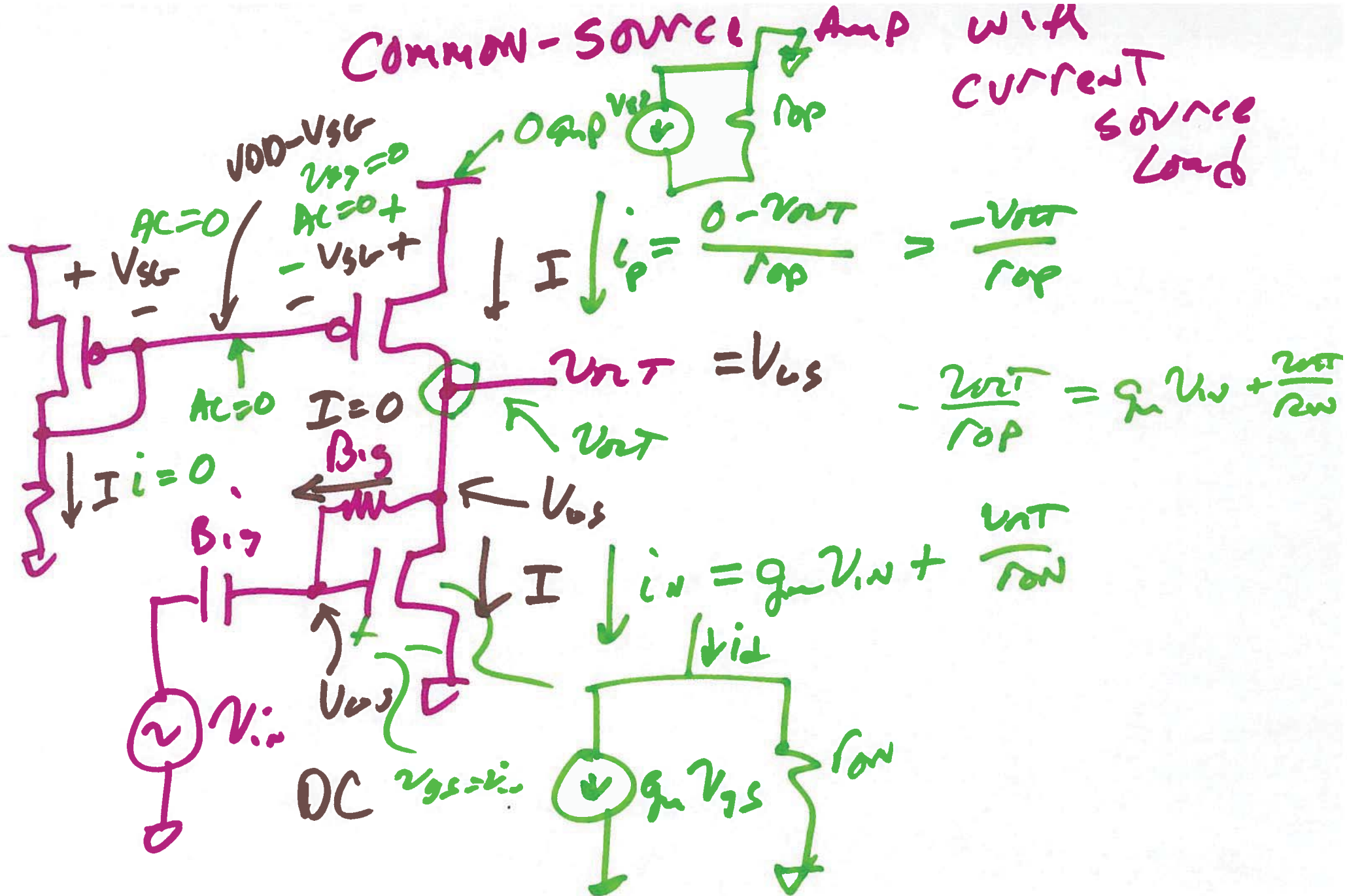

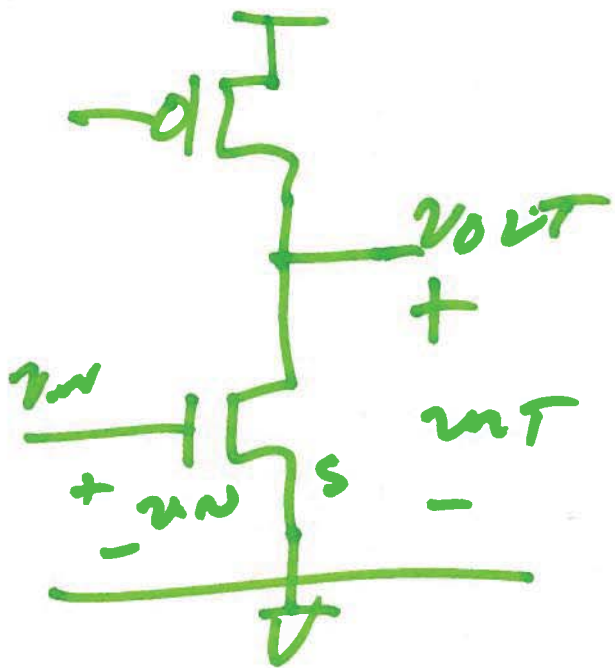2)

$$-\frac{v_{out}}{r_{op}} = g_m v_{in} + \frac{v_{out}}{r_{on}}$$


$$-v_{out} \left(\frac{1}{r_{op}} + \frac{1}{r_{on}} \right) = g_m v_{in}$$



$$\frac{v_{out}}{v_{in}} = -g_m \frac{1}{\frac{1}{r_{on}} + \frac{1}{r_{op}}}$$

$$\frac{v_{out}}{v_{in}} = -g_m r_{on} \parallel r_{op}$$

C.S. Amp Gain

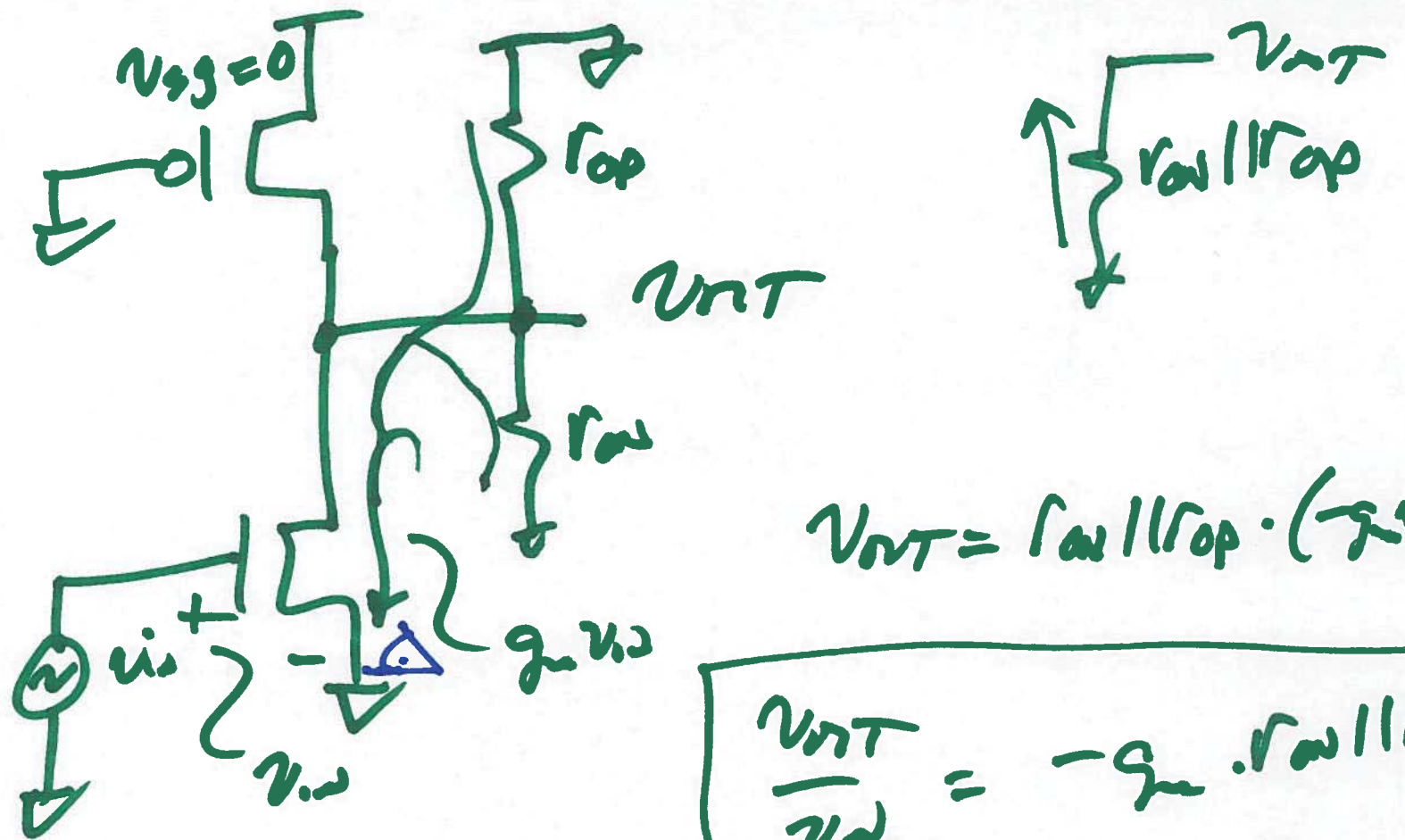


$$v_{OUT} = r_{O1} \parallel r_{OP} \cdot (-g_m v_{in})$$

$$\frac{v_{OUT}}{v_{in}} = -g_m \cdot r_{O1} \parallel r_{OP}$$


C.S.

$$= \frac{-\text{res. in drain}}{\text{res in source}}$$
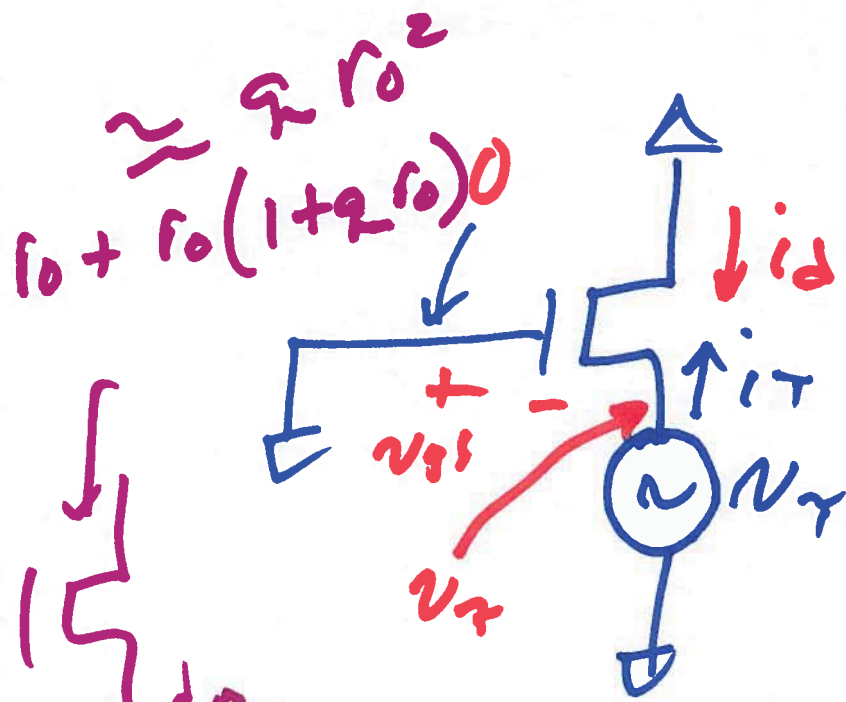
$$= \frac{-r_{O1} \parallel r_{OP}}{1/g_m}$$




$$R_{out, source} = \frac{v_T}{i_T}$$

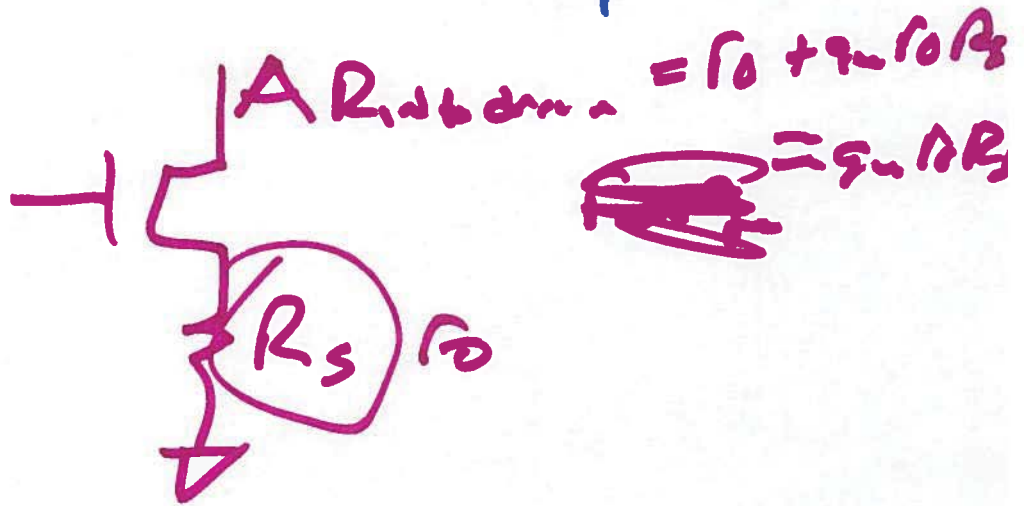

$$v_{gs} = 0 - v_T = -v_T$$


$$g_m v_{gs} = i_d = -i_T = g_m (-v_T)$$
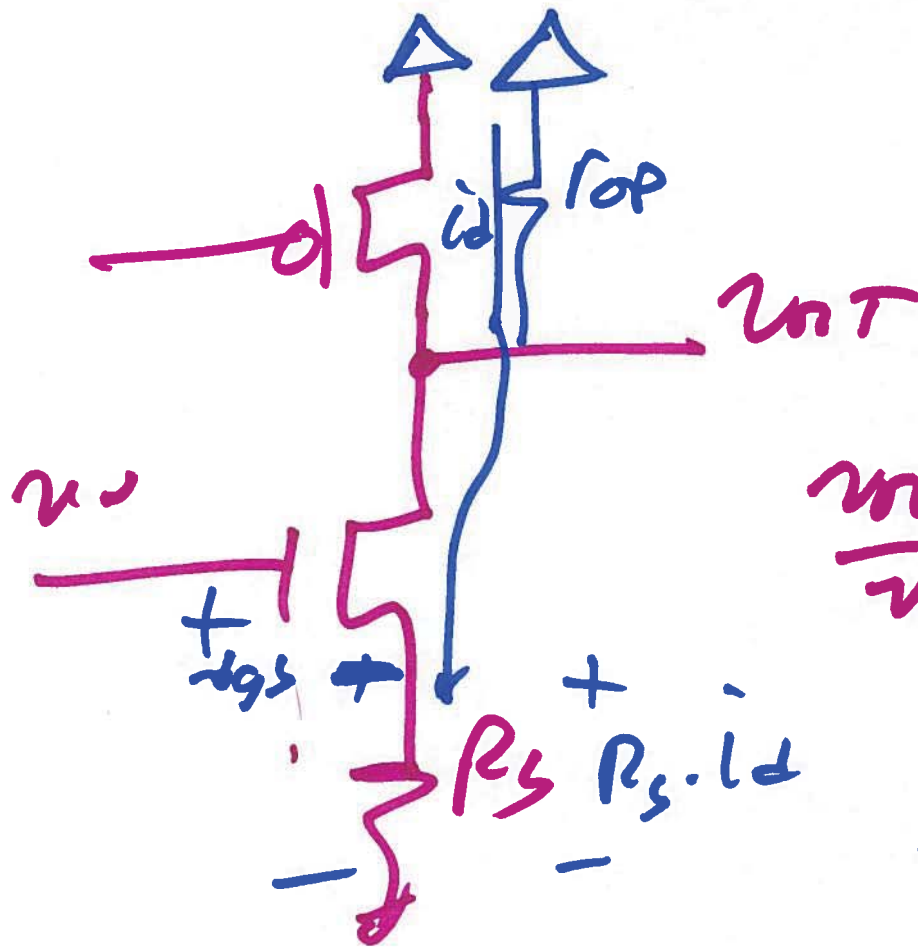
$$\frac{v_T}{i_T} = \frac{1}{g_m} = R_{out, source}$$



$$\frac{v_{out}}{v_{in}} \approx - \frac{r_{oP} \parallel r_o R_s}{\frac{1}{g_m} + R_s}$$
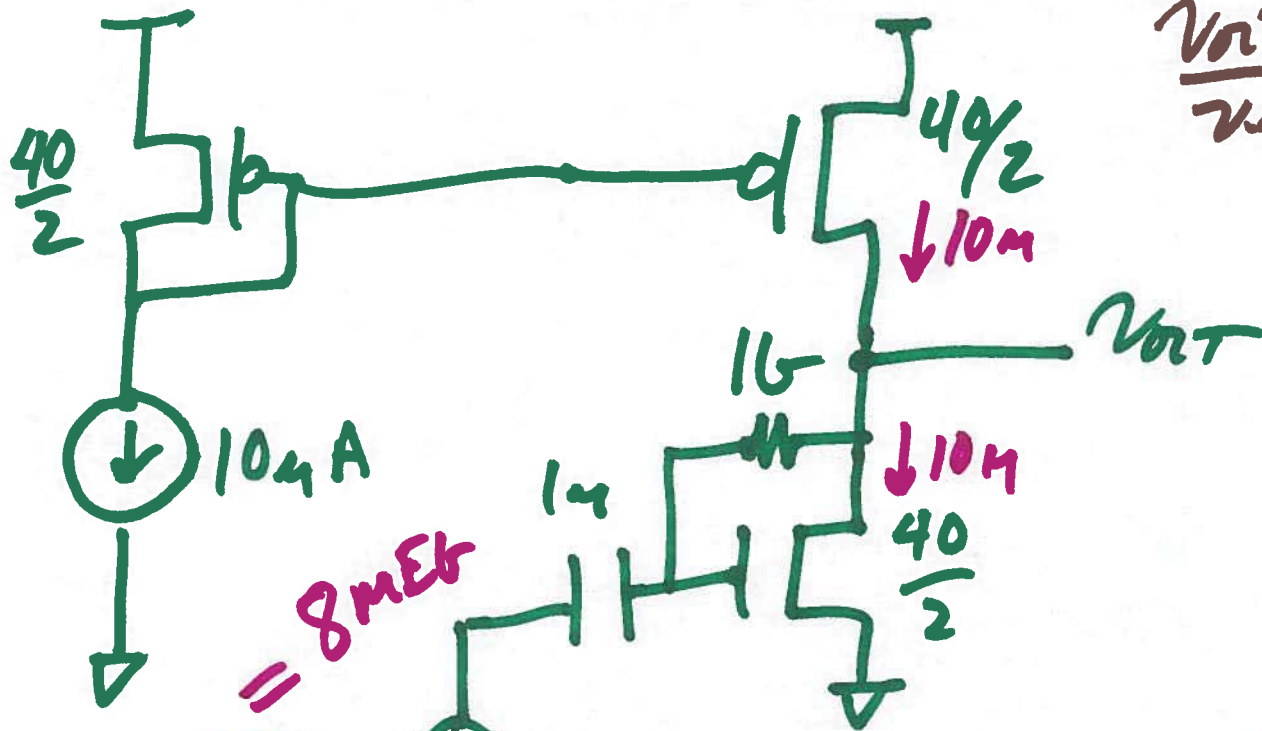
$$\frac{v_{out}}{v_{in}} = \frac{- \frac{1}{g_m} \cdot r_{oP}}{\frac{1}{g_m} + j\omega \cdot R_s}$$



$$\frac{V_{out}}{V_{in}} = ?$$

$$r_{op} = \frac{1}{10\mu \cdot 0.0125} = 8\text{MEG}$$

$$r_{os} = \frac{1}{10\mu \cdot 0.01} = 10\text{MEG}$$


$$\frac{V_{out}}{V_{in}} = -g_m (r_{os} || r_{op})$$

$$= 219\mu \cdot 8\text{MEG} / 10\text{MEG}$$

$$g_m = \sqrt{2 \cdot 120\mu \cdot 10\mu \cdot \frac{40}{2}} = 219\mu$$

$$= 219 \cdot 4.4 = 964 \frac{V}{V}$$

7)

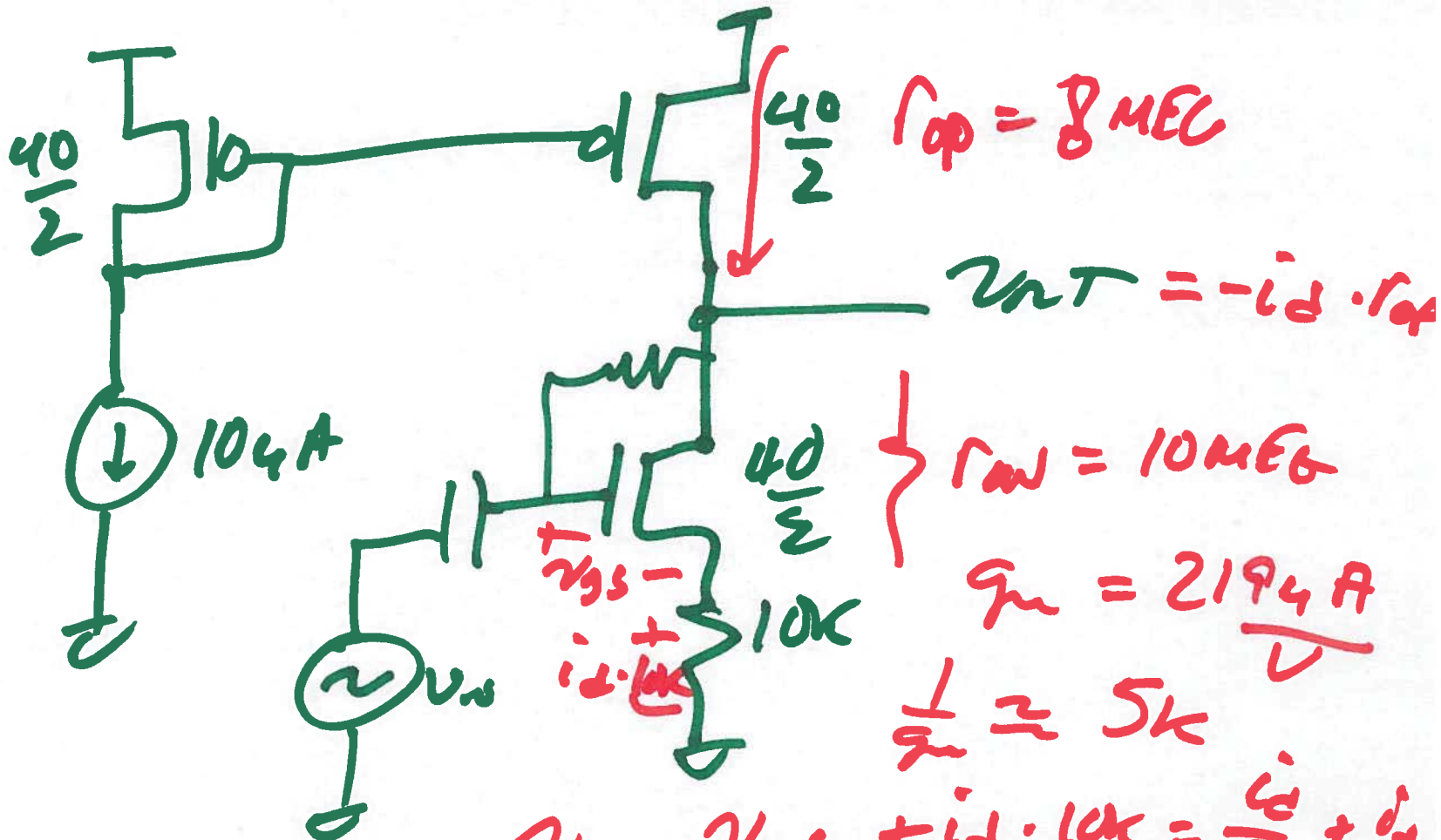

$$r_{op} = 8 \text{ MEG}$$

$$v_{out} = -i_d \cdot r_{op}$$

$$r_{on} = 10 \text{ MEG}$$

$$g_m = 2194 \frac{\text{A}}{\text{V}}$$

$$\frac{1}{g_m} = 5 \text{ k}$$

$$v_{in} = v_{gs} + i_d \cdot 10\text{k} = \frac{v_{out}}{2} + i_d \cdot 10\text{k}$$

$$\frac{v_{out}}{v_{in}} = \frac{-i_d \cdot r_{op}}{\frac{1}{g_m} + 10\text{k}} = -\frac{8 \text{ MEG}}{15 \text{ k}}$$