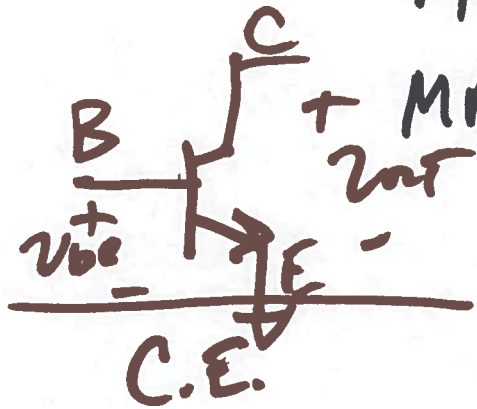


EE ~~420~~ 420 / ELG 620



Analog IC DESIGN

MARCH 27, 2019

Lecture 15



C.S.

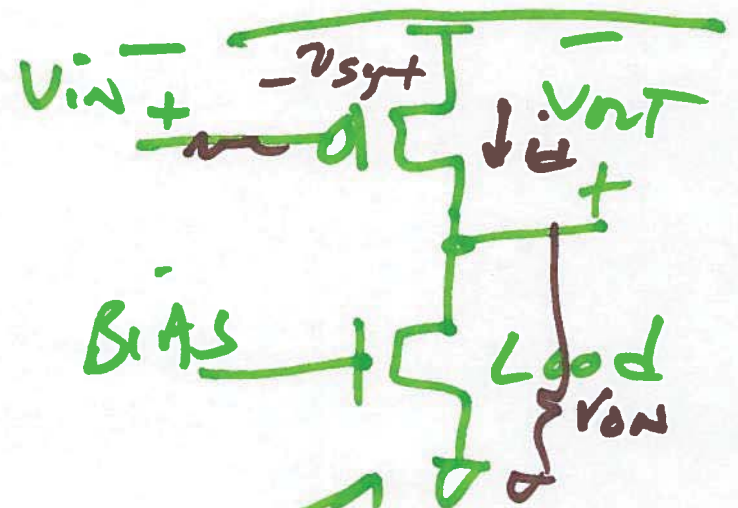
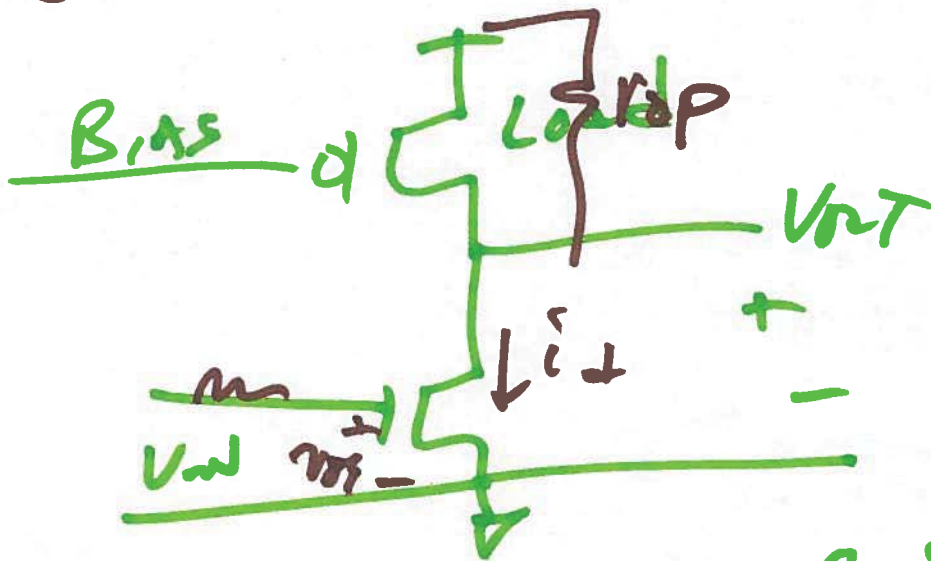


C.S.

1)
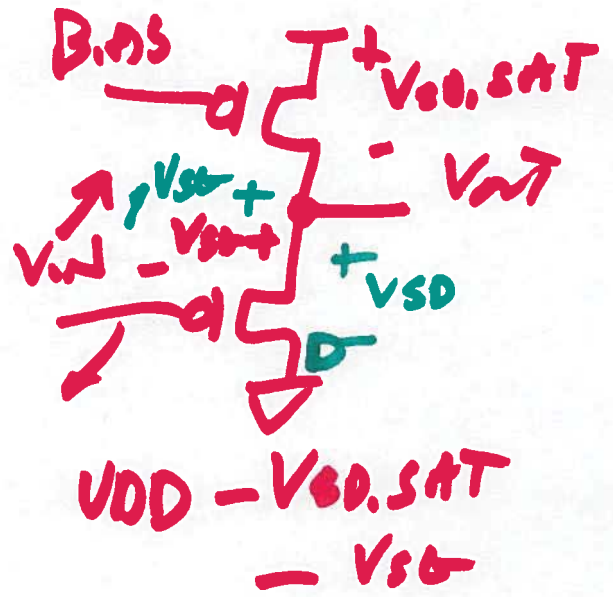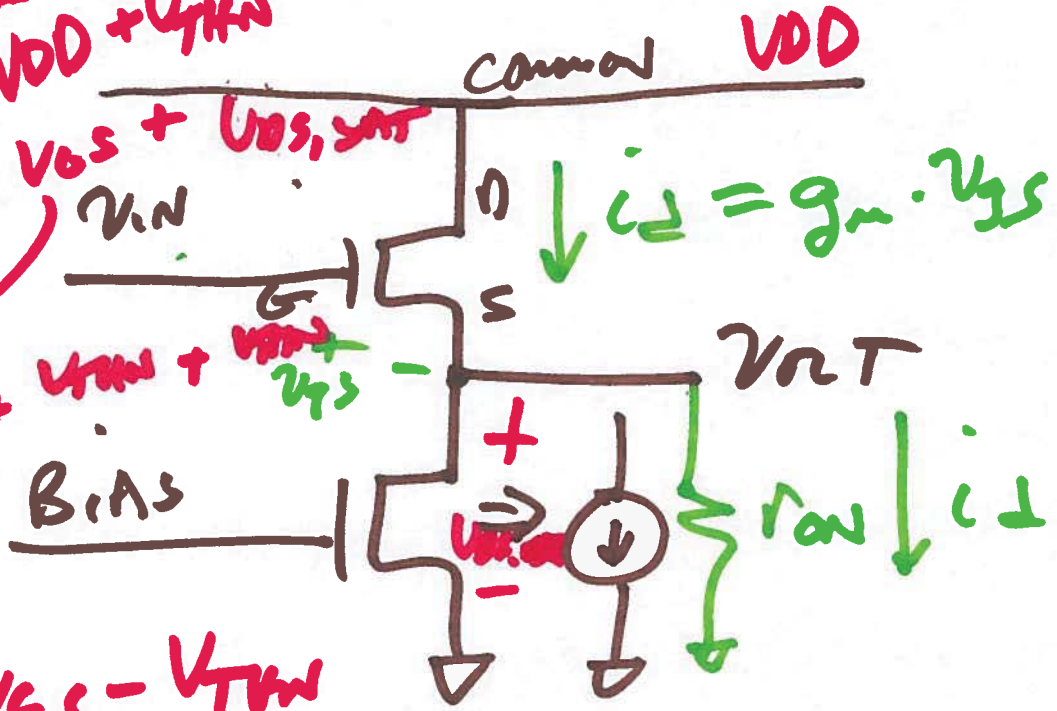
# COMMON-DRAIN (CD) (Source-follower)

$V_{in,MAX} = V_{DD} + V_{THN}$   
 $V_{in,min} = V_{GS} + V_{DS,SAT}$   
 $V_{DS,SAT} = V_{THN} + V_{GS}$




$V_{GS} \geq V_{GS} - V_{THN}$   
 $V_{GS} \geq V_{GS} - V_{THN}$   
 $V_{DD} \geq V_{in,MAX} - V_{THN}$   
 $V_{in,MAX} \leq V_{DD} + V_{THN}$

$V_{in} = V_{GS} + V_{out}$   
 $= i_d \left( \frac{1}{g_m} + r_{o_n} \right)$   
 $V_{out} = \frac{i_d \cdot r_{o_n}}{i_d \left( \frac{1}{g_m} + r_{o_n} \right)}$



$V_{DS} \geq V_{GS} - V_{THP}$   
 $V_{GS} \leq V_{GS} + V_{THP}$   
 $0 \leq V_{in,MIN} + V_{THP}$   
 $V_{in,MIN} = -V_{THP}$   
 $\frac{V_{out}}{V_{in}} \approx 1$

2)

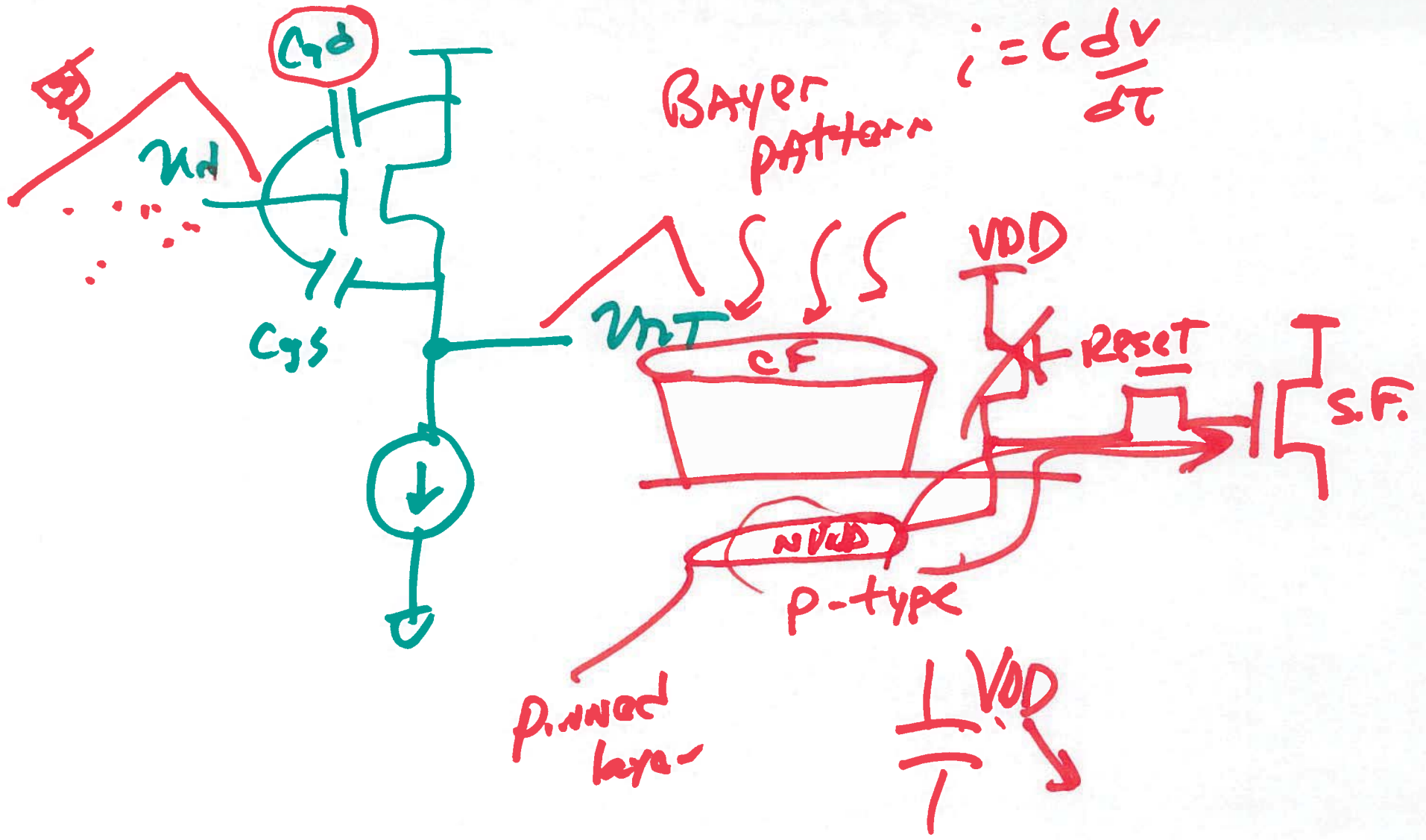


3)

# source follower gain revisited

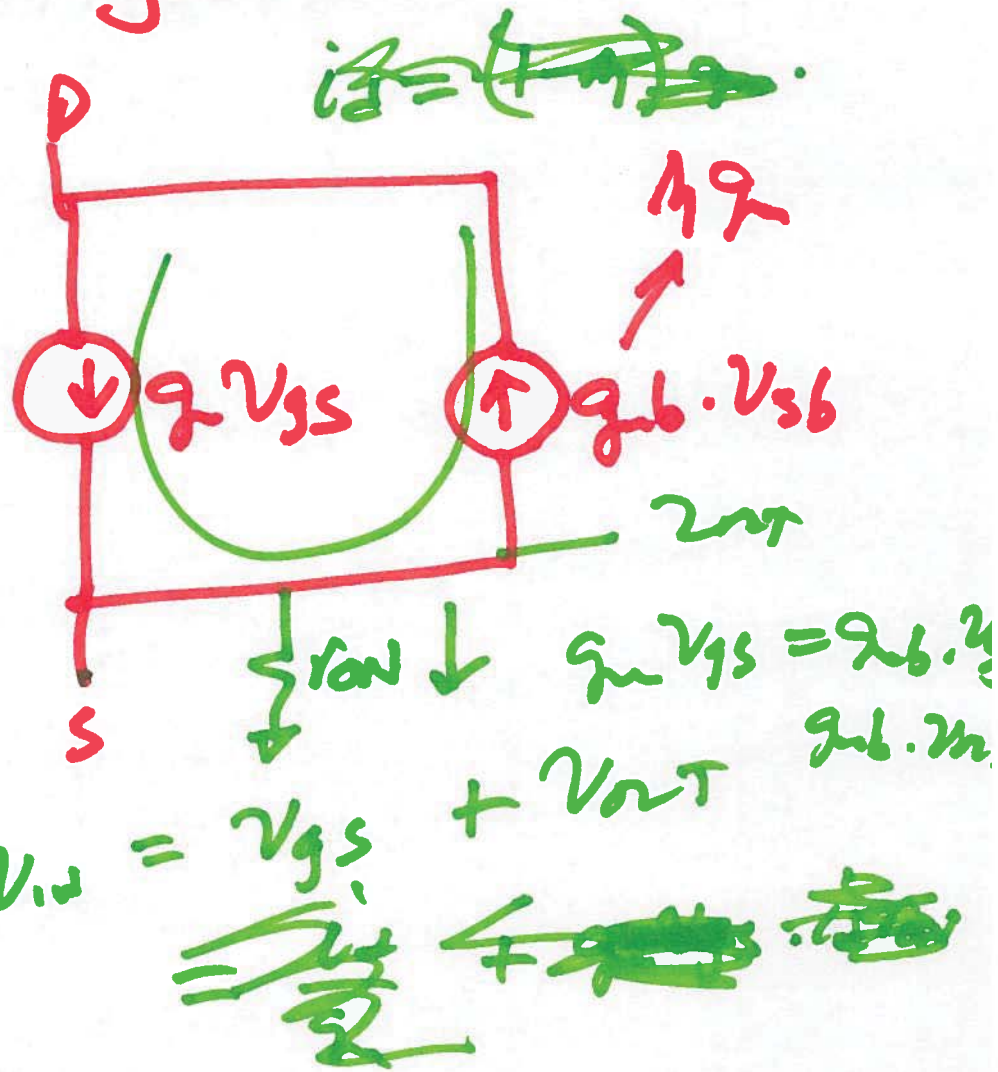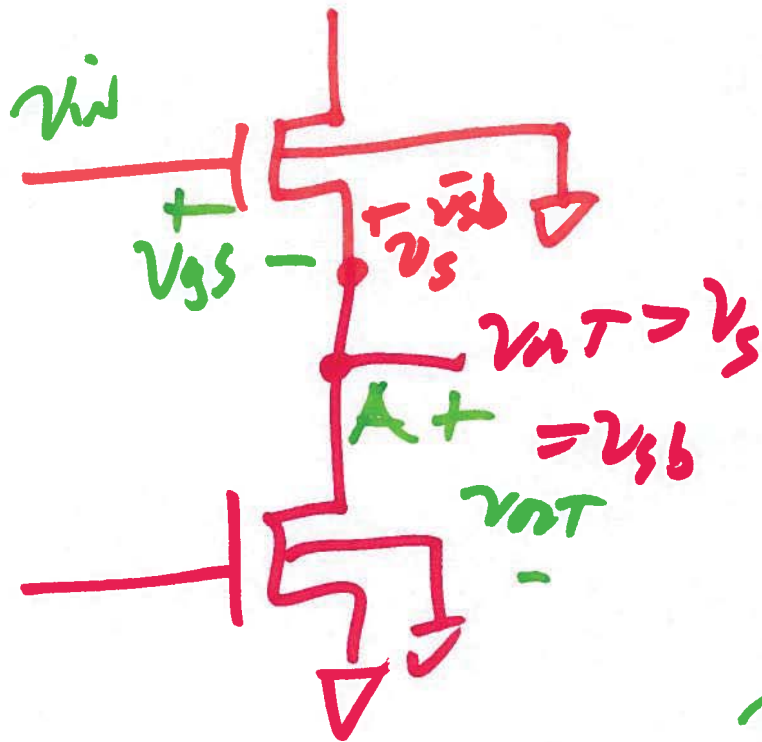

~~...~~

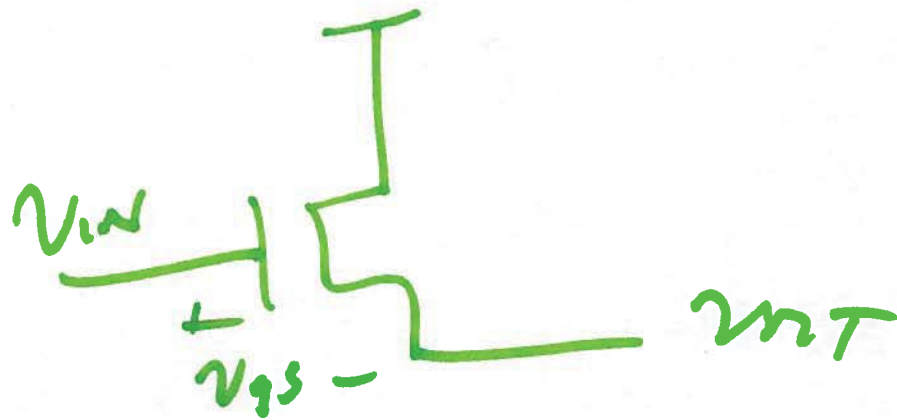

$$v_{in} = v_{gs} + v_{out}$$

$$g_m v_{gs} = \mu g_m \cdot v_{out}$$

$$v_{gs} = \frac{v_{out}}{\mu}$$

$$v_{in} = \mu v_{out} + v_{out}$$

$$= v_{out} (1 + \mu)$$




$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_{out} (1 + \mu)}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \mu}$$

$$0 < \mu < .3$$

5)


# Common-GATE (CG)

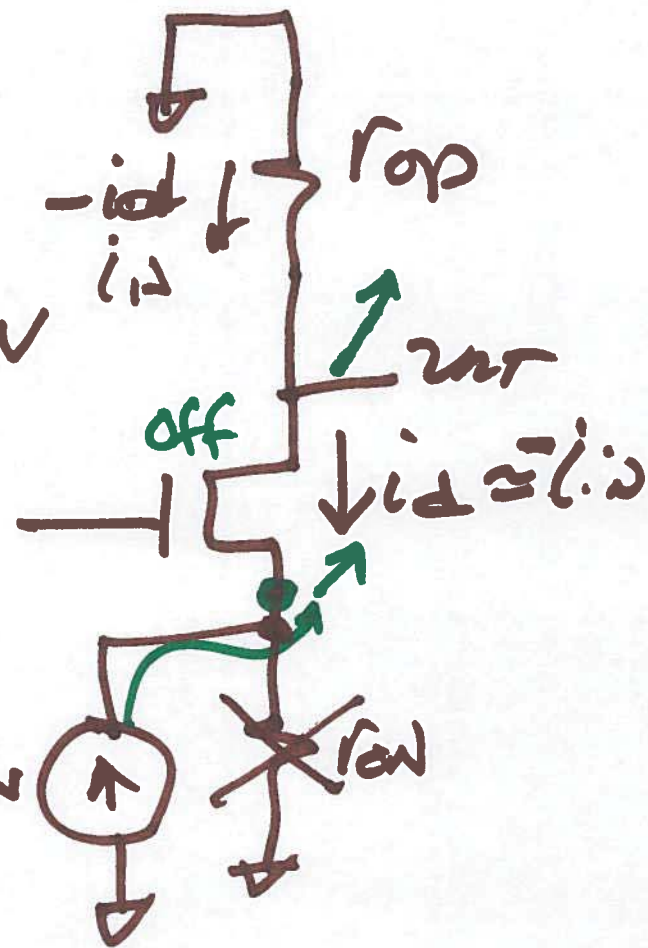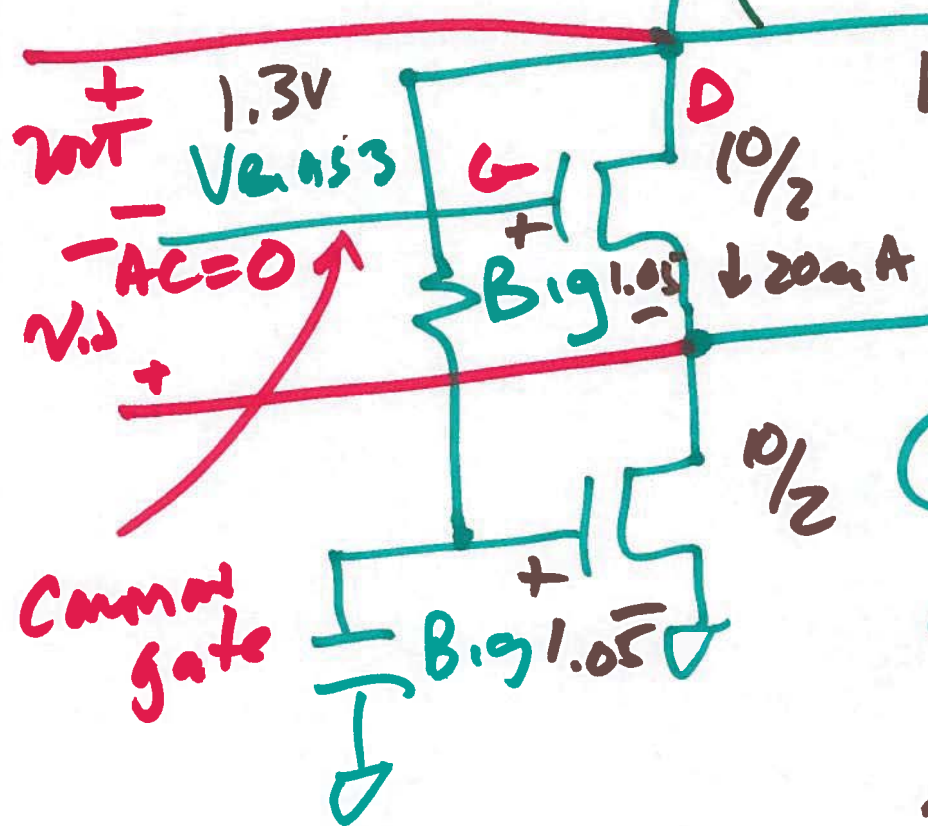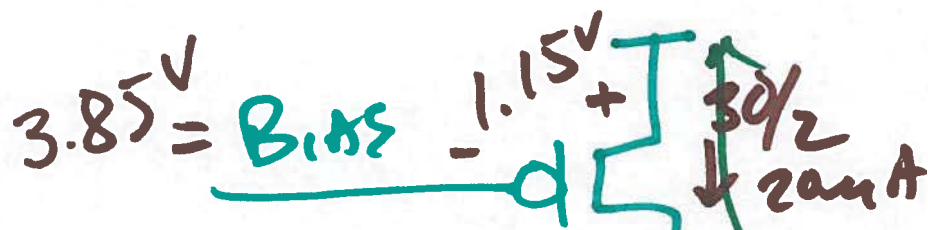

$$V_{out} = +i_{in} \cdot r_{op}$$

$$\frac{V_{out}}{i_{in}} = \frac{+i_{in} \cdot r_{op}}{i_{in}} = \underline{\underline{+r_{op}}}$$

6)

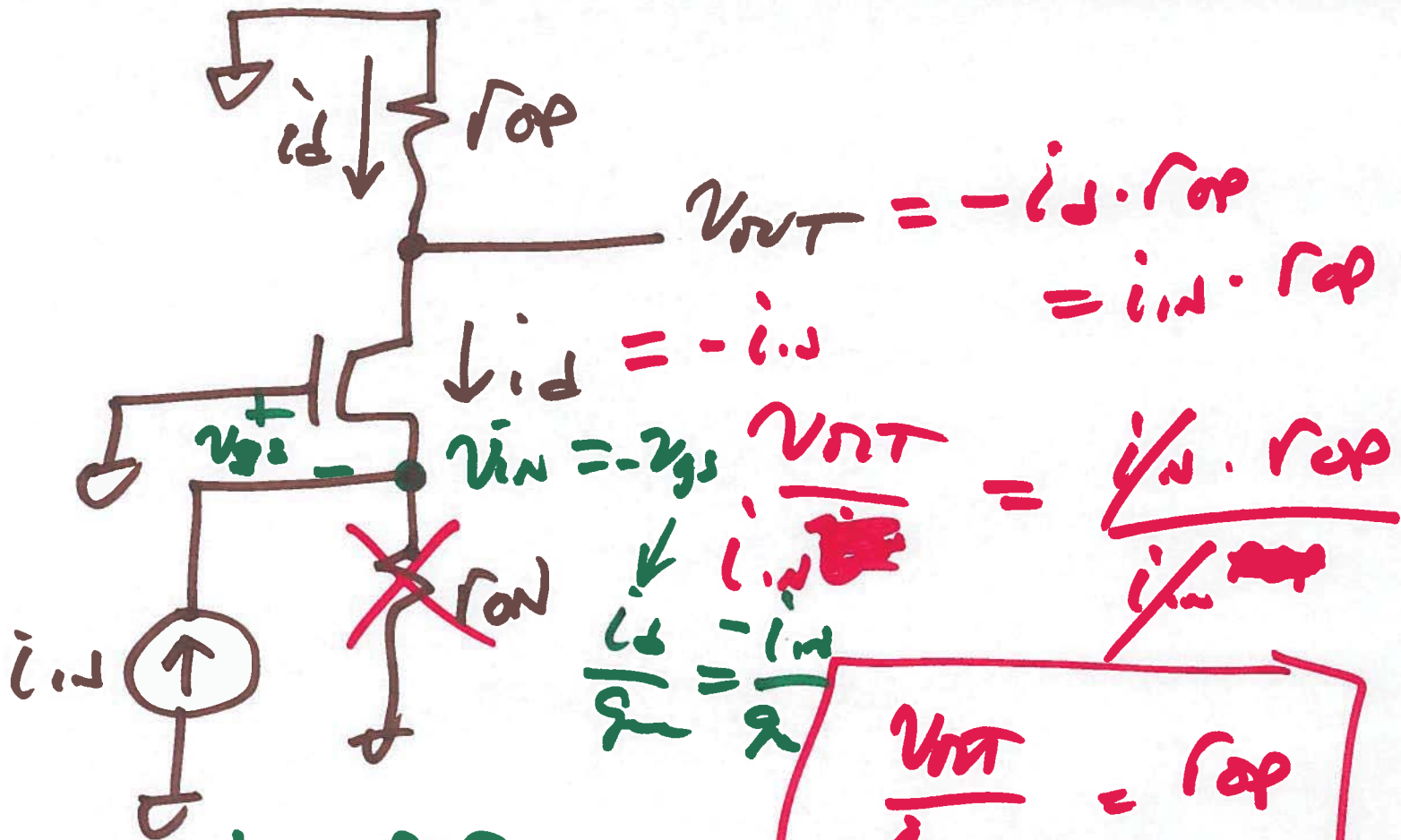


$$\frac{v_{OUT}}{v_{IN}} = \frac{i_{IN} \cdot r_{OP}}{-v_{GS}}$$

$$\Rightarrow \frac{i_{IN} \cdot r_{OP}}{+ \left( \frac{i_{IN}}{g_m} \right)}$$

transimpedance,  $\frac{V}{A}$  ( $\Omega$ )  
resistance

$$\frac{v_{OUT}}{i_{IN}} = g_m r_{OP}$$

7)

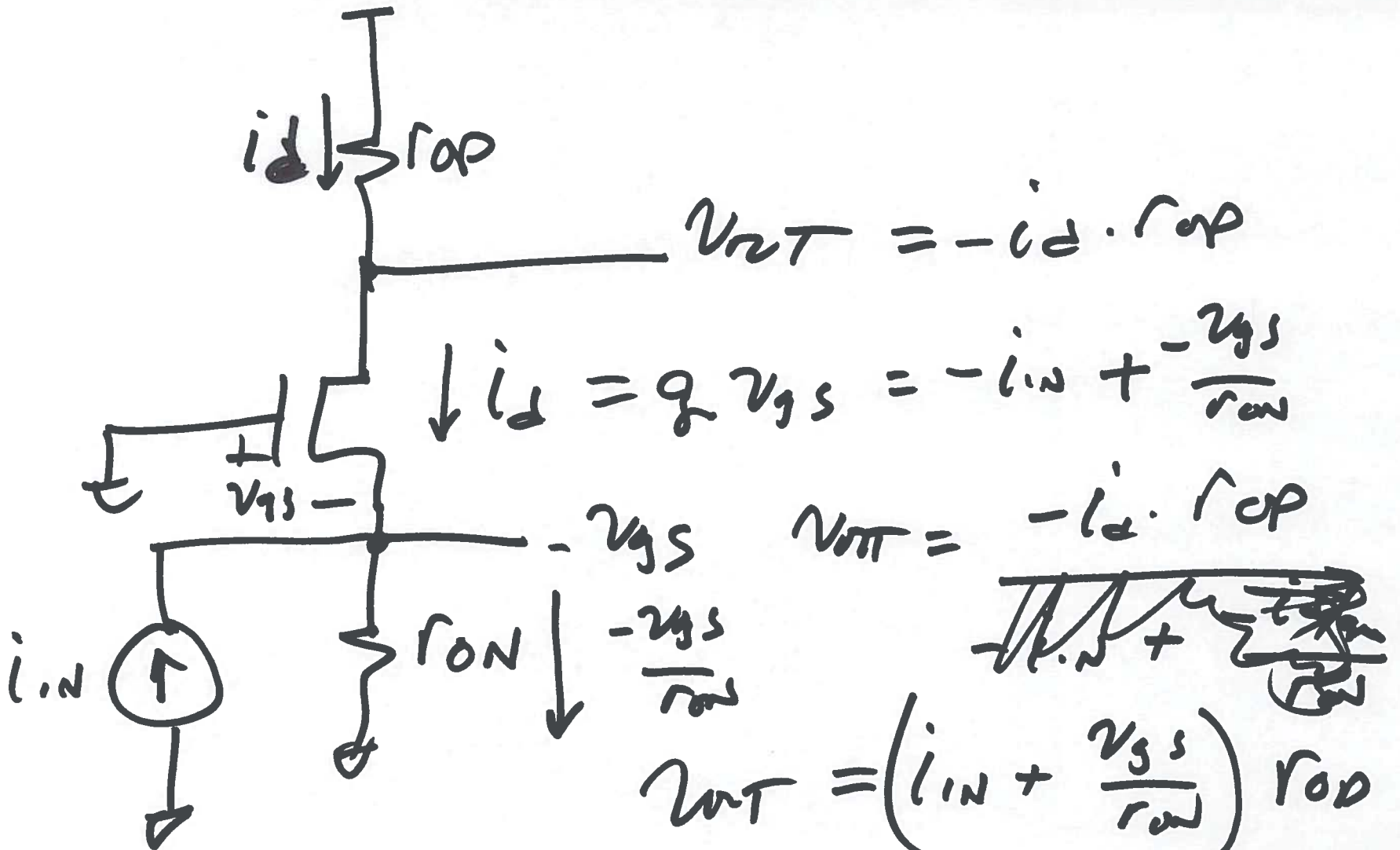

$$v_{OT} = \left( i_{in} + \frac{i_{id}/g_m}{r_{ON}} \right) r_{OD}$$

$$= i_{in} r_{OD} + i_{id} \cdot \frac{r_{OD}}{r_{ON}} \cdot \frac{1}{g_m}$$

$$\frac{v_{OT}}{i_{in}} \approx r_{OD}$$