
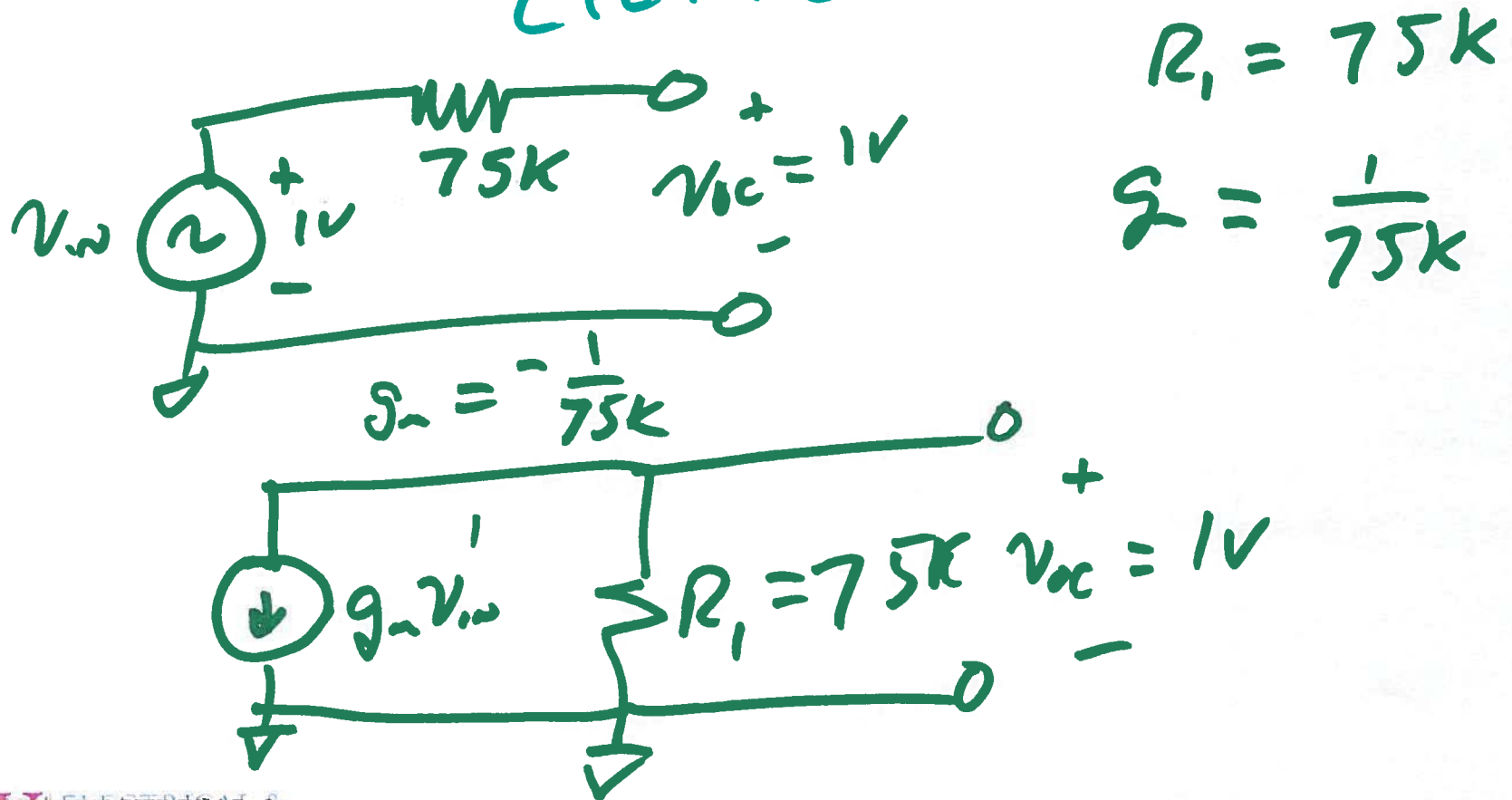


EE 420 / ECG 620
Analog IC Design

April 8, 2019

Lecture 18

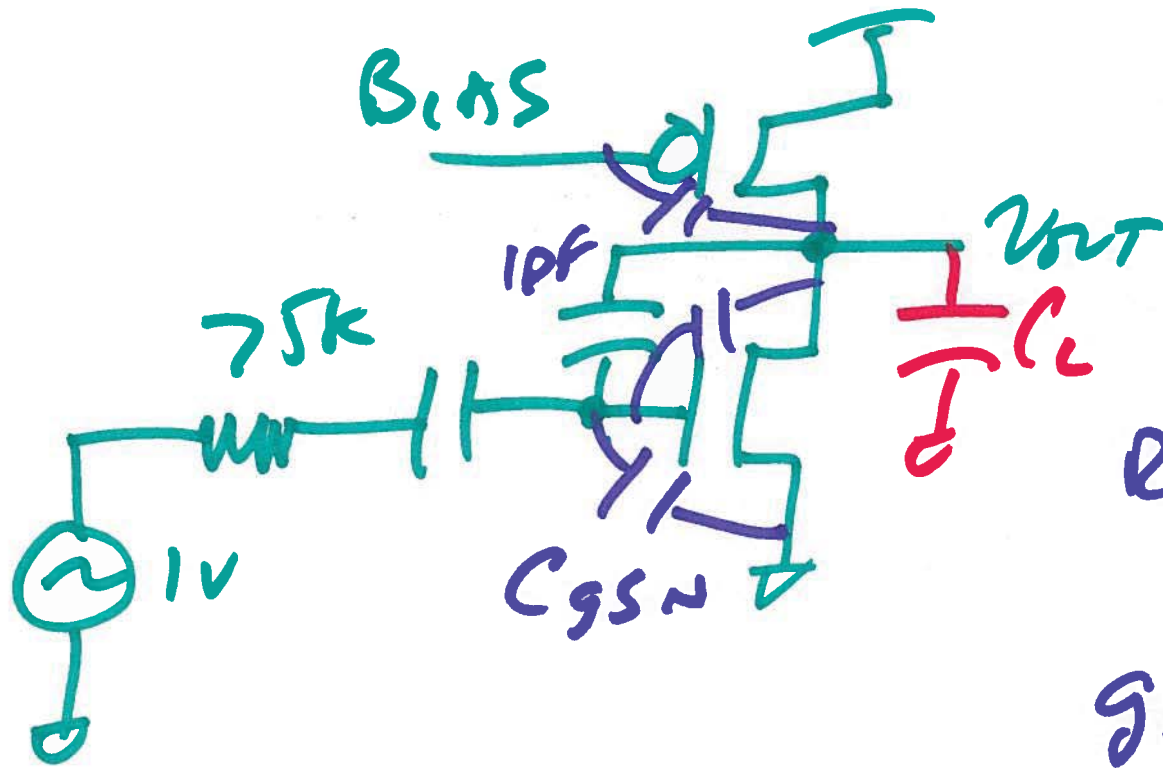



$$R_1 = 75k$$

$$C_1 = C_{gsn} = 23.3fF$$

$$C_2 = 1pF$$

$$R_2 = r_{on} || r_{ov} = 2.2M\Omega$$


$$g_{m2} = 150 \frac{\mu A}{V}$$

$$C_2 = C_{gdp} = 6fF$$

f_1

f_2
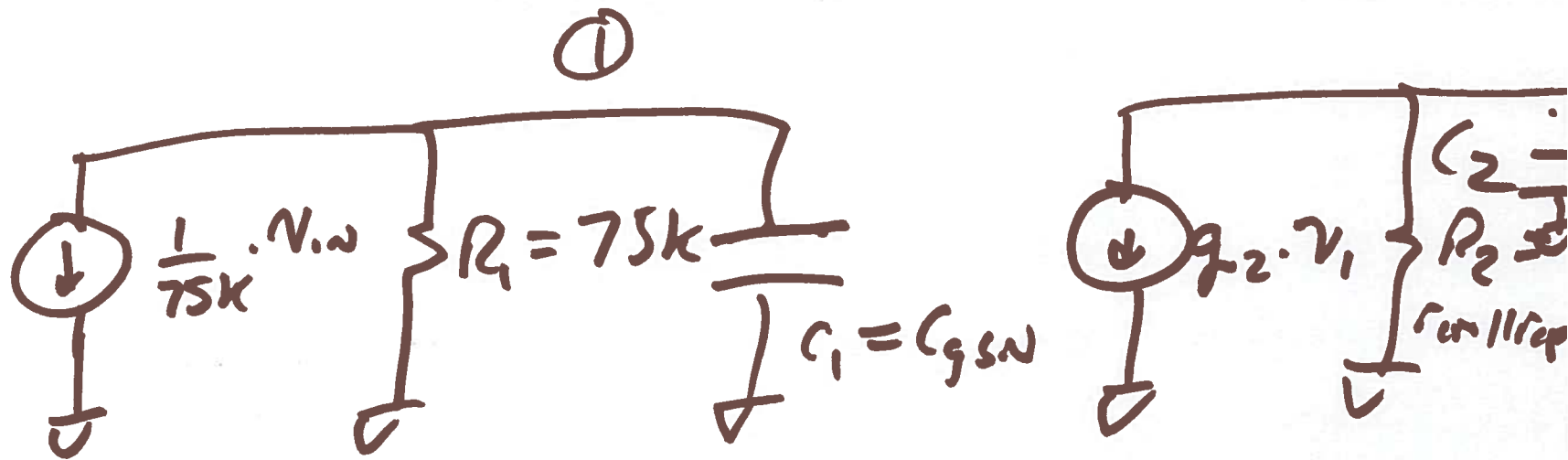
$$f_2 = \frac{g_{m2}}{2\pi R_2 C_L} = \frac{150\mu A}{2\pi \cdot 1p} = \underline{\underline{23MHz}}$$



$1 - \frac{f}{f_z} = 1 - \frac{2\pi f}{2\pi f_z}$

$s = j\omega$

$\left(1 - \frac{s}{2\pi f_z} \right) = 0$

$s = 2\pi f_z$


$-\tan^{-1} \frac{j\omega f}{2\pi f_z}$


LHP ←

→ RHP

$$\left| \frac{1 + j \frac{f}{f_2}}{1 + j \frac{f}{f_p}} \right| = \frac{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}}$$
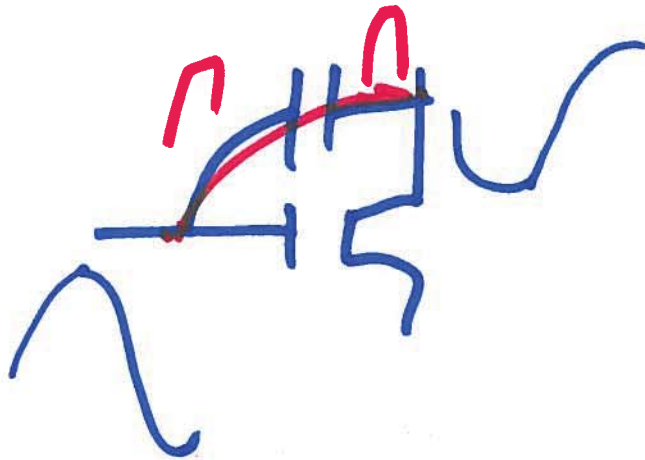
$$\rightarrow -\tan^{-1} \frac{f}{f_2} - \tan^{-1} \frac{f}{f_p}$$




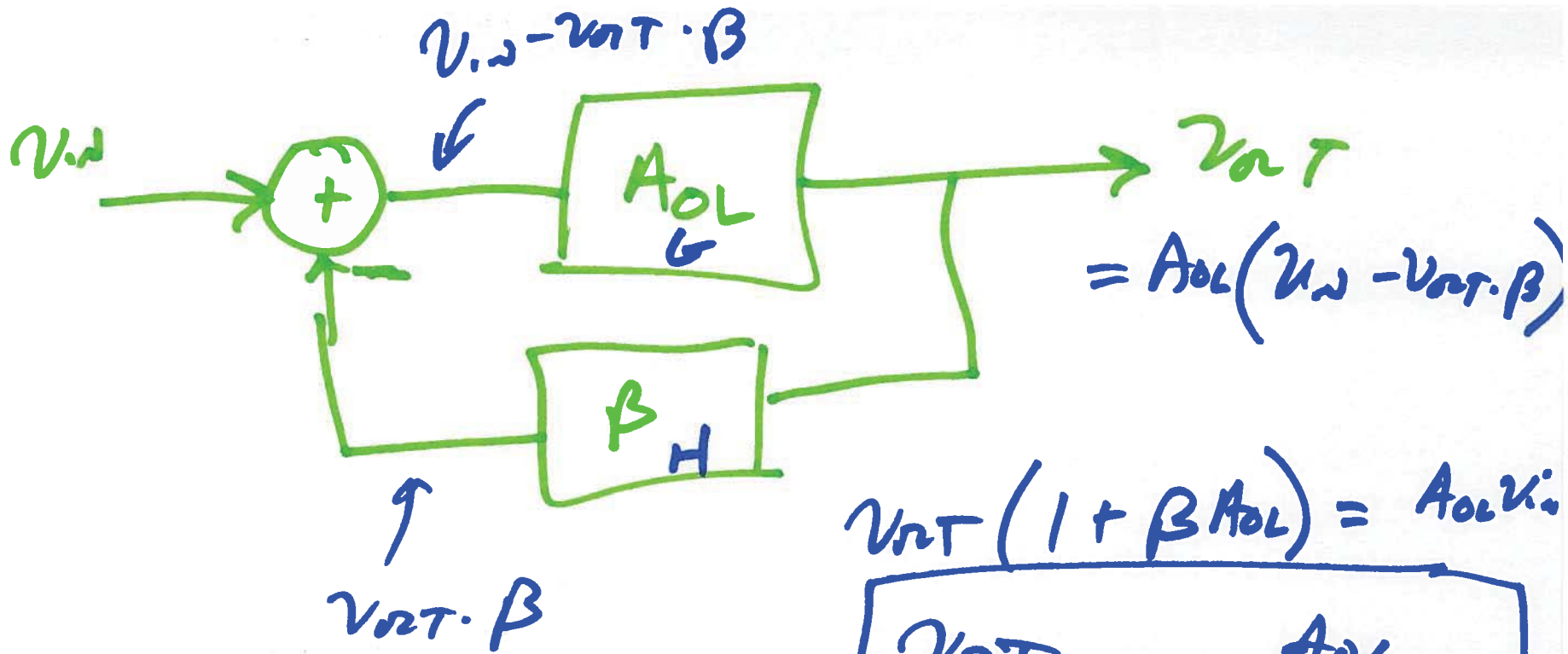

$$= A_{OL}(v_{in} - v_{out} \cdot \beta)$$

$$v_{out}(1 + \beta A_{OL}) = A_{OL} v_{in}$$
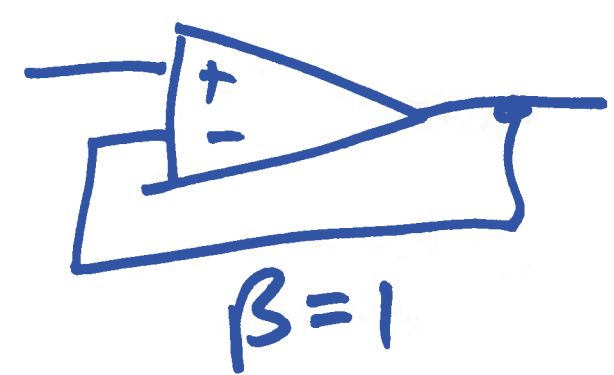
$$\frac{v_{out}}{v_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}}$$





UNstable when $\beta \cdot A_{OL} = -1$

$$|\beta \cdot A_{OL}| = 1$$

$$\pm 180^\circ$$

5)


CASCADE Amplifier (Miller killer)

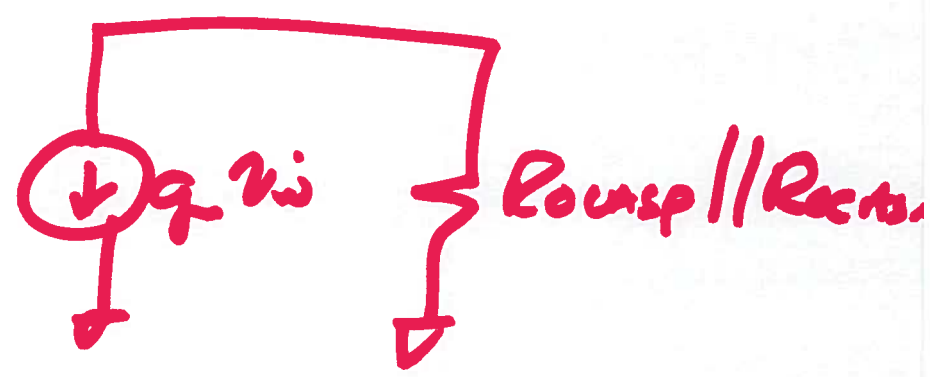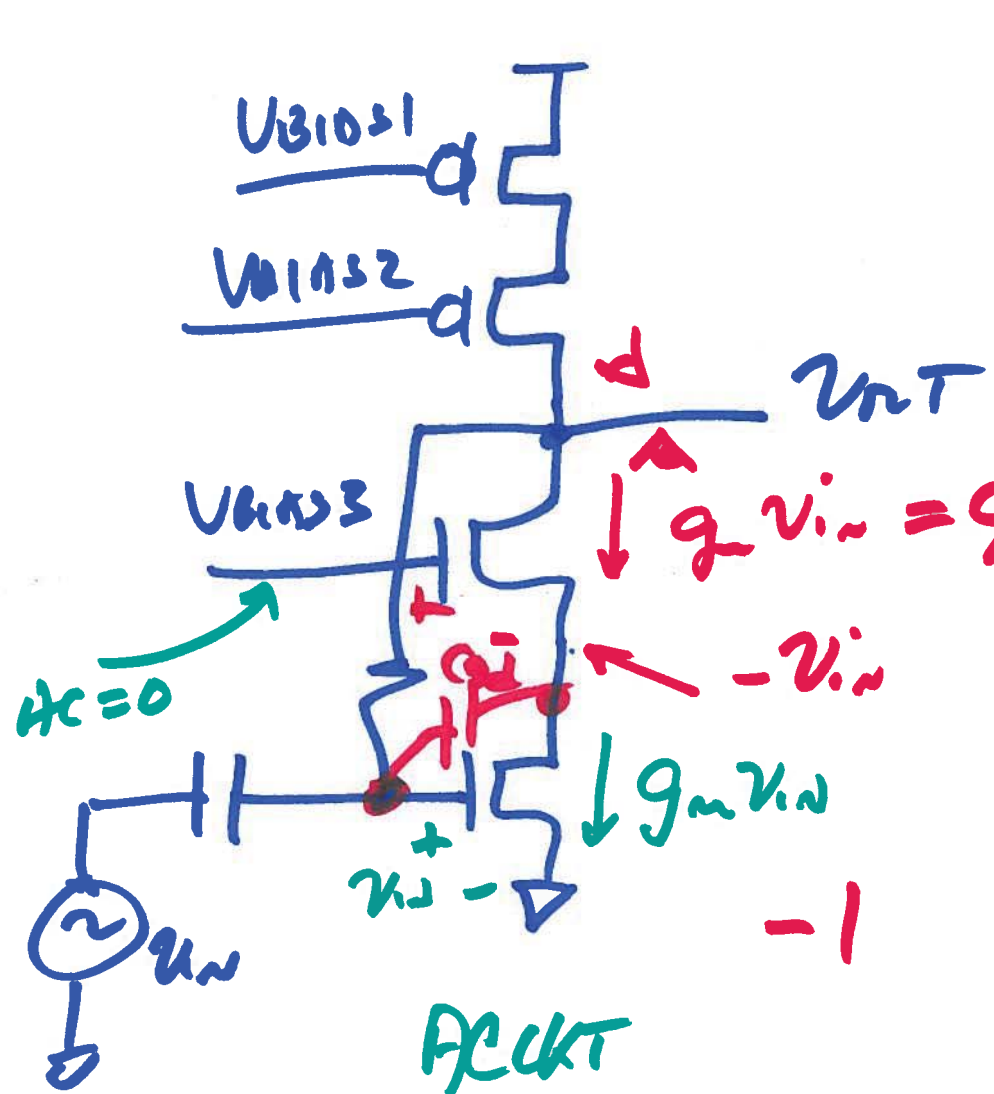

$$g_m v_{in} = g_m v_{gs} = g_m (0 - (-v_{in}))$$

$$\frac{v_{out}}{v_{in}} = -g_m (R_{comp} || R_{out})$$


6)

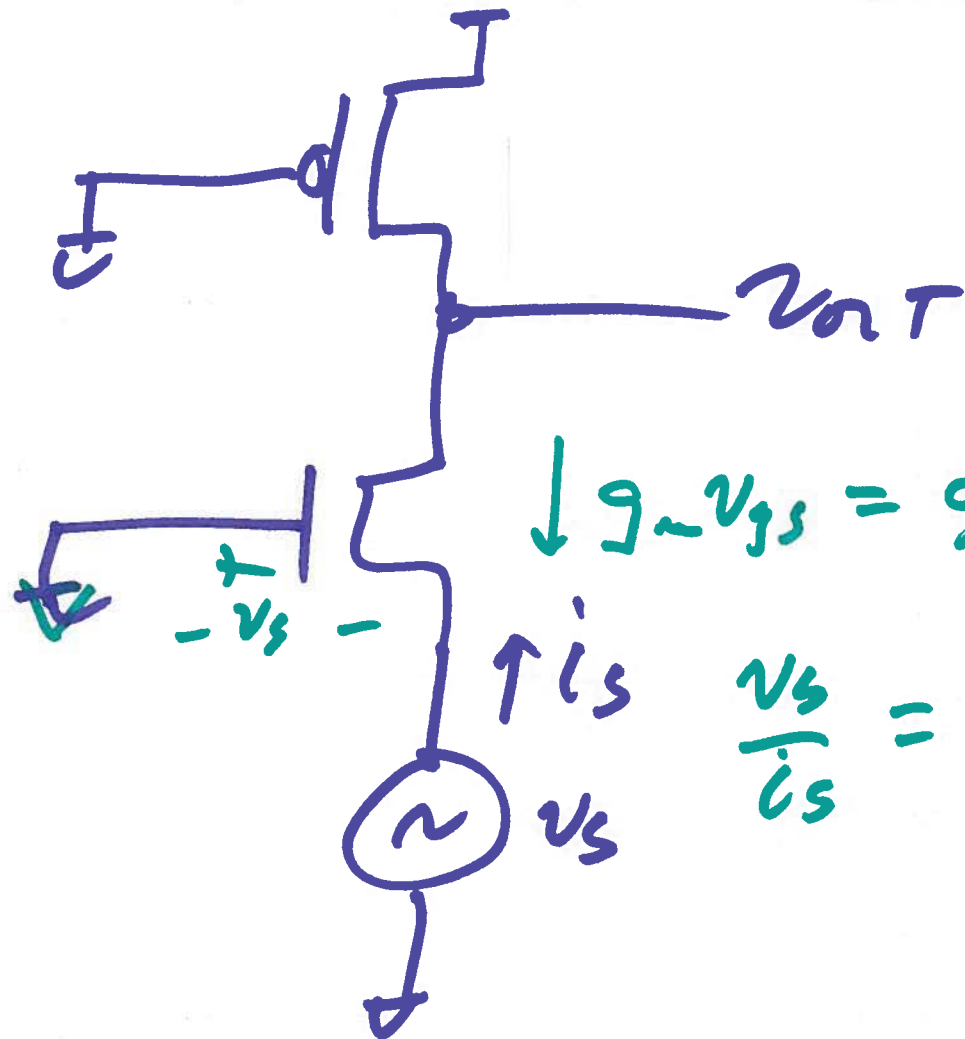

$$\downarrow g_m v_{gs} = g_m (0 - v_s) = -i_s$$

$\uparrow i_s$
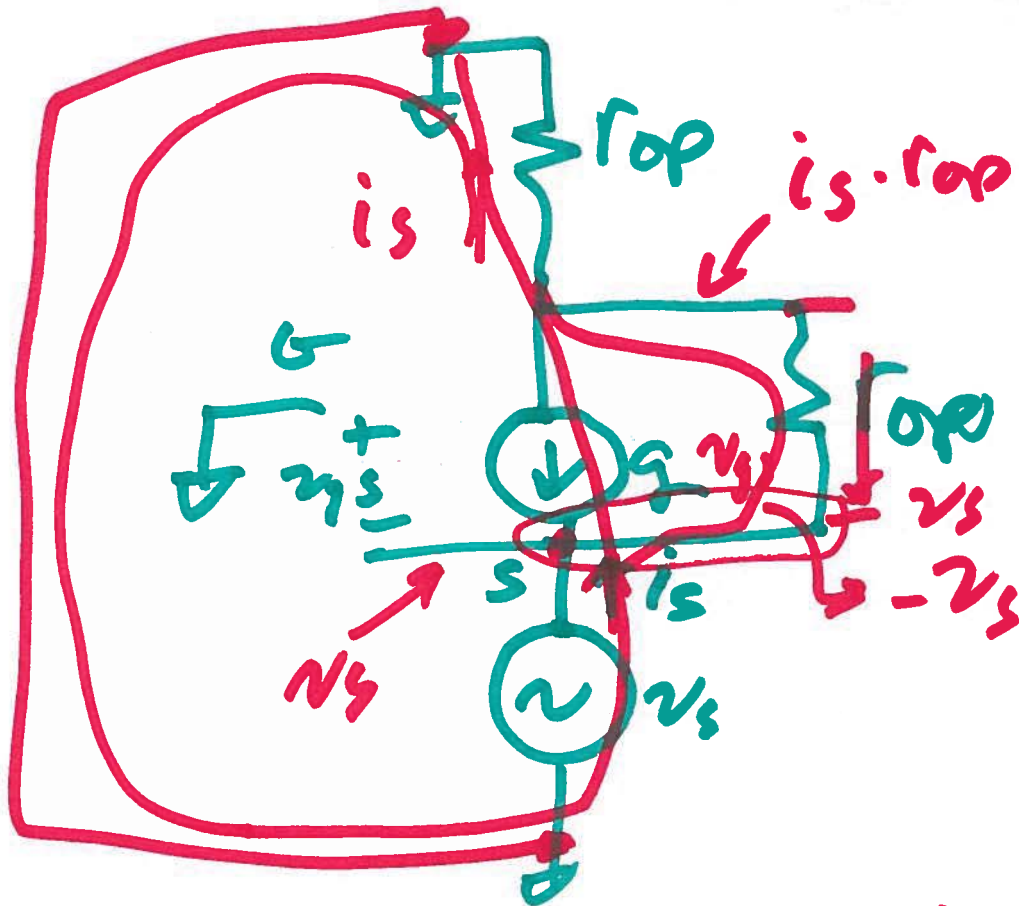
$$\frac{v_s}{i_s} = \frac{-1}{g_m} = \boxed{\frac{1}{g_m}}$$



$$i_s = -g_m(-v_s)$$

$$\frac{v_s}{i_s} = \frac{r_{ON} + r_{OP}}{1 + g_m \cdot r_{ON}} = \frac{1 + \frac{r_{OP}}{r_{ON}}}{\frac{1}{r_m}}$$

$$i_s + g_m(-v_s) + \frac{i_s \cdot r_{OP} - v_s}{r_{OP}}$$

$$= 0 \quad \left[\approx \frac{2}{g_m} \right]$$

$$(r_{ON} + r_{OP}) i_s = v_s (1 + g_m r_{ON})$$