


EE 420 / ECG 620

Analog IC Design

April 15, 2019

Lecture 19


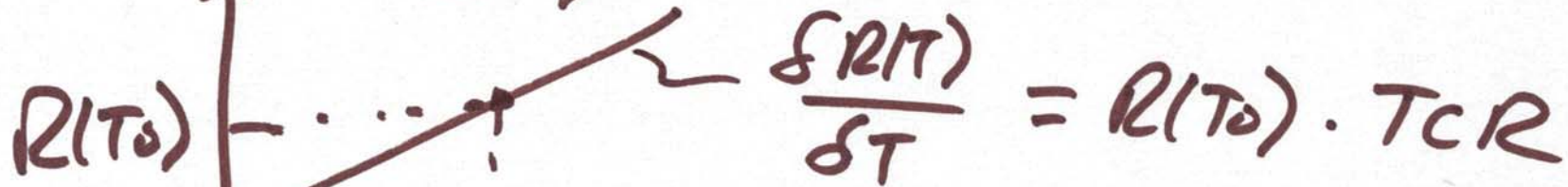
$$R(T) = \frac{R(T_0)}{R(T_0)} (1 + TCR(T - T_0))$$



$$TCR = \frac{1}{R(T_0)} \cdot \frac{\delta R}{\delta T}$$


$$0.002 = 2,000 \text{ ppm}/^\circ\text{C}$$

$$\text{ppm} = 10^{-6}$$

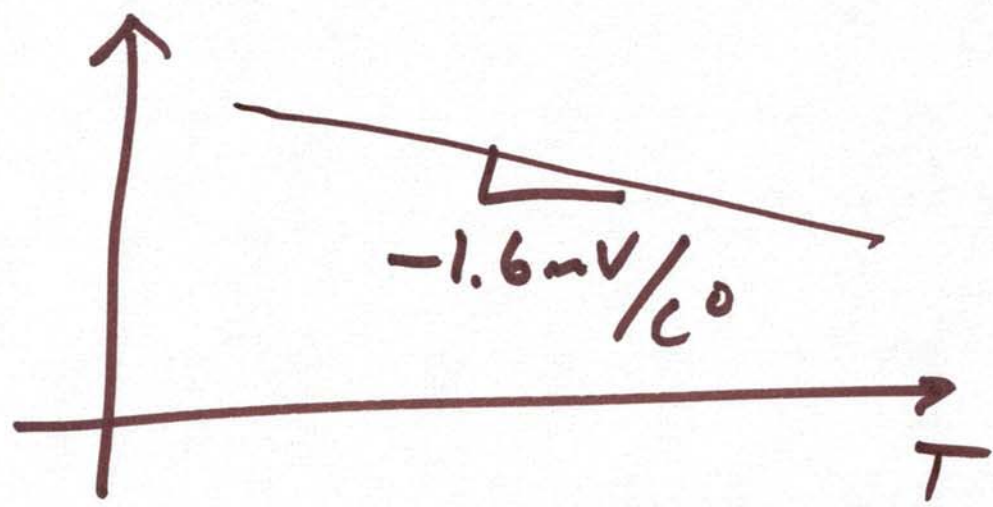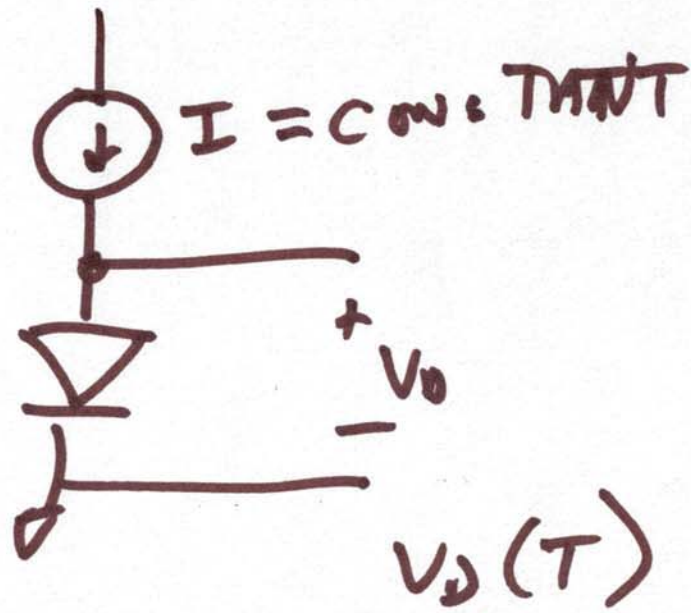

2)

BM R
Temp
behavior

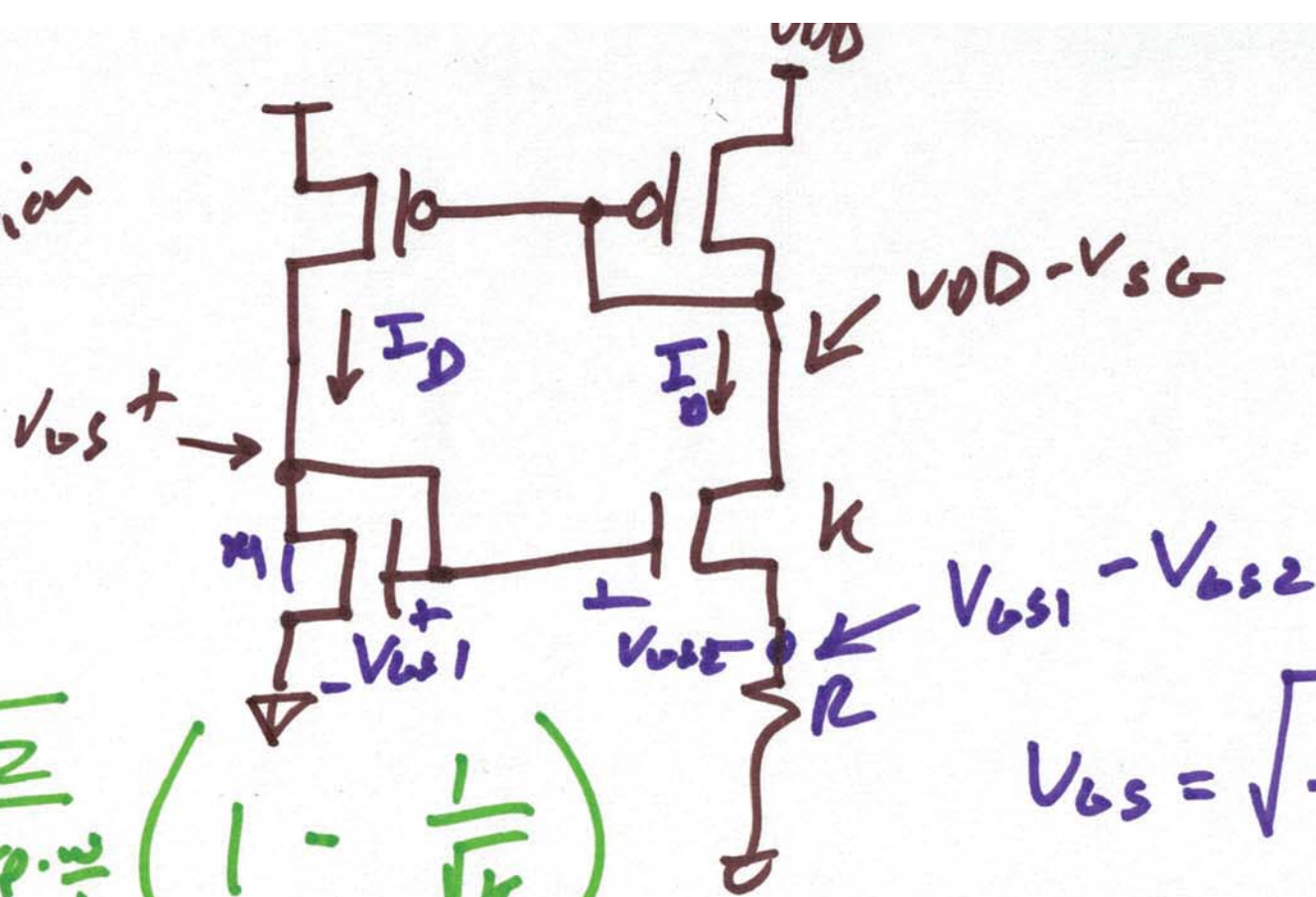

$$\sqrt{I_D} = \frac{1}{R} \sqrt{\frac{2}{k \cdot \frac{W}{L}}} \left(1 - \frac{1}{\sqrt{k}} \right)$$

$$I_D = \frac{2}{R^2 k \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{k}} \right)^2 \sqrt{I_D} =$$

$$V_{GS} = \sqrt{\frac{2 I_D}{k \cdot \frac{W}{L}}} + V_{THN}$$

$$\sqrt{\frac{2 I_D}{k \cdot \frac{W}{L}}} - \sqrt{\frac{2 I_D}{k \cdot \frac{W}{L}}}$$

R

$$I_0 = \frac{2}{R^2 \cdot k_P \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{\alpha}}\right)^2$$

$$\text{let } X = \frac{2}{\frac{W}{L}} \left(1 - \frac{1}{\sqrt{\alpha}}\right)^2$$


$$I_0 = R^{-2} \cdot k_P^{-1} \cdot X$$

$$\frac{\delta I_0}{\delta T} = X \left(-2 R^{-3} \frac{\delta R}{\delta T} \cdot k_P^{-1} + \left[R^{-2} \cdot (-1) k_P^{-2} \frac{\delta k_P}{\delta T} \right] \right)$$

$$= X \cdot R^{-2} \cdot k_P^{-1} \left(-2 \cdot \frac{1}{R} \frac{\delta R}{\delta T} - \frac{1}{k_P} \frac{\delta k_P}{\delta T} \right)$$


$$TCI = \frac{1}{I_0} \frac{\delta I_0}{\delta T} = \underbrace{\frac{2}{R/LKP} \left(1 - \frac{1}{V\alpha}\right)^2}_{I_0} \underbrace{\left(-2 \frac{1}{R} \frac{\delta R}{\delta T} - \frac{1}{KP} \frac{\delta KP}{\delta T}\right)}_{TCR} = I_0 \cdot TCI$$
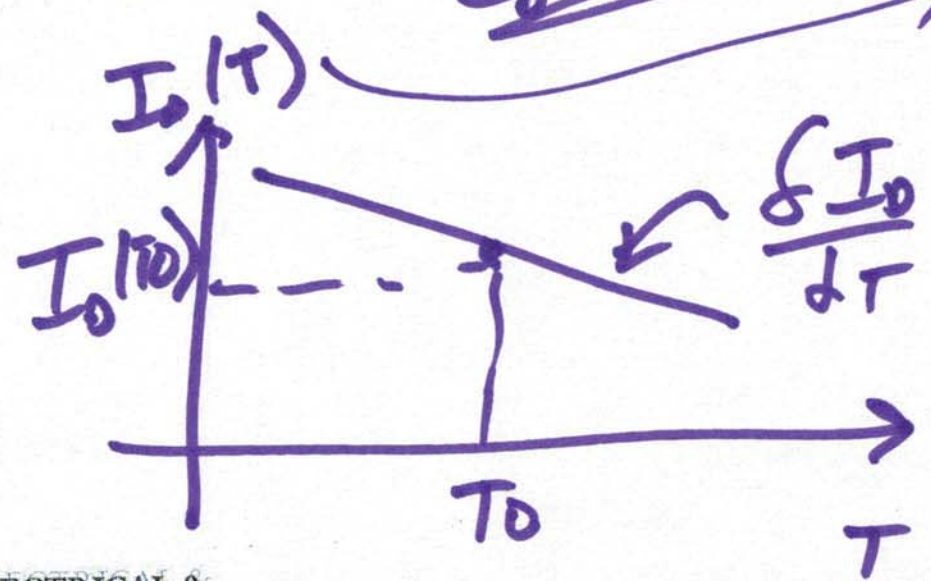
$$I_0(T) = \frac{\delta I_0}{I_0} I_0(T_0) (1 + TCI \cdot (T - T_0))$$



$$TCI = \frac{1}{I_0} \frac{\delta I_0}{\delta T}$$

5)

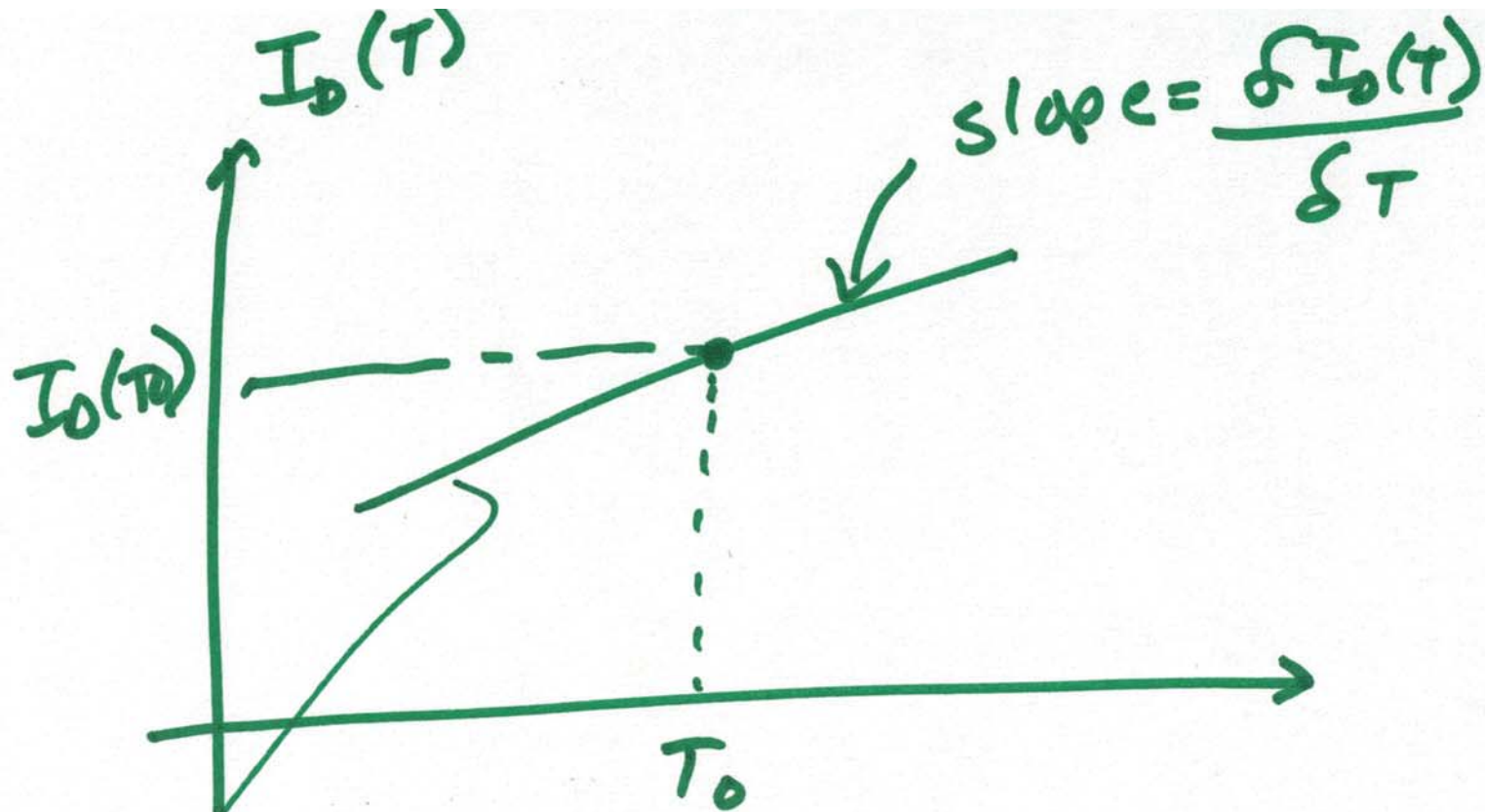

$$I_D(T) = I_D(T_0) (1 + TCI(T - T_0))$$

$$TCI = \frac{1}{I_0} \frac{\delta I_0}{\delta T}$$

$$= I_D(T_0) + TCI \cdot I_D(T_0) \cdot T$$

$$\frac{\delta I_D(T)}{\delta T} = TCI \cdot I_D(T_0) + TCI \cdot I_D(T_0) \cdot T_0$$

$$TCI = \left(-2 \cdot TCR + \left(\frac{+1.5}{T} \right) \right)$$


$$TCR = \frac{0.002}{C^{\circ}} = 2,000 \text{ ppm}/C^{\circ}$$

$$T = 300^{\circ} K \cdot 0.005 = \frac{1.5}{300} = 5,000 \text{ ppm}$$

$$TCI = (-0.004 + 0.005)$$

$$TCI = 1,000 \text{ ppm}/C^{\circ}$$
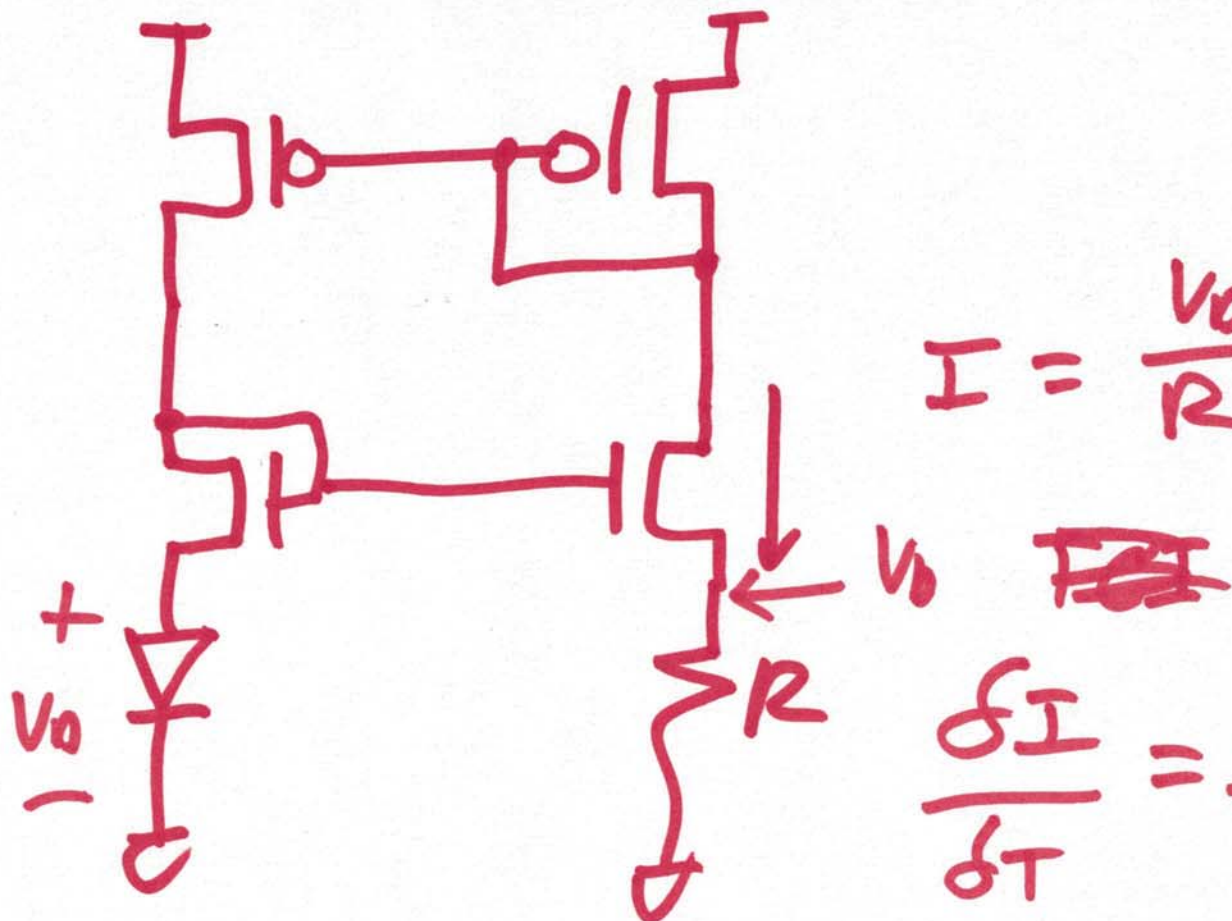
$$I = I(T_0) \left(1 + 0.001(T - T_0) \right)$$



$$I = \frac{V_0}{R} = V_0 \cdot R^{-1}$$


$$\frac{\delta I}{\delta T} = \frac{\delta V_0}{\delta T} \cdot R^{-1}$$


TCI

$$\frac{1}{I} \cdot \frac{\delta I}{\delta T} = \frac{R}{V_0} \left(\frac{1}{R} \frac{\delta V_0}{\delta T} + \left(-1 \cdot R^{-2} V_0 \cdot \frac{dR}{dT} \right) \right)$$

$$TCI = \frac{1}{I} \frac{\delta I}{\delta T} = \left(\frac{1}{V_D} \frac{\delta V_D}{\delta T} - \frac{1}{R} \frac{\delta R}{\delta T} \right)$$
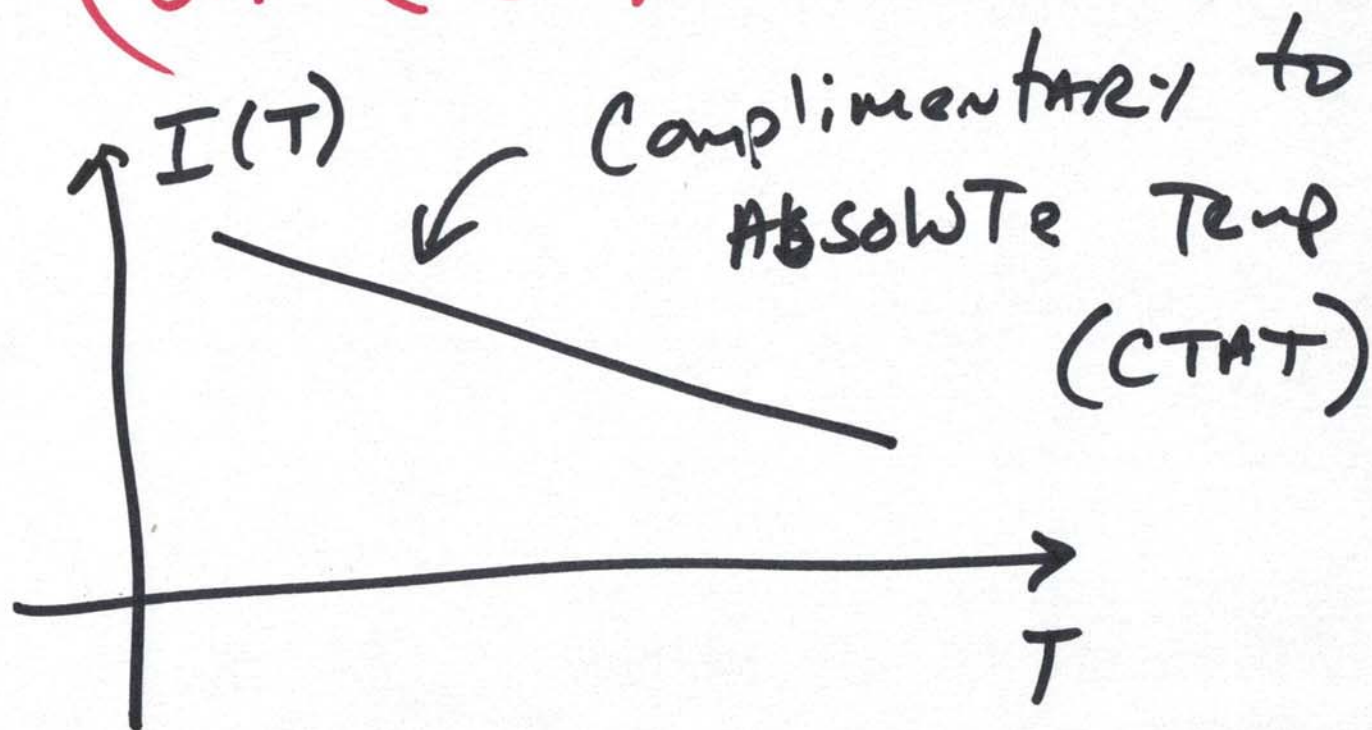
$$TCI = \left(\frac{1}{0.7} \left(\frac{-1.6 \text{ mV}}{C_0} \right) - TCR \right)$$



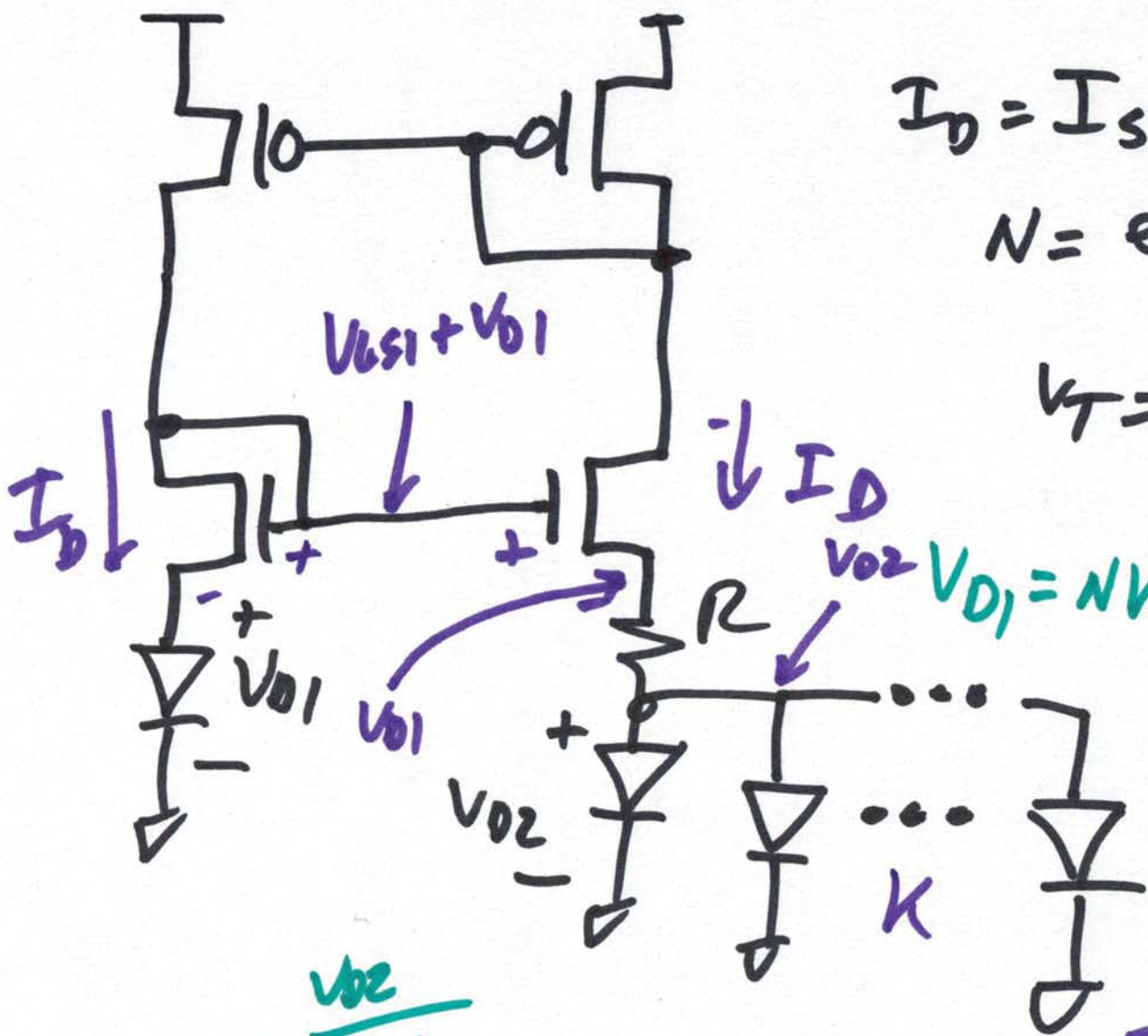

$$I_D = I_S e^{V_D / nV_T}$$

$n =$ emission coefficient

$V_T = \frac{kT}{q} =$ thermal voltage

$$V_{D1} = nV_T \ln \frac{I_D}{I_S}$$

$$I_D = K \cdot I_S e^{\frac{V_{D2}}{nV_T}}$$

$$V_{D2} = nV_T \ln \frac{I_D}{KI_S}$$

$$I_D = \frac{V_{D1} - V_{D2}}{R}, \quad I_{n a} - I_{n b} = I_{n \frac{a}{b}}$$

$$= \frac{N V_T R \frac{I_D}{I_S} - N V_T R \frac{I_D}{k I_S}}{R}$$

$$I_D = \frac{N V_T I_{n k}}{R}$$

$$N = 1$$

$$V_T = 25 \text{ mV}$$

$$k = 8$$

$$R = 10 \text{ k}\Omega$$


$$I_D = \frac{25 \cdot 50 \mu\text{V}}{10 \text{ k}\Omega}$$

$$= 5 \mu\text{A}$$

$$\underline{I_D} = N V_T R^{-1} \ln K$$

$$\frac{\delta I_D}{\delta T} = N \frac{\delta V_T}{\delta T} \cdot R^{-1} \ln K +$$

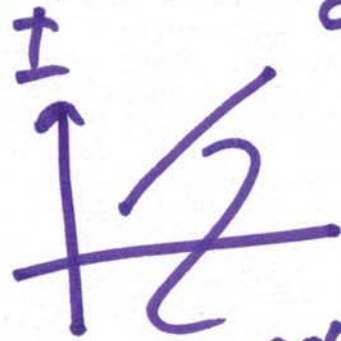
$$\frac{\delta I_D}{\delta T} \approx N V_T (-1) R^{-2} \cdot \frac{\delta R}{\delta T} \cdot \ln K$$



proportional
to
Absolute
temp

$$(PTAT) \quad V_T = \frac{KT}{q}, \quad \frac{\delta V_T}{\delta T} = \frac{K}{q} = 0.085 \frac{mV}{^\circ C}$$
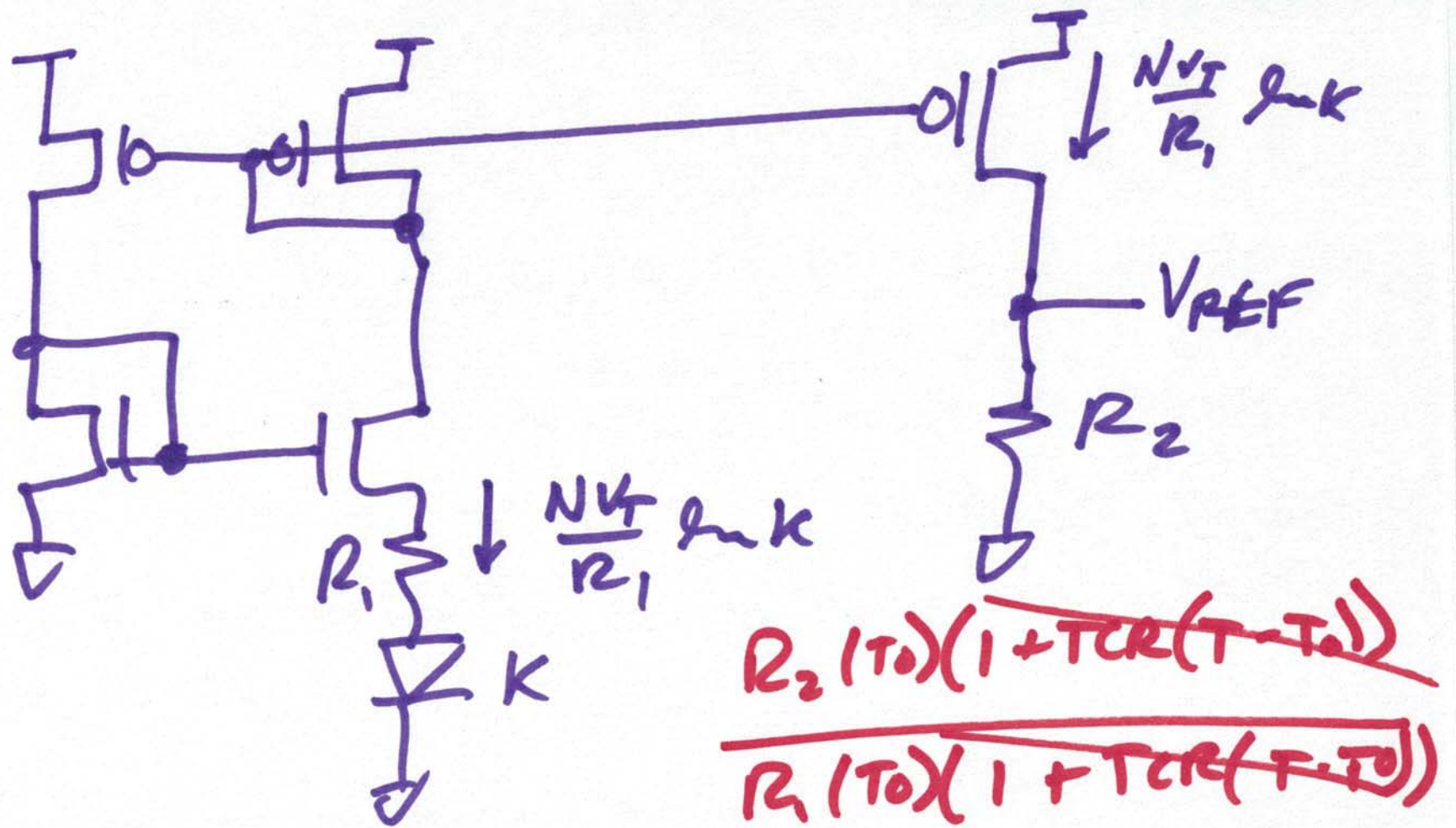
$$\left(\overset{\text{pos}}{\frac{1}{V_T} \frac{\delta V_T}{\delta T}} + \overset{\text{neg}}{-\frac{1}{R} \frac{\delta R}{\delta T}} \right)$$



$$V_{REF} = NV \frac{R_2}{R_1} \ln k$$