

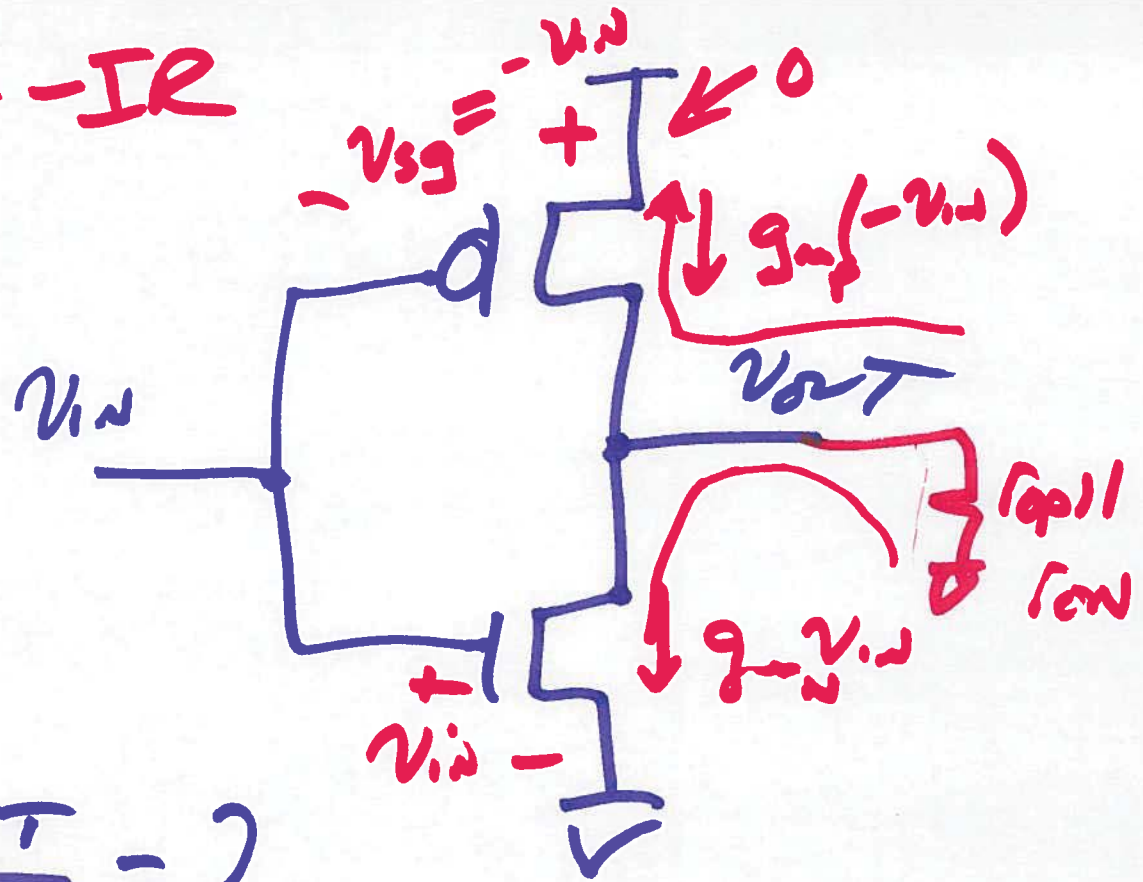
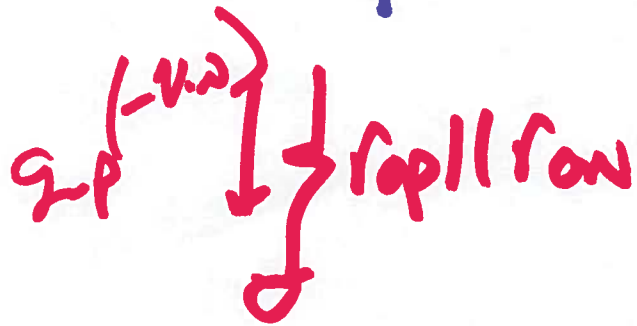


2)

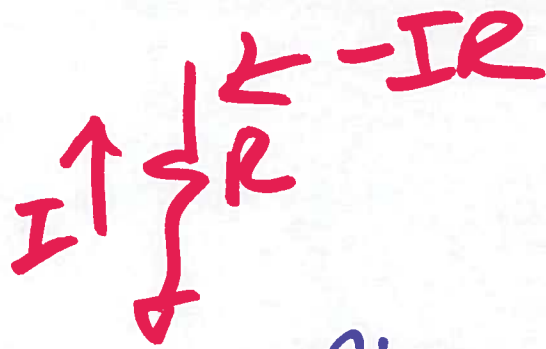


$$\frac{v_{out}}{v_{in}} = (g_{mN} || r_{on} || r_{op}) \frac{v_{out}}{v_{in}} = ?$$

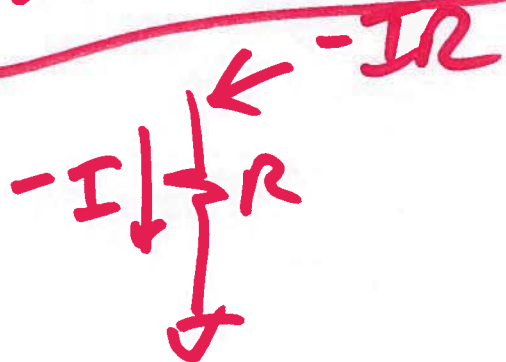

$$v_{out} = -(\cancel{I_{in}})$$

$$-(g_{mN} + g_{mP}) v_{in} \cdot r_{op} || r_{on}$$

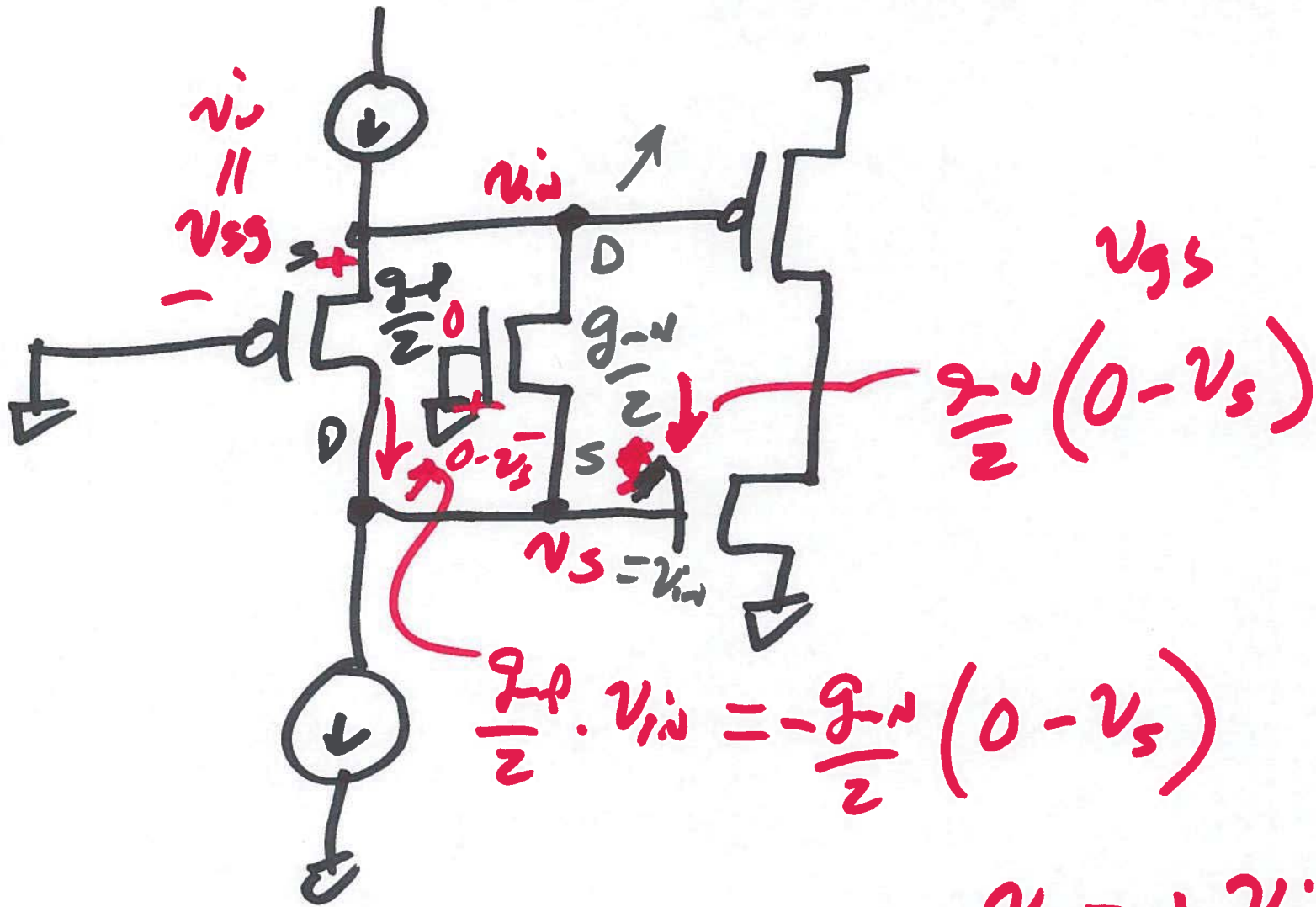


$$\frac{g_{m,p}}{2} \cdot V_{in} = -\frac{g_{m,n}}{2} (0 - V_s)$$


$$V_s = +V_{in}$$

assuming $\frac{g_{m,p}}{2} = \frac{g_{m,n}}{2}$

4)

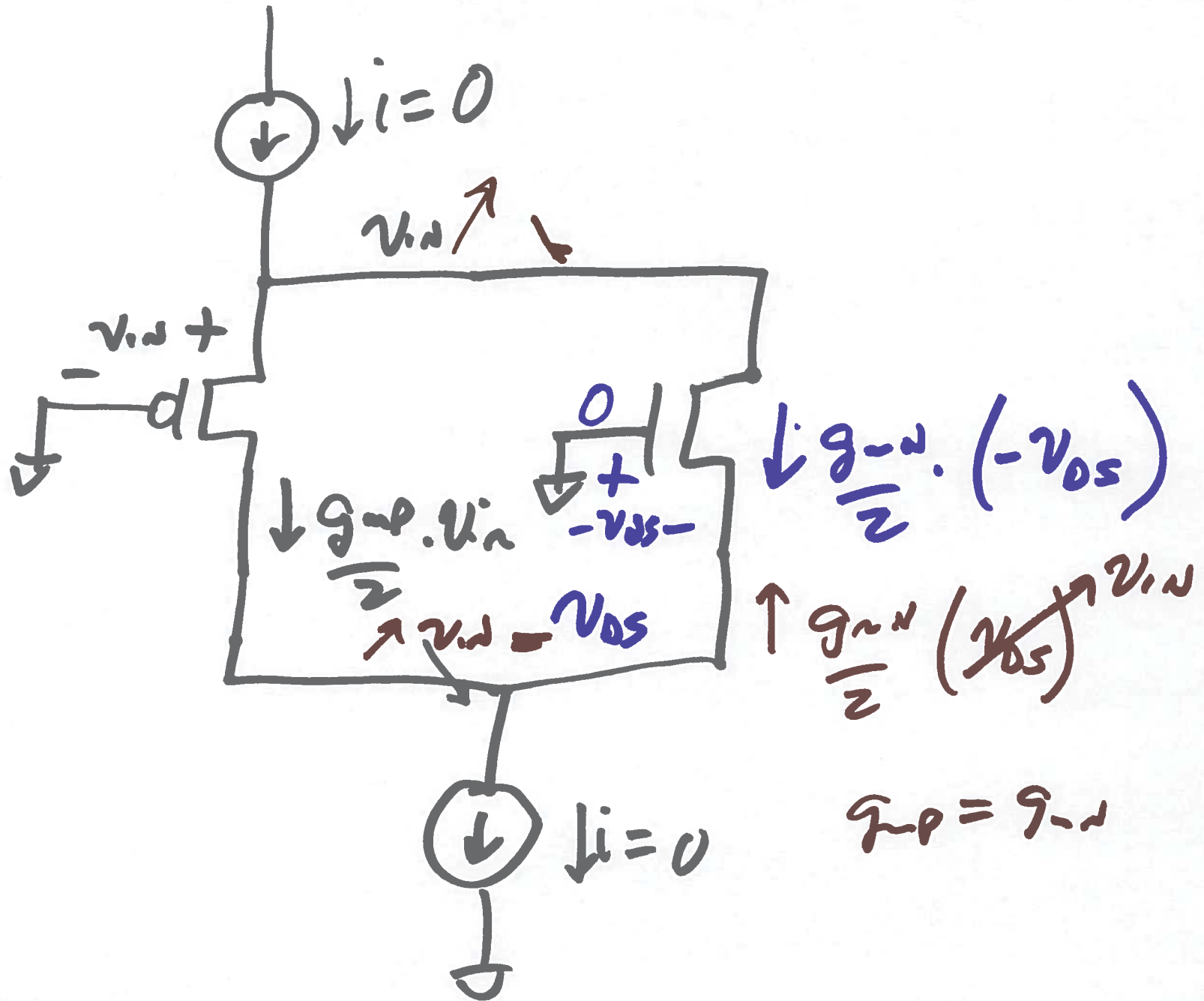

5)

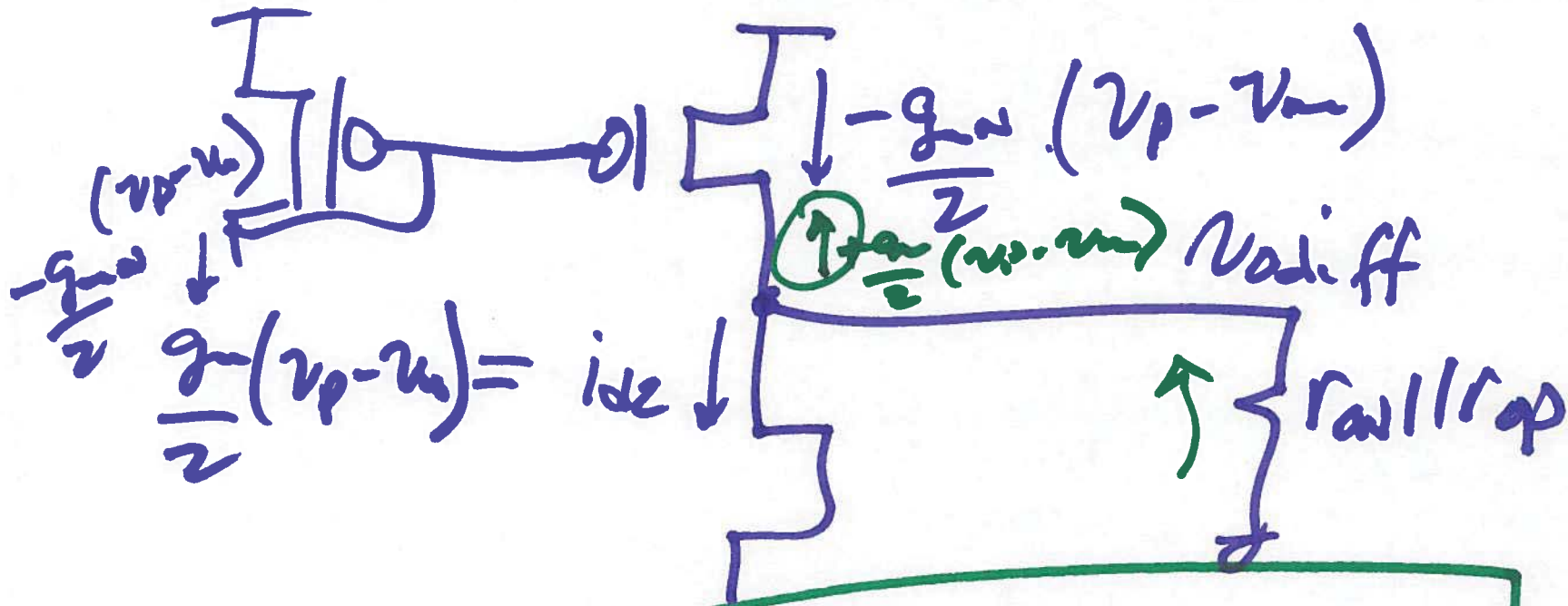


$$\frac{v_{odiff}}{v_p - v_m} = g_m (r_o || r_{op})$$

7)

$$K \cdot g_m = \frac{K_P \cdot W \cdot K}{L} \cdot V_{OV}$$

$$= \frac{K_P \cdot W \cdot K}{L} \cdot (V_{DS, SAT}) =$$
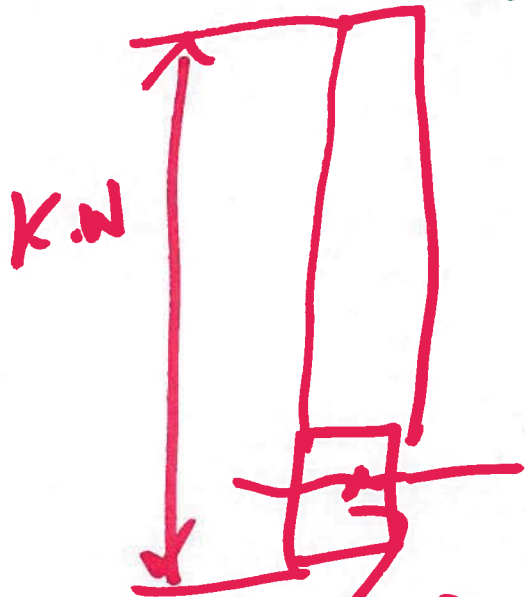
$$\frac{K_P \cdot W \cdot K}{L} \cdot (V_{DS} - V_{THN})$$




$$I_{D, new} = k \cdot I_{D, old}$$



$$r_{on} = \frac{1}{\lambda I_D}$$

$$r_{on} \downarrow k$$


$$g_m \cdot r_{on} = \text{const.}$$

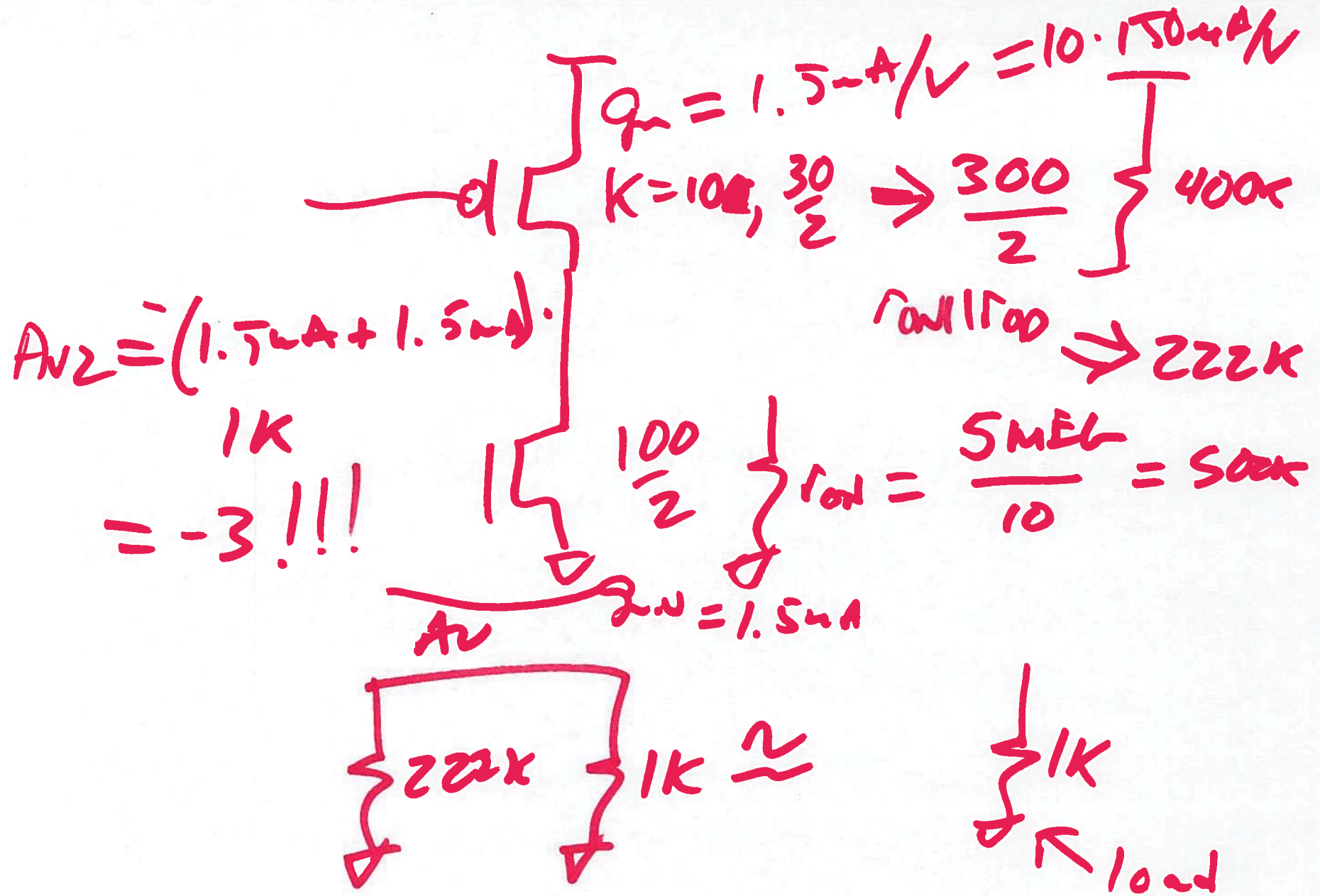

9)

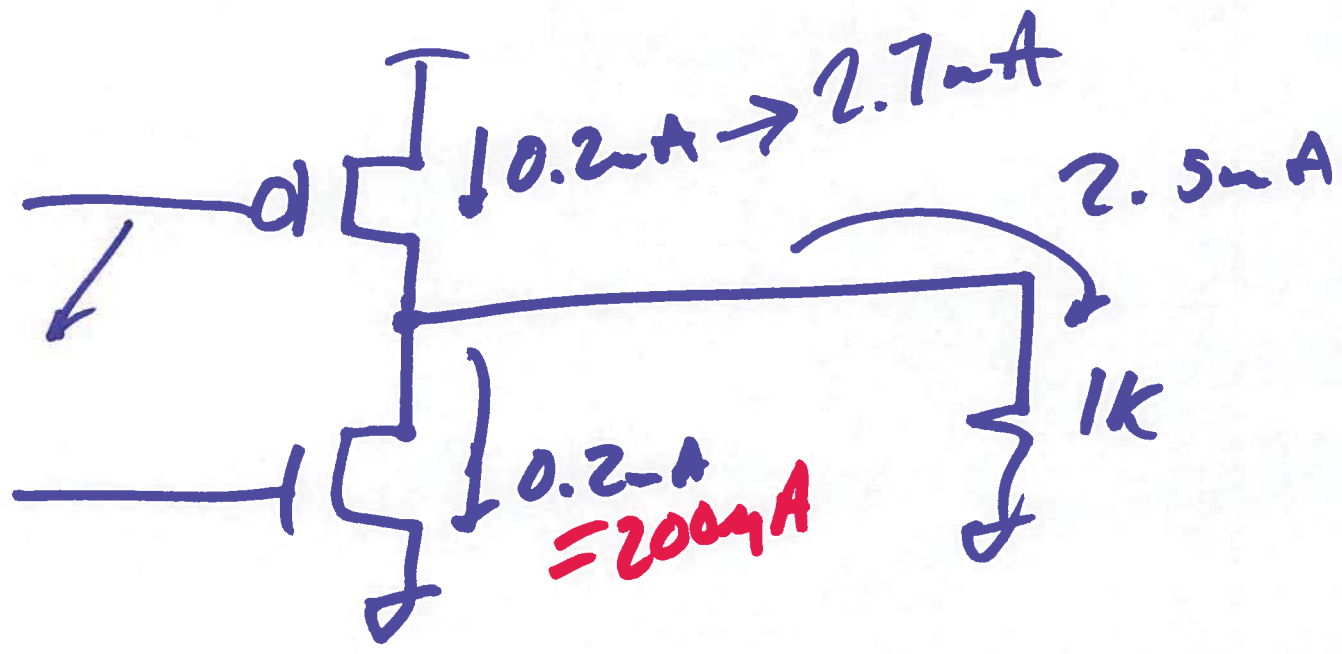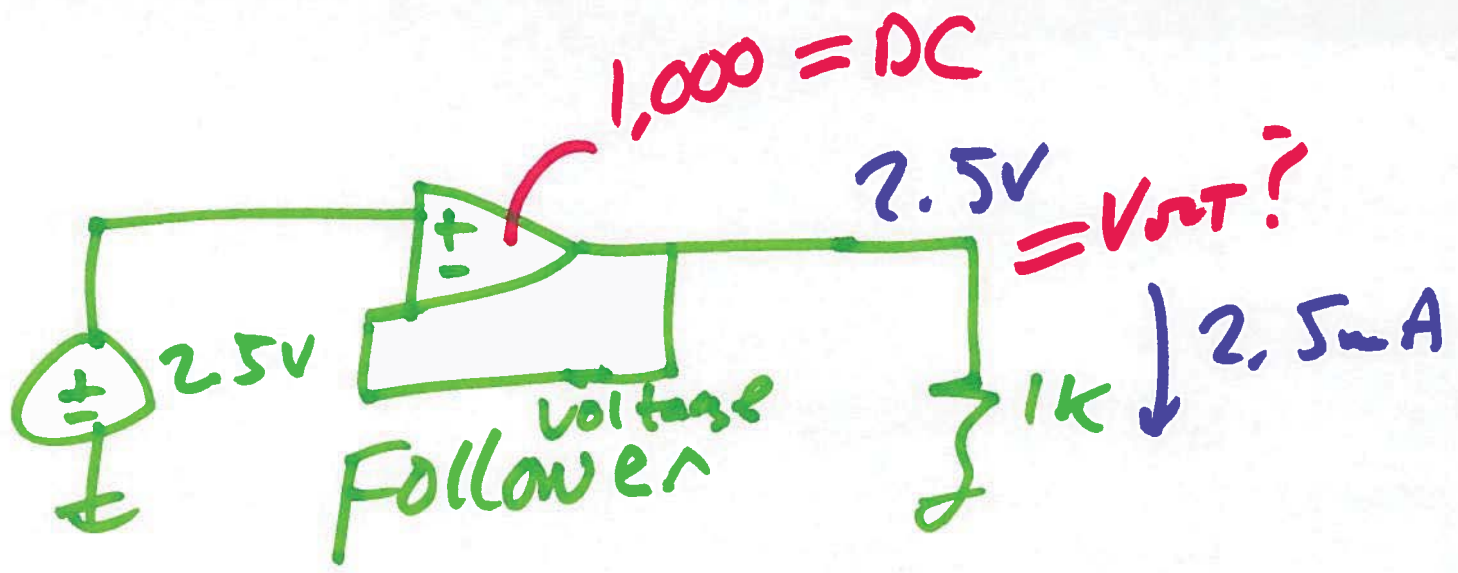

10)

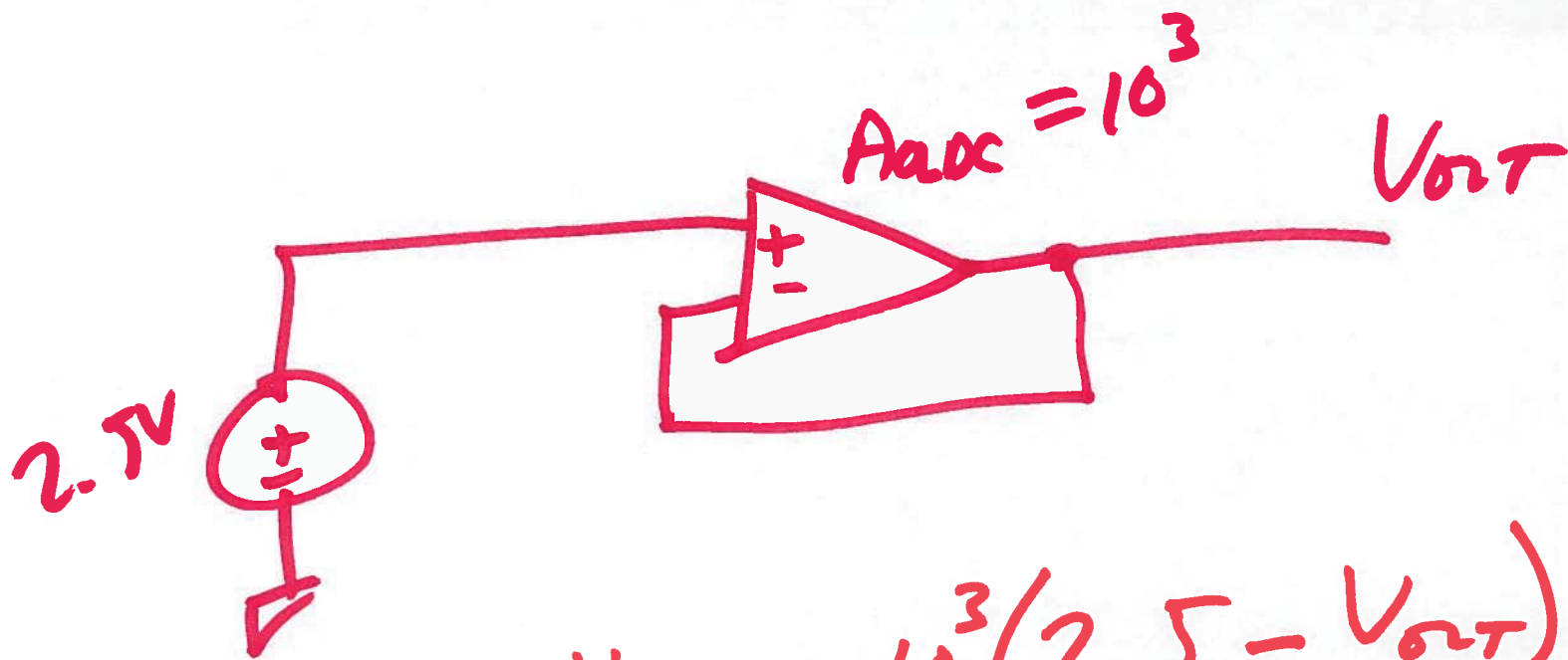

$$V_{OUT} = 10^3 (2.5 - V_{OUT})$$

$$V_{OUT} = 2,500 - 1,000 V_{OUT}$$

$$V_{OUT} = \frac{2,500}{1,001} = 2.499 \text{ V}$$