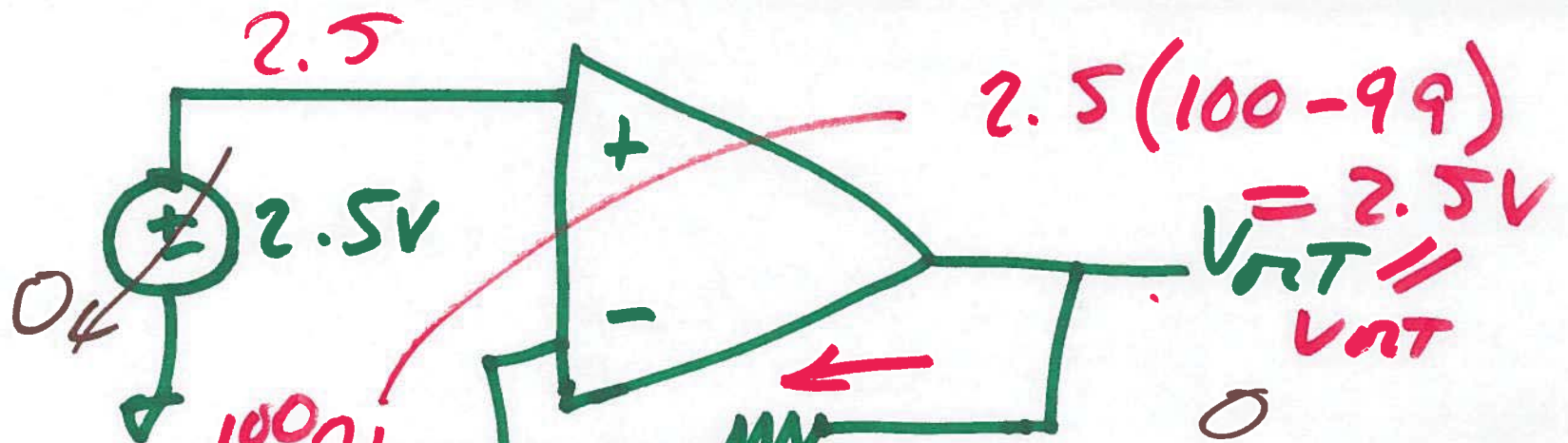


$$\begin{aligned}
 V_{OUT} &= A_{OL} \cdot (V_P - V_N) \\
 &= A_{OL} \cdot (V_{OS} - V_{OUT}) = \text{finite}
 \end{aligned}$$



$$V_{out} = (2.5) - 99 \cdot 2.5$$

$$\frac{V_{out} - v_{in}}{99k} = \frac{v_{in} - 2.5}{1k}$$


$$0 = 2.5 - \frac{v_{out}}{100} - 99 \cdot 2.5$$

$$v_{out} - v_{in} = 99(v_{in} - 2.5)$$

$$v_{out} = A_{OL} \left(2.5 - \frac{v_{out}}{100} - \frac{99 \cdot 2.5}{100} \right) - v_{in}$$


$$v_{out} + 99 \cdot 2.5 = 100 \cdot 2.5$$

4)

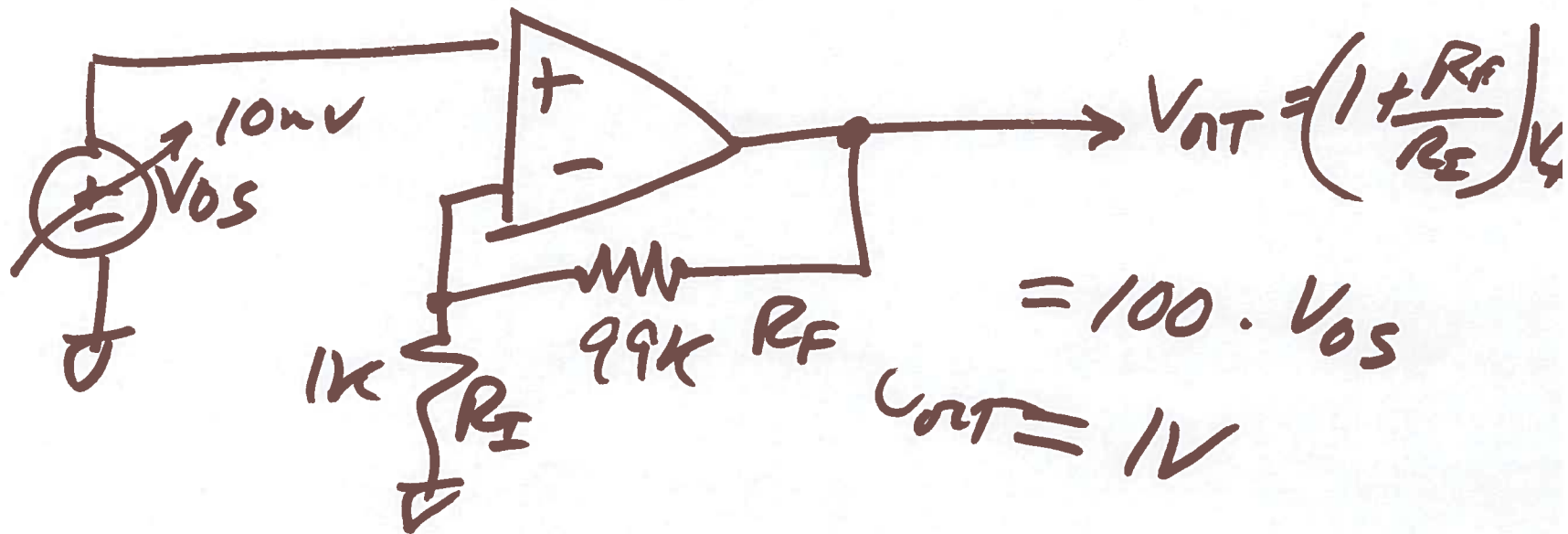

5)

$$CMRR = \frac{A_d}{A_c} = \frac{g_m(r_{o1} || r_{o2})}{A_c}$$

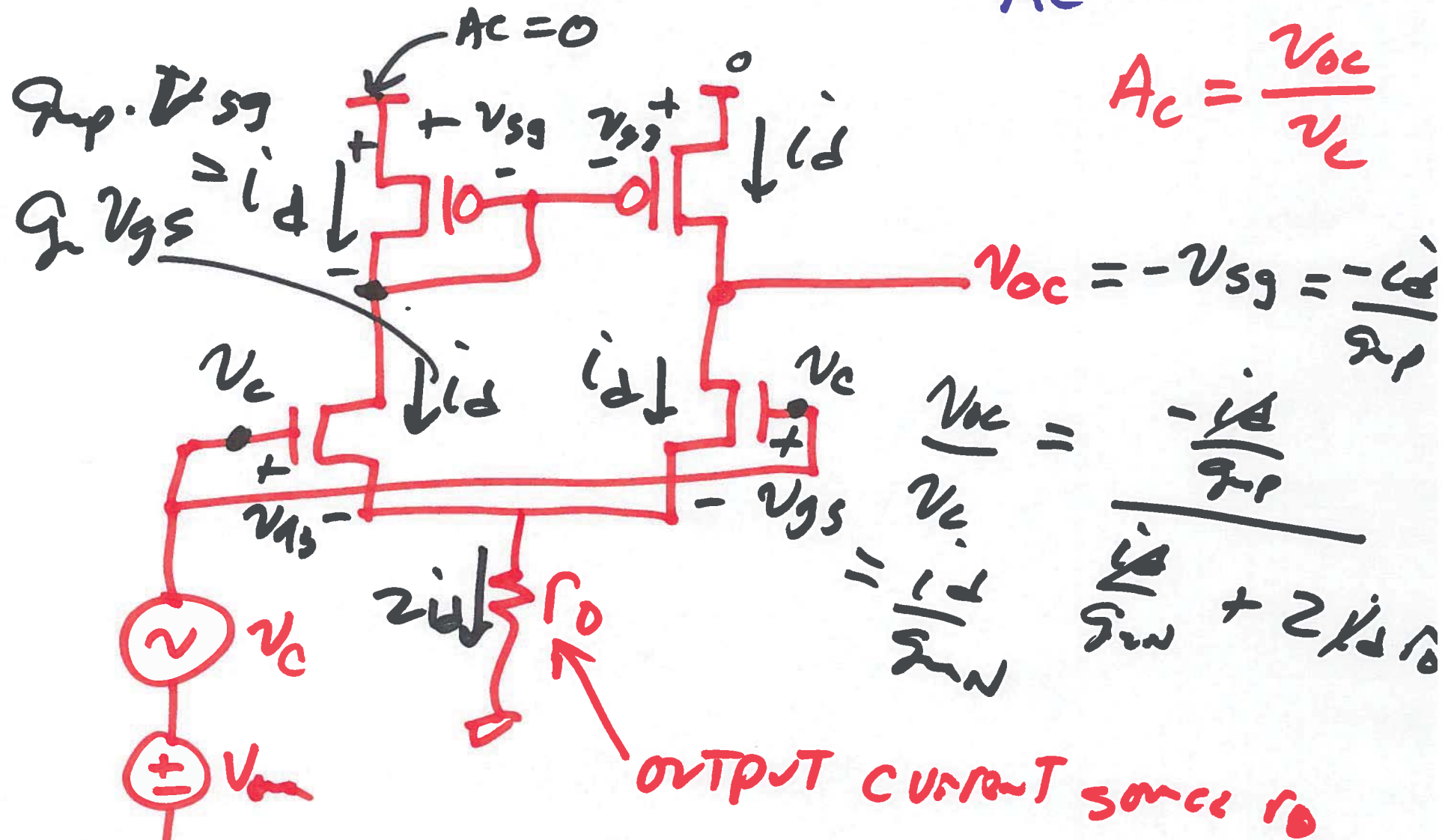

6)



$$A_c = \frac{v_{oc}}{v_c} = \frac{-\frac{1}{g_{mP}}}{\frac{1}{g_{mN}} + 2r_o}$$

$$\approx -\frac{\frac{1}{g_{mP}}}{2r_o}$$


MAXIMIZE r_o
 (OUTPUT RESISTANCE)
 OF CURRENT BIAS
 OF DIFFAMP

$$CMRR = 20 \log \left| \frac{-\frac{1}{g_{mP} \cdot 2r_o}}{\frac{1}{g_{mN} \cdot r_{oN} || r_{oP}}} \right|$$


7)

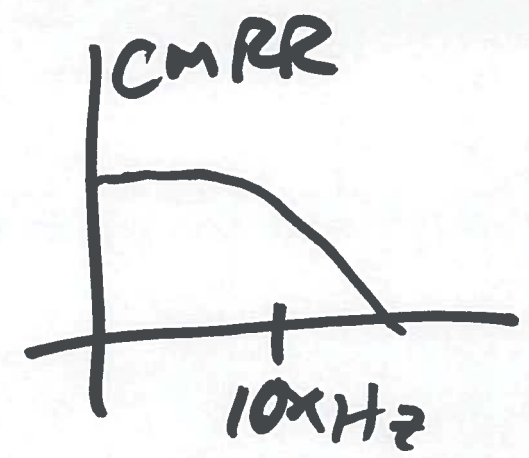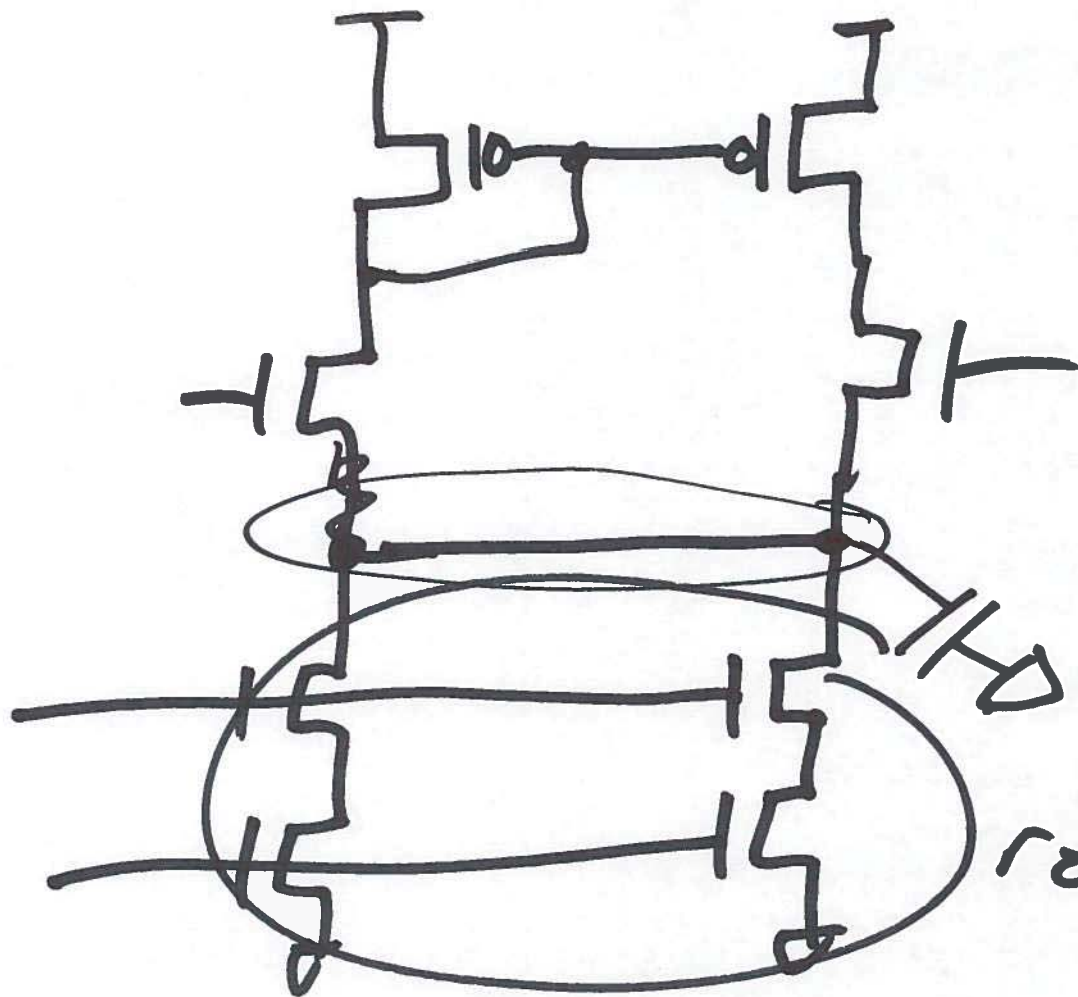

$$|z| \ll r_o$$

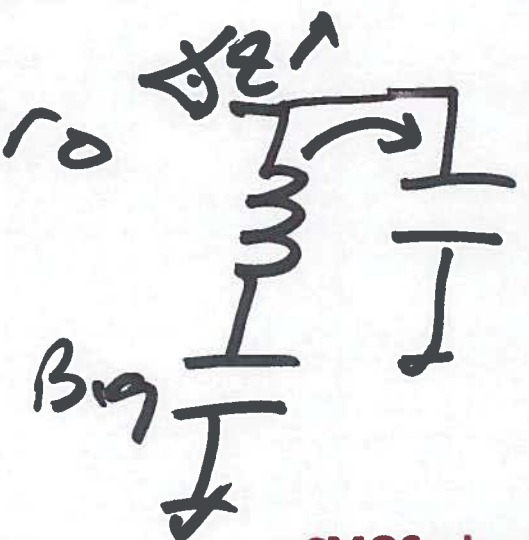

8)

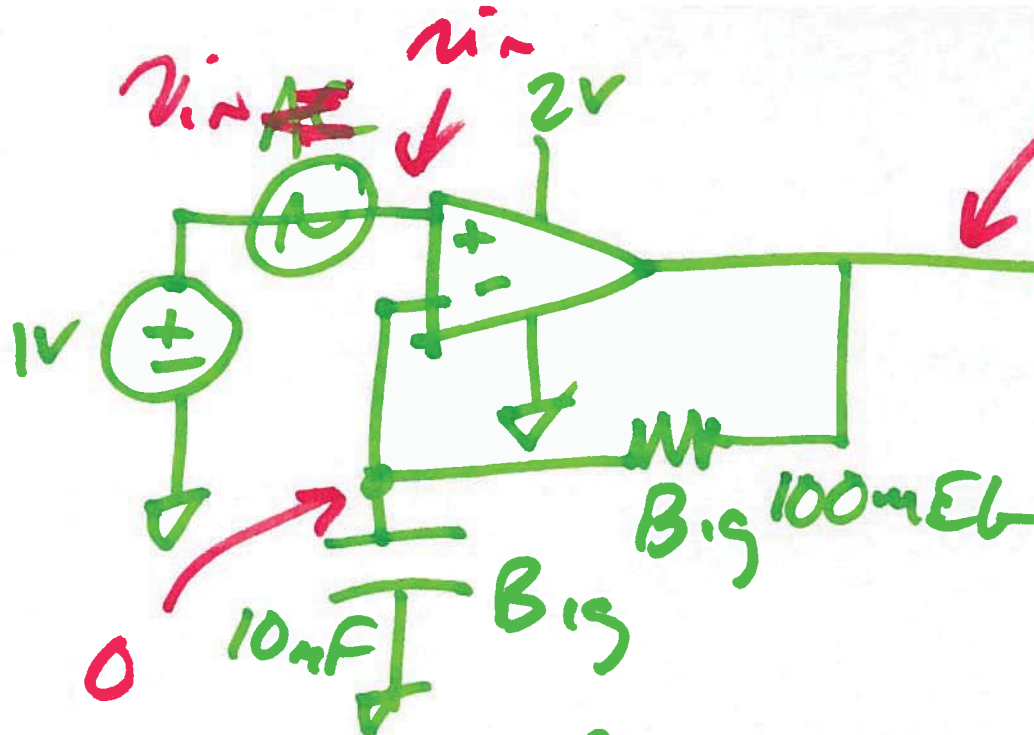

$$A_{OL} \cdot v_{in} = 2mV$$

$$1V \cdot$$

$$\Rightarrow A_{OL} = AC \cdot g_{M2}$$

$$\tau = 100mE6 \cdot 10nF = 1,000 \text{ seconds}$$

9)