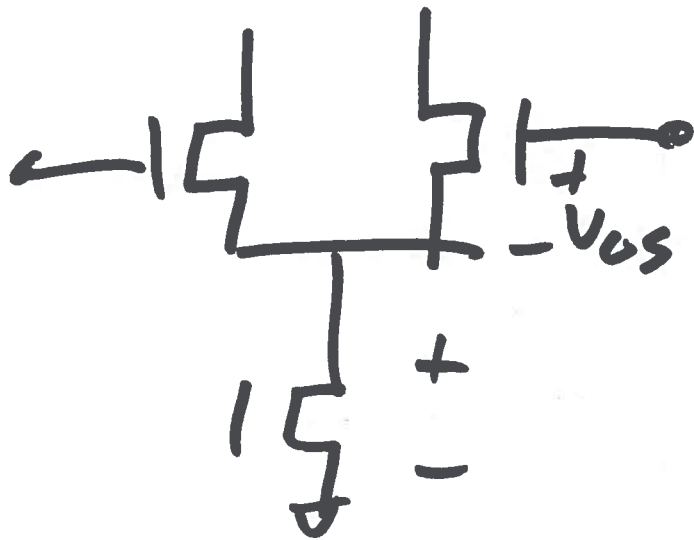


EE 420 / ECG-620


Analog IC Design

April 29, 2019


Lecture 23



Folded - Cascode

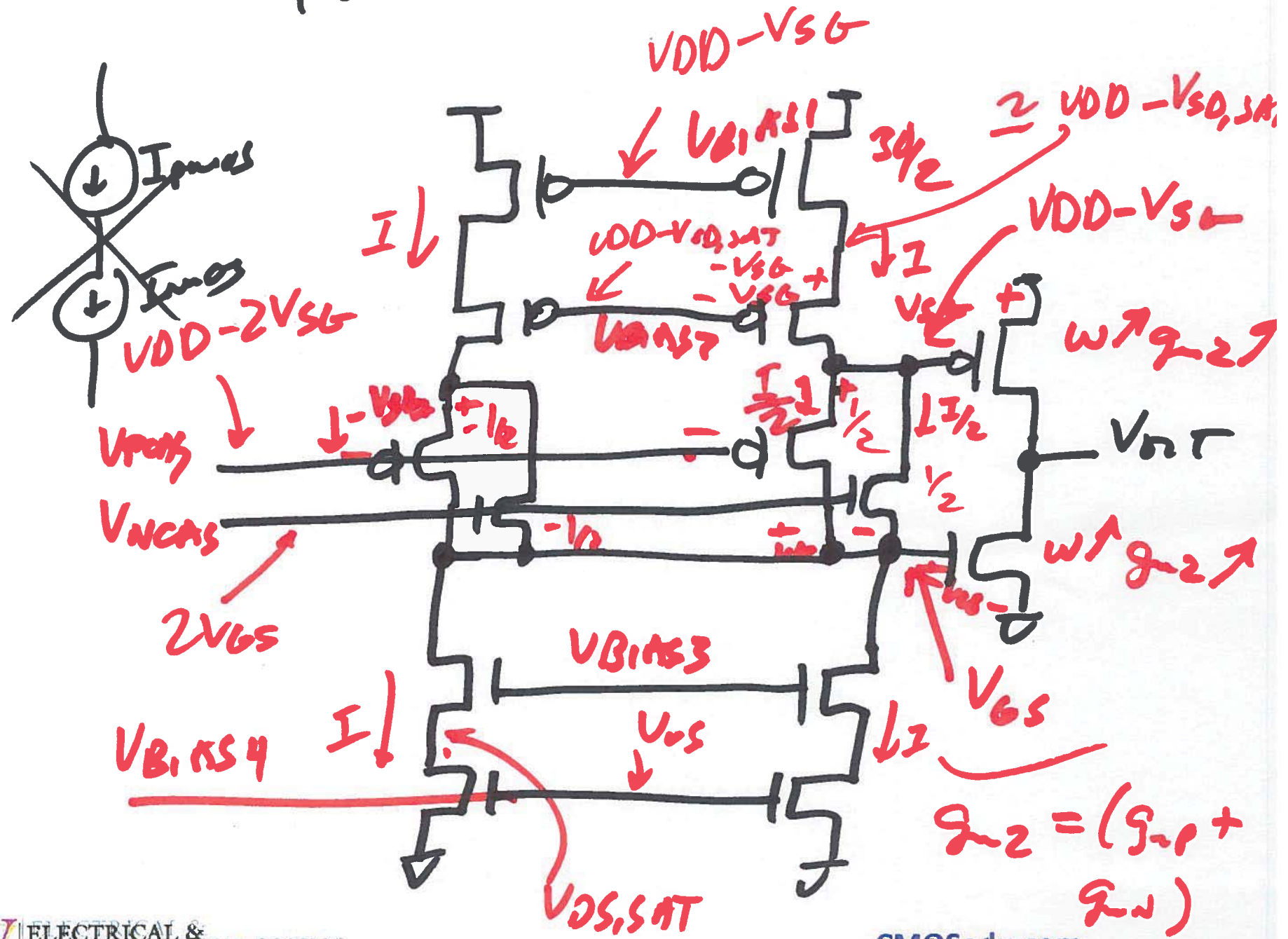

2)

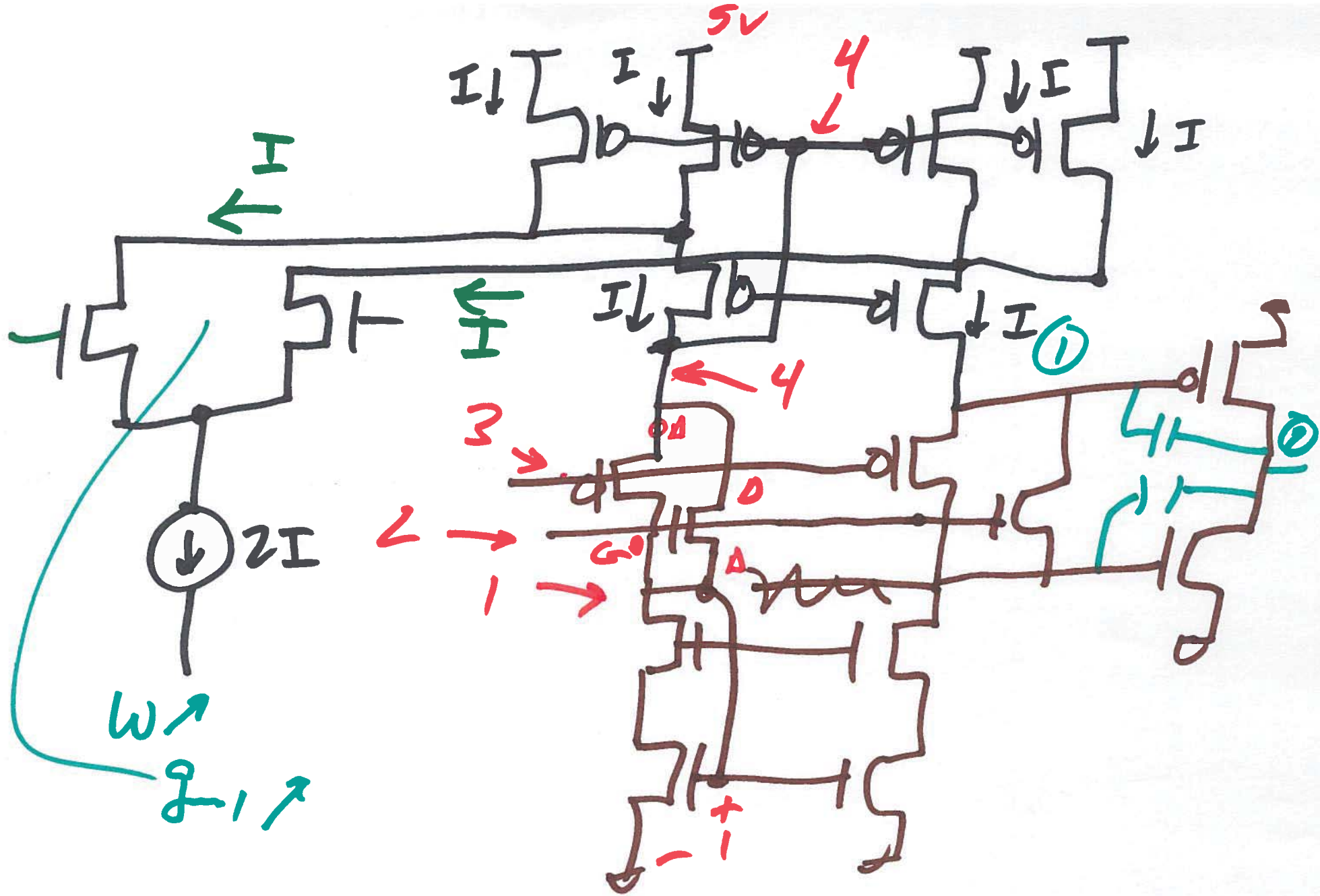

3)

Both NMOS & PMOS $\omega \rightarrow A_{OL} = (g_{mN} + g_{mP})$

NMOS $\omega \vee g_{mP} \rightarrow 0$

PMOS $\omega \vee g_{mN} \rightarrow 0$

$\cdot R_{oens} \parallel R_{oensP}$


$\cdot r_{oN} \parallel r_{oP} \parallel R_L$

$(g_{mN} + g_{mP})$

$A_{AOLDC} = 10,000$


\rightarrow only one diff-amp \sim

$A_{AOLDC} = 5,000$

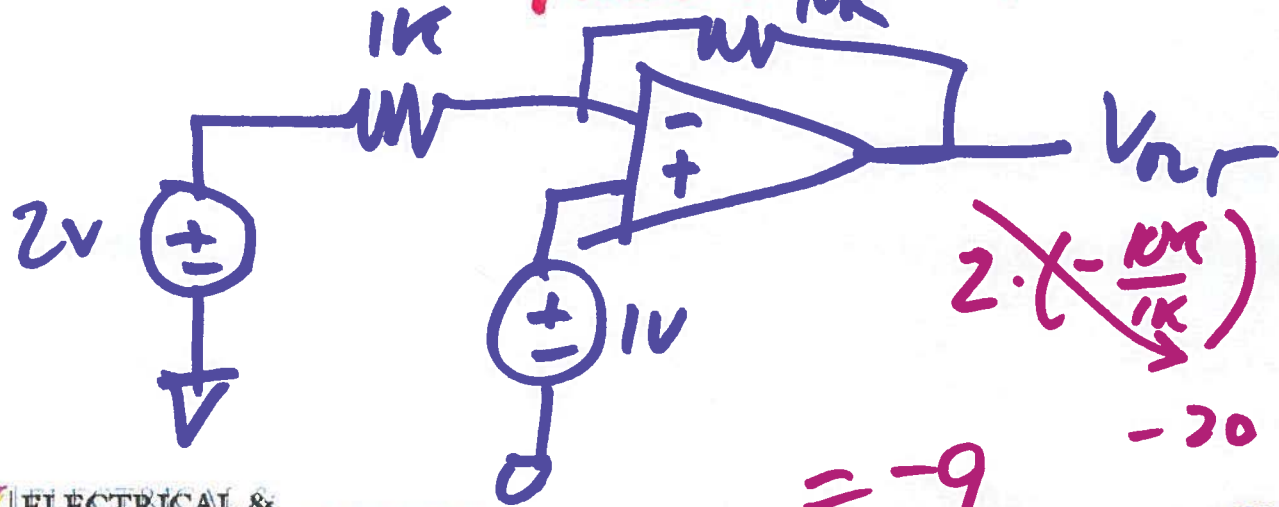

$$2 \cdot \left(-\frac{10k}{1k} \right) + 1 \cdot \left(1 + \frac{10}{1k} \right)$$

$= -9$

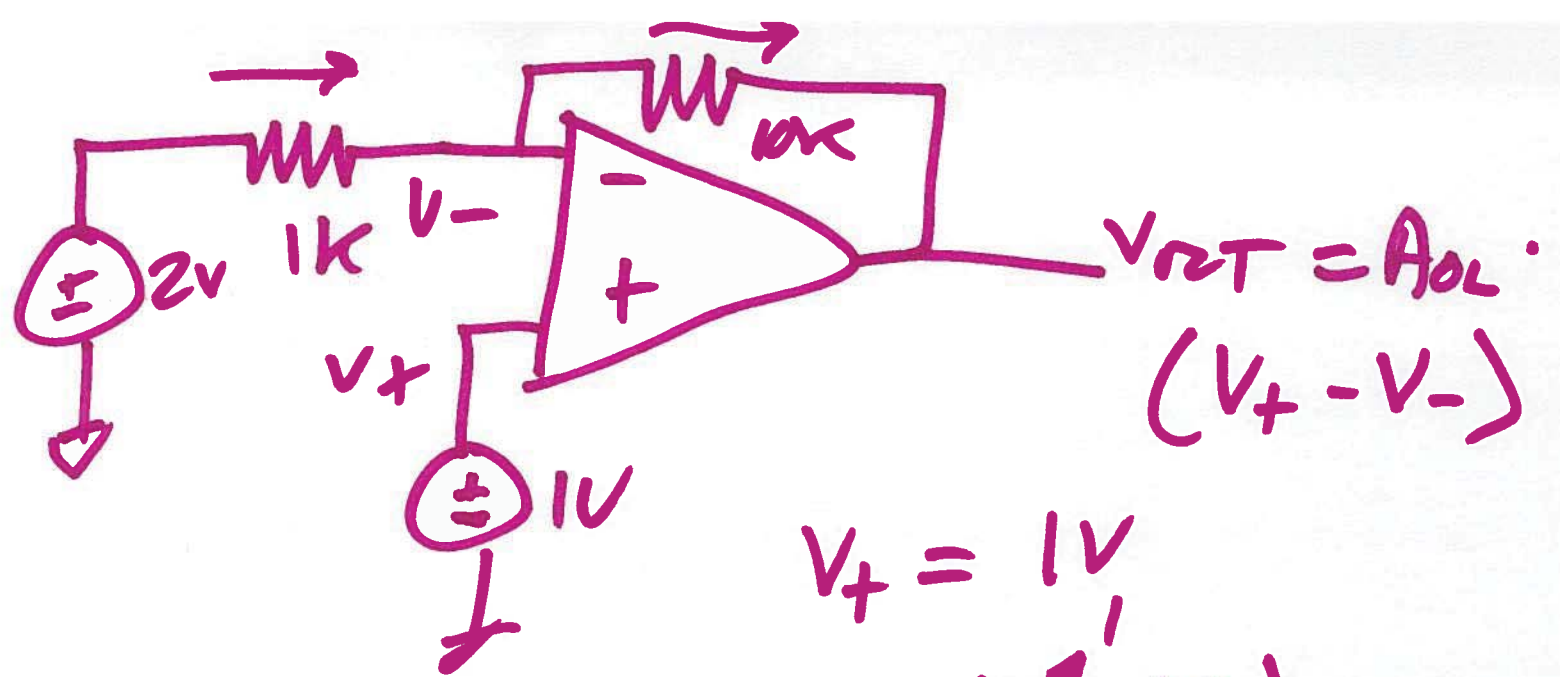

$$V_+ = 1V$$

$$\frac{2 - V_-}{1k} = \frac{V_- - V_{out}}{10k}$$

$$V_- = \frac{20 + A_{OL}}{A_{OL} + 10}$$

$$20 - 10V_- = V_- - A_{OL} \cdot 1 + A_{OL} \cdot V_-$$

$$20 + A_{OL} = V_- (A_{OL} + 10)$$

5)

$$V_{OT} = A_{OL} \left(1 - \frac{\frac{20}{A_{OL}} + 1}{1 + \frac{10}{A_{OL}}} \right)$$

$$= A_{OL} \left(\frac{1 + \frac{10}{A_{OL}} - \frac{20}{A_{OL}} - 1}{1 + \frac{10}{A_{OL}}} \right)$$


$$= \frac{-10}{1 + \frac{10}{A_{OL}}}$$

$$A_{OL} \rightarrow -10$$

$$A_{OL} \rightarrow 10k$$

$$\rightarrow 5k$$

6)

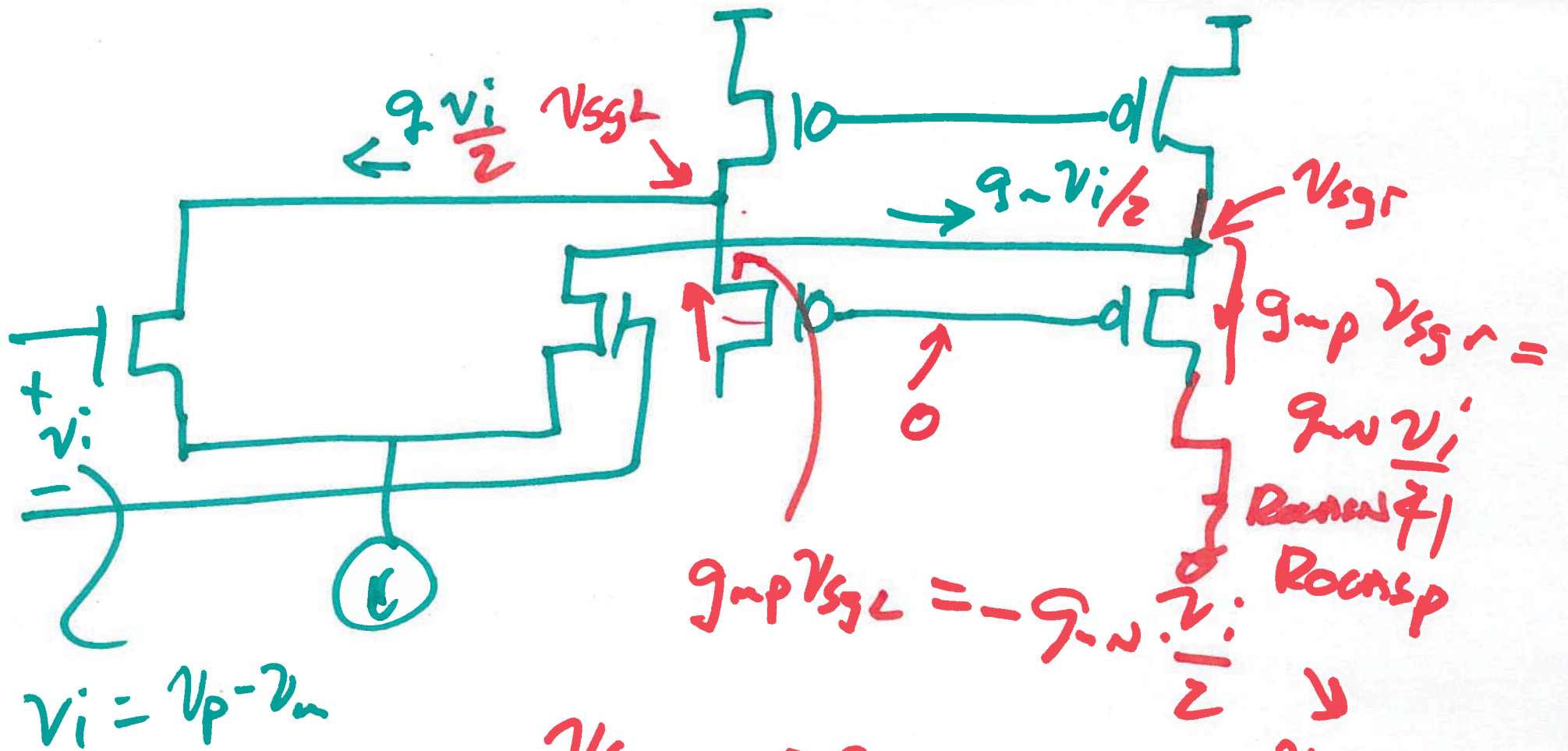

$$g_{mP} V_{SG_L} = -g_{mN} \cdot \frac{v_i}{2}$$

$$V_{SG_L} = \frac{-g_{mN}}{g_{mP}} \cdot \frac{v_i}{2}$$

$$\frac{V_{SG_L}}{v_i} \approx \frac{-g_{mN}}{2g_{mP}} \approx -\frac{1}{2}$$

$$\frac{V_{SG_R}}{v_i} = \frac{+g_{mN}}{2g_{mP}}$$

$$\approx \frac{1}{2}$$

8)