

EE420 / ECG 620


Analog IC Design

Gain · BW product

Lecture 24

May 1, 2019

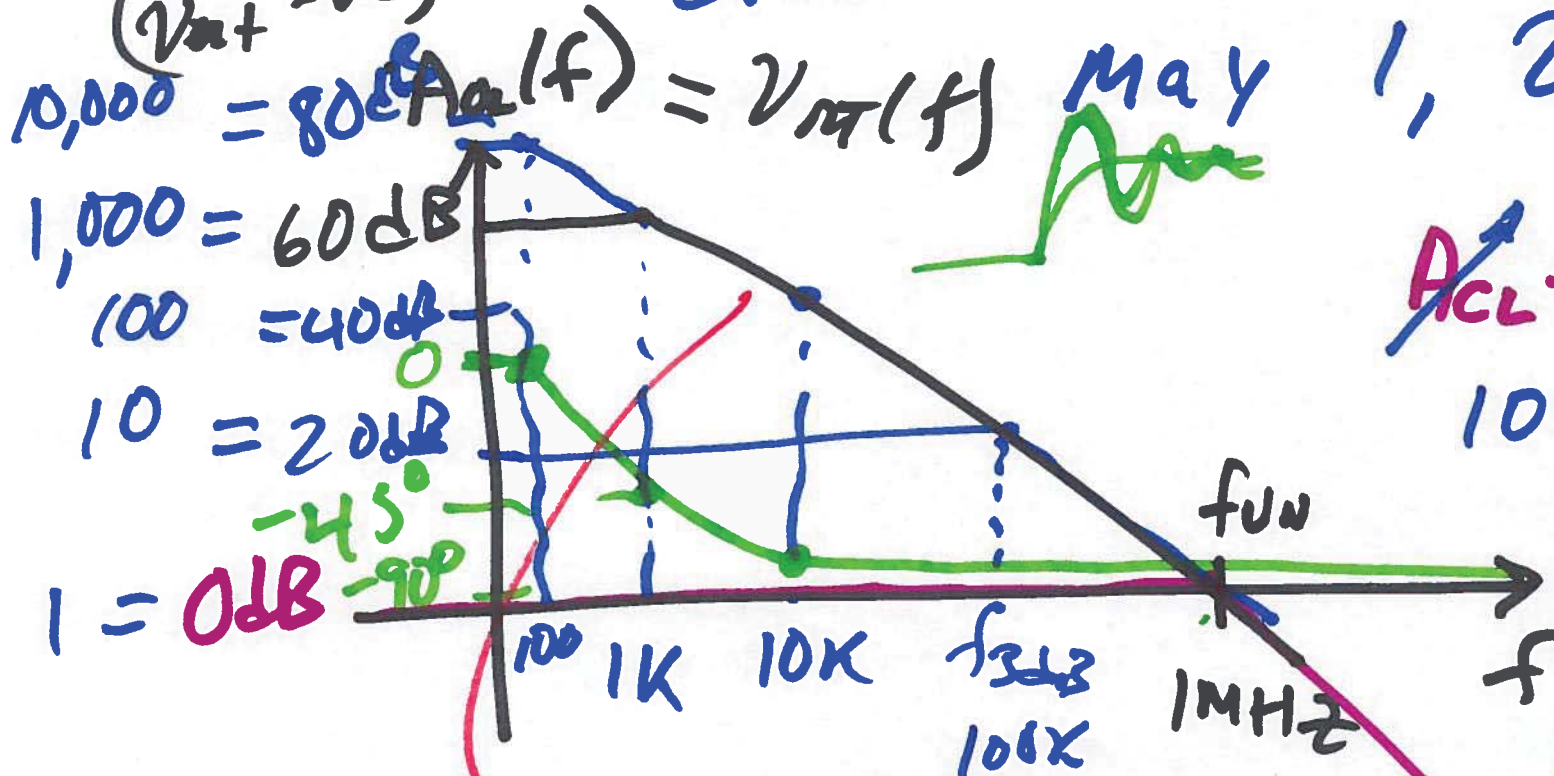$(v_{in} - v_{out})$
 $10,000 = 80 \text{ dB}$
 $1,000 = 60 \text{ dB}$
 $100 = 40 \text{ dB}$
 $10 = 20 \text{ dB}$
 $1 = 0 \text{ dB}$



$A_{CL} \cdot f_{3dB} = f_{un}$


$10 \cdot f_{3dB} = f_{un}$

$f_{3dB} = \frac{f_{un}}{10}$

Phase Margin
 $= 90^\circ$

$A_{OL}(f) = \frac{1,000}{1 + j \frac{f}{1K}}$

1)

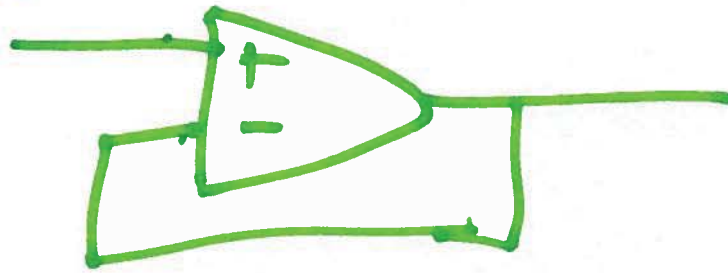v_{in} 

$$v_{out} = A_{OL}(f) \cdot (v_{in} - v_{out})$$

$$v_{out} = \frac{1000}{1 + j \frac{f}{10^3}} \cdot (v_{in} - v_{out})$$


$$v_{out} \left(\frac{1000 + 1 + j \frac{f}{10^3}}{1 + j \frac{f}{10^3}} \right) = \frac{v_{in} \cdot 1000}{1 + j \frac{f}{10^3}}$$

$$\frac{v_{out}}{v_{in}} = \frac{1,000}{1,000 + 1 + j \frac{f}{10^3}}$$

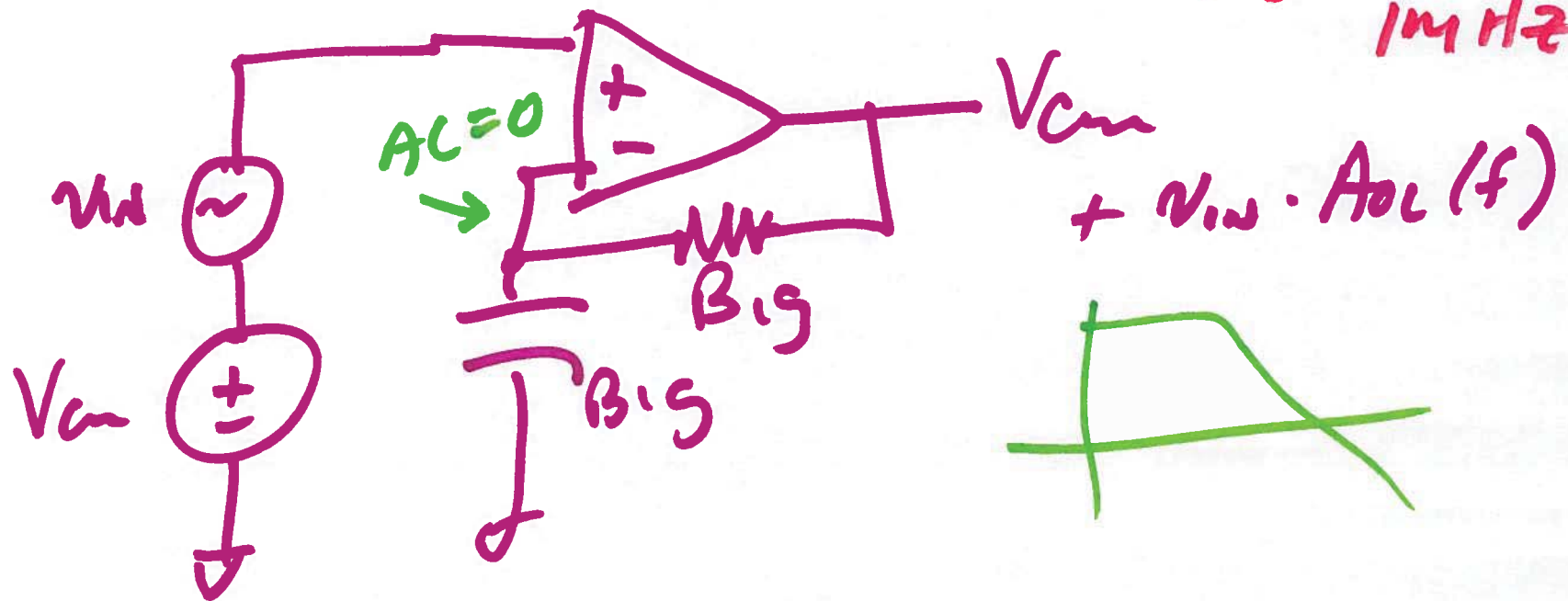
2)

$$\frac{V_{OUT}}{V_{IN}} \approx \frac{1}{1 + j \frac{f}{10^3 \cdot 10^3}} \quad \text{ACLOE FREQUENCY}$$

$$= \frac{1}{1 + j \frac{f}{10^6 \text{ Hz}}}$$



3)

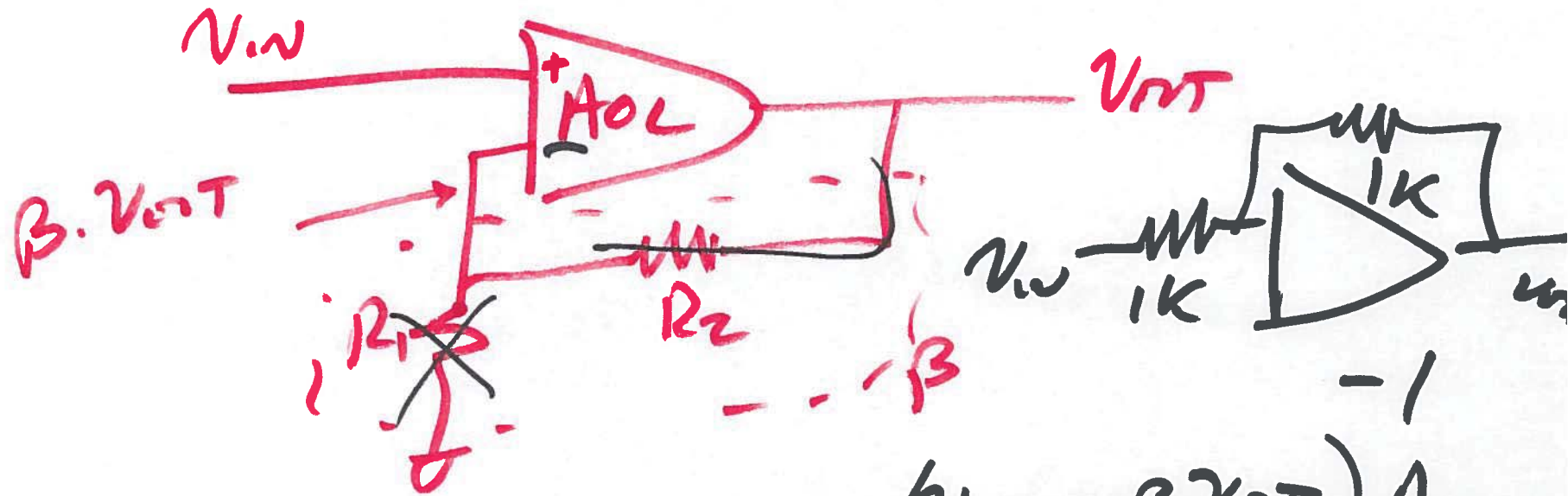

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$V_{OUT} = (V_{in} - \beta V_{OUT}) A_{OL}$$


$$V_{OUT} (1 + \beta A_{OL}) = \frac{A_{OL} \cdot V_{in}}{1 + \beta A_{OL}}$$

$$\frac{V_{OUT}}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

$$\beta A_{OL} \approx 1$$

$$A_{CL} = \frac{1}{\beta}$$

CMOSedu.com


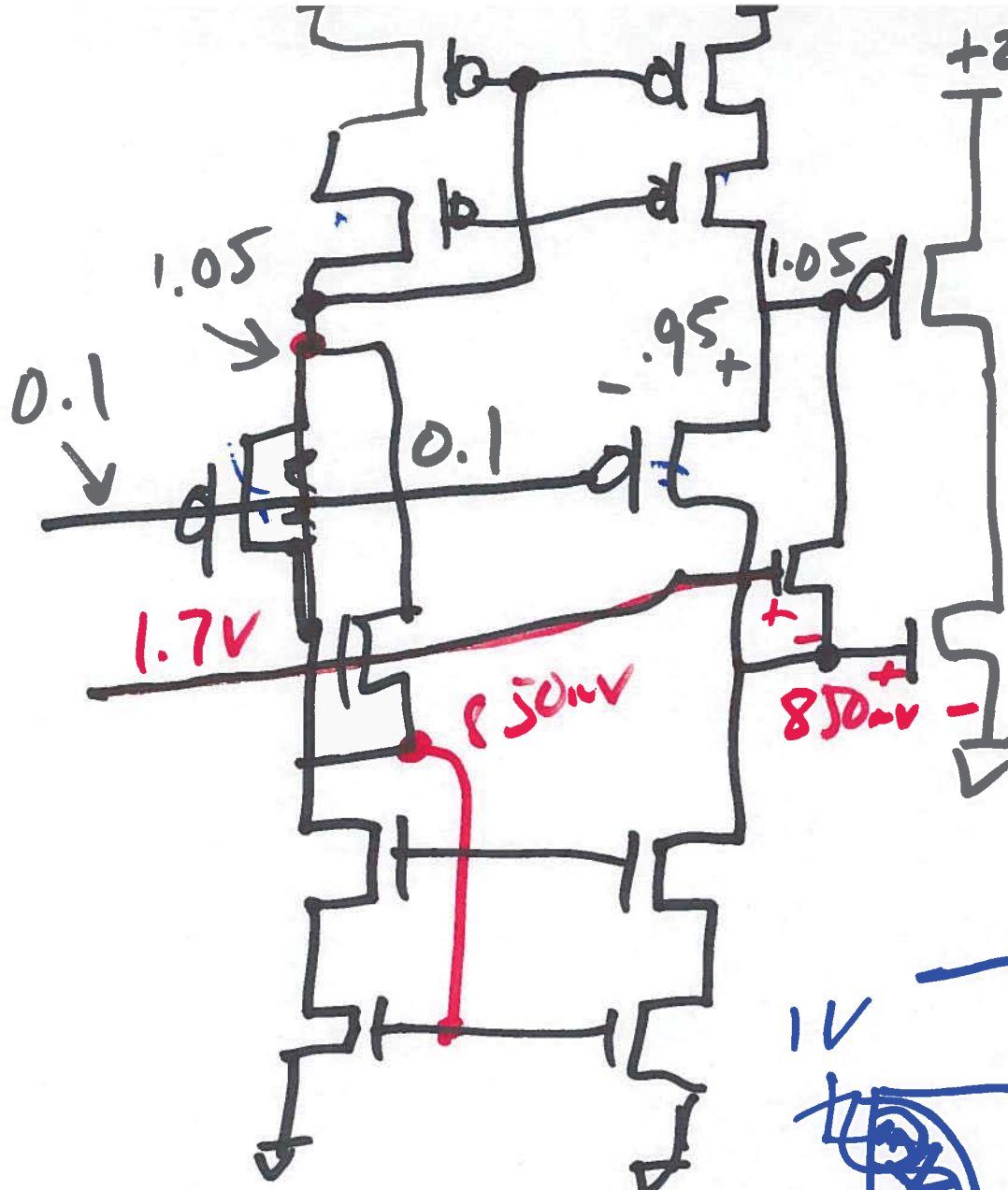


$$V_{GS} = V_{TKN} + 0.05$$


↑
V_{DS, SAT}
= 50mV

$$V_{SG} = V_{TKP} + 0.05$$

950mV

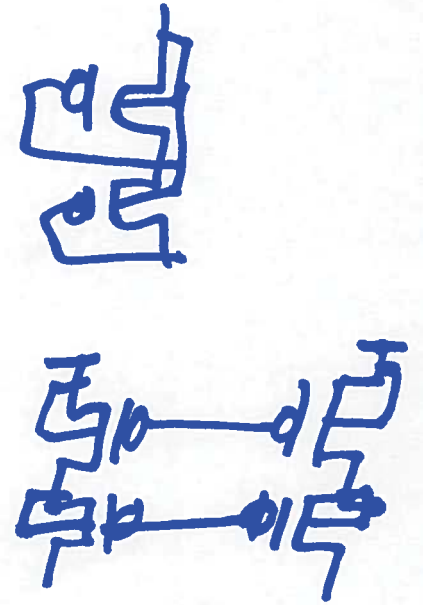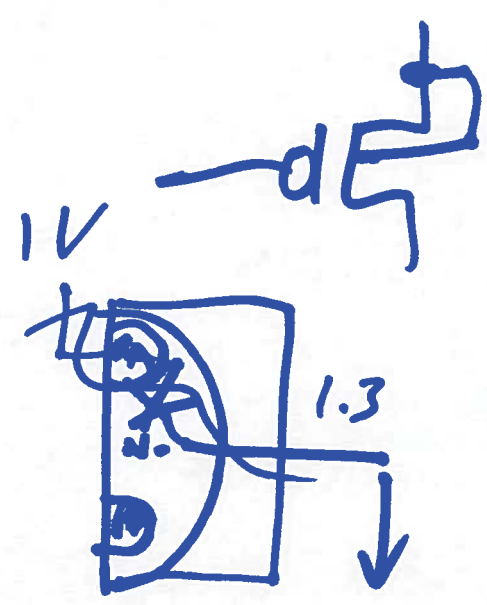

5)

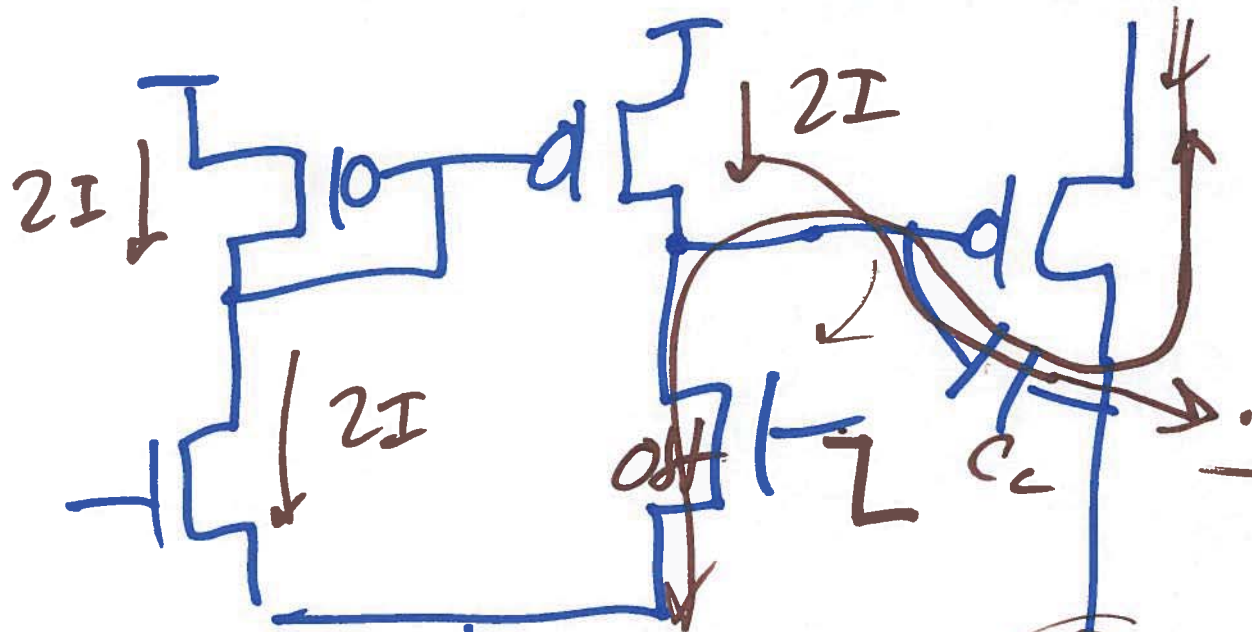

$$104 \text{ A} = I \quad \frac{10 \text{ V}}{5 \text{ ns}}$$


$$C = 1 \text{ pF}$$

$$\frac{C(I)}{1 \text{ pF}} = \frac{104}{1 \text{ pF}} = \frac{10^{-5}}{10^{-10}}$$

$$\frac{I}{C} = \frac{dV_{out}}{dt}$$


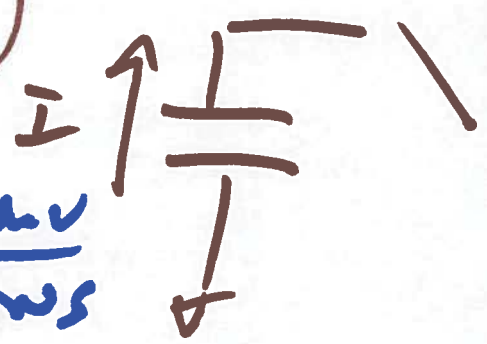
$$SR = \frac{10 \text{ V}}{4 \text{ ns}} = \frac{1 \text{ V}}{100 \text{ ns}} = \frac{10 \text{ mV}}{10 \text{ ns}}$$



6)