

I_D
 V_{GS} EE420 / ELG 620

$V_{GS} > V_{THP}$

Analog IC Design

$V_{SD} \geq V_{GS} - V_{THP}$

Lecture 2


JAN. 28, 2019

$V_S - V_D \geq V_S - V_G - V_{THP}$

$V_D \leq V_G + V_{THP}$


$0 \leq V_{THP}$

$V_{GS} = V_{BIAS} = V_{DD} - V_{SG}$

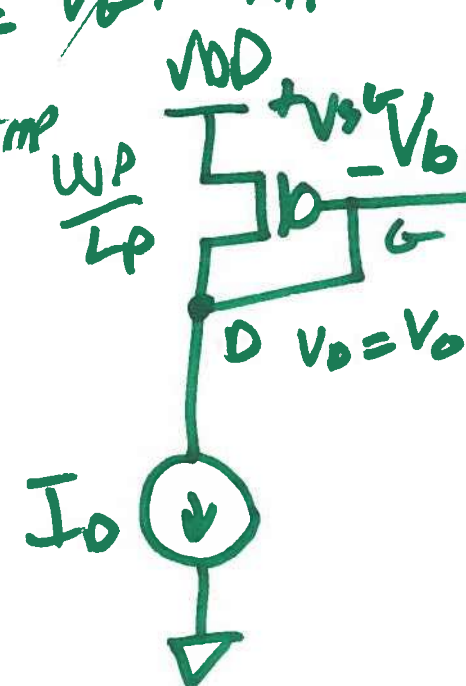


CURRENT MIRROR

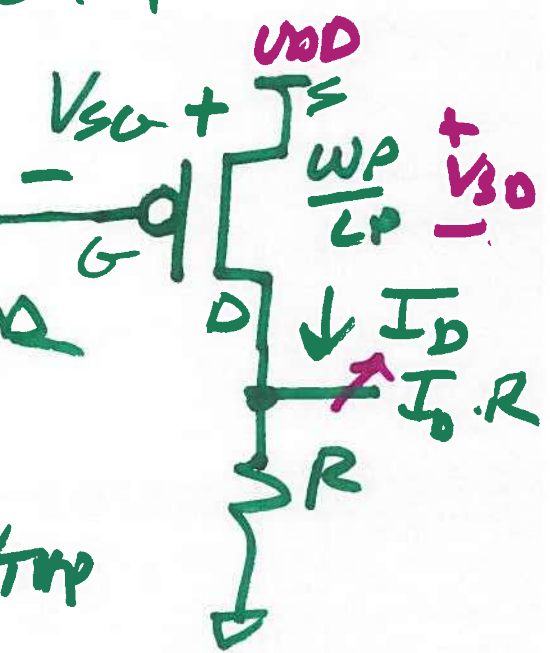$V_{SG} = \sqrt{\frac{2 \cdot I_D}{K_P \cdot \frac{W_P}{L_P}}} + V_{THP}$



11

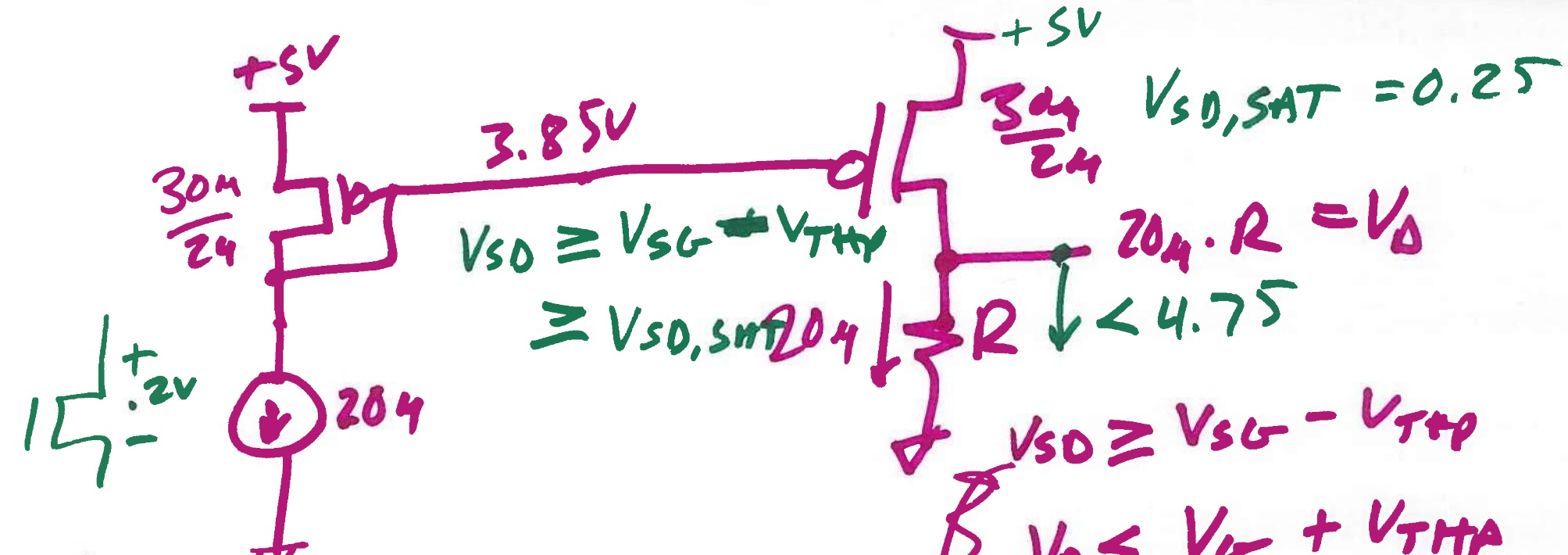

$$V_{SG} = \sqrt{\frac{2 \cdot 20k}{40k \cdot 20 \frac{\mu A}{V^2}}} + 0.9$$

$$= \sqrt{\frac{2}{30}} + 0.9 = 1.15V$$

Overdrive $\quad V_{SD, SAT}$

$$V_{SD} \geq V_{SG} - V_{THP}$$

$$V_D \leq V_G + V_{THP}$$

$$20k \cdot R \leq 3.85 + 0.9$$

$$\leq 4.75V$$



$$V_{DD} - V_{SD, SAT}$$

$$V_{SD, SAT} = V_{SG} - V_{THP}$$

$$R \leq \frac{4.75}{20k}$$

CMOSedu.com

2)

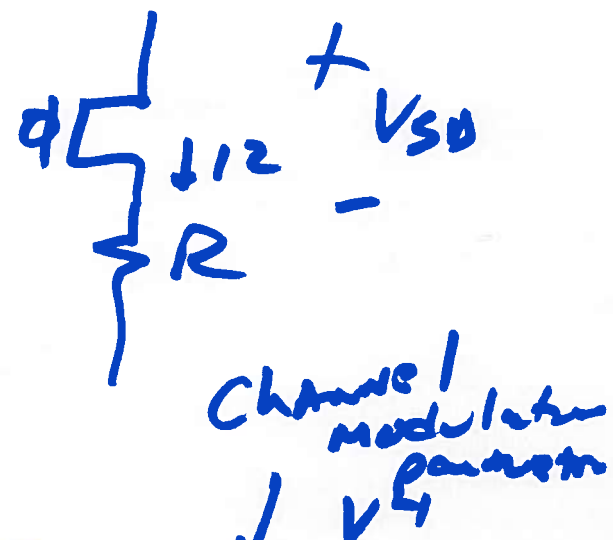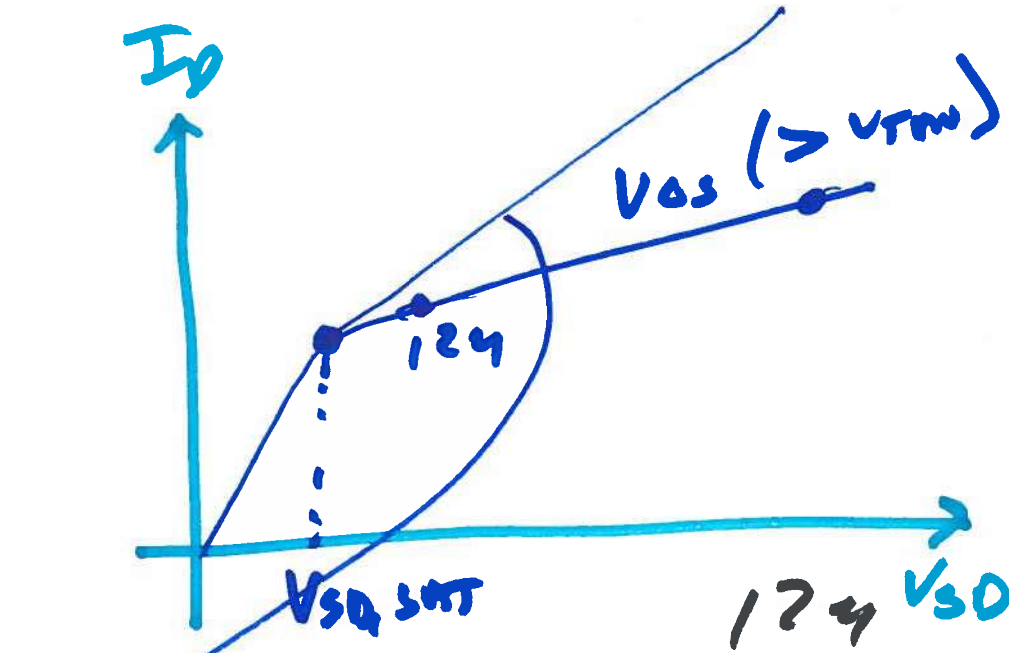




$$I_D = \frac{K_P P}{2} \frac{W_P}{L_P} (V_{SG} - V_{THP})^2 (1 + \lambda (V_{SD} - V_{SD,sat}))$$

$$V_{SG} > V_{THP} \quad \left. \begin{array}{l} \\ \end{array} \right\} 0.02 \cdot 2$$

$$V_{SD} \geq V_{SG} - V_{THP}$$



$$.04 \cdot 124 = \frac{1}{2} 4$$


3)

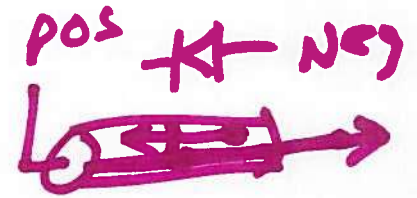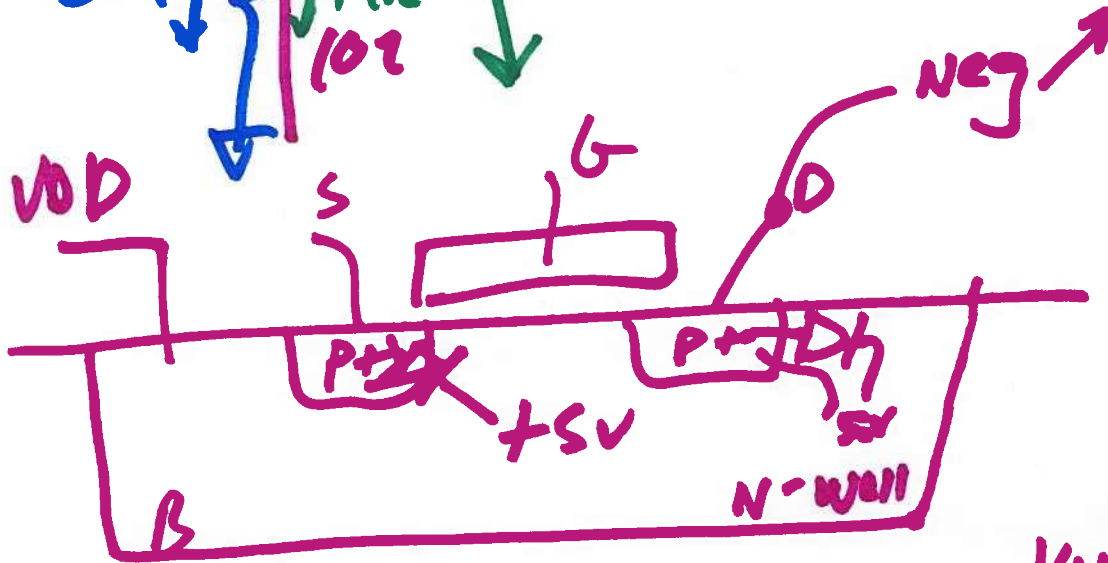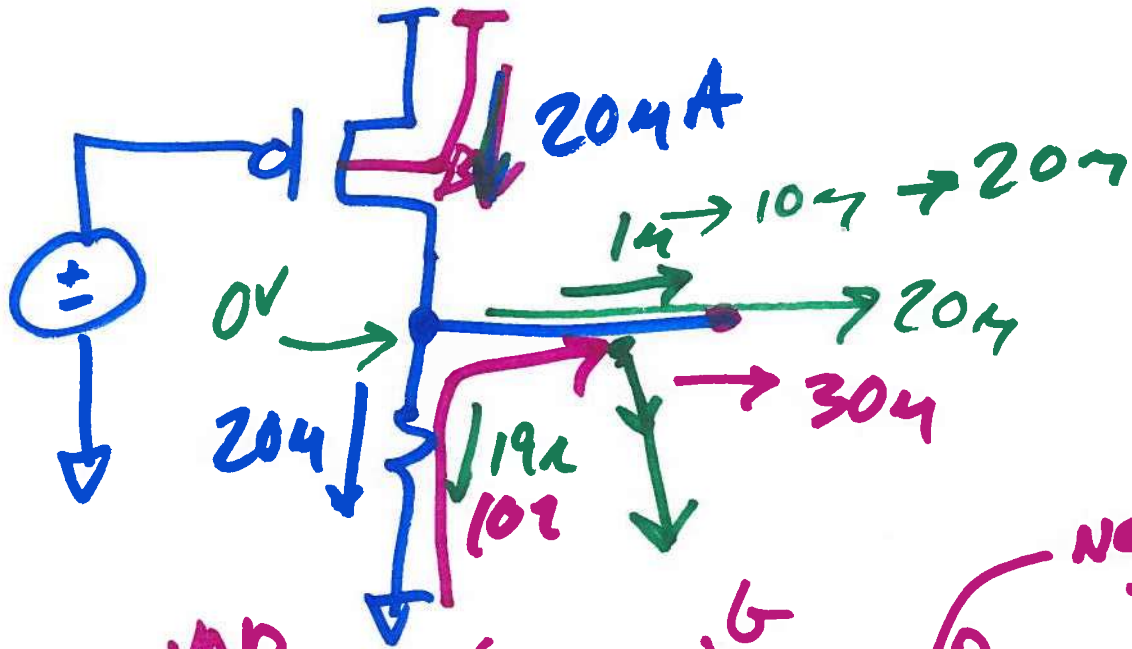

CMOSedu.com


4)

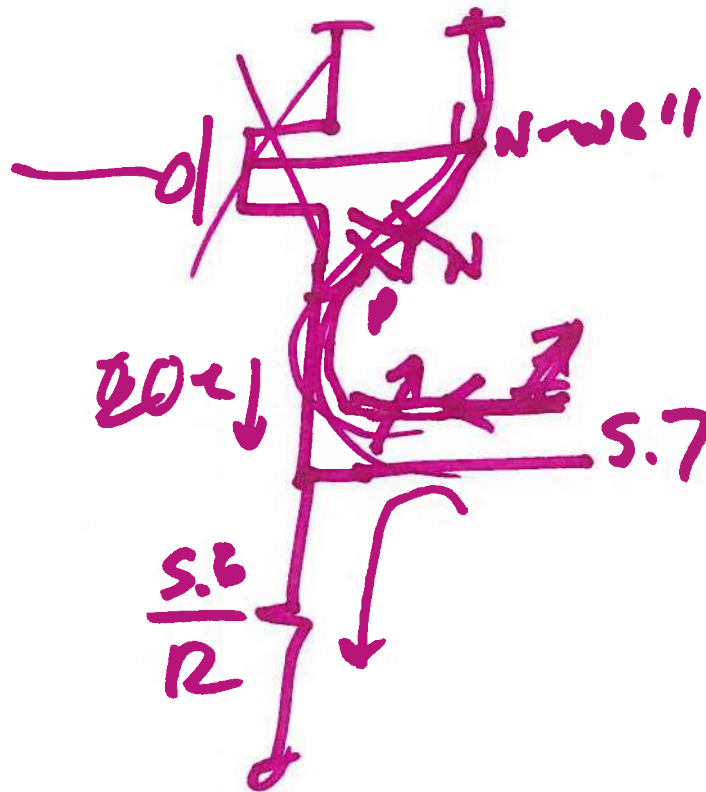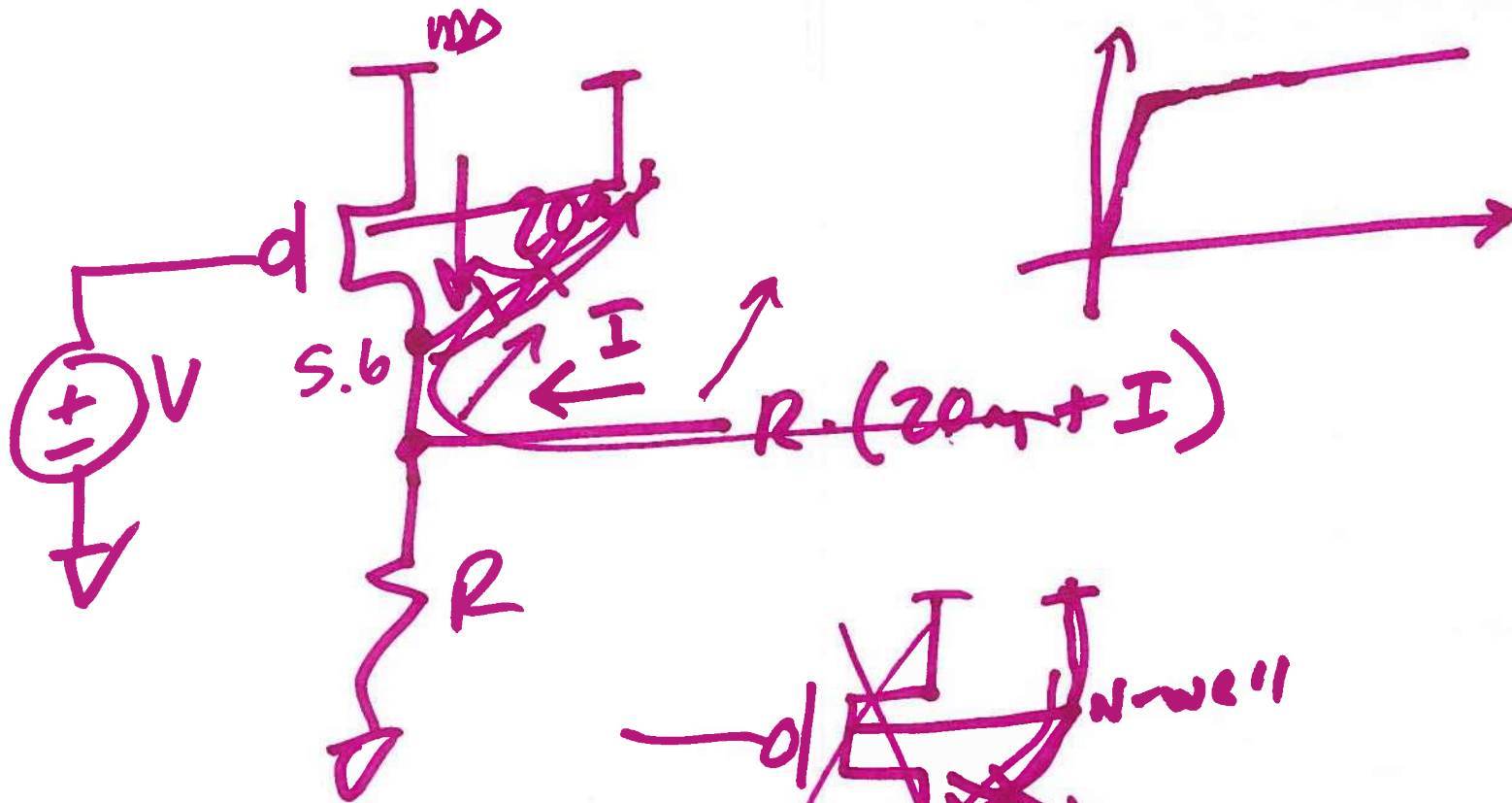

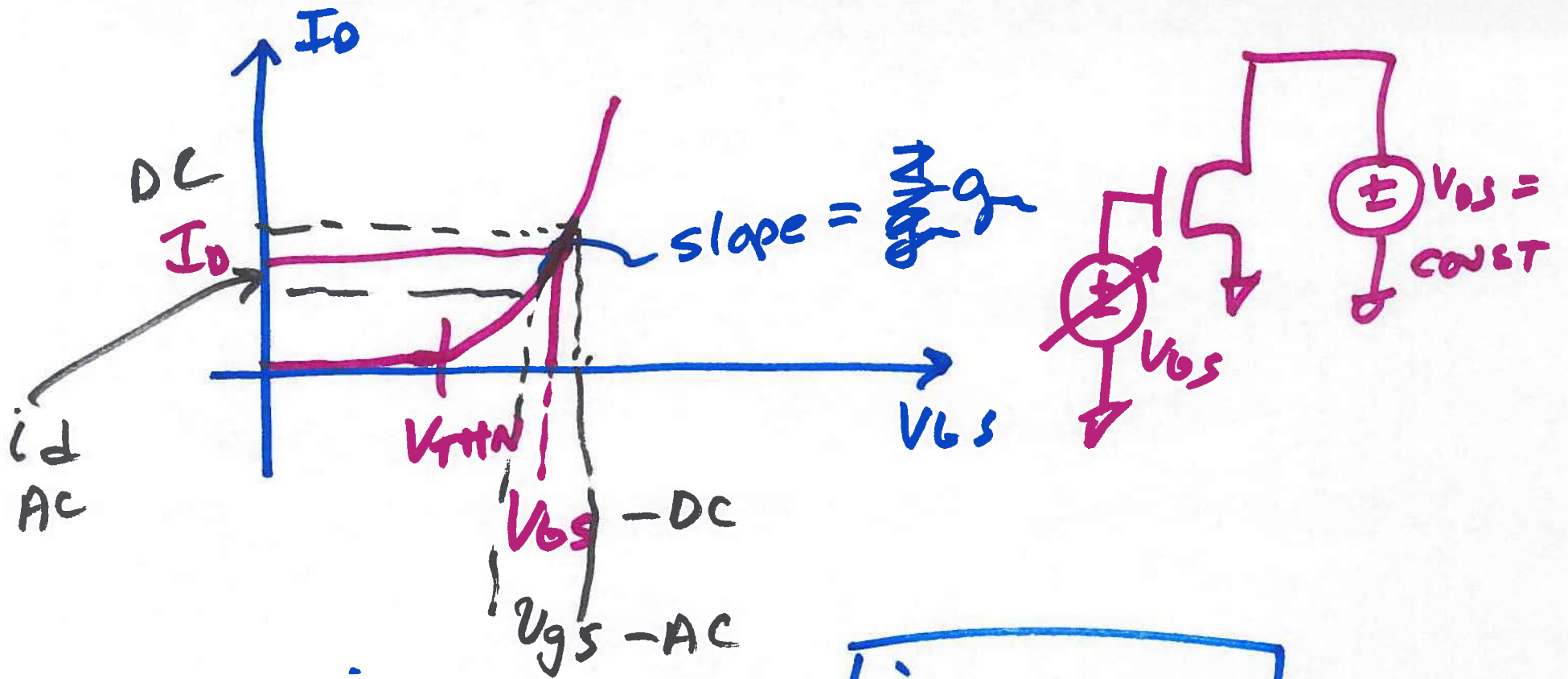


$$\frac{i_d}{v_{gs}} = g_m \rightarrow \boxed{i_d = g_m v_{gs}}$$

6)

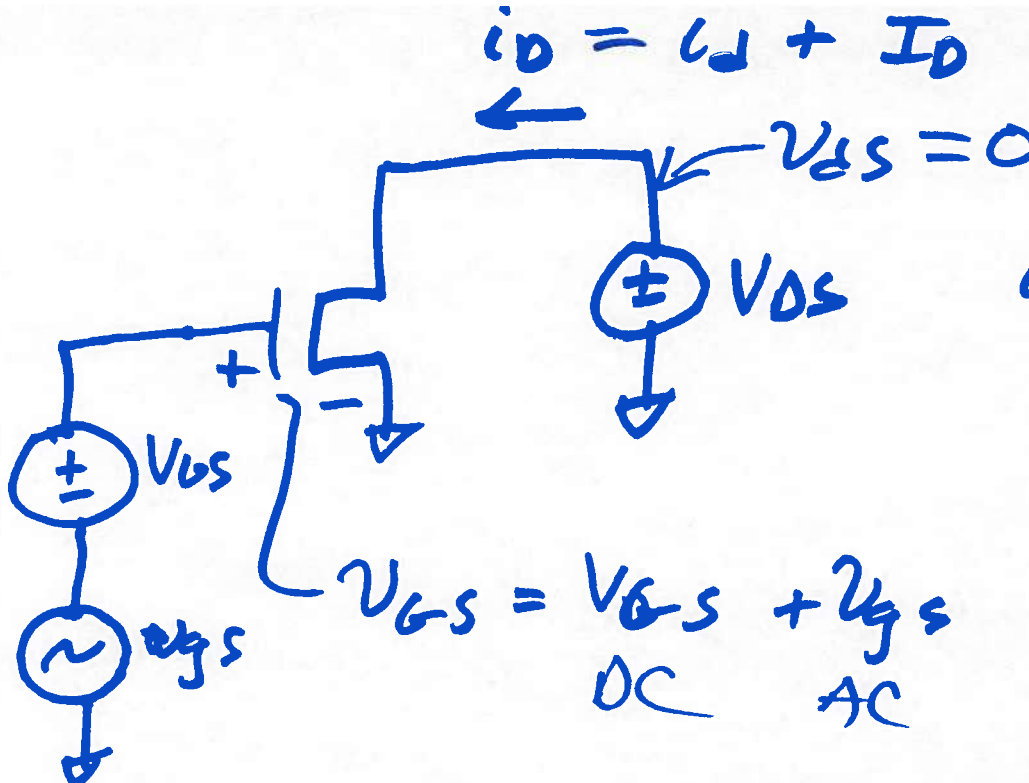
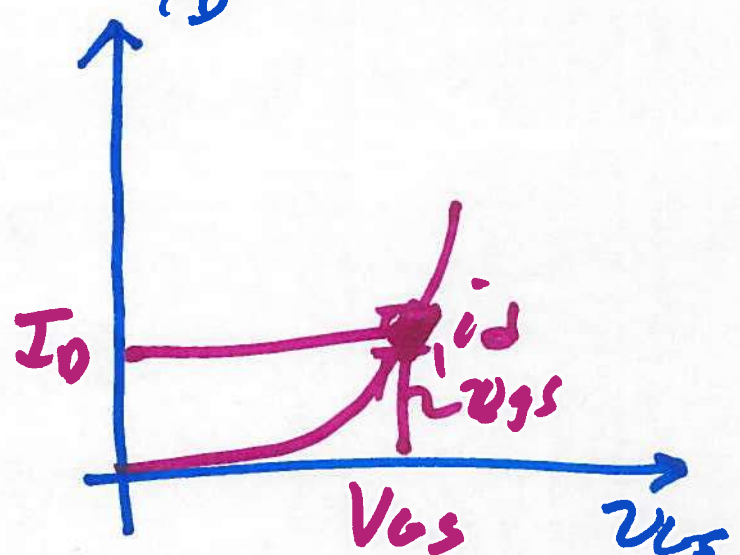
$$i_D = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2$$



$$g_m \equiv \frac{\delta i_D}{\delta V_{GS}} \bigg|_{\substack{I_D = \text{CONST} \\ V_{GS} = \text{CONST}}} = \frac{\delta}{\delta V_{GS}} \frac{\beta_N}{2} \left(\underbrace{V_{GS} + v_{gs}}_{V_{GS}} - V_{THN} \right)^2$$

$(I_D + i_d)$

$$g_m = \beta_N (V_{GS} + v_{gs} - V_{THN})$$

$$\approx \beta_N (V_{GS} - V_{THN})$$

7)


$$g_m \approx \beta_n (V_{GS} - V_{THN})$$

$$g_m \cdot V_{GS} = 150 \mu A$$

$$\leftarrow V_D = 3V$$

$$V_{GS} \gg V_{THN}$$

SMALL-SIGNAL
APPROXIMATION

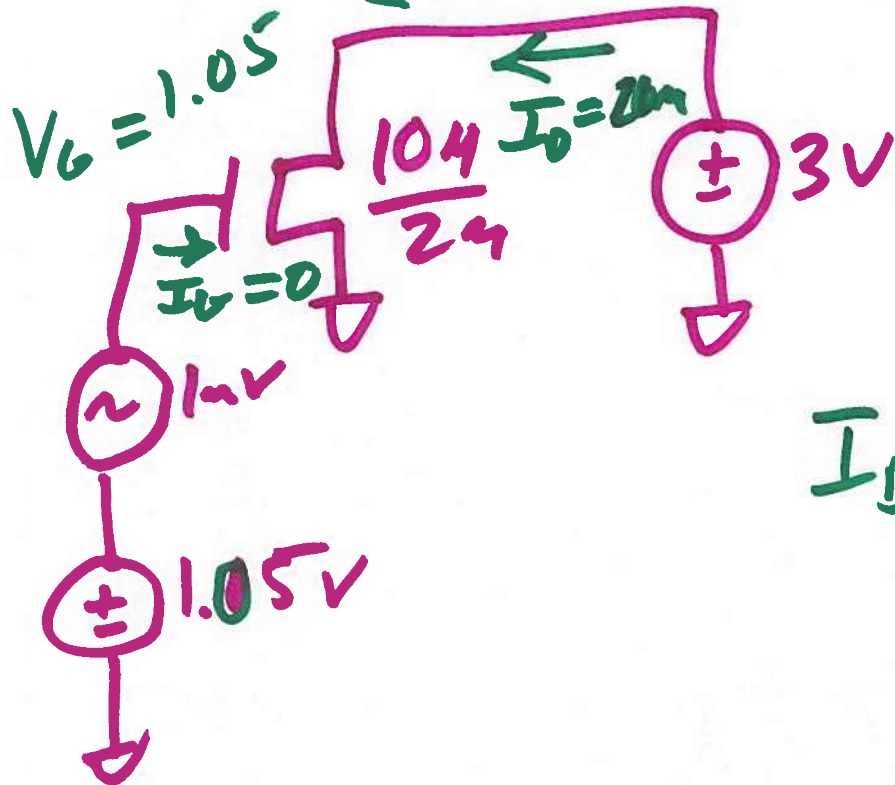

$$I_D = \frac{120 \mu A}{2} \cdot \frac{10}{2} (1.05 - 0.8)^2$$

$$= 204 \mu A$$

$$g_m = 120 \mu A \cdot \frac{10}{2} (1.05 - 0.8)$$

$$= 150 \mu A/V$$