


EE 420 / ECG 620

Analog IC Design

Feb. 11, 2019

Lecture 6

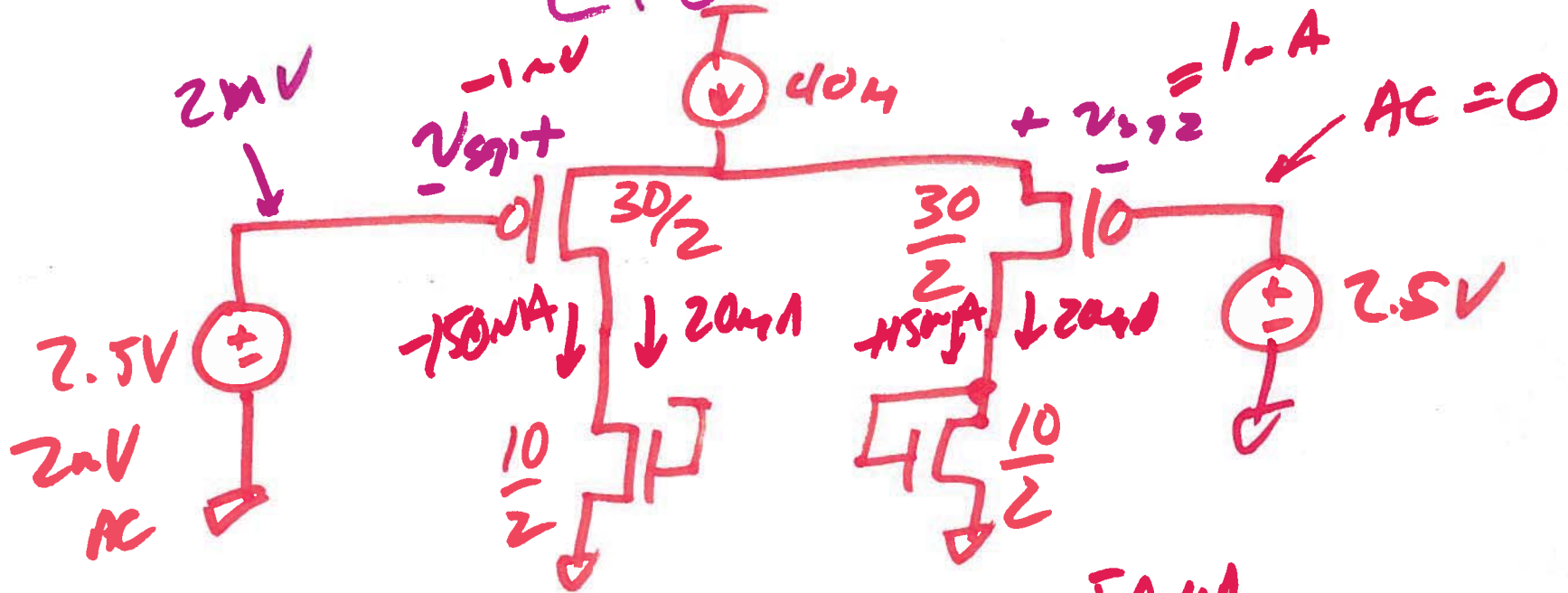
$$2\mu V + \frac{-1\mu V}{591} - \frac{+1\mu V}{592} = 0$$



$$g_{-p, d} = 150 \frac{\mu A}{V}$$

1)


$$g_m \cdot V_{gs} = i_d$$

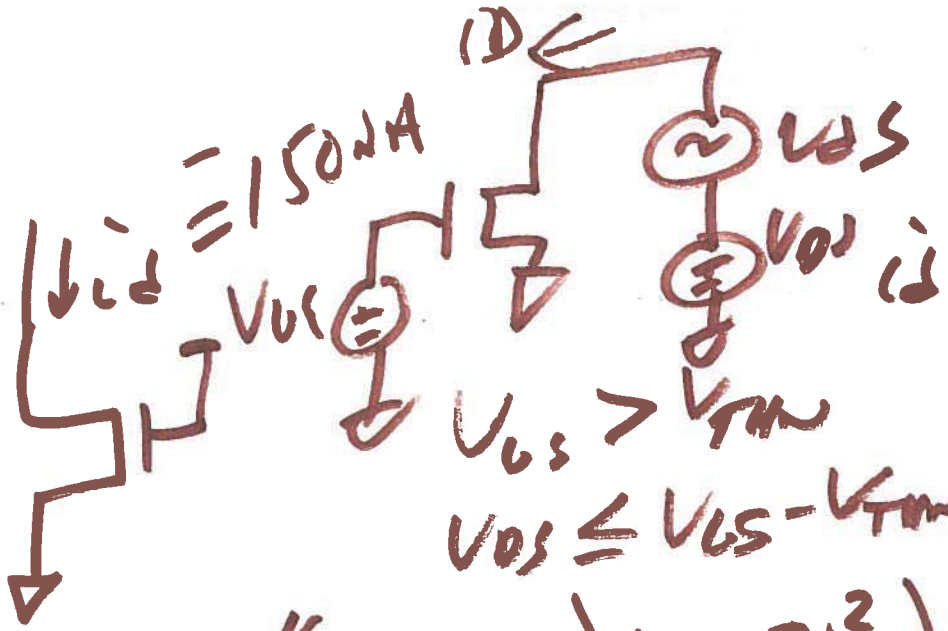

$$V_{GS} > V_{TH}$$

$$V_{DS} \leq V_{GS} - V_{TH}$$
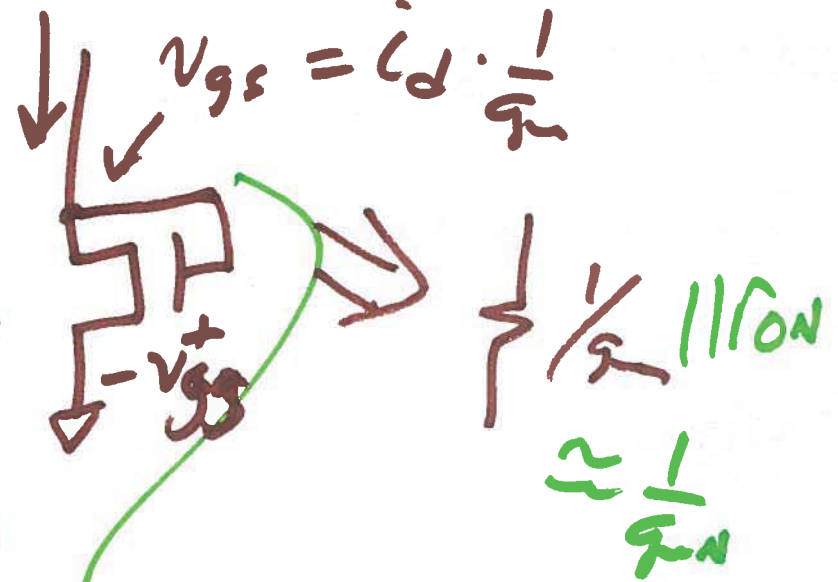
$$i_D = K_P \frac{W}{L} \left( (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$



$$v_{gs} = i_d \cdot \frac{1}{g_m}$$

$$\frac{1}{g_m} \parallel 11 \Omega$$

$$\approx \frac{1}{g_m}$$

$$v_{ds} = i_d \cdot \frac{1}{g_m}$$

$$= 150 \mu A \cdot \frac{1}{150 \frac{\mu A}{V}}$$

$$= 1 mV$$


$$\left. \frac{\partial i_D}{\partial V_{GS}} \right|_{\substack{I_D = \text{CONST} \\ V_{DS} = \text{CONST}}} = K_P \frac{W}{L} \left( (V_{GS} - V_{TH}) - V_{DS} \right)$$

$$R_{eff} = \frac{1}{K_P \frac{W}{L} \left( (V_{GS} - V_{TH}) - V_{DS} \right)}$$

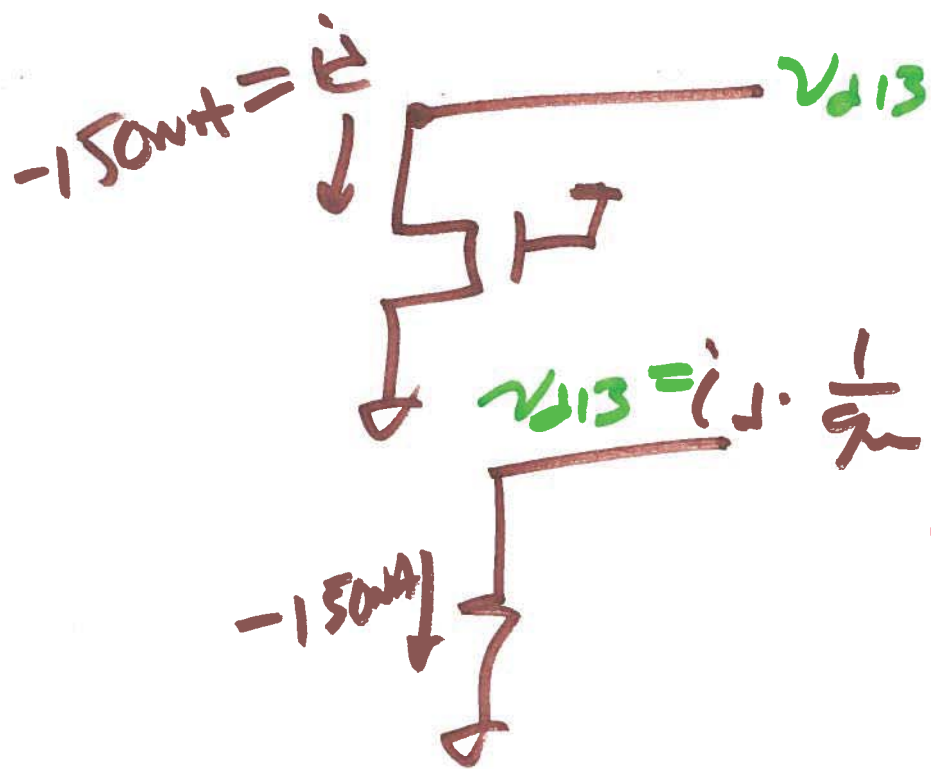2)

if  $V_{DS} \ll V_{DS,SAT} = V_{GS} - V_{T0N}$

$$R_{eff} \approx \frac{1}{k_n \cdot \frac{W}{L} (V_{GS} - V_{T0N})} = \frac{1}{g_m}$$




$$5V = \frac{1}{1704 \cdot \frac{10}{2} (5 - 0)}$$

$$v_{d13} = i_d \cdot \frac{1}{g_m} = i_d \cdot R_{eff} = 150n \cdot 396 = 59\mu V$$

~~$-1\mu V$~~


3)

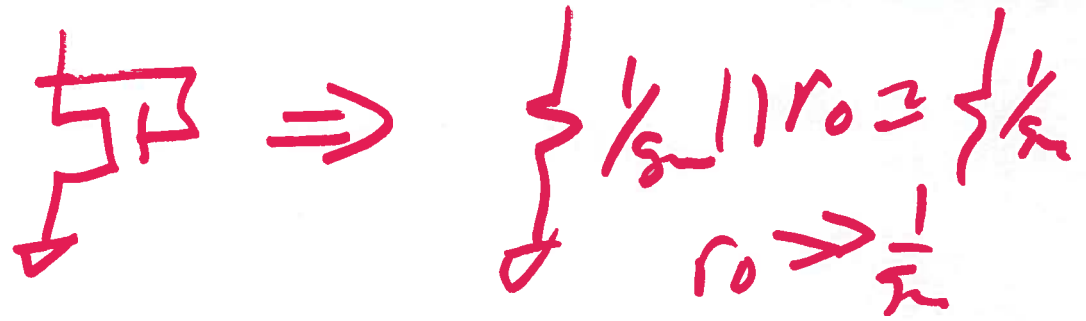

$g_m = \sqrt{2k_p \frac{W}{L} I_D}$  open-ckt gain (AC)

$r_o = \frac{1}{\lambda I_D}$

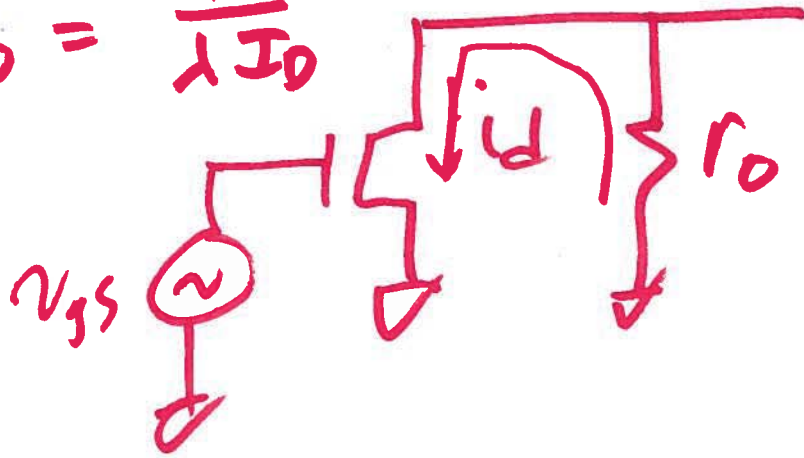$v_{out} = -i_d \cdot r_o = -g_m v_{gs} \cdot r_o$



open-ckt gain =  $-g_m r_o$   
 $|A_v| = g_m r_o = \frac{r_o}{1/g_m}$

open-ckt gain =  $\frac{\sqrt{2k_p \frac{W}{L} I_D}}{\lambda I_D} \propto \frac{1}{\sqrt{I_D}}$


4)



$$g_m = kP_n (V_{GS} - V_{THN}) = kP_n V_{DS,SAT}$$

$$I_D = \frac{kP_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2, \quad r_o = \frac{1}{\lambda I_D} = kP_n \cdot V_{OVN}$$
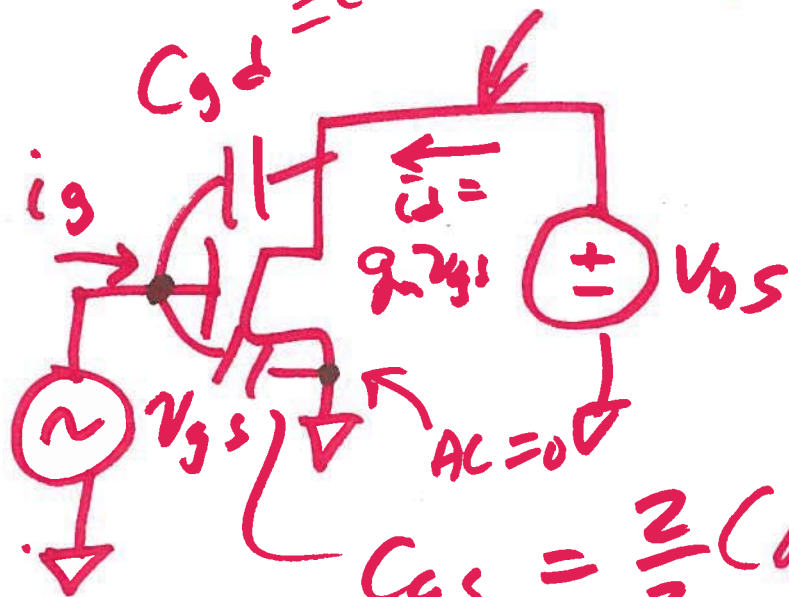
$$g_m r_o = \frac{kP_n \cdot \frac{W}{L} (V_{GS} - V_{THN})}{\lambda \frac{kP_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2} \propto \frac{1}{V_{GS} - V_{THN}} \propto \frac{1}{V_{OVN}}$$



$$i_g = \frac{v_{gs}}{j\omega (C_{gd} + C_{gs})}$$

$$i_d = g_m v_{gs}$$

$$C_{gs} = \frac{2}{3} C_{ox} = \frac{2}{3} C_{ox} \cdot W \cdot L$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

5)

$$\frac{i_d}{i_g} = \frac{g_m v_{gs}}{v_{gs} \cdot j\omega (C_{gs} + C_{gs})}$$

define

$$\left| \frac{i_d}{i_g} \right| = 1 @ f = f_T = \text{transition}$$

$$\frac{i_d}{i_g} > 1 \text{ to } \frac{i_d}{i_g} < 1$$


$$1 = \left| \frac{i_d}{i_g} \right| = \frac{g_m}{2\pi f \cdot (C_{gs} + C_{gd})} = \frac{K_P \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})}{2\pi f_T \left( \frac{2}{3} W \cdot L C_{ox} \right)}$$

$$C_{gs} \gg C_{gd}, \quad K_P = \mu_n \cdot C_{ox}$$


$$f_T = \frac{\mu_n \cdot (V_{GS} - V_{TH})}{2\pi \cdot L^2 \cdot \frac{2}{3}}$$

$$f_T \propto \frac{V_{GS} - V_{TH}}{L^2}$$

CMOSedu.com

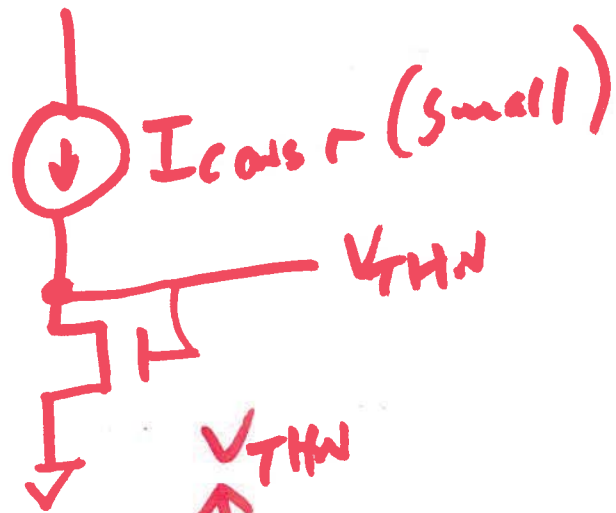

$T \uparrow V_{THN} \downarrow$

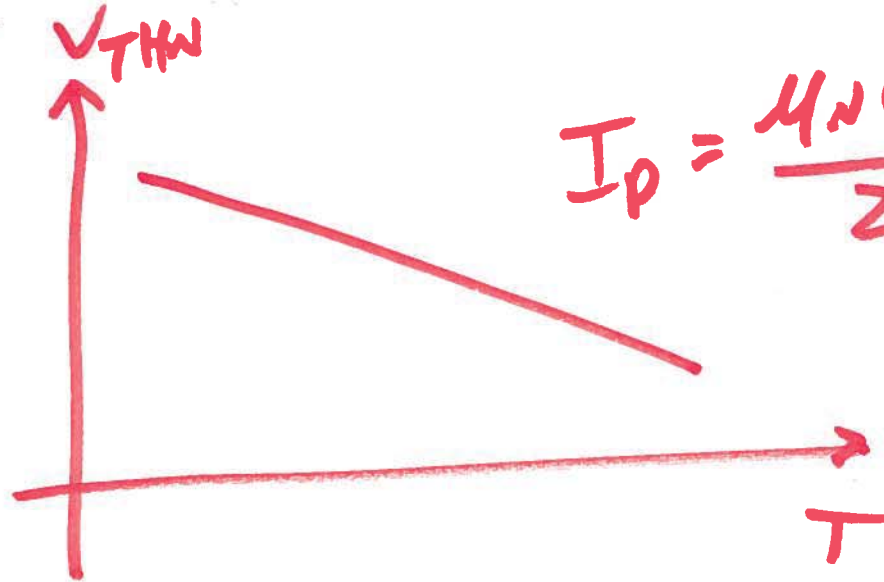

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

mobility  $\mu$

$T \uparrow \mu \downarrow$