

EE 420 / ECG 620

Lecture 7

Feb. 13, 2019

Analog IC Design

$$r_o = \frac{1}{\lambda I_D}$$


$$g_m \cdot r_o = \frac{K_P \frac{W}{L} (V_{GS} - V_{THN})}{\lambda \frac{K_P \cdot W}{2} (V_{GS} - V_{THN})^2}$$

$$I_D = \frac{K_P \cdot W}{2} \frac{L}{L} (V_{GS} - V_{THN})^2 = \frac{2}{\lambda \cdot (V_{GS} - V_{THN})}$$

$$g_m r_o \propto \frac{2}{\lambda \cdot (V_{GS} - V_{THN})}$$

$g_m r_o \downarrow$

$V_{GS} \uparrow$

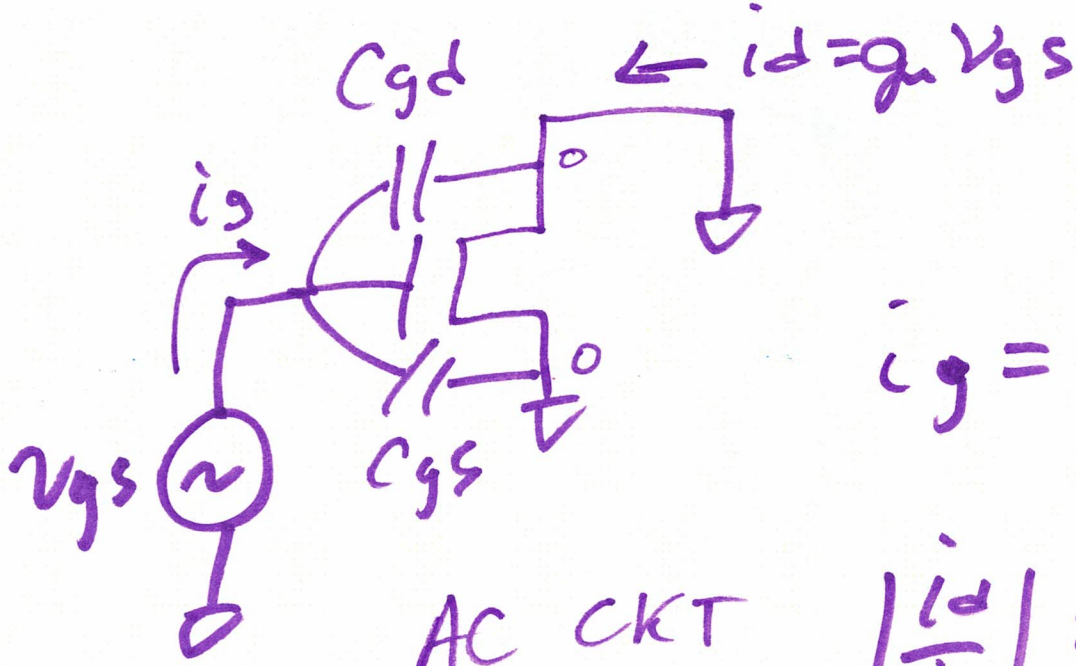

$$i_g = \frac{v_{gs}}{j\omega(C_{gs} + C_{gd})}$$

$$\left| \frac{i_d}{i_g} \right| = 1 @ f_T$$

$$1 = \left(\frac{i_d}{i_g} \right) = \left(\frac{g_m}{j\omega_T(C_{gs} + C_{gd})} \right)$$

$$f_T = \frac{K_D \cdot \mu \cdot (V_{GS} - V_{THN})}{2\pi(C_{gs} + C_{gd})}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$


$$f_T \propto (V_{GS} - V_{THN}) = V_{OVN} = V_{OS, SAT}$$

2) $V_{GS} \nearrow f_T \nearrow$

CURRENT MIRRORS

201132

1μ process

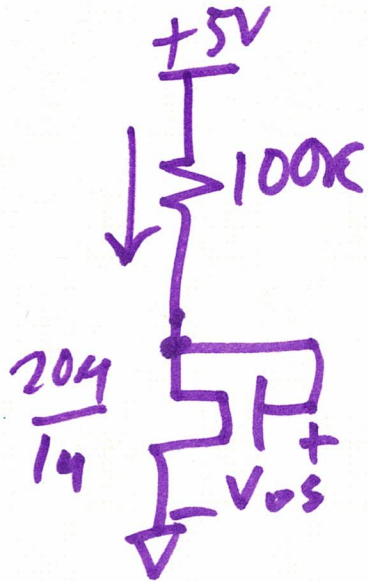

$$\frac{5 - V_{O5}}{100k} = \frac{120\mu}{L} \cdot \frac{1}{1} \cdot \frac{(V_{O5} - V_{TH})^2}{R}$$

$$\frac{5 - V_{O5}}{100k} = 120 (V_{O5} - .8)^2$$


$$\frac{5 - 1}{100k} = \underline{\underline{40\mu A}}$$

$$\frac{4 \cdot 10}{10^6} = \underline{\underline{40\mu A}}$$



L	R	V _{O5}
4	4.8	1
4.05	2.7	.95
3.9	16.8	1.1
4.03	3.9	.97
4.02	3.88	.98
4.01	4.37	.99

$V_{O5} \approx 1V$


.985

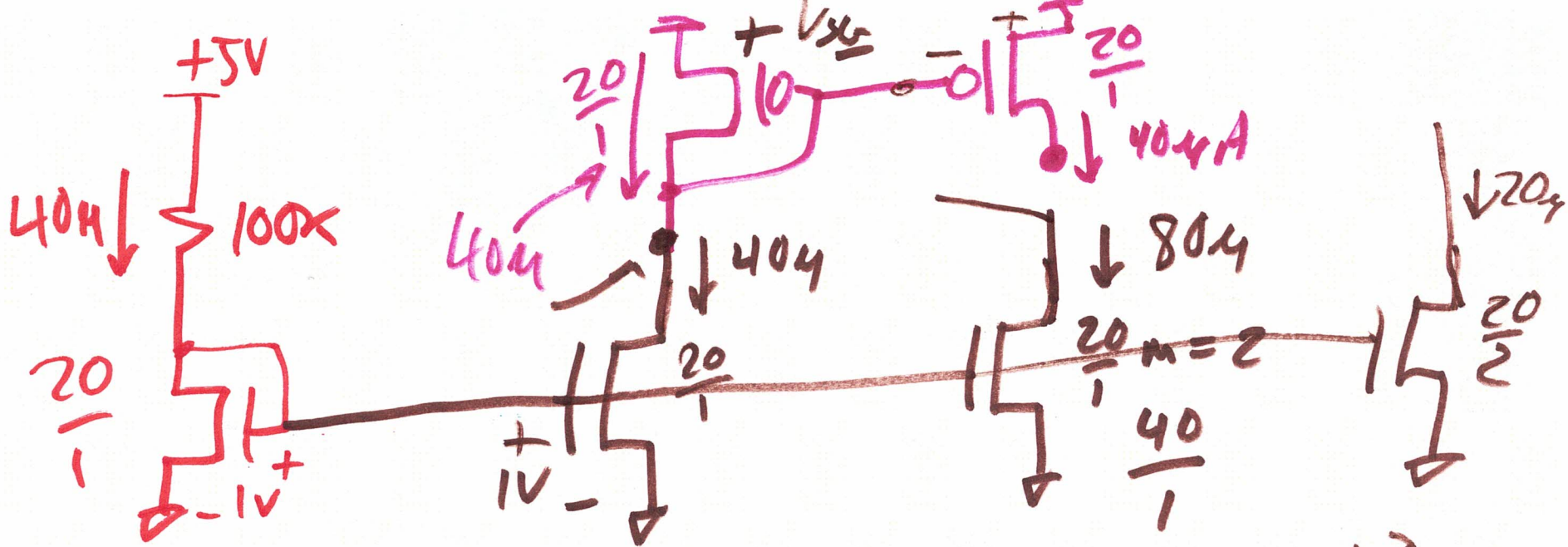
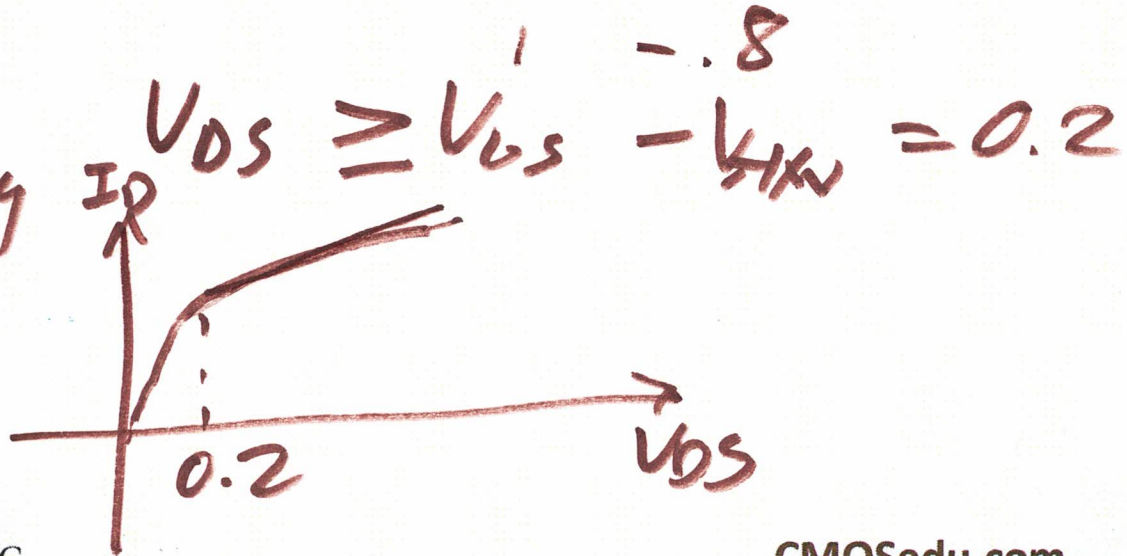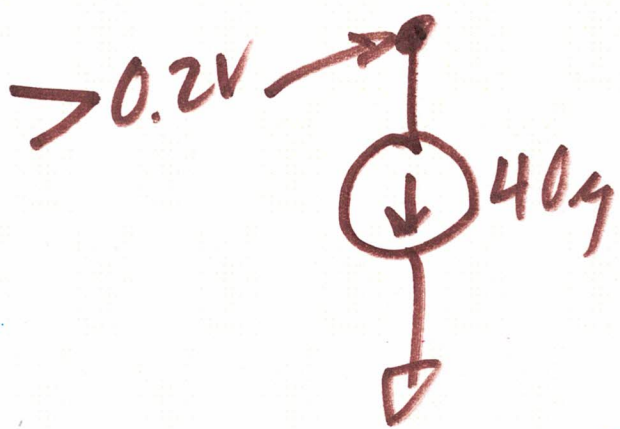
$$80\mu = \frac{K_P}{2} \cdot \frac{2W}{L} (V_{GS} - V_{THN})^2$$




4)

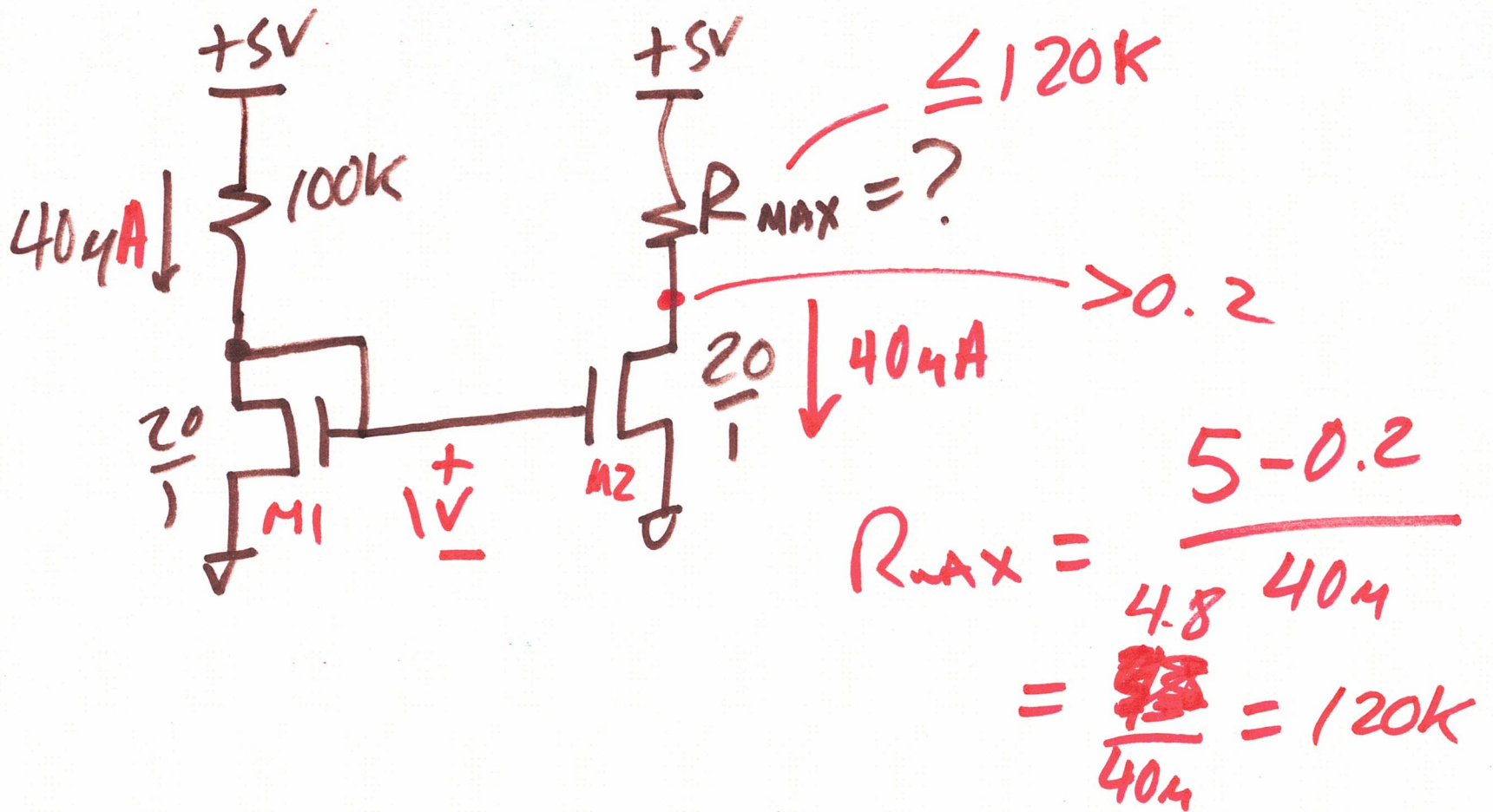

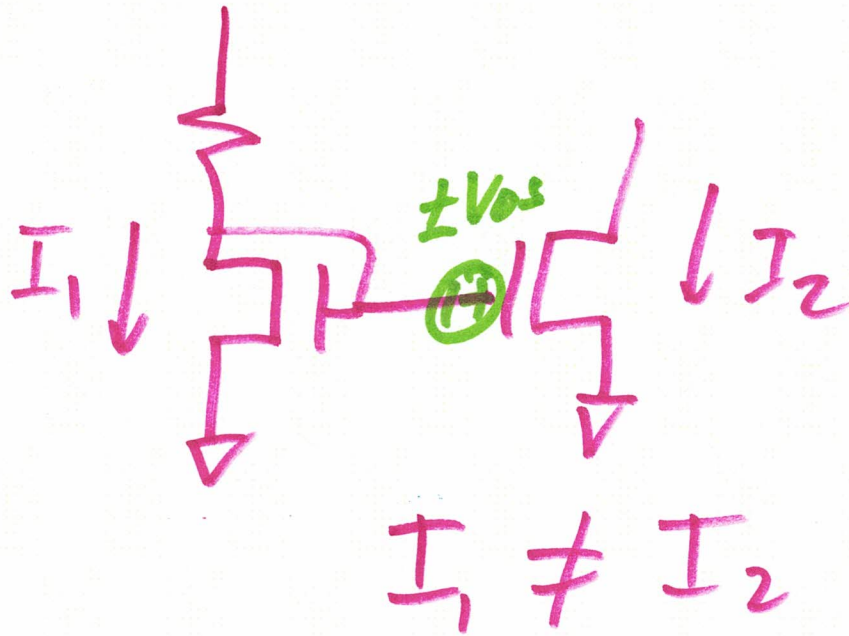5)

$$I_D = \frac{K_P}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$



6)