

Quiz #12 EE 420/ECG 620 Spring 2019 Name: _____

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Plot the current that flows in V_{in} against V_{in} for V_{in} varying between -5 and 5 V. (5 points)

