

Quiz #5 EE 420/ECG 620 Spring 2019

Name: _____

Open book and closed notes.

Show your work for credit and place a box around each of your answers.

For the 1 μm book process used below: $V_{THN} = 800 \text{ mV}$, $V_{THP} = 900 \text{ mV}$, $KP_n = 120 \text{ } \mu\text{A}/\text{V}^2$, and $KP_p = 40 \text{ } \mu\text{A}/\text{V}^2$.

1. Calculate the AC and DC voltages and currents in the following circuit. (5 points)

