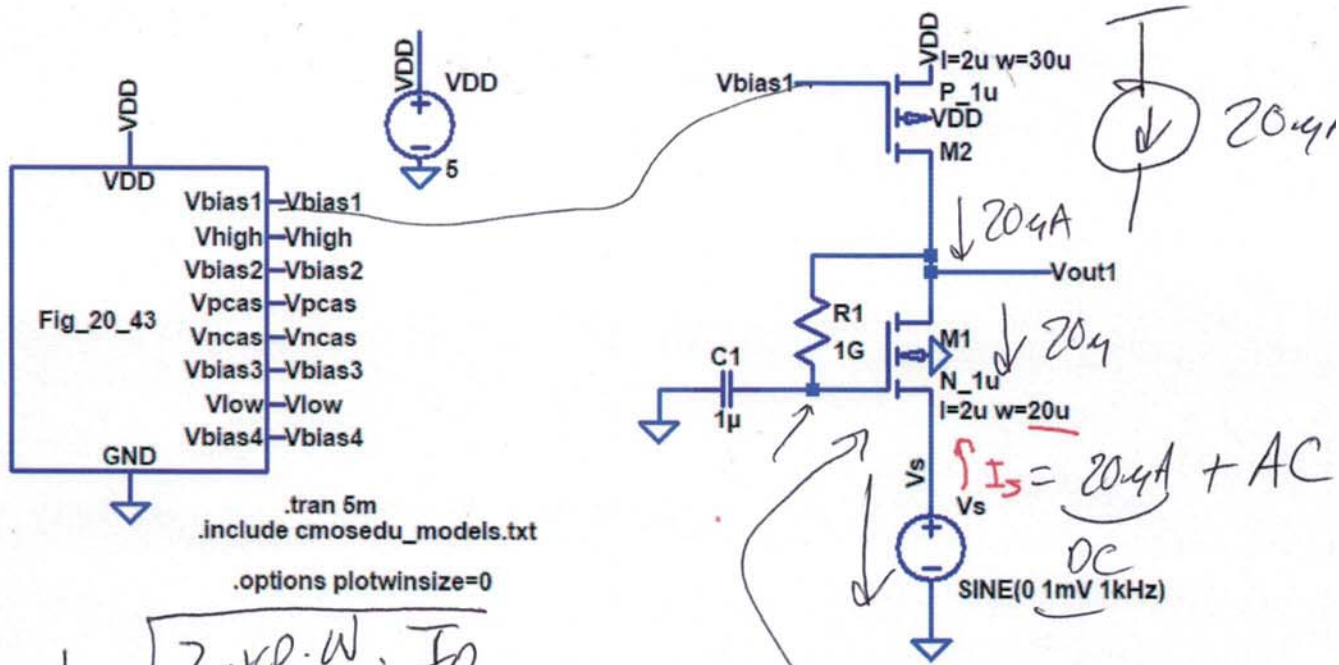


Open book and closed notes.

Show your work for credit and place a box around each of your answers.

$$1\mu V = 10^{-3} V \rightarrow 20 \log 10^{-3} = -60 \text{ dB} = 1\mu V$$

1. Estimate the input current, I_s , and thus the input resistance in the following circuit. (5 points)



$$g_m = \sqrt{2 \cdot \mu_p \cdot \frac{W}{L} \cdot I_D}$$

$$g_m = 150\mu = \sqrt{2 \cdot 120\mu \cdot \frac{10}{2} \cdot 20\mu}$$

$$g_m = \sqrt{2} \cdot 150\mu = \sqrt{2} \cdot 212\mu A = g_m$$

AC Ckt

$$\frac{1\mu V}{120\mu A} = 8.3K$$

