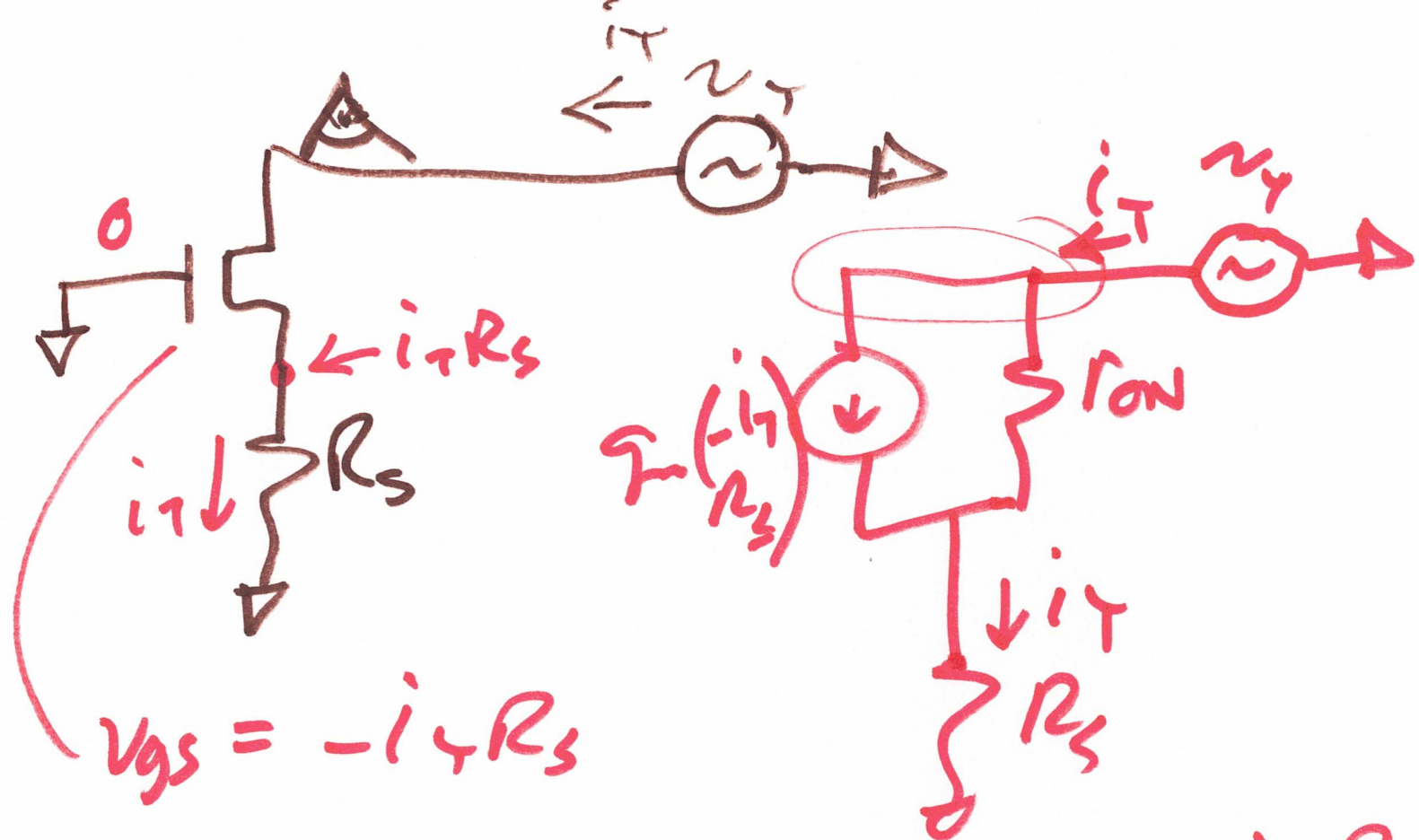


$$\frac{v_{out}}{v_{in}} = -g_m (r_{01} \parallel r_{02})$$

$$\frac{v_{out}}{v_{in}} = \frac{-333.3 \frac{V}{V}}{\frac{1}{g_m}}$$

2



$$i_S = g_m (-i_T R_s) + \frac{v_T - i_T R_s}{r_{on}}$$

$$i_T (r_{on} + g_m R_s r_{on} + R_s) = v_T$$


$$\frac{v_T}{i_T} = r_{on} (1 + g_m R_s) + R_s$$

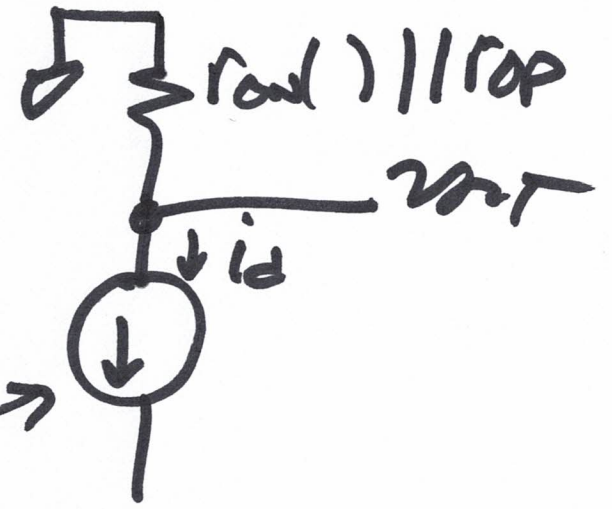3)



$R_S = \frac{1}{g_m}$
 $2 \cdot R_S$

$$\frac{v_{OUT}}{v_{IN}} = \frac{-i_D \cdot r_{OD} \parallel r_{OP}}{g_m \left(\frac{1}{g_m} + R_S \right)}$$




$$g_m (v_{IN} - i_D \cdot R_S) = i_D$$

$$v_{IN} = i_D \left(\frac{1}{g_m} + R_S \right)$$

4)


Miller's Theorem

$$Cv = Q$$

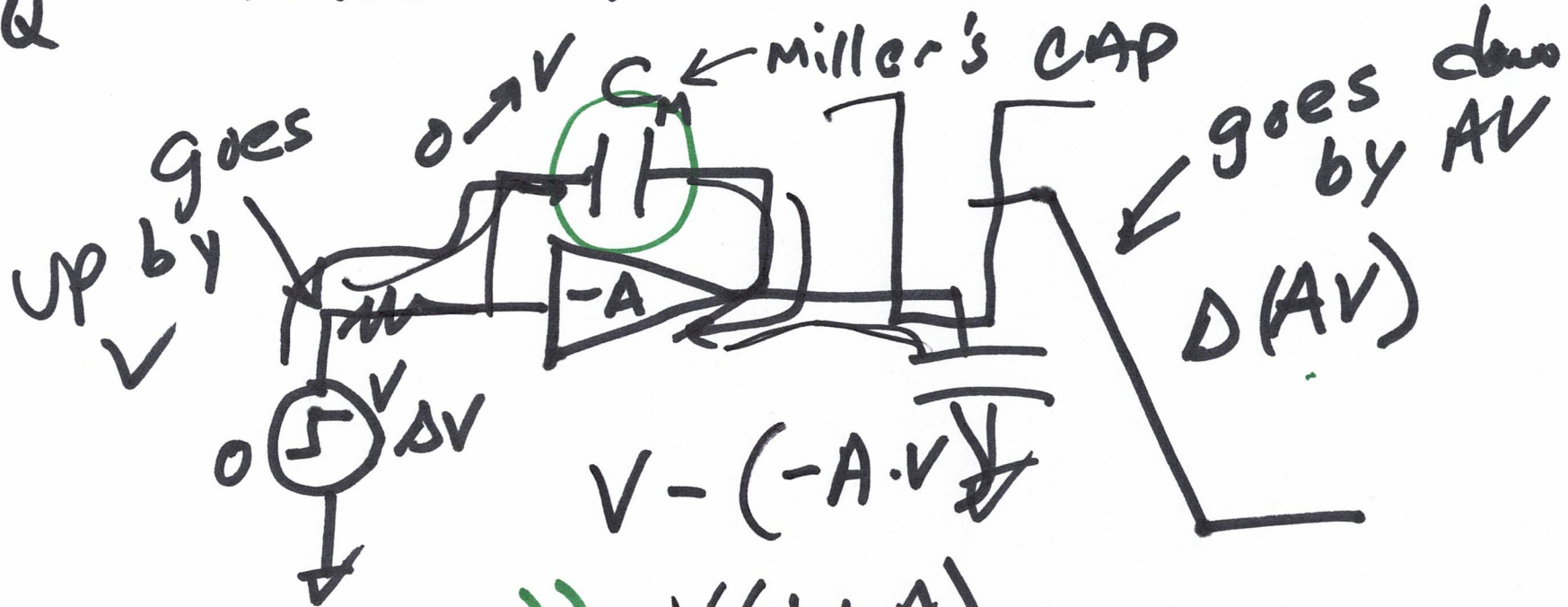

$$Q = C_m (V - (-AV)) = C_m V (1 + A)$$


$$= C_m V (1 + A)$$

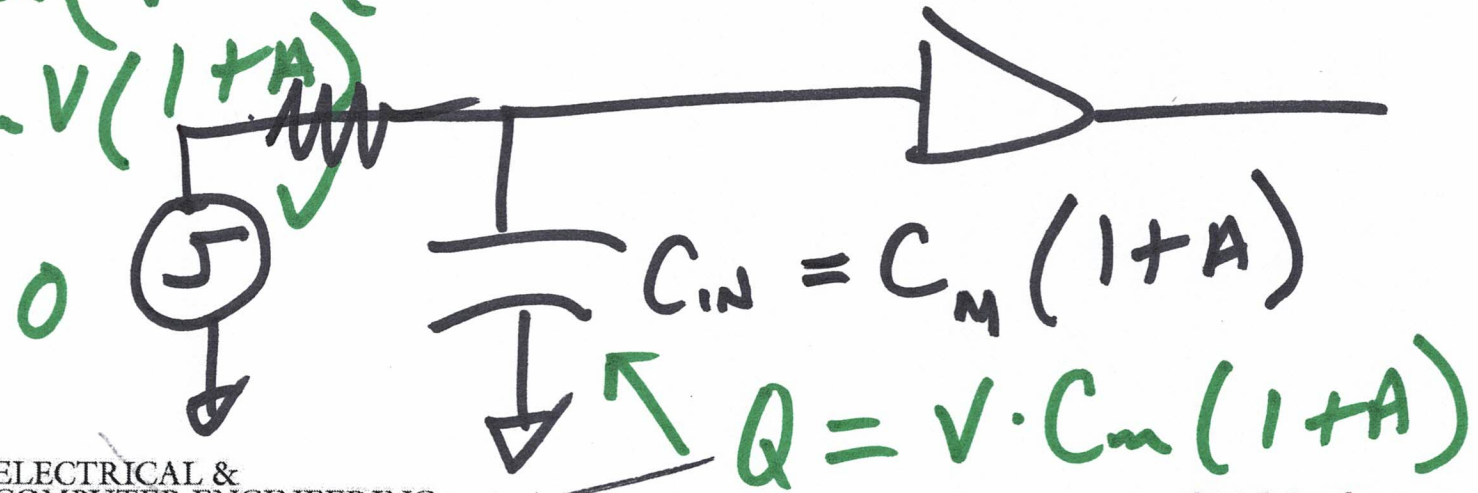


5)

RC

Millers Theorem

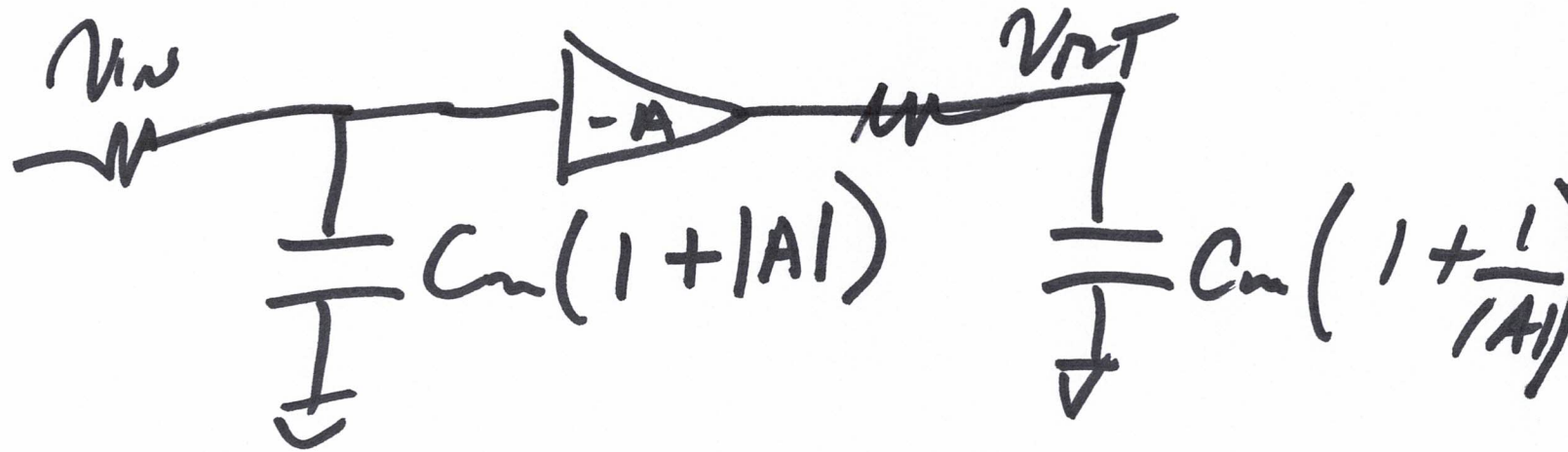


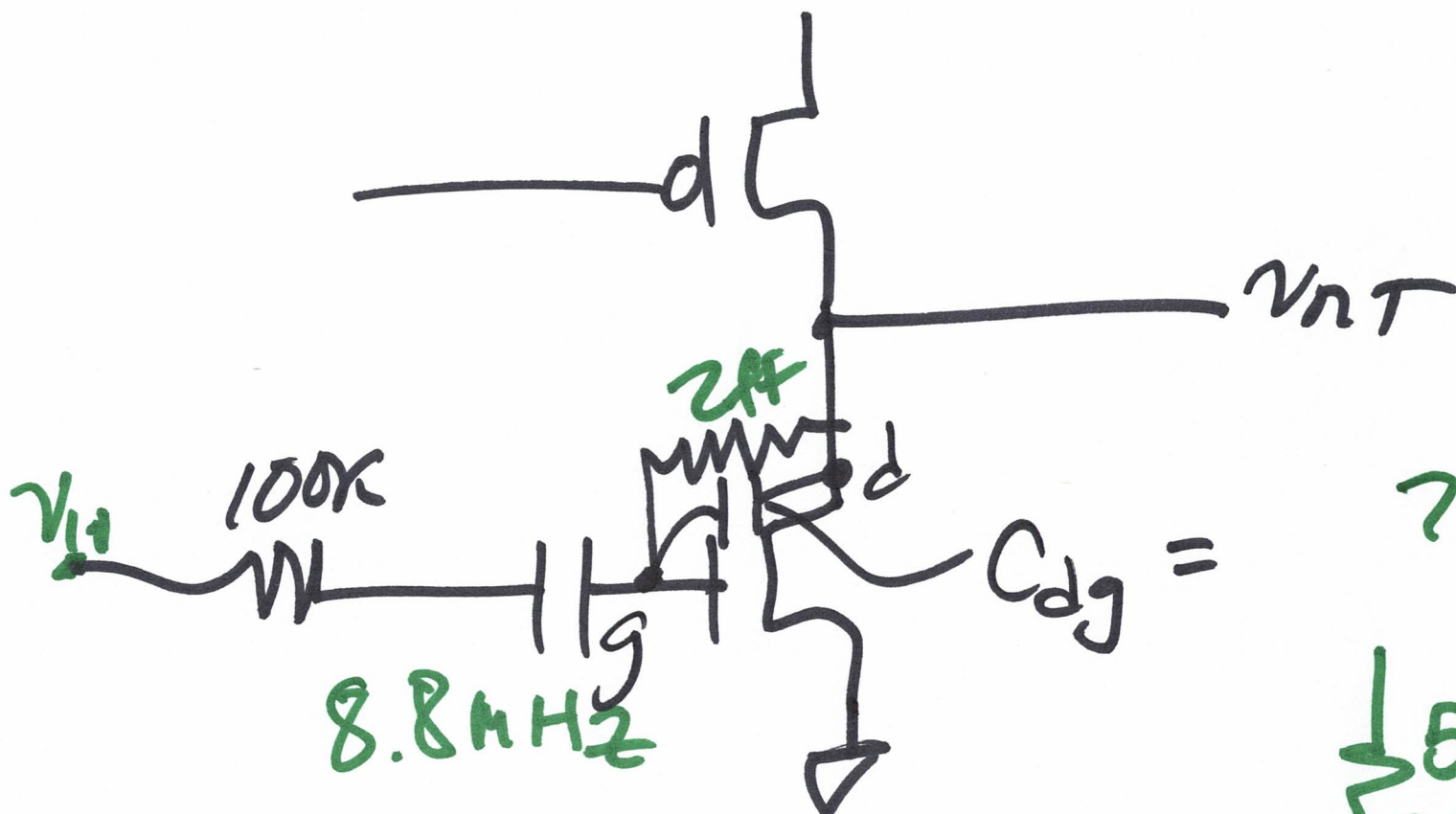

8.8 MHz

$C_{dg} =$

79 MHz

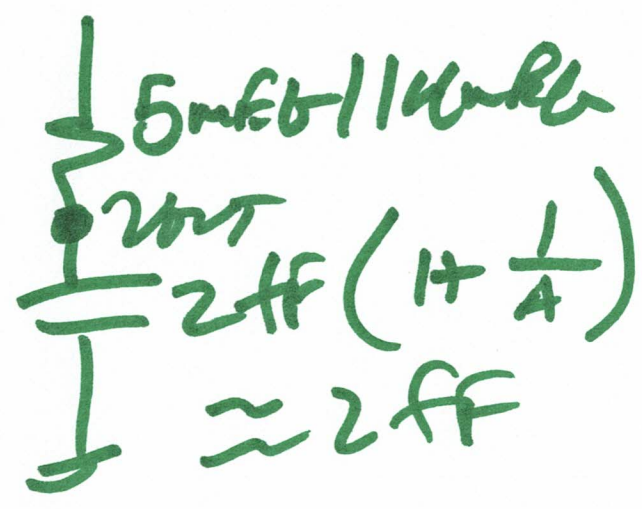

$$2fF (1 + 90) \approx 180fF$$

$$f_{3dB} = \frac{1}{2\pi \cdot 10^5 \cdot 180fF}$$

7)