

EE 420 / ECG 620


Analog IC Design

Semper Fidelis

Sempiternus

Lecture 13

March 9, 2020

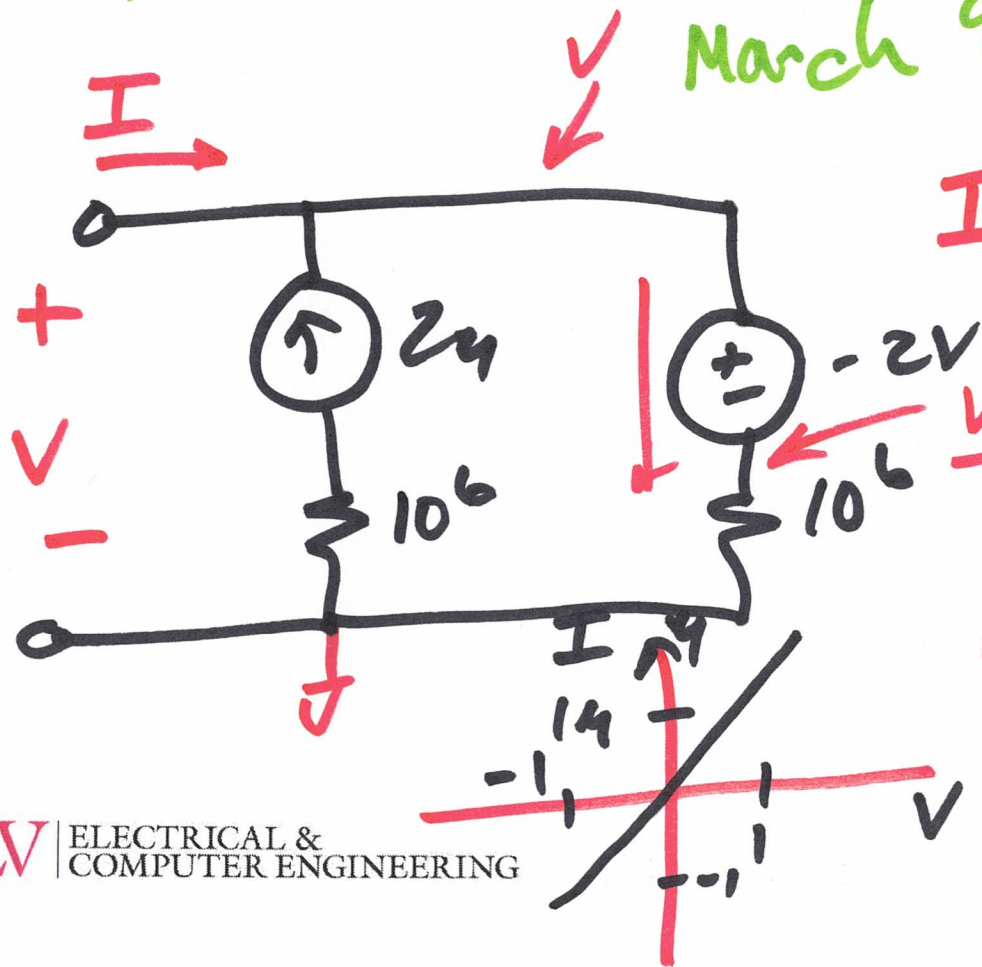

$$I + 2 = \frac{V - (-2)}{10^6}$$


$$\frac{V + 2}{10^6}$$

$$10^6 \cdot I + 2 = V + 2$$

$$I = V \cdot 10^{-6}$$

$$V_{SG} = \sqrt{\frac{2I_D}{K_P \frac{W}{L}}}$$


+44HP

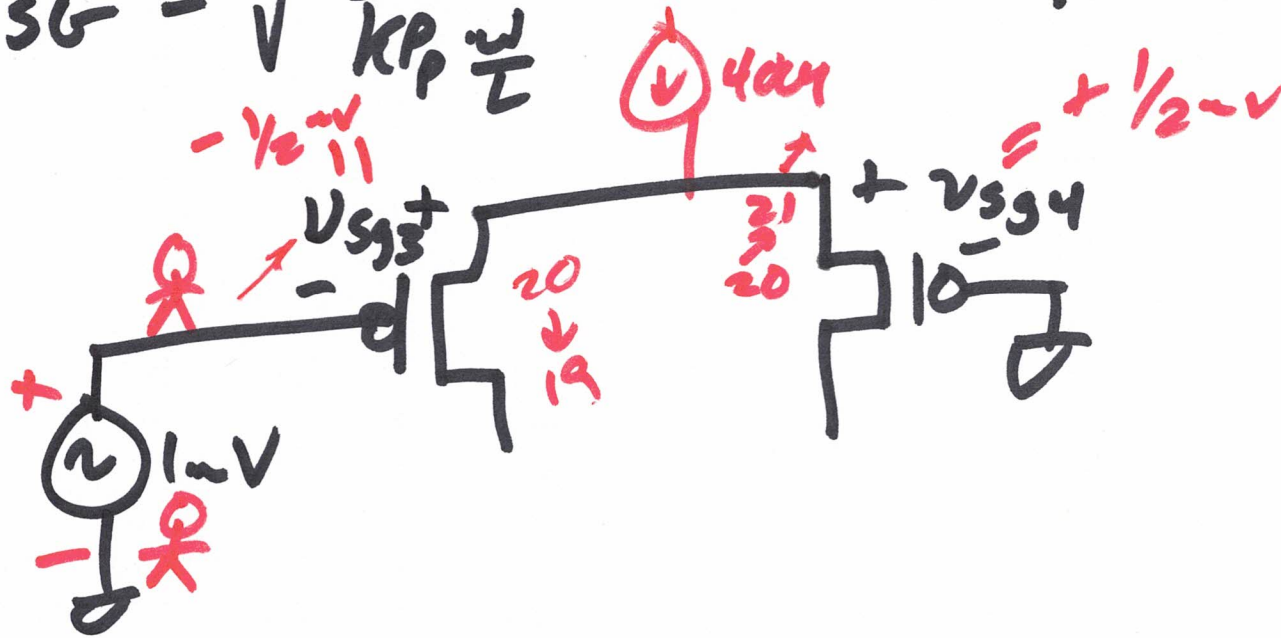


$$1\text{mV} + V_{sg3} - V_{sg4} = 1/2\text{mV} - 1/2\text{mV}$$


$$1\text{mV} = V_{sg4} - V_{sg3}$$

2)

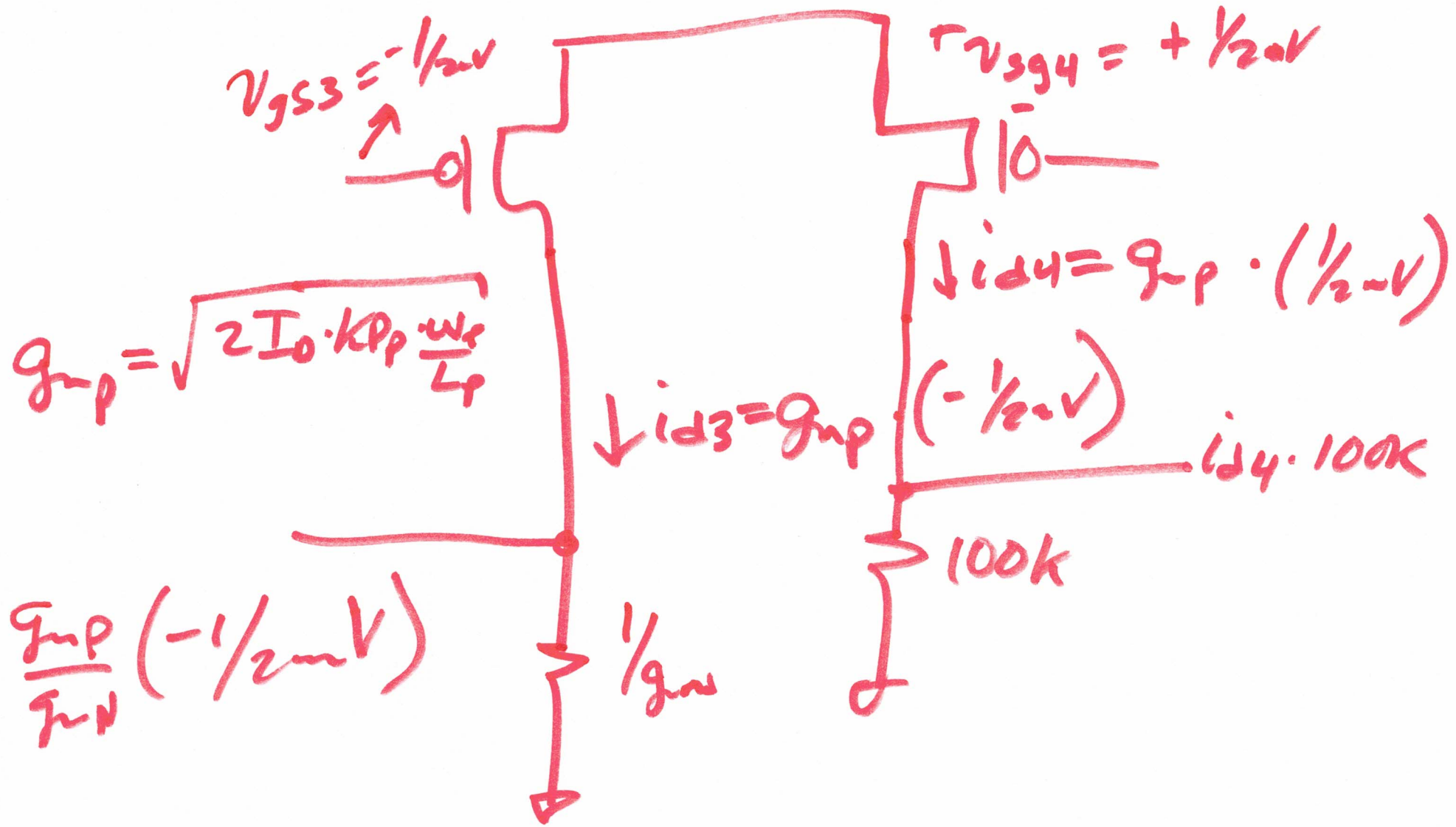

3)

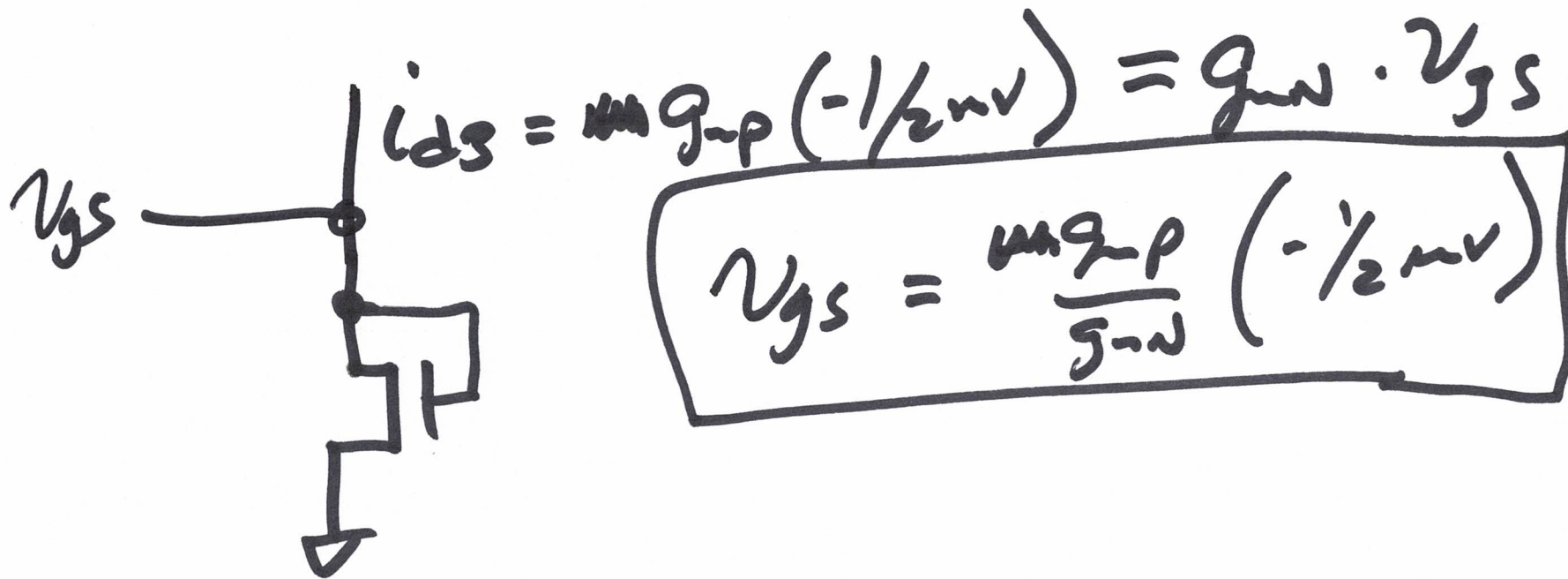

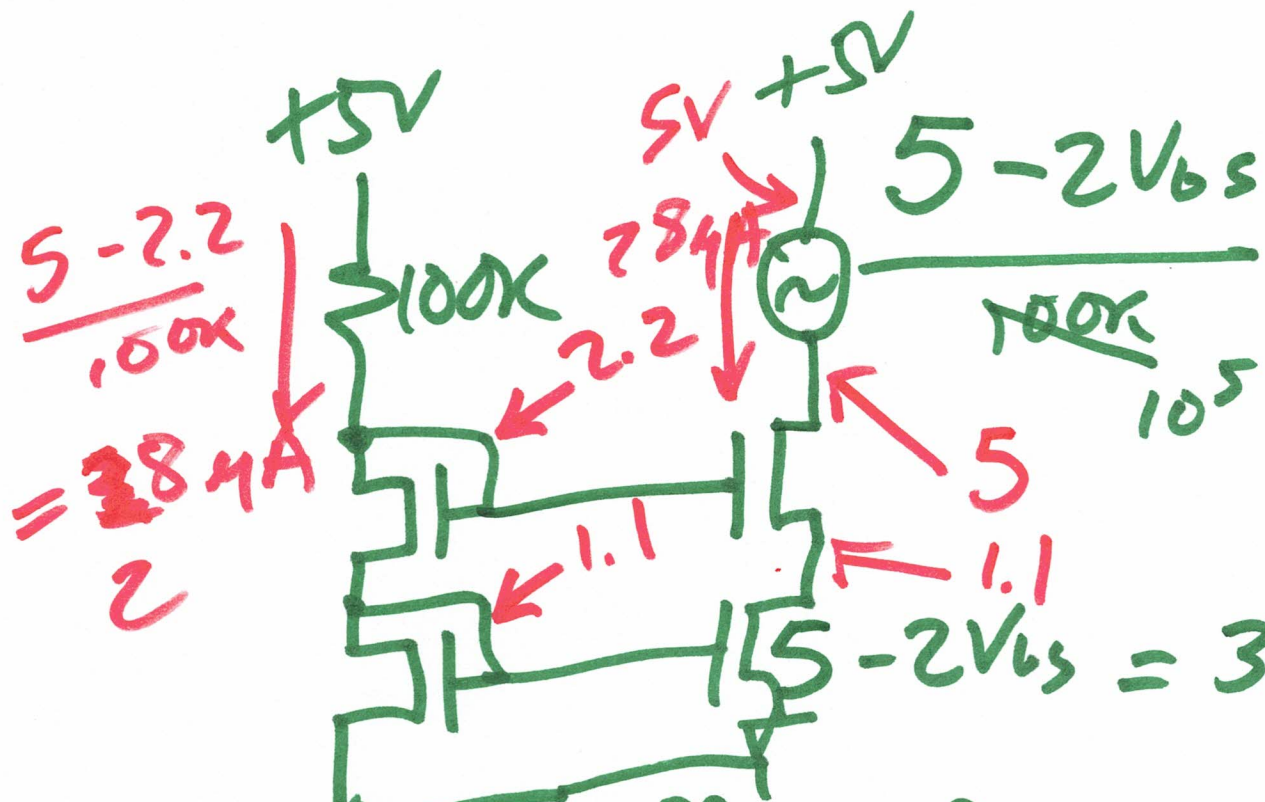

$$= \frac{1200 \cdot 10^{-5}}{2} \left( V_{bs} - 0.8 \right)^2$$

$$5 - 2V_{bs} = 30 \left( V_{bs}^2 - 1.6V_{bs} + 0.64 \right)$$


$$V_{bs} = \frac{1.53 \pm \sqrt{2.34 - 1.89}}{2} \quad 48 \quad -1.6V_{bs} + 19.2 = 5 - 2V_{bs}$$

$$= \frac{1.53 \pm .67}{2} \quad 30V_{bs}^2 - 46V_{bs} + 14.2 = 0$$

$$V_{bs}^2 - 1.53V_{bs} + .473 = 0$$

$V_{bs} = 1.1V$

5)

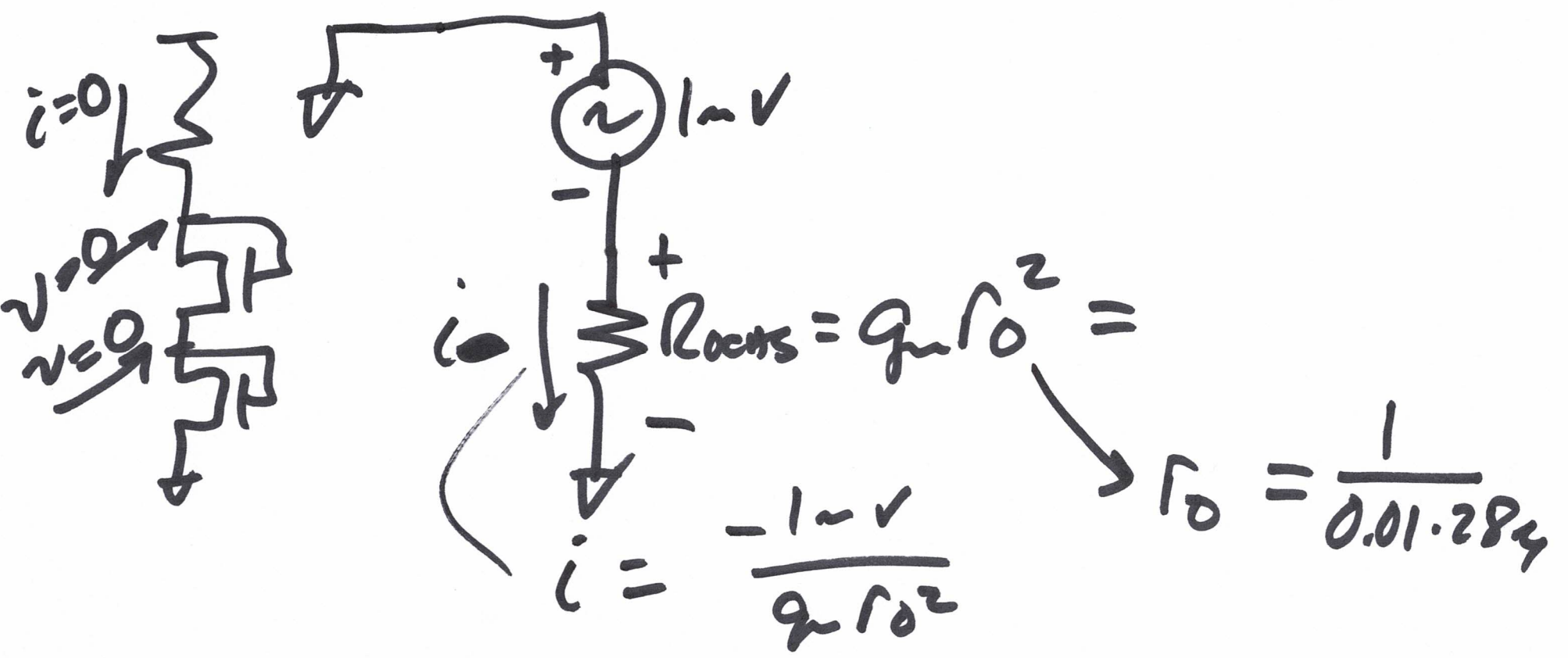

$$V_{GS1} = \sqrt{\frac{4I \cdot 2'}{K_P \cdot 10}} + 0.8$$

$$V_{GS2} = \sqrt{\frac{2I}{K_P \cdot \frac{10}{2}}} + 0.8$$

$$I = \frac{V_{GS1} - V_{GS2}}{R}$$

