
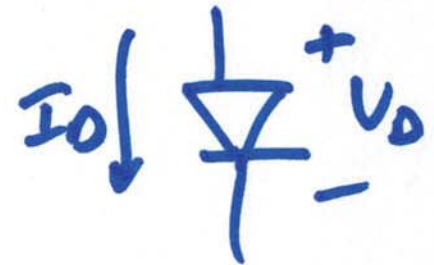


EE 420/ELG 620

Analog IC Design


Jan. 22, 2020

Lecture 1

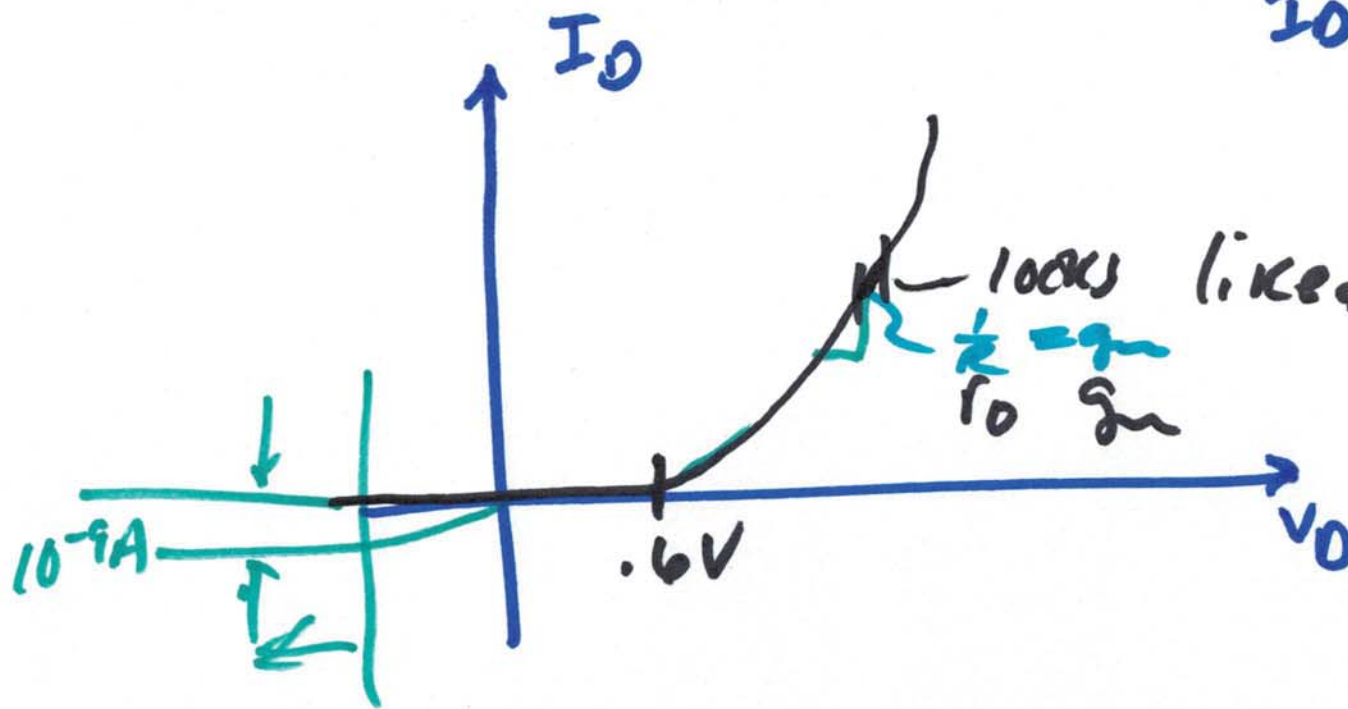

looks like a resistor  
 $\frac{1}{I_D} = \frac{1}{I_0}$

# IV curves

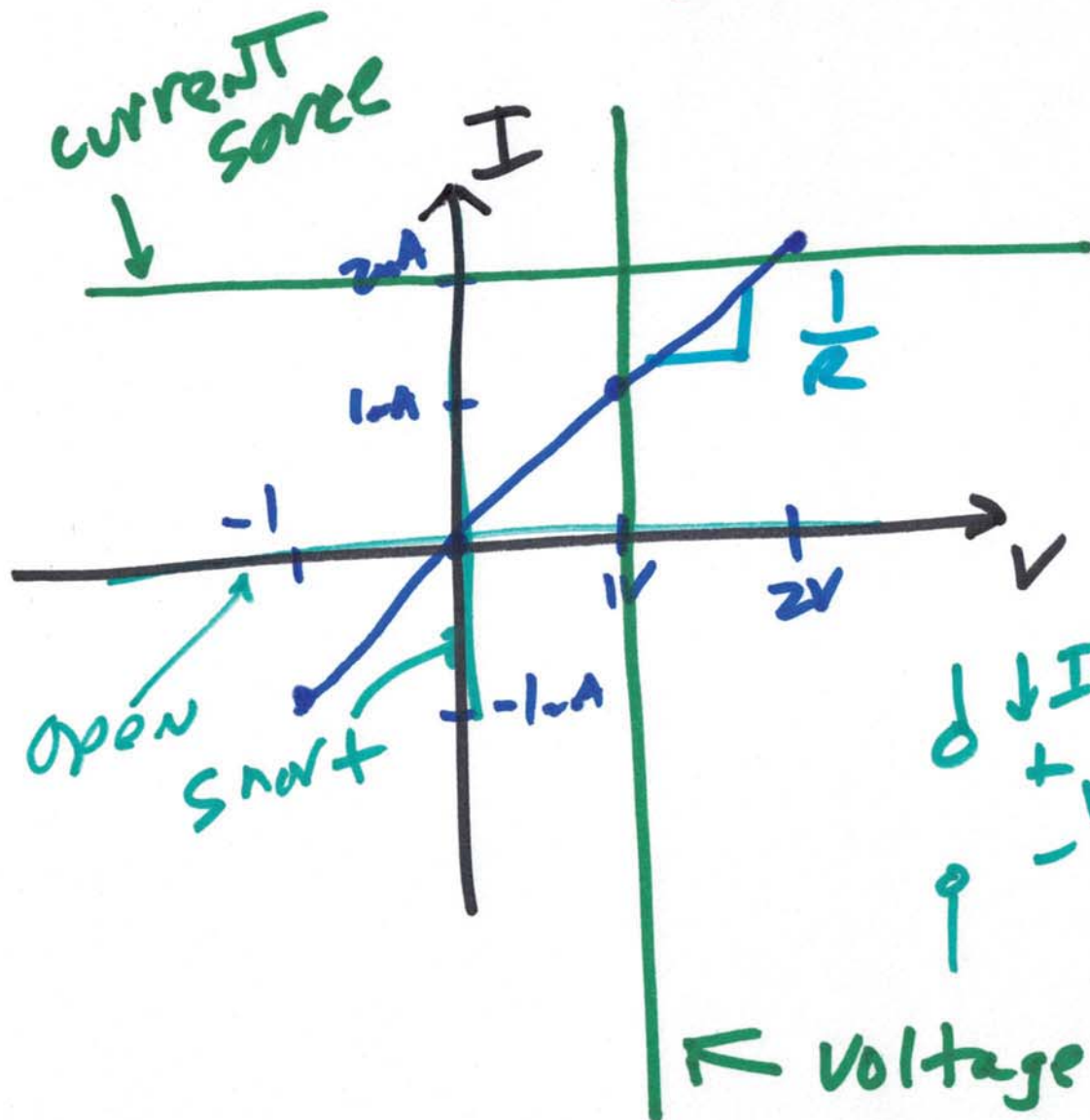



$I \downarrow$

$\sqrt{+}$


$-V$

$1K$


$$I = \frac{1V}{1K} = 1\mu A$$

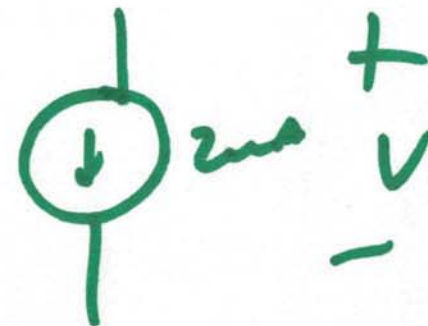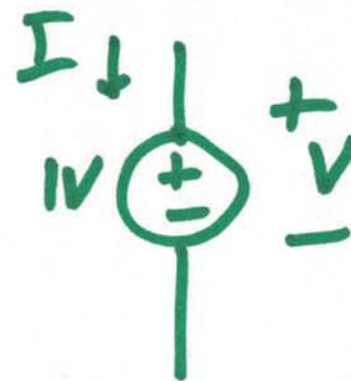


2)

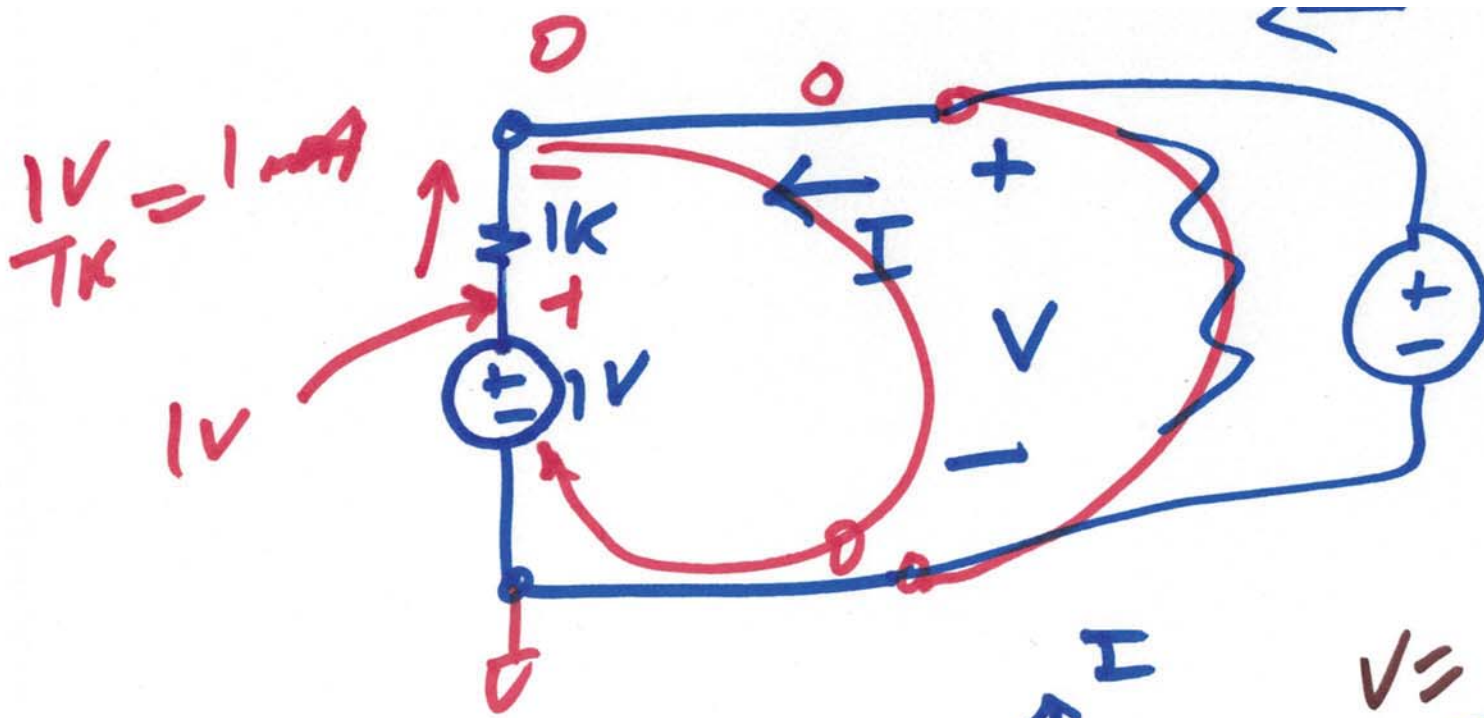

$1V$   
 $1k$   
 $= 1mA$

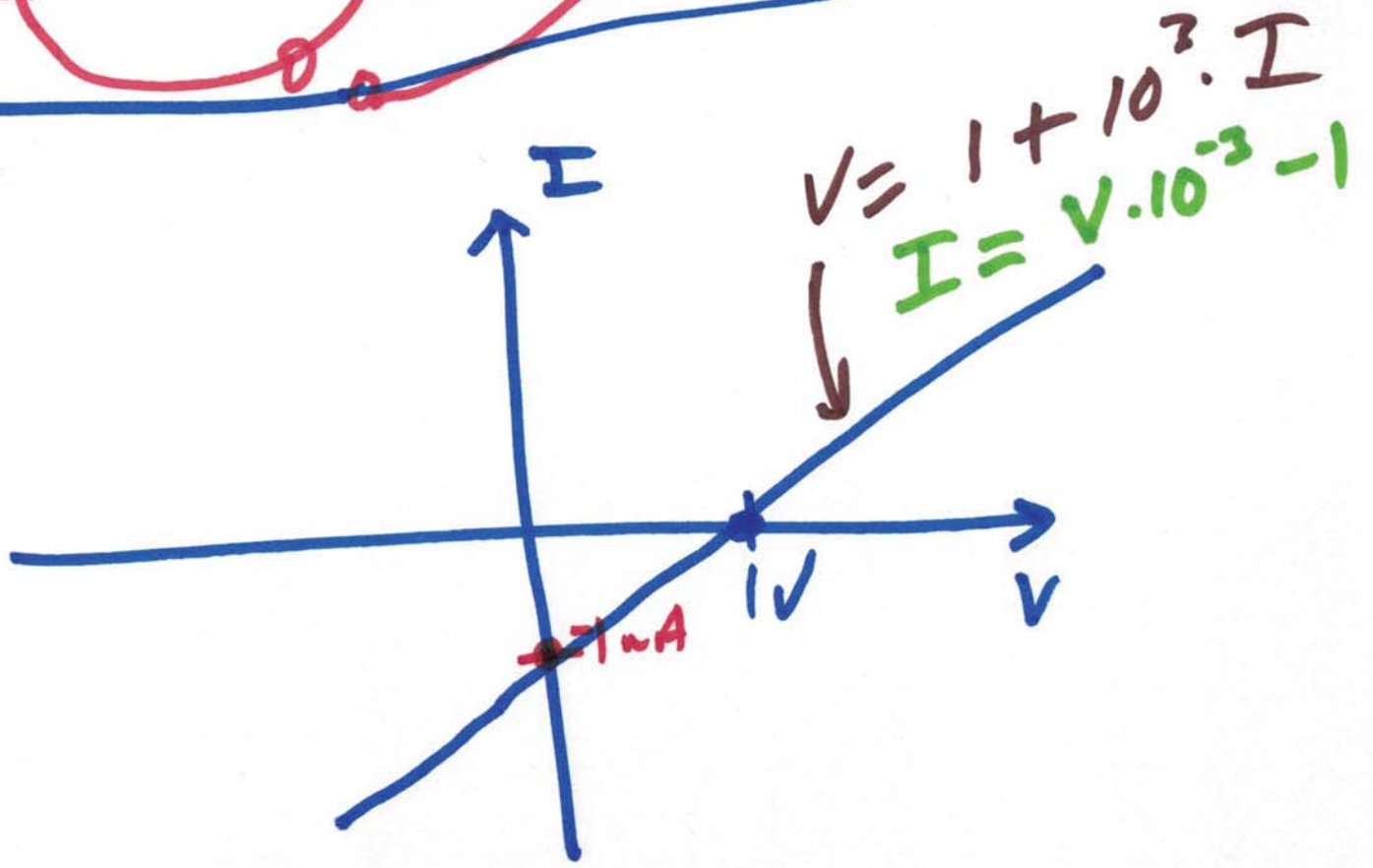


3)

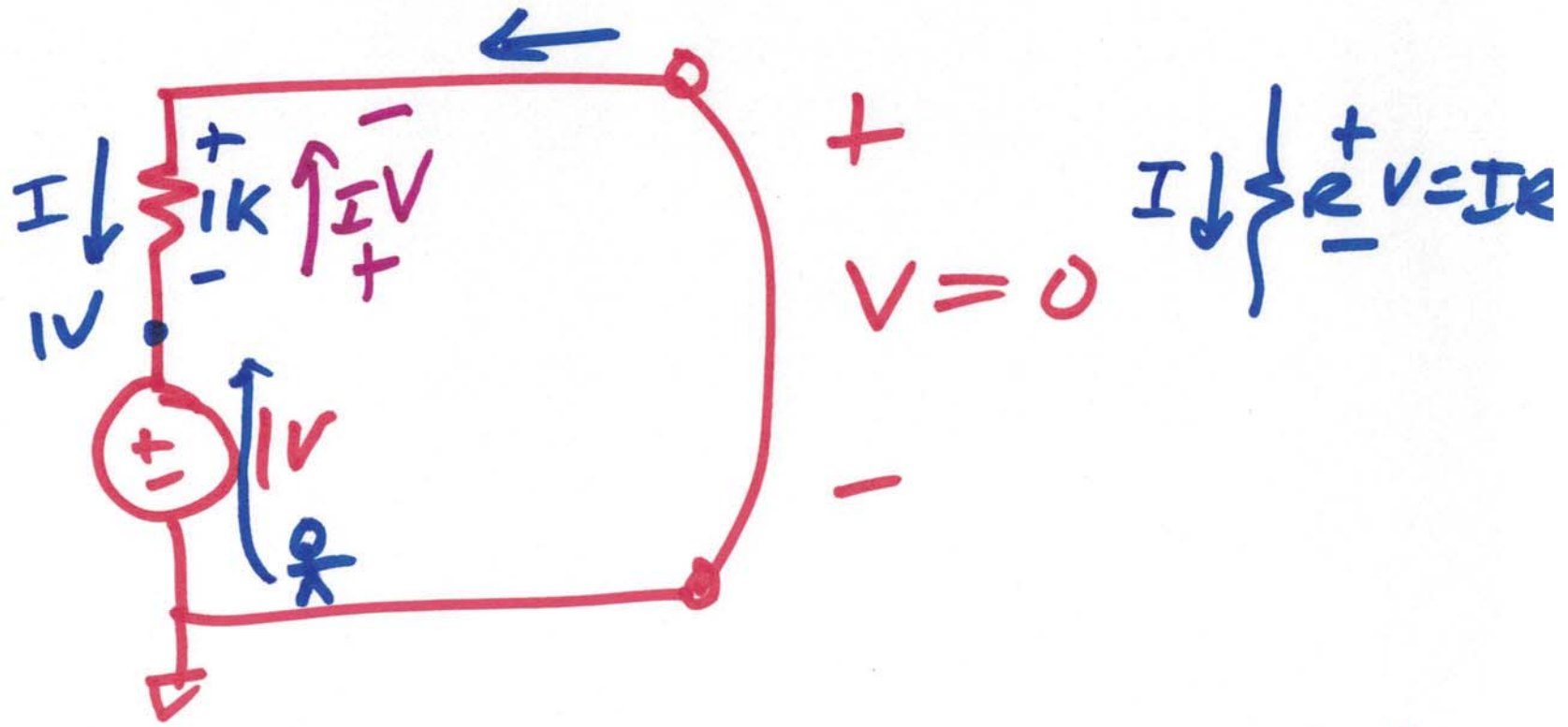

$$+1V + I \cdot 1k = 0, I = -1mA$$


$$+1V - I \cdot 1k = 0, I = 1mA$$

4)

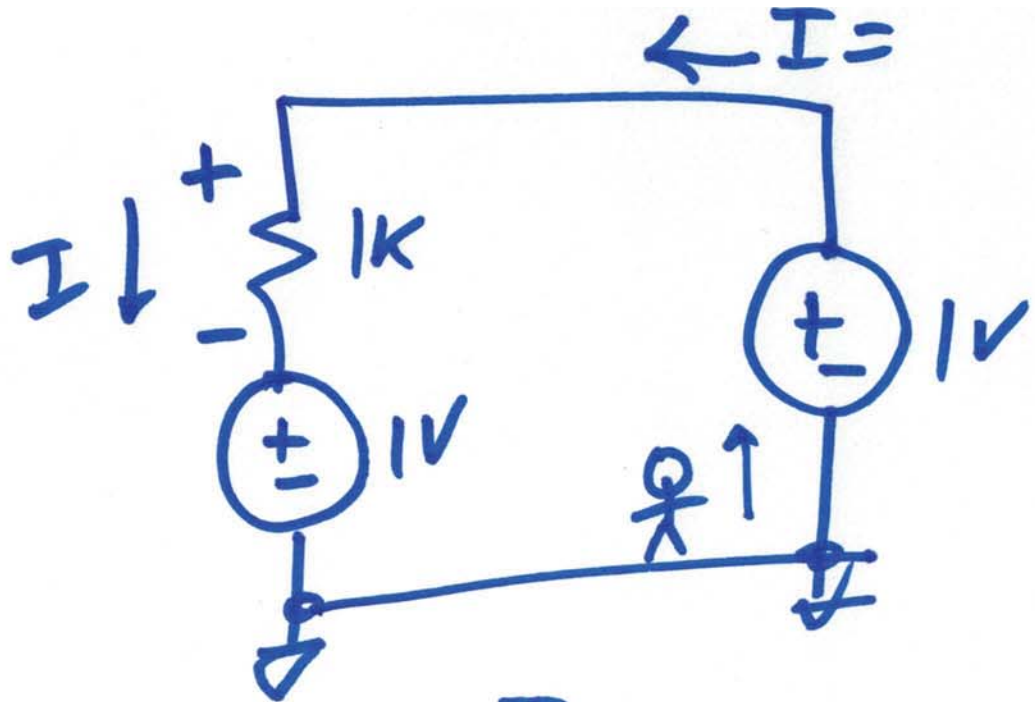

$$1V - I \cdot 1k - 1V = 0$$

$$I = 0$$

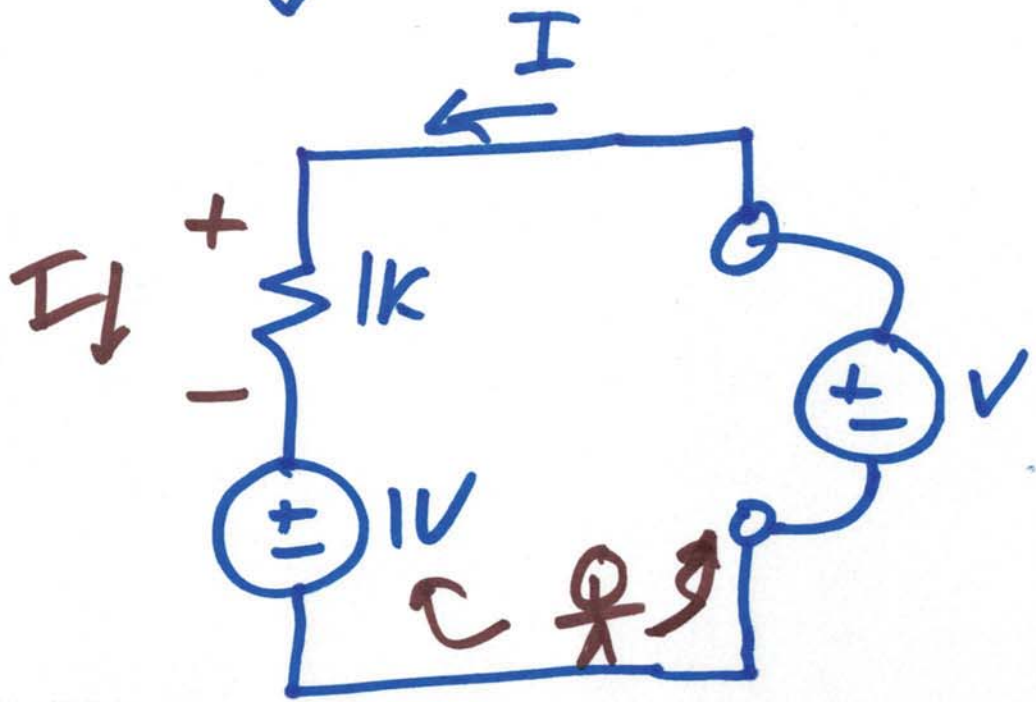


$$1 + I \cdot 1k - V = 0$$


$$V = 1 + 10^3 \cdot I$$

$$I = 10^{-3} V - 1$$



5)

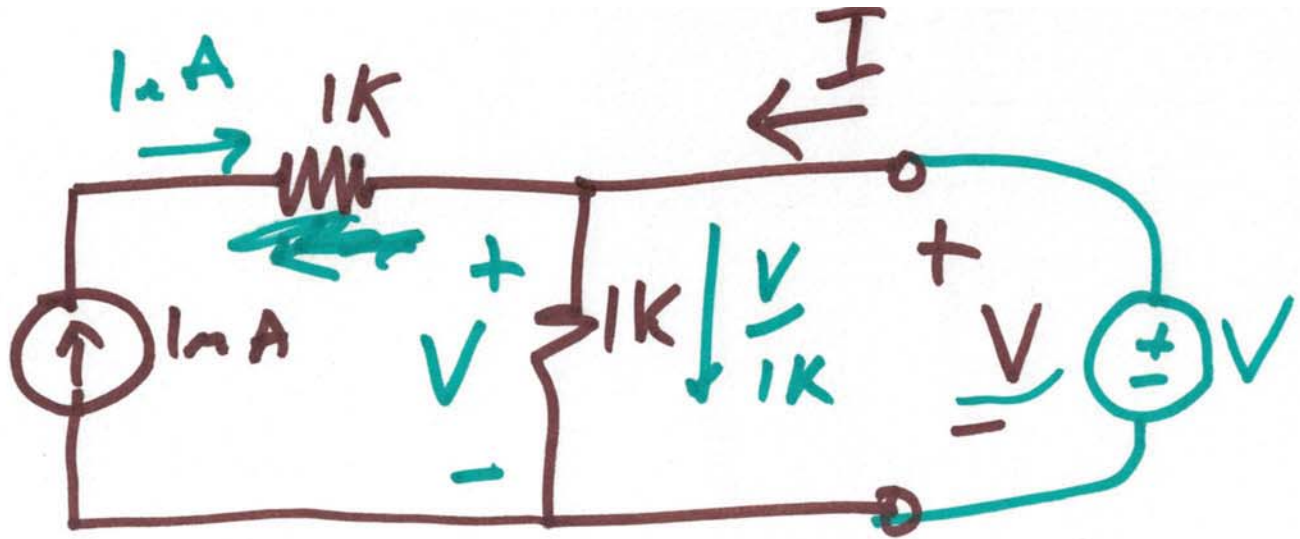
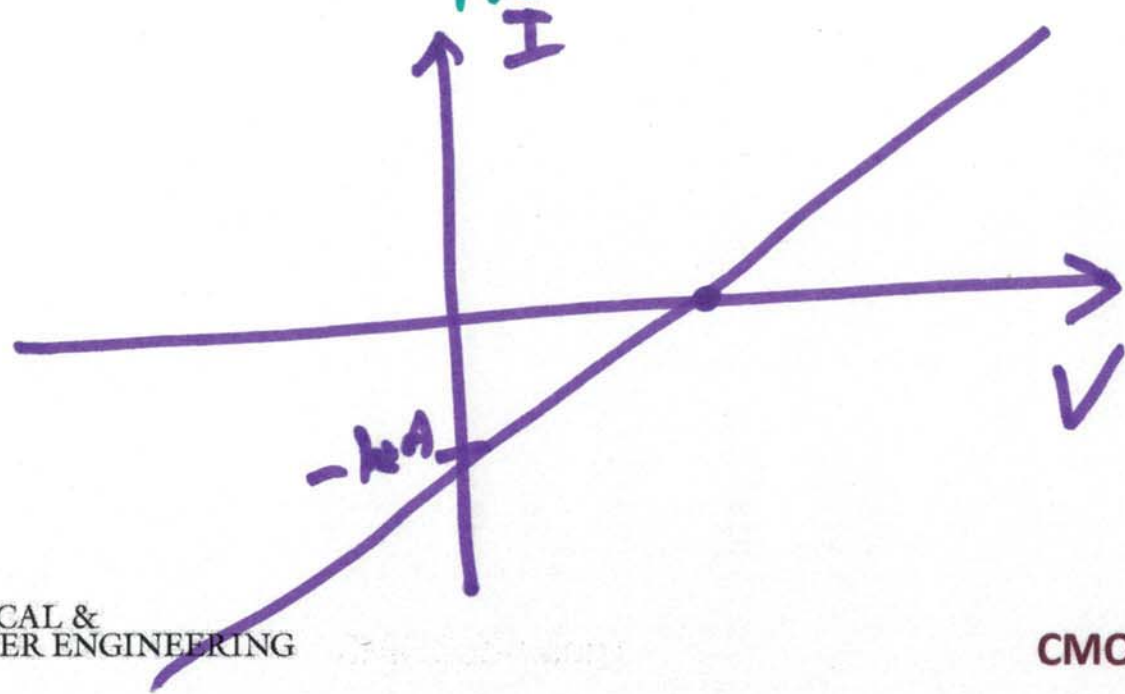
$$1\text{mA} + I = \frac{V}{1\text{k}} \rightarrow I = 10^{-3} V - 1\text{mA}$$



6)

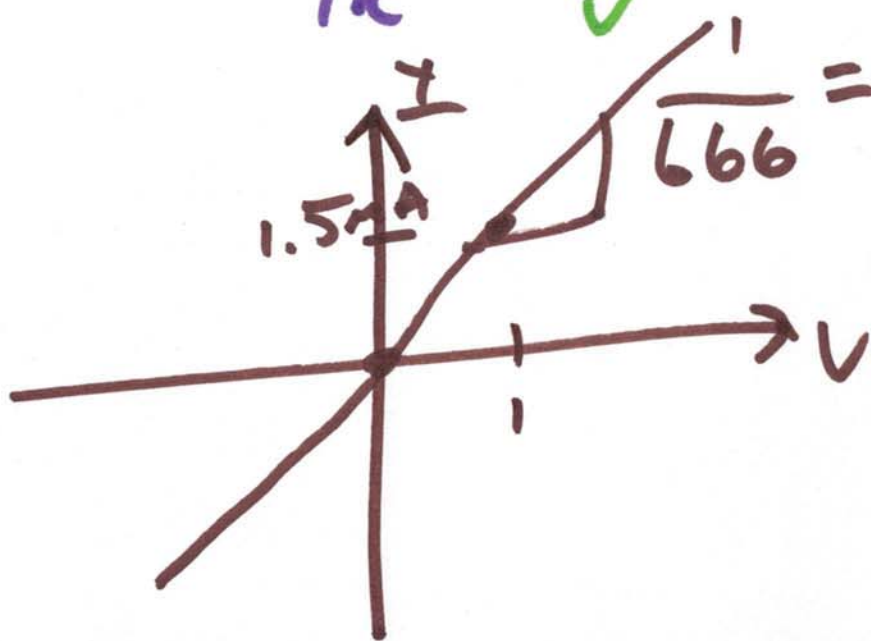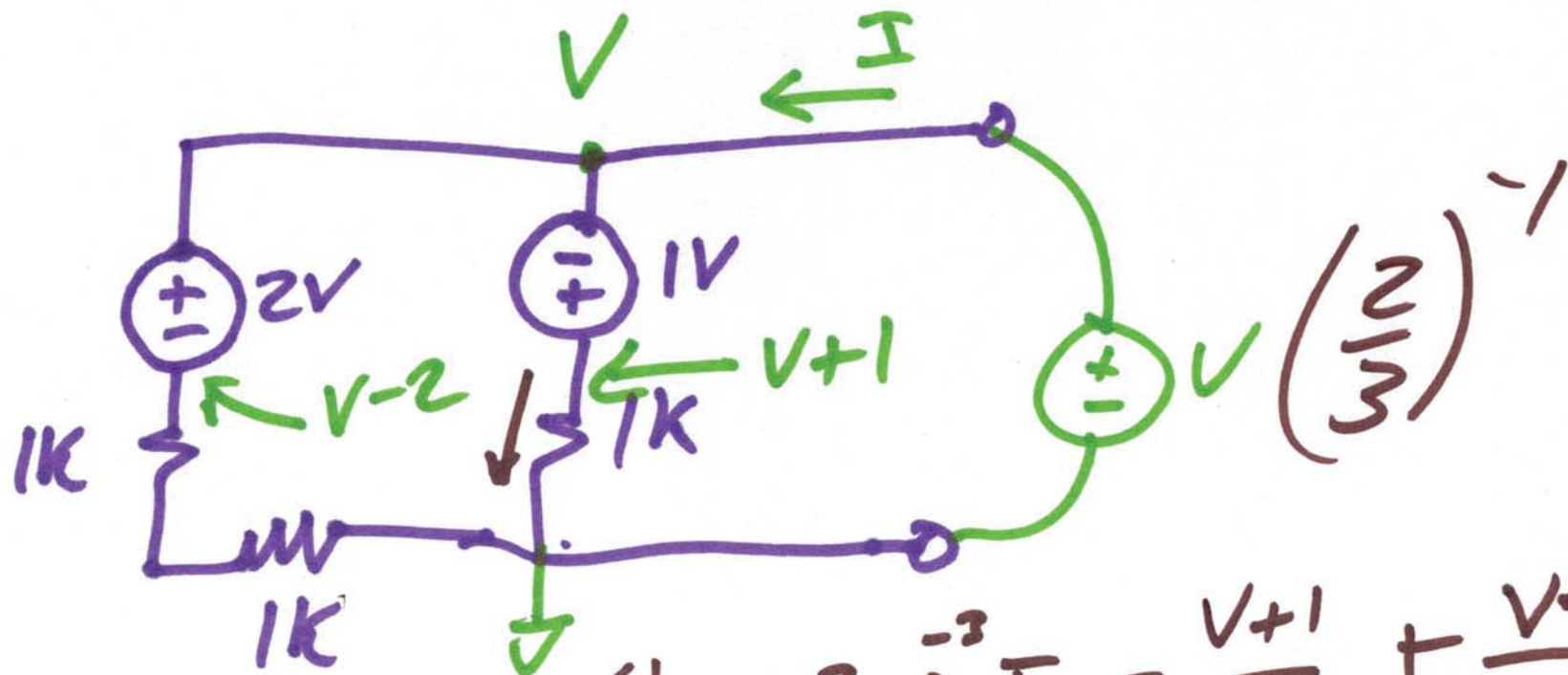


$$2kI = \frac{V+1}{1k} + \frac{V-2}{2k}$$

$$V = \frac{2}{3} k I$$

$$V = 666 I$$

$$I = \frac{1}{666} \cdot V$$


7)

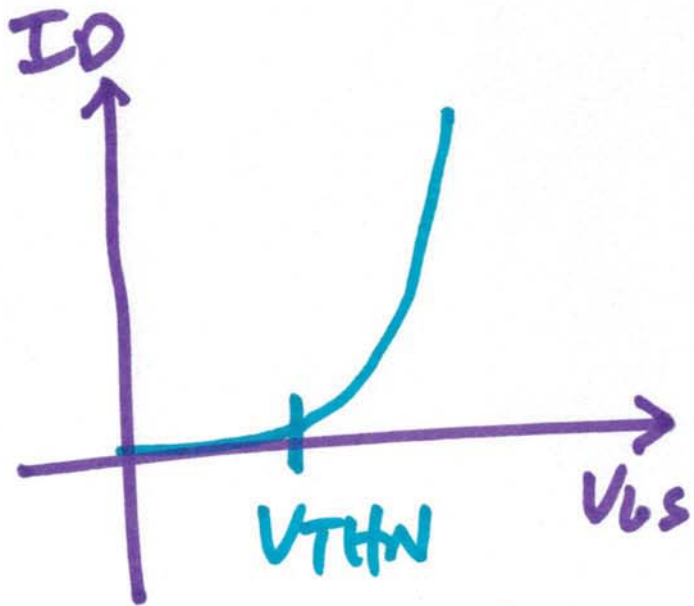

$\frac{3}{4}$  turn

$$V_{THN} = 0.8V$$

KP

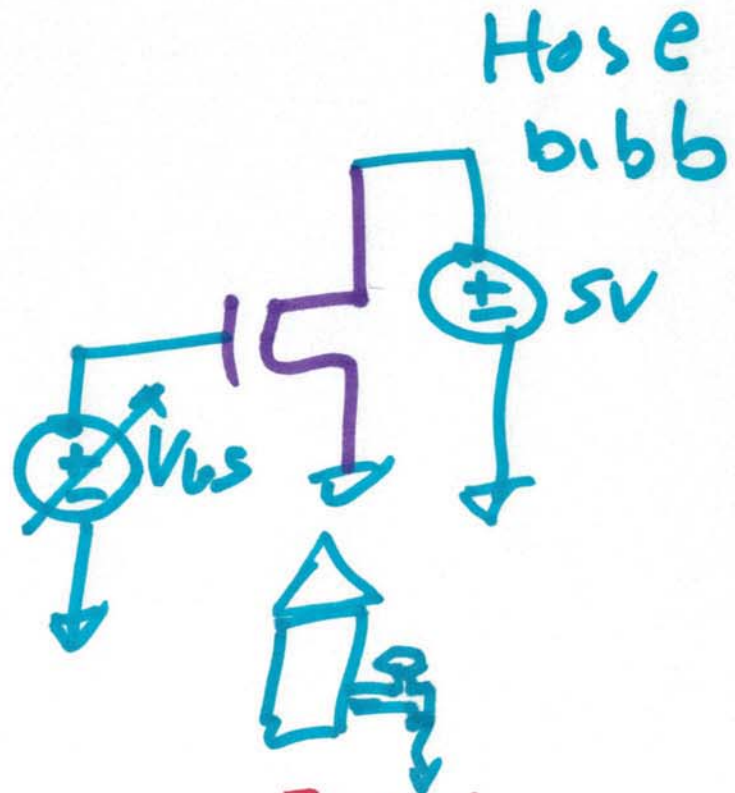


$$KP = \frac{.525\mu A}{5} \approx \frac{100\mu A}{V^2}$$



$$I_D = \frac{KP_N}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$\frac{104}{14}$





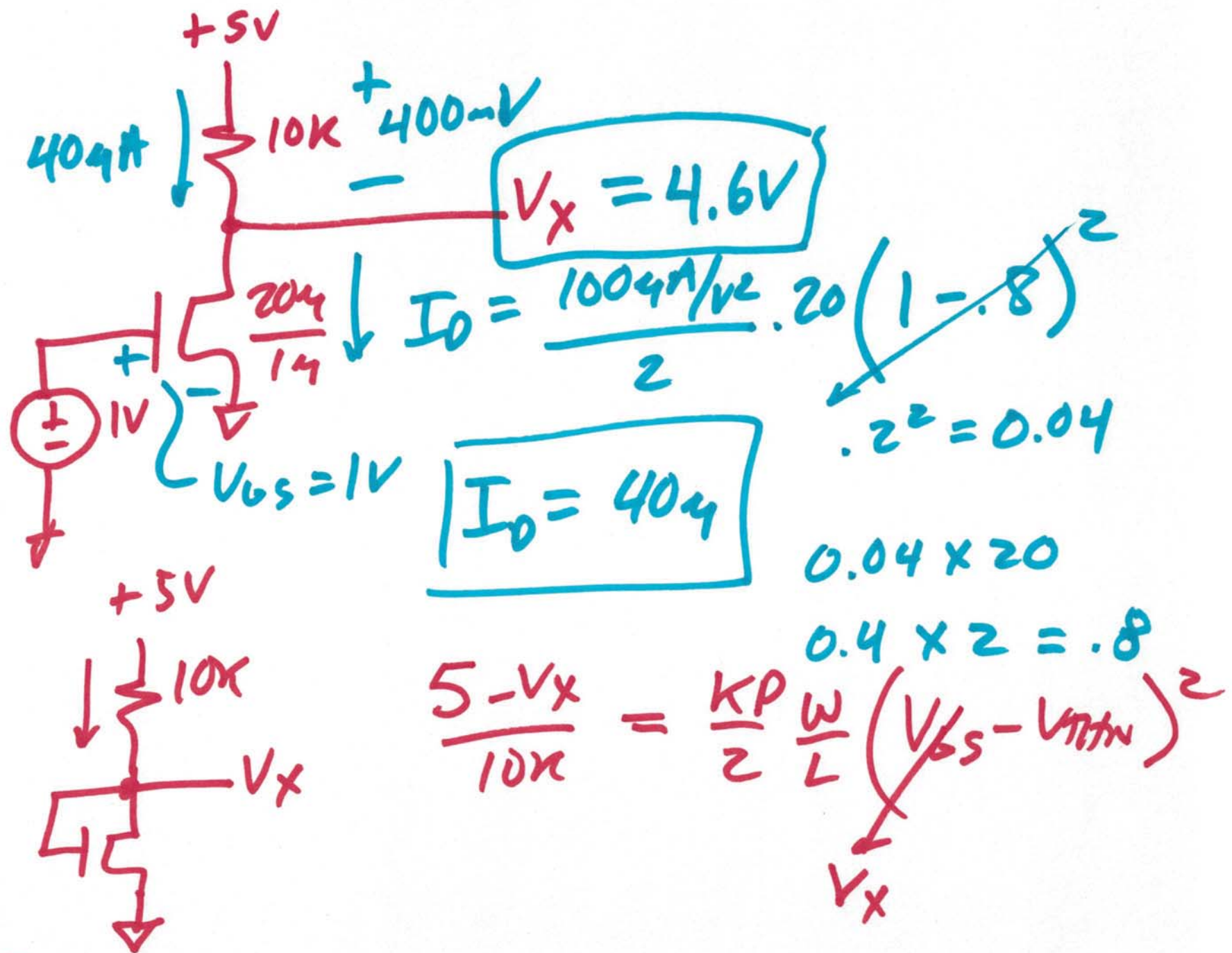

9)

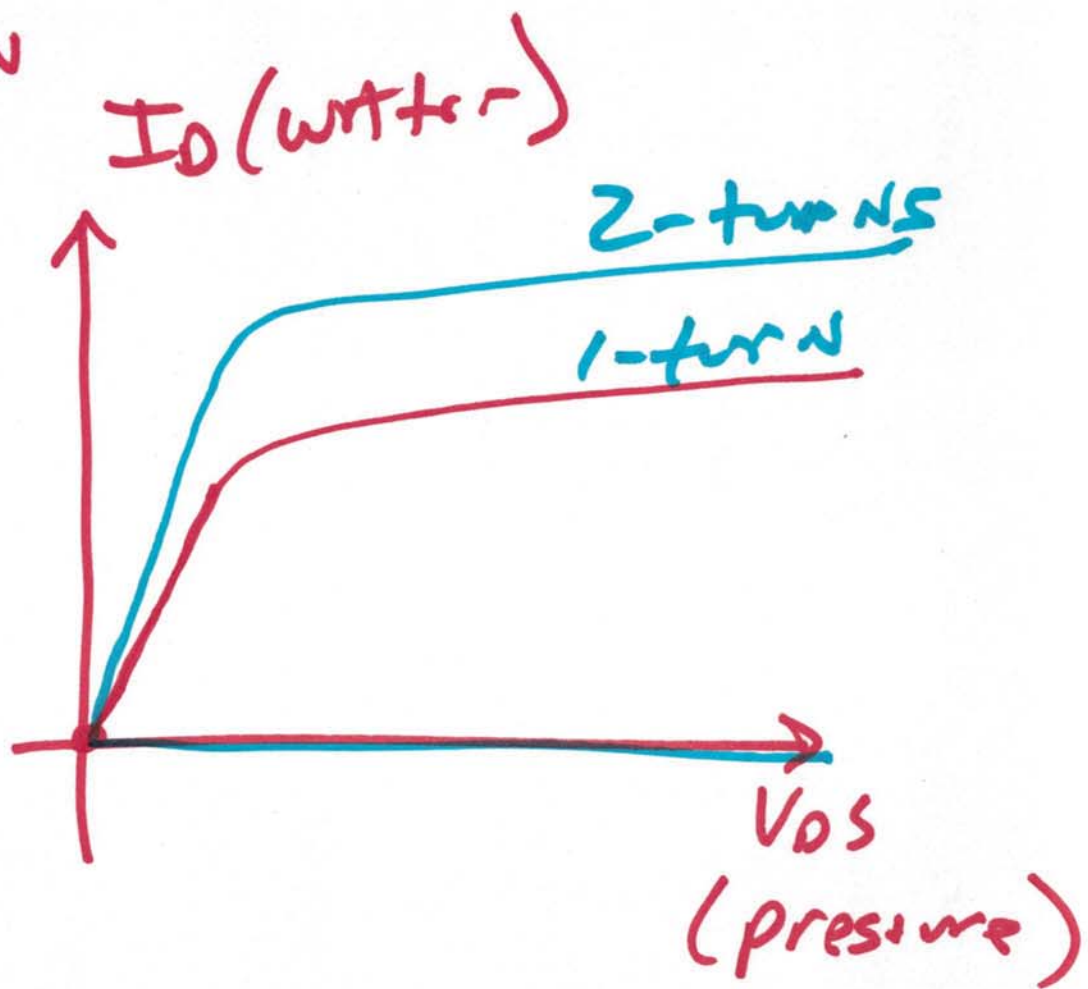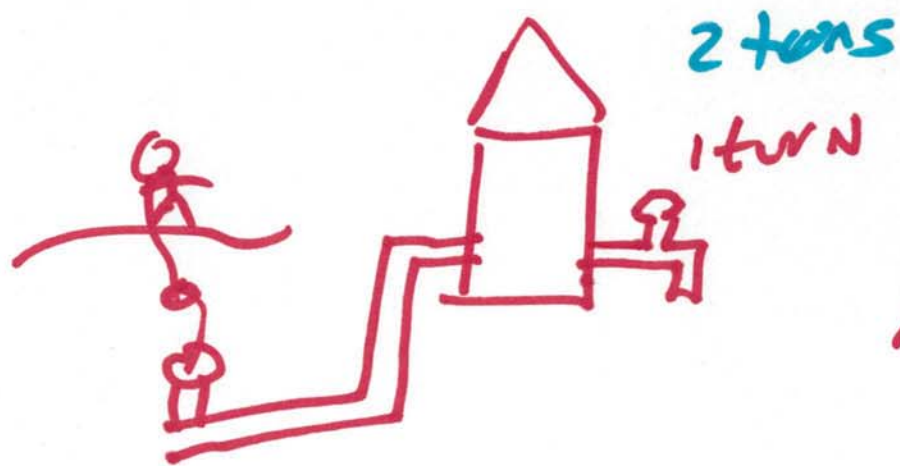

10)

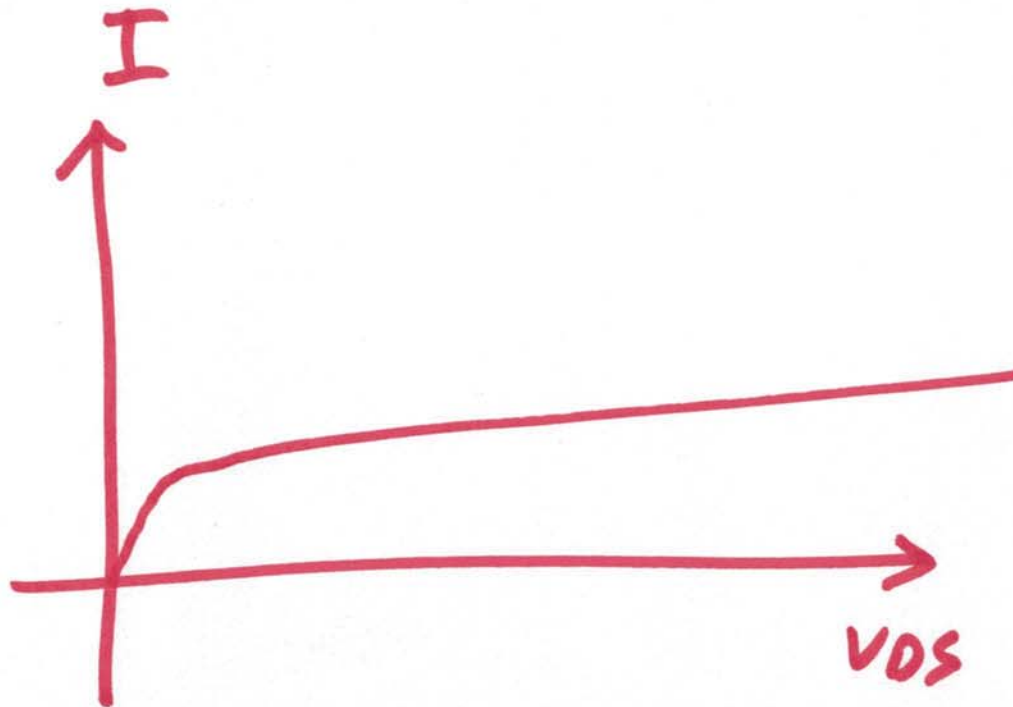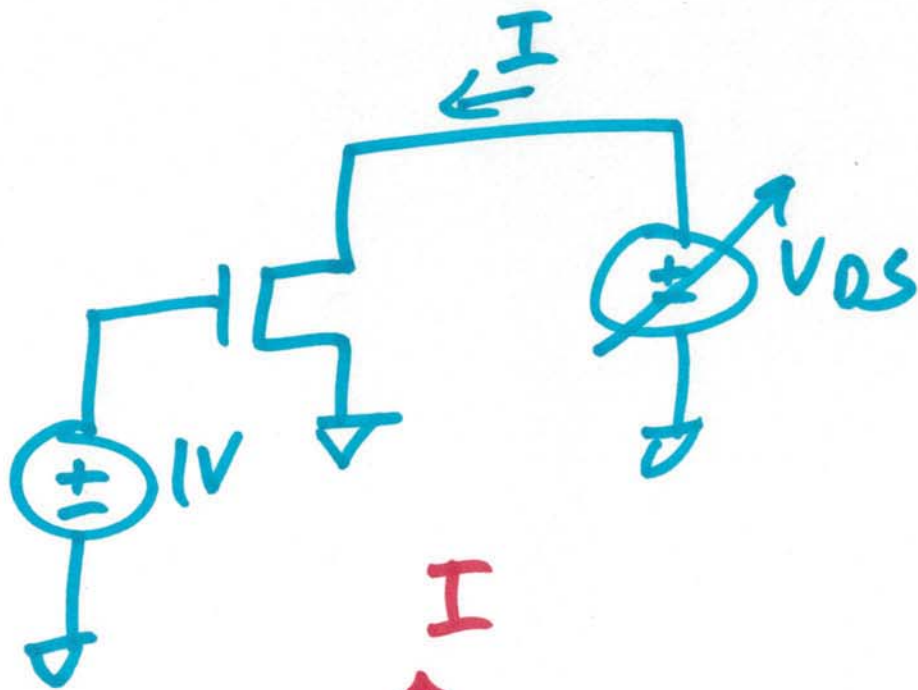

(1)