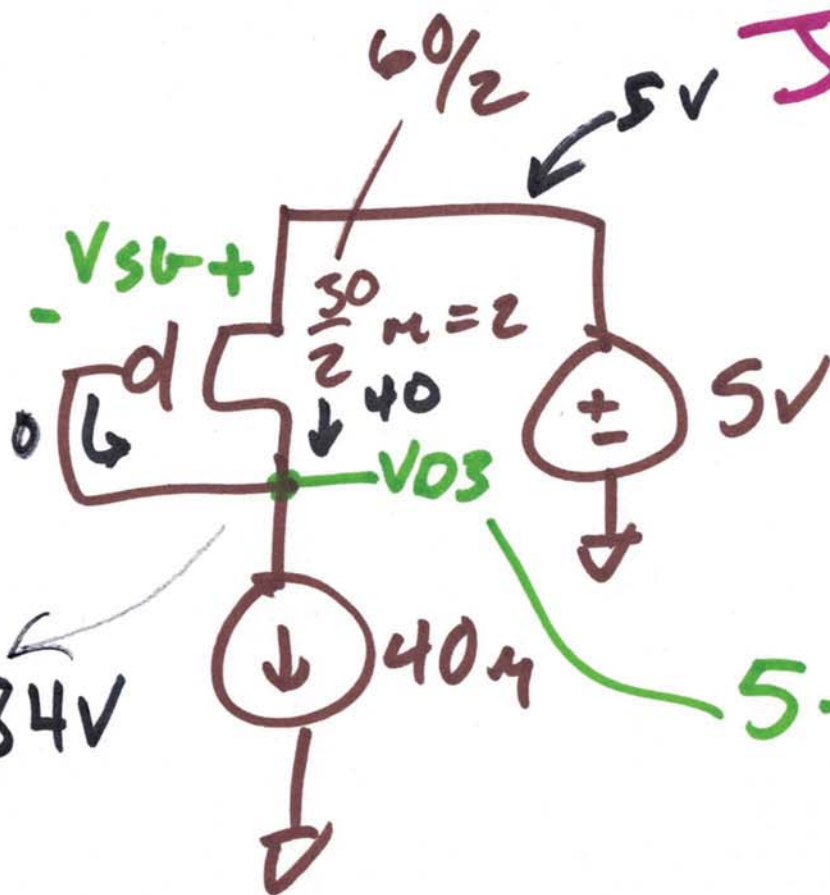


EE 420 / EEL 620

Analog IC Design

Lecture 2

JAN. 27, 2020



3.84V

$$5 - V_{GS} = V_{DS}$$

$$I_D = \frac{K_P \mu W}{2 L} (V_{GS} - V_{THP})^2$$






$$V_{GS} = V_{THP} + \sqrt{\frac{2 I_D}{K_P \cdot \frac{W}{L}}}$$

$$0.9 + \sqrt{\frac{2 \cdot 40 \mu A}{40 \mu A \cdot \frac{60}{2}}}$$


$$0.9 + \sqrt{\frac{4}{60}}$$

$$0.9 + \frac{1}{\sqrt{15}}$$

$$\approx 0.9 + 0.26 = 1.16V$$

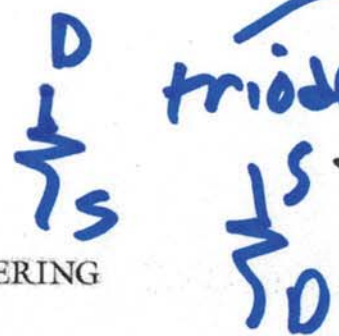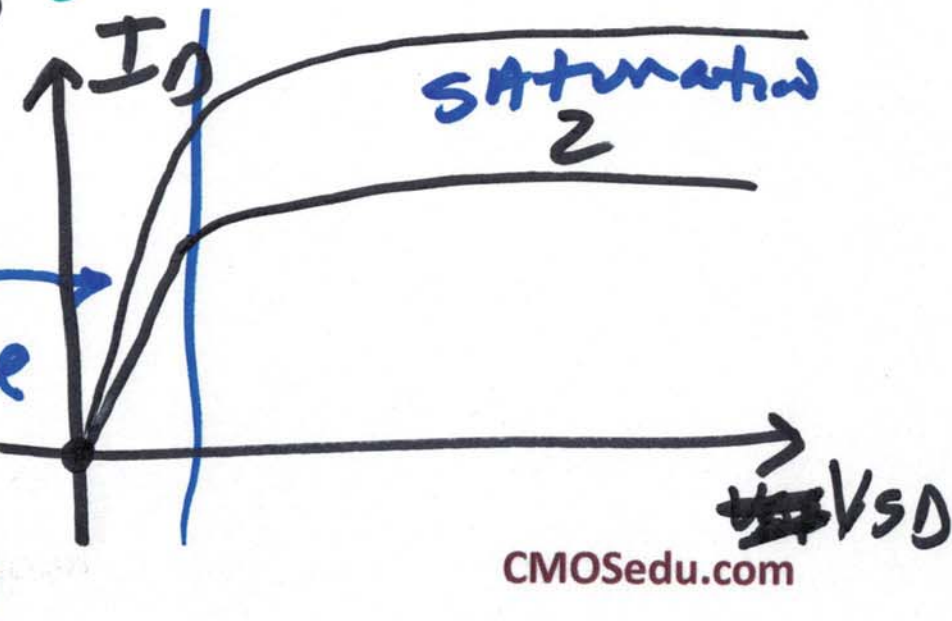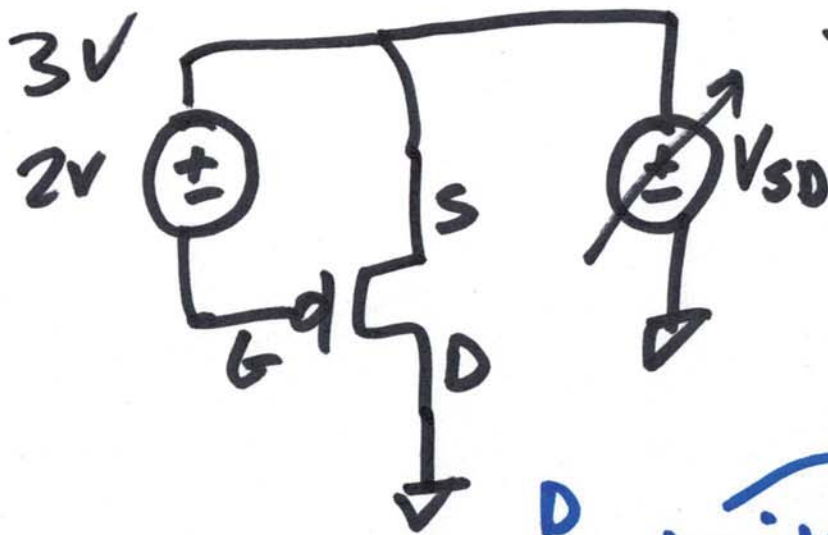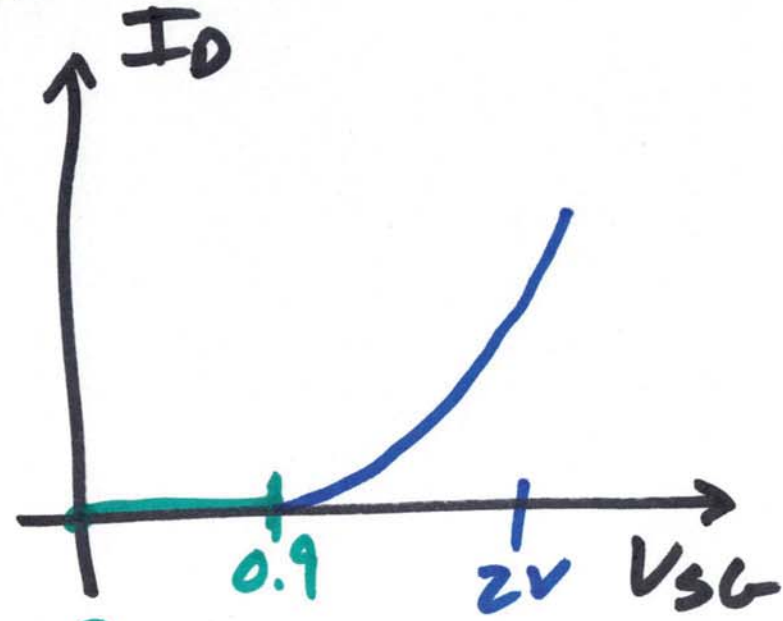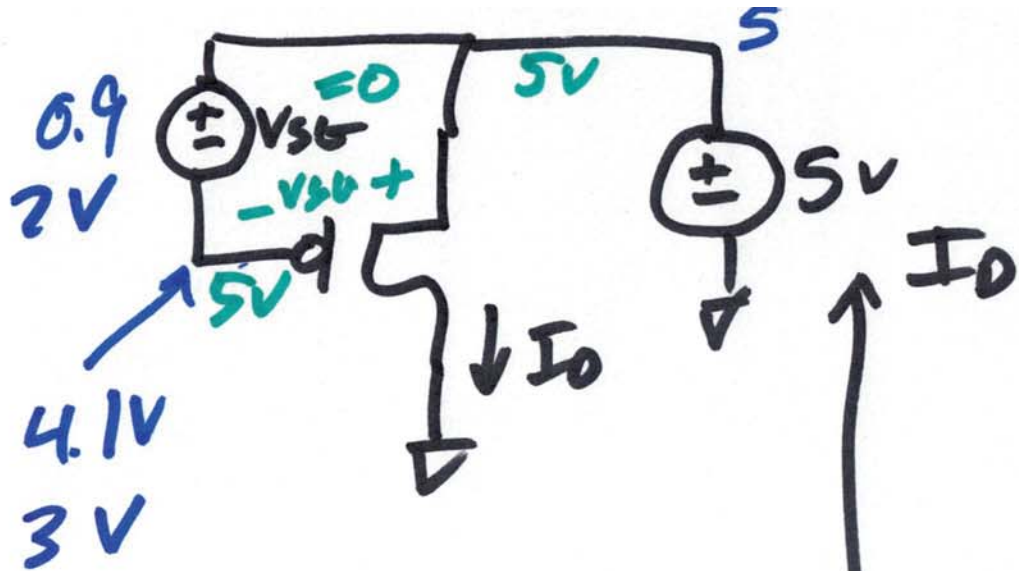

2)

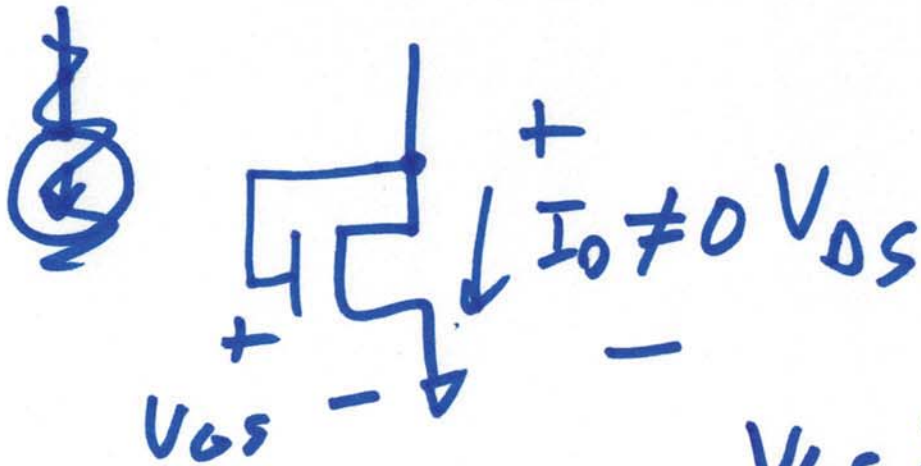


$$V_{GS} > V_{THN}$$

for sat. operation

$$\leftarrow V_{DS} \geq V_{GS} - V_{THN}$$

$$0 \geq -V_{THN}$$




Always true when $I_D = 0$

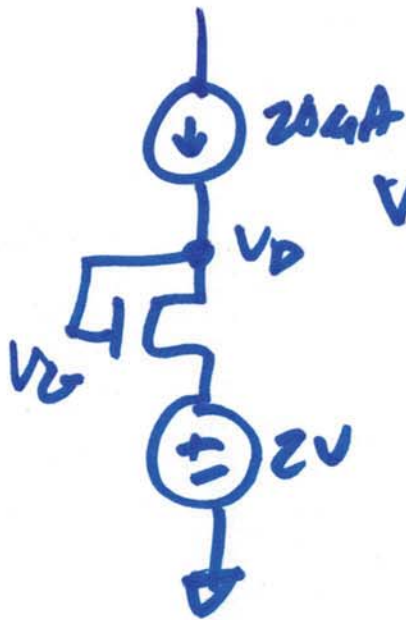



$$V_D \geq V_G - V_{THN}$$

$$0 \geq V_G - V_{THN}$$

$$0 \geq -V_{THN}$$

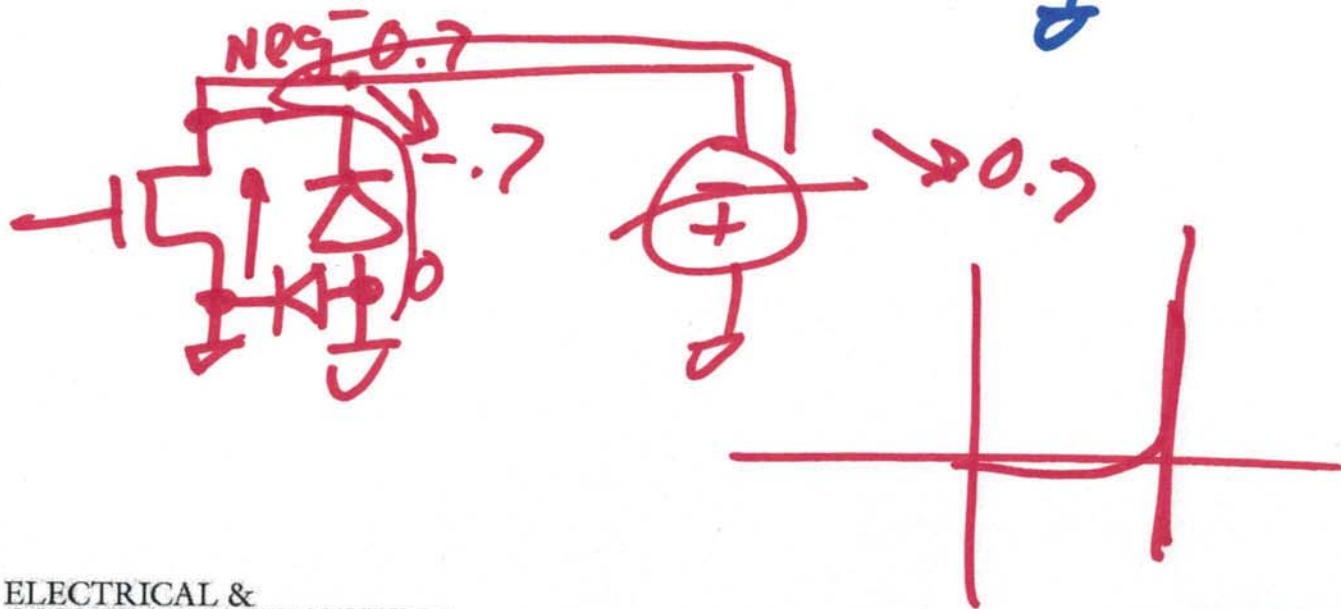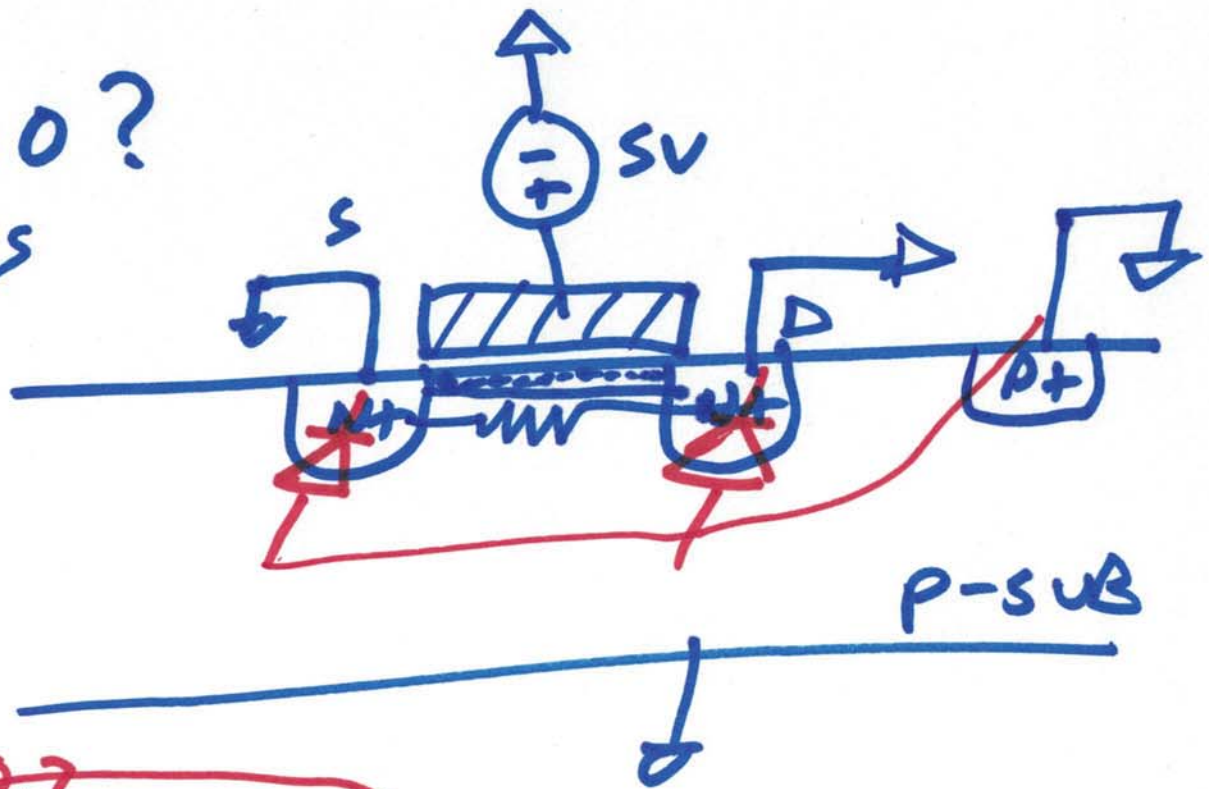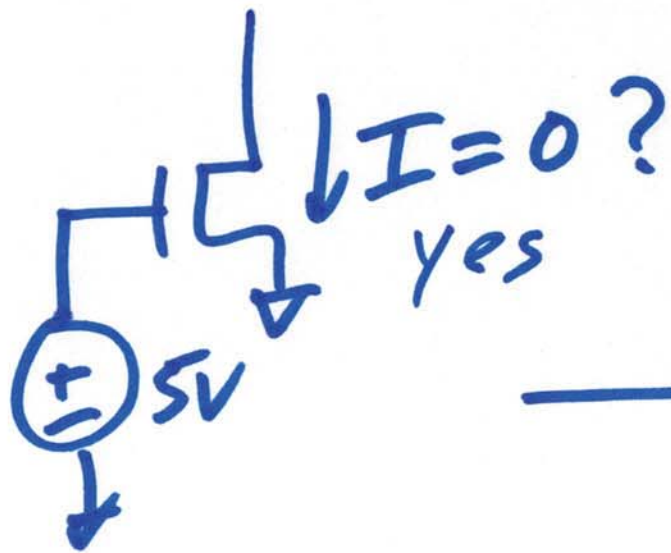

4)

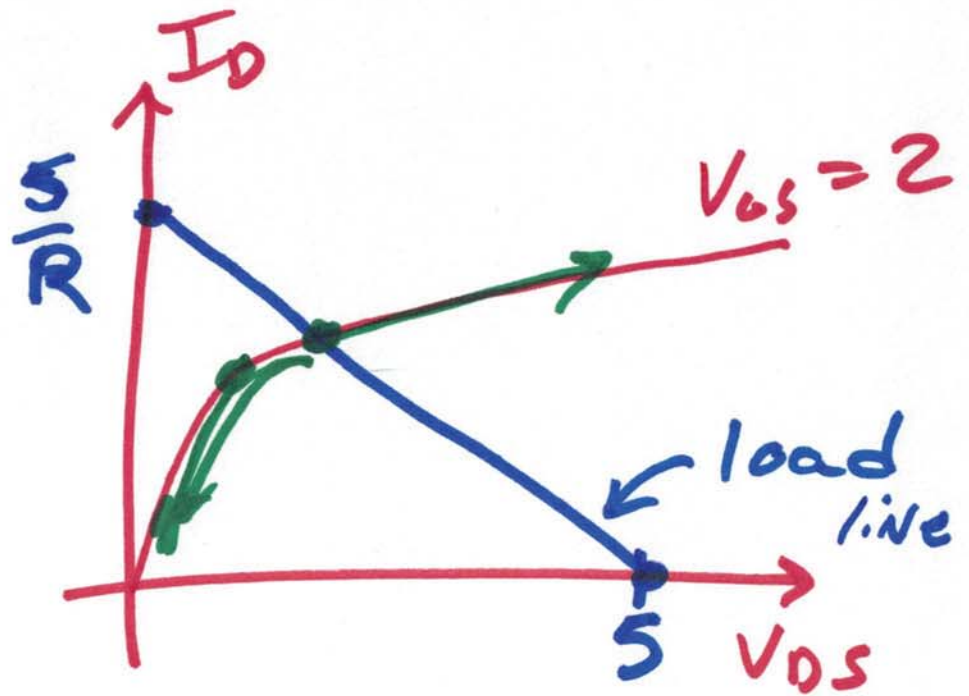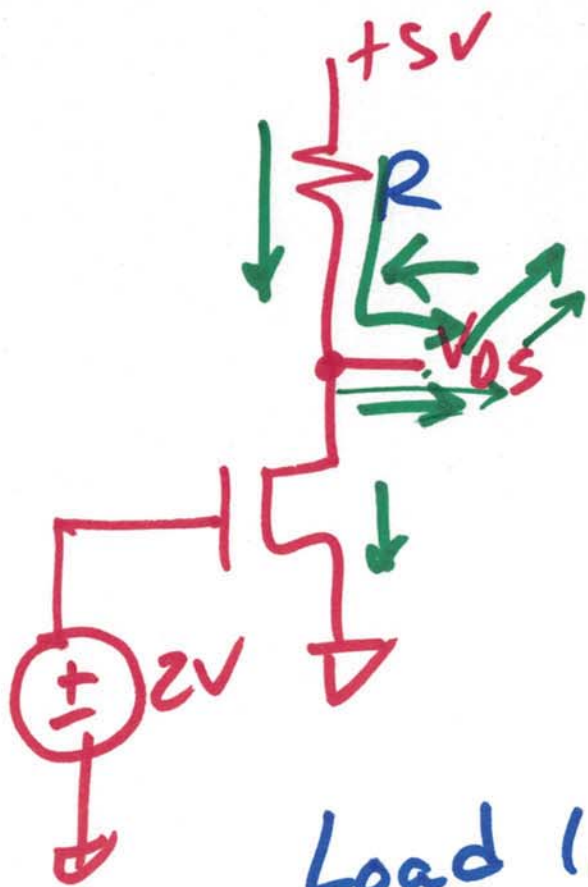

Load line

$$I_D = \frac{5 - V_{Os}}{R}$$

5)

Small-Signal

