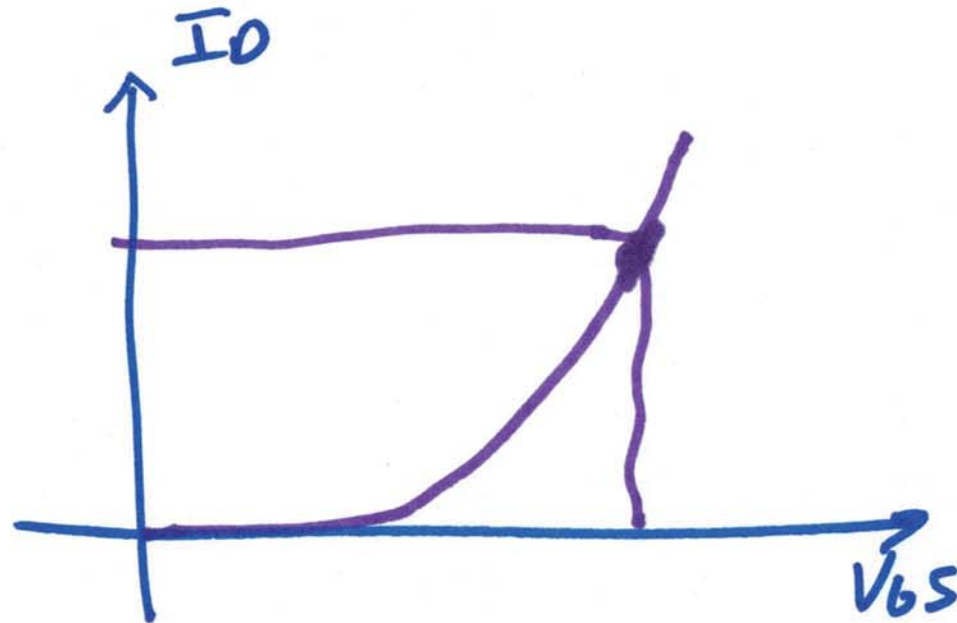




EE 420 / ELG 620

Analog IC Design

Lecture 3

JAN. 29, 2020



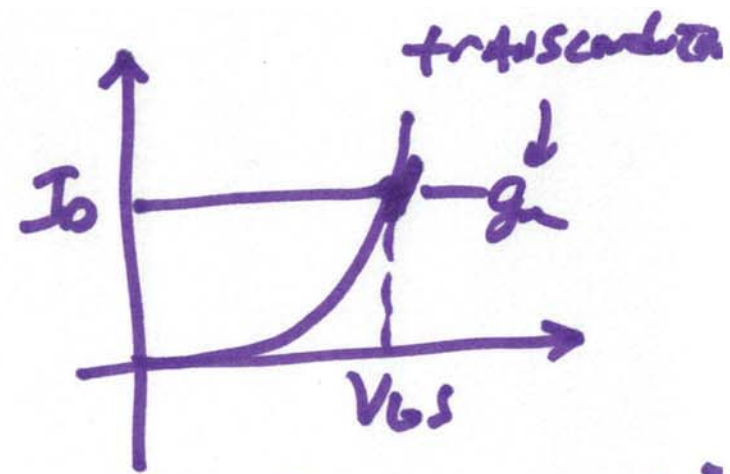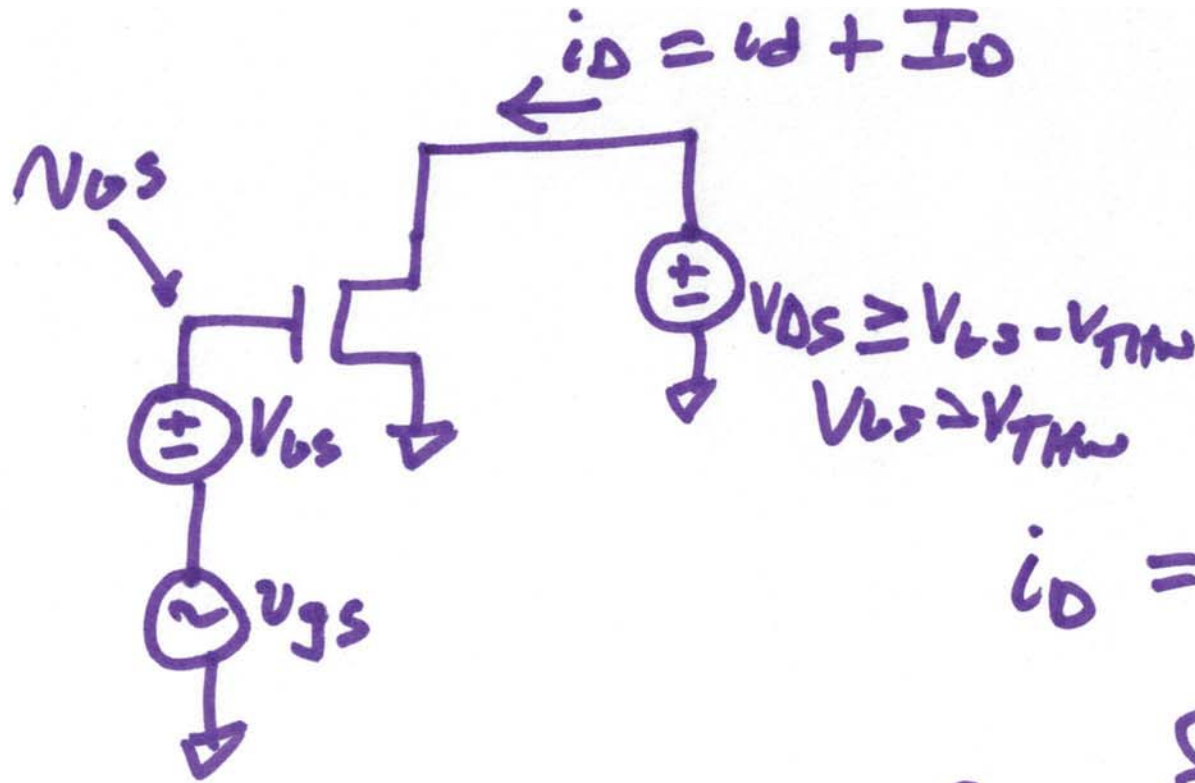

$$i_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{TH})^2$$

$$g_m = \frac{\delta i_D}{\delta V_{GS}} \Big|_{I_D = \text{CONST}, V_{DS} = \text{CONST}}$$

$$V_{GS} = V_{GS} \text{ DC} + v_{gs} \text{ AC}$$


$$\beta_N = K_{PN} \cdot \frac{W}{L}$$

$$g_m = \frac{2 K_P W}{L} (V_{GS} - V_{TH}) \delta (V_{GS} - V_{TH})$$

$$g_m = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH})$$

2)

C5

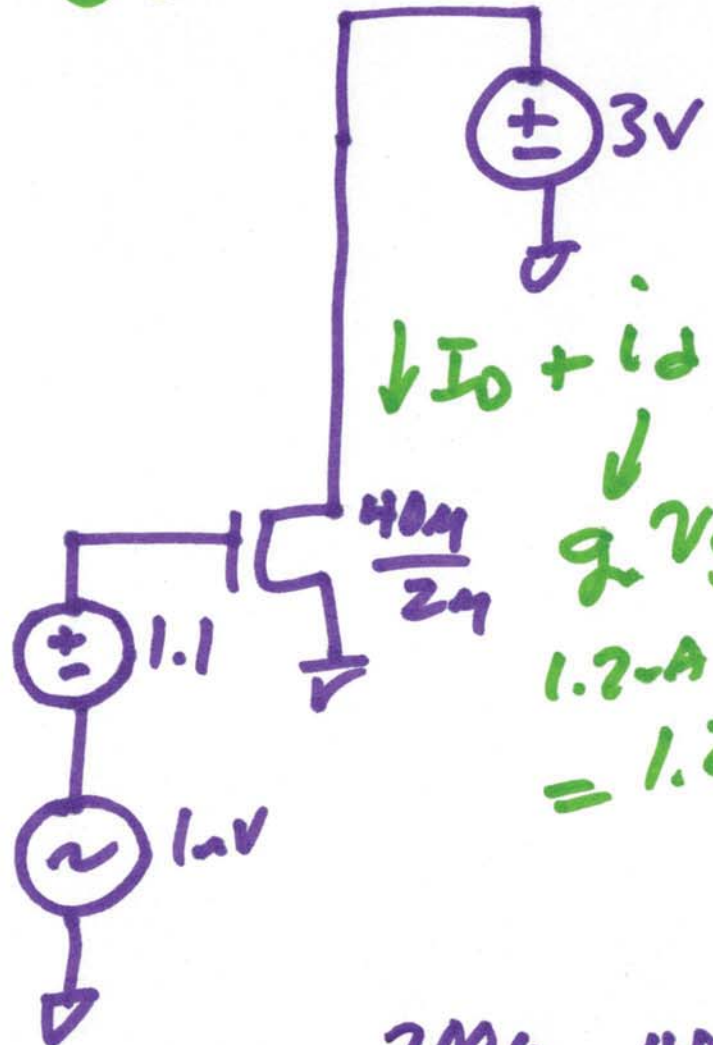

$$I_D = \frac{100\mu}{2} \cdot \frac{40}{2} \cdot (1.1 - .8)^2$$

$$= 0.2\text{mA} \cdot 0.09$$

$$= 108\mu\text{A}$$

$$I_D = 90\mu\text{A}$$

$$g_m = 1.2\text{mA/V} \cdot 1\mu\text{V}$$

$$= 1.2\mu\text{A/V} \cdot 90\mu\text{A} = \frac{K_P}{2} \cdot \frac{40}{2} (1.1 - .8)^2$$


$$19\mu = K_P \cdot 0.09$$

$$g_m = \frac{200\mu}{2} \cdot \frac{40}{2} (1.1 - .8)$$


$$K_P = \frac{200\mu\text{A}}{\text{V}^2}$$

$$4\mu\text{A} \cdot .3 = \frac{1.2\mu\text{A}}{\text{V}}$$

3)

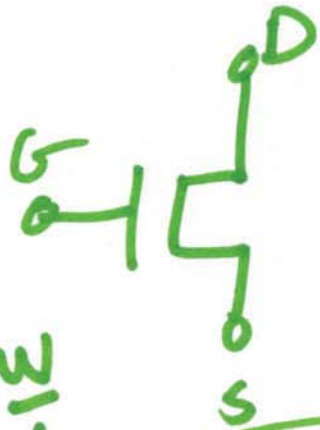

AC
→
CKT

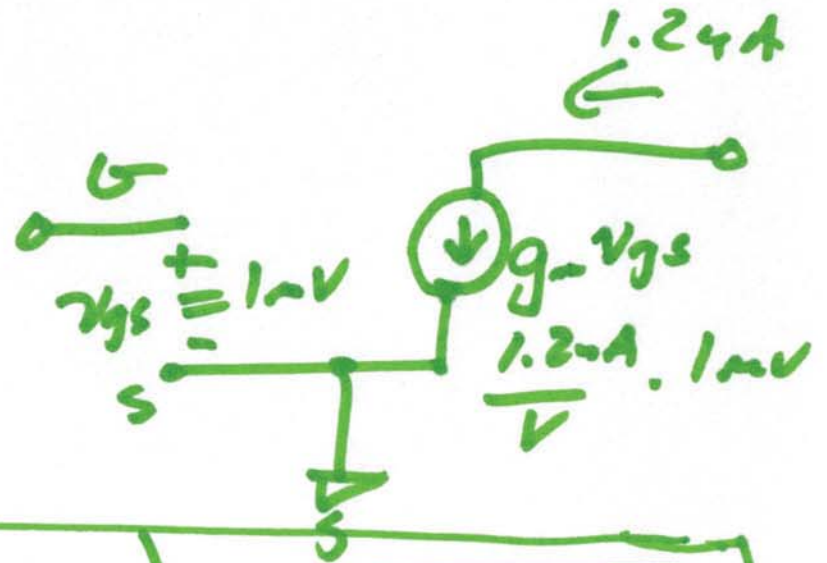

$$\beta_N = k_{DN} \cdot \frac{W}{L}$$


$$g_m = \beta_N (V_{GS} - V_{THN}) = \sqrt{2I_D \cdot \beta_N}$$

$$I_D = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2$$


$$V_{GS} = \sqrt{\frac{2I_D}{\beta_N}} + V_{THN}$$


$$(V_{GS} - V_{THN}) = \sqrt{\frac{2I_D}{\beta_N}}$$

4)


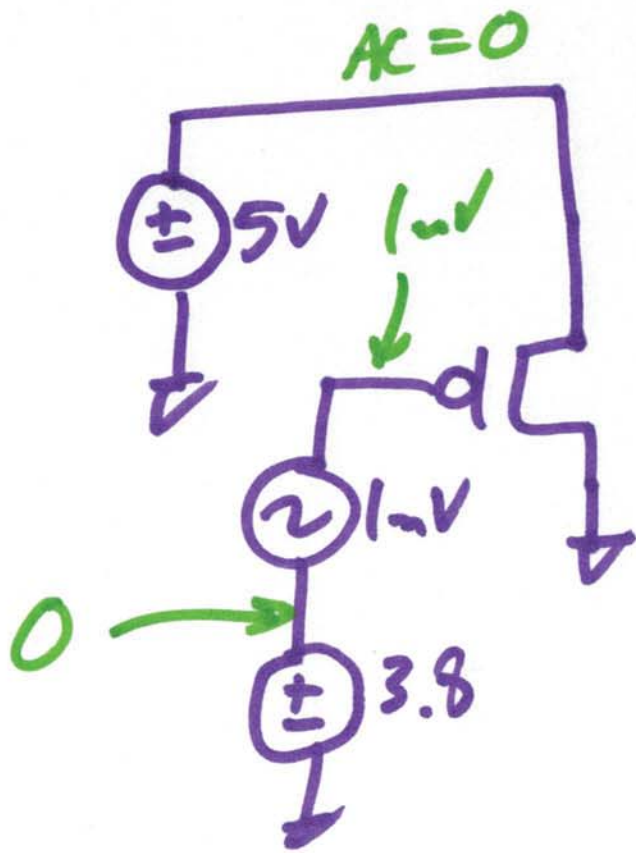


AC voltages

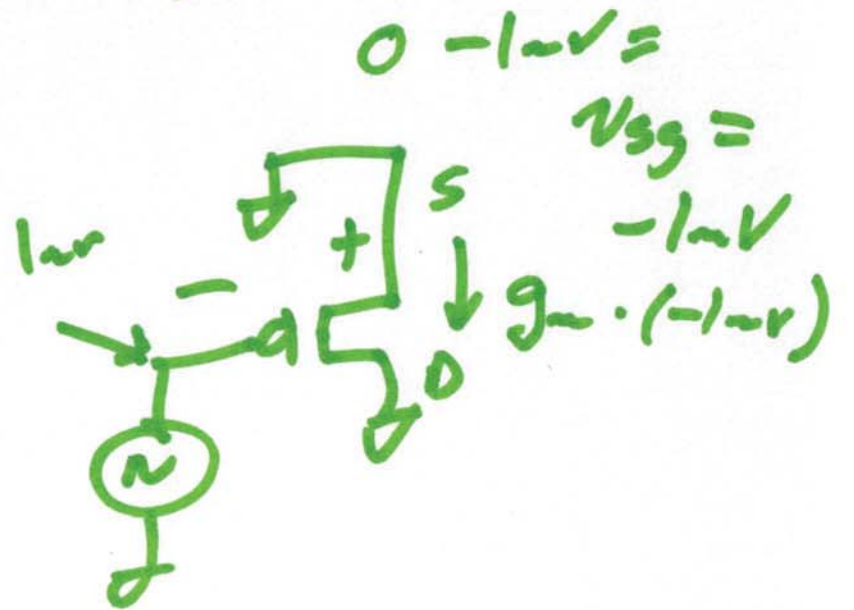

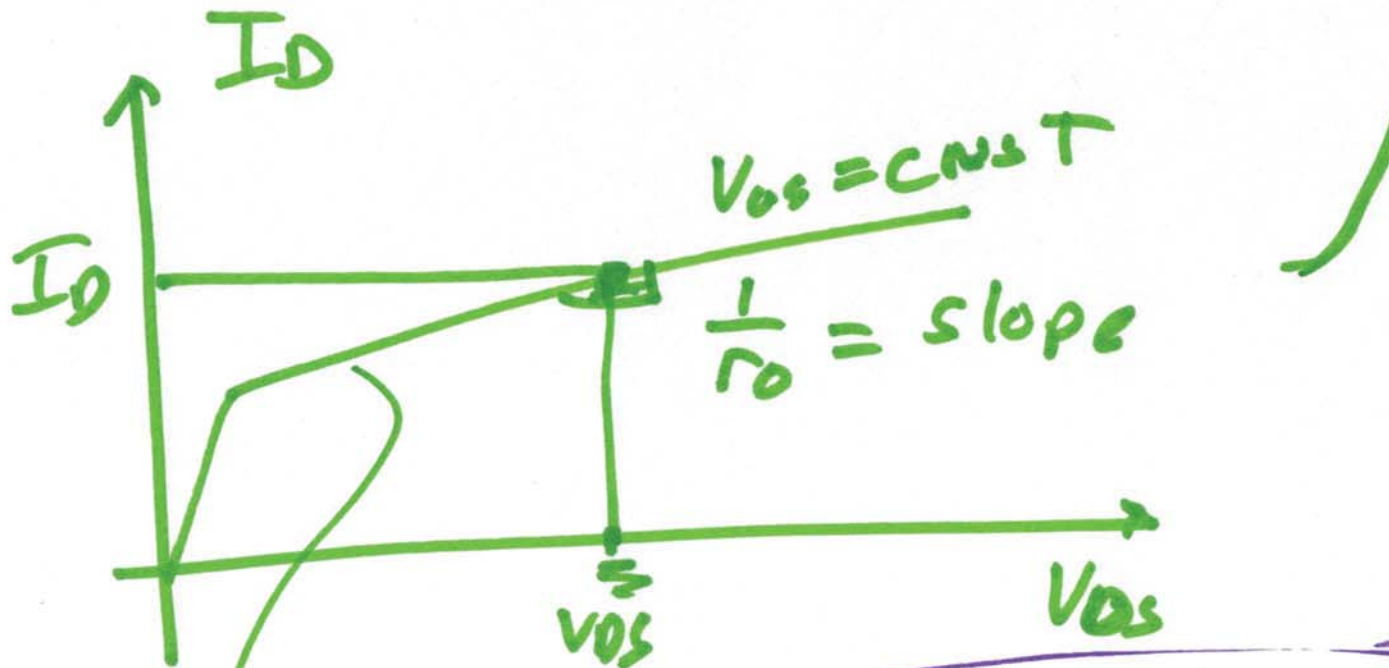

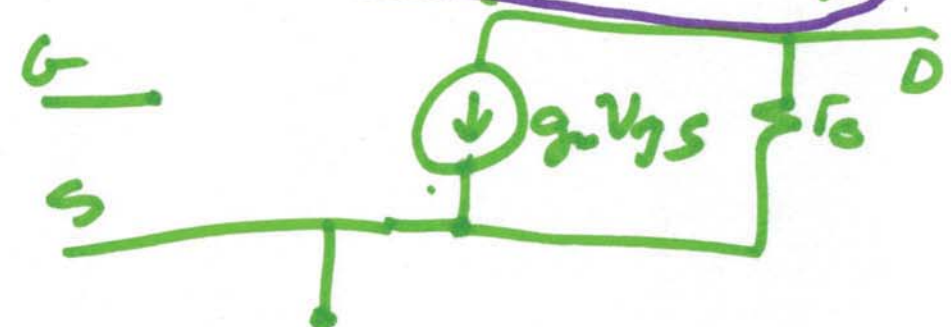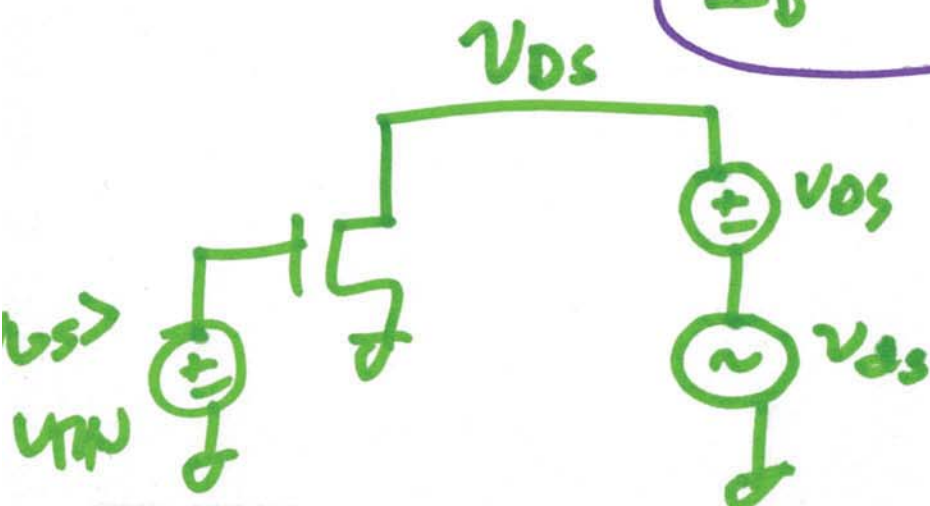
$$I_D = \frac{K_P \mu W}{2 L} (V_{GS} - V_{TH})^2 \cdot (1 + \lambda V_{DS})$$



b)

$$r_o^{-1} = \frac{\delta i_D}{\delta v_{DS}} \quad \left| \begin{array}{l} I = \text{CONST} \\ v_{DS} = \text{CONST} \end{array} \right.$$

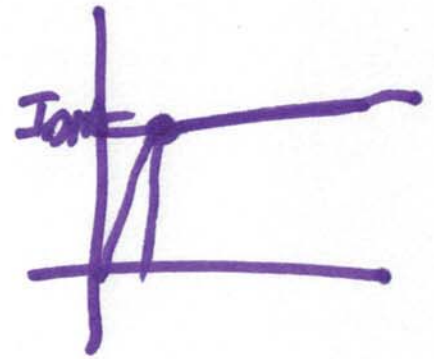

$$r_o^{-1} = \frac{K_P W}{2 L} (v_{DS} - V_{TN})^2 \cdot \lambda$$


$I_{D,SAT}$

$$r_o = \frac{1}{\lambda \cdot I_{D,SAT}}$$

$$r_o = \frac{v_{DS}}{\delta I} = \frac{1}{2.5 \mu} \approx 400 \text{ K} = \frac{1}{\lambda \cdot I_D}$$


$$\boxed{\lambda = 0.01 \text{ V}^{-1}} = \frac{1}{400,000 \cdot 1.86 \mu}$$

7)

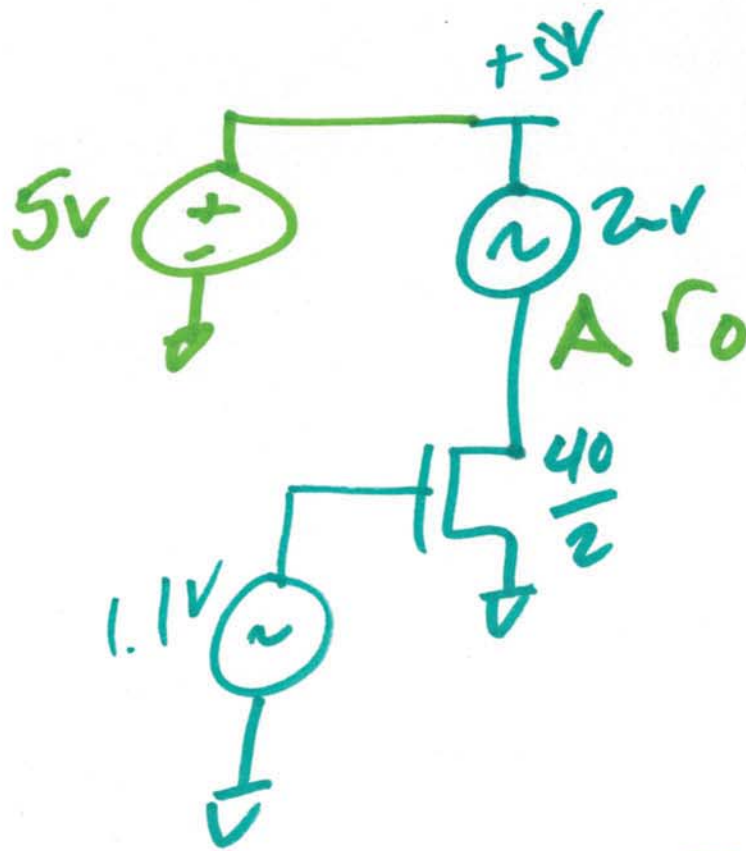

$$K_P = \frac{200 \mu A}{\sqrt{2}}, \quad \lambda = 0.01 V^{-1}$$
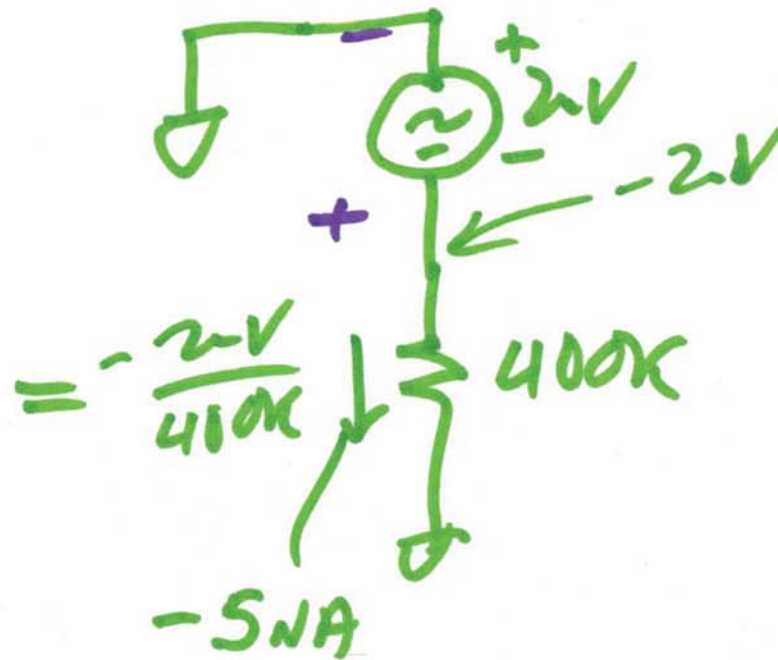
$$r_o = \frac{1}{\lambda I_D} = 400 k\Omega$$



8)