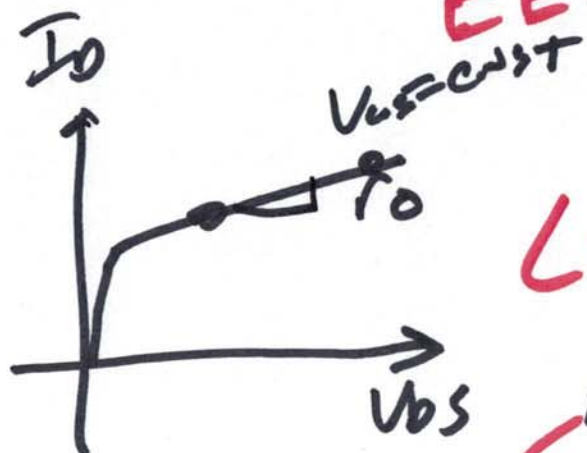


EE420 / ELG 620


Analog IC Design

Lecture 4,

Feb. 3, 2020



AC = 0

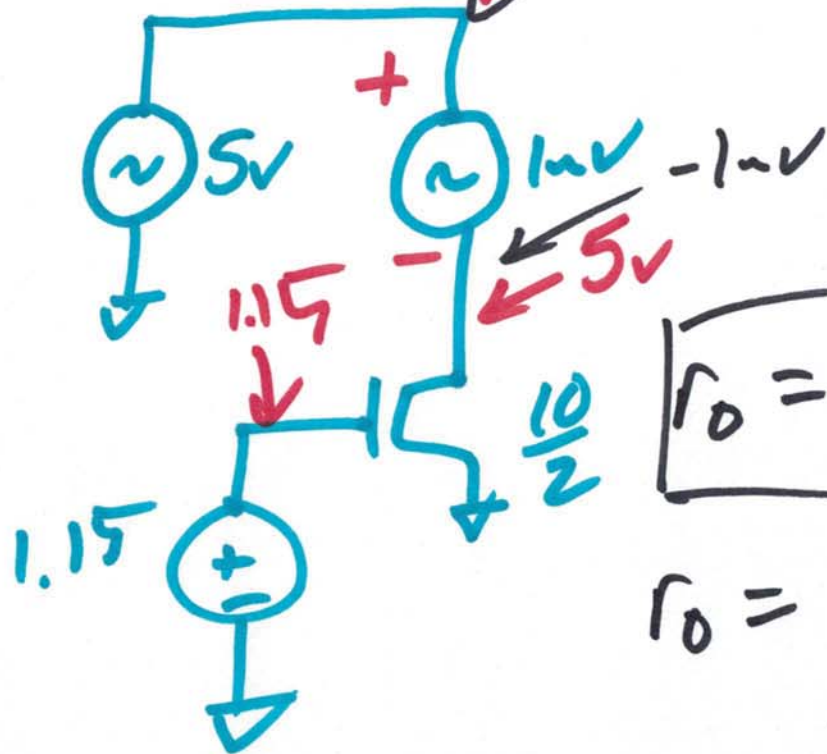

$$I_D = \frac{120\mu}{2} \cdot \frac{10}{2} (1.15 - 0.8)^2 = 300\mu \cdot 0.1225$$


$$r_D = 1750\Omega \quad \text{Sim AC}$$

$$I_D = 36.75\mu\text{A}$$

$$r_D = \frac{1}{0.01 \cdot 36\mu\text{A}} = \frac{1}{\lambda I_D} = 2.7\text{M}\Omega$$


$$r_D = 3.6\text{M}\Omega \quad (\text{transient})$$

NOS 10/2 pmos 30/2


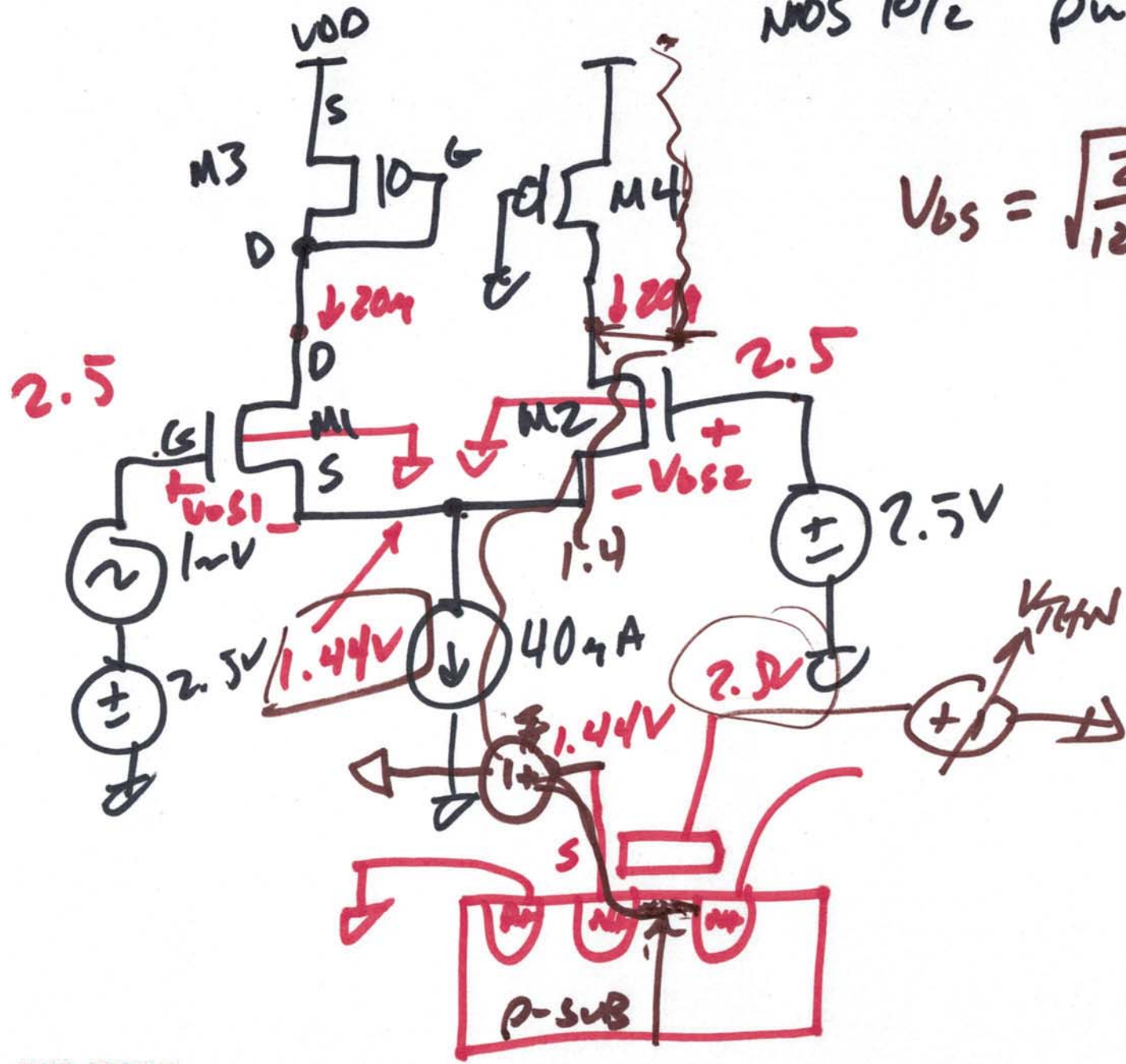


$$V_{GS} = \sqrt{\frac{2 \cdot 20 \mu}{120 \mu \cdot \frac{10}{2}}} + 0.8$$

$$V_{GS} = 1.058V$$

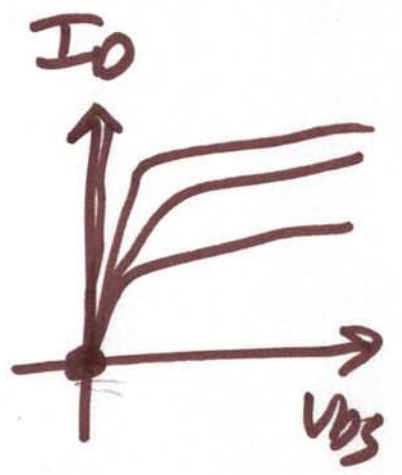


2)

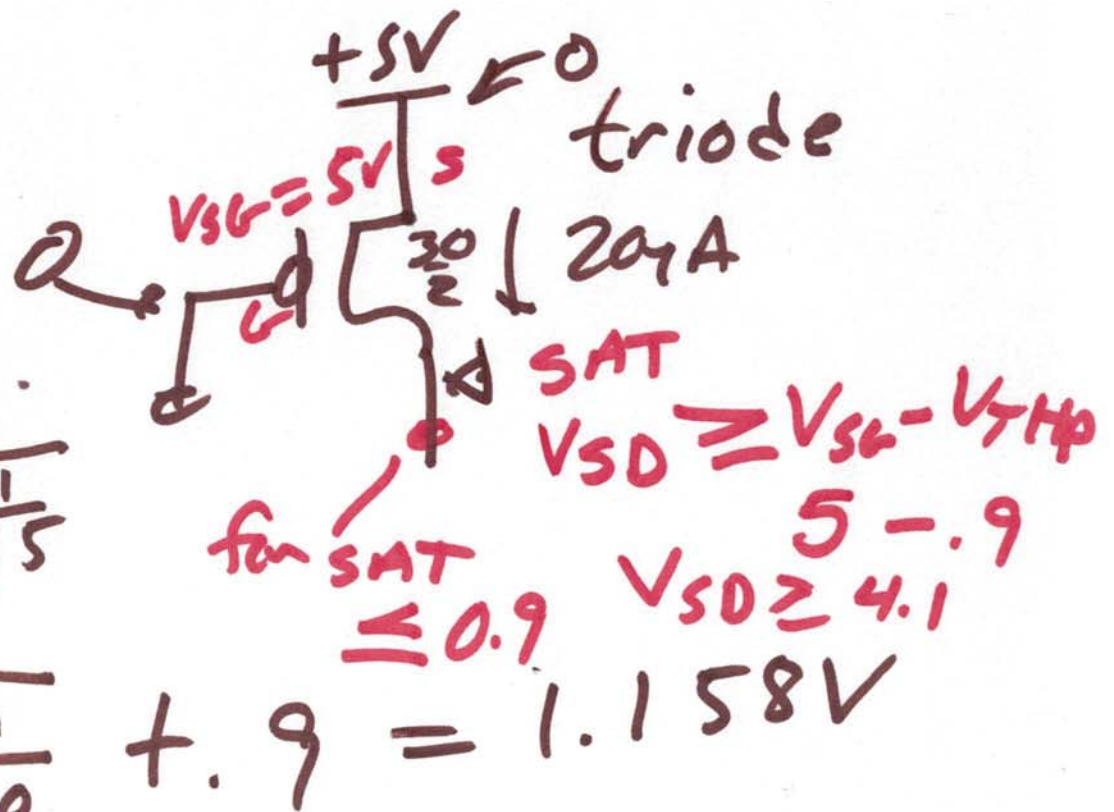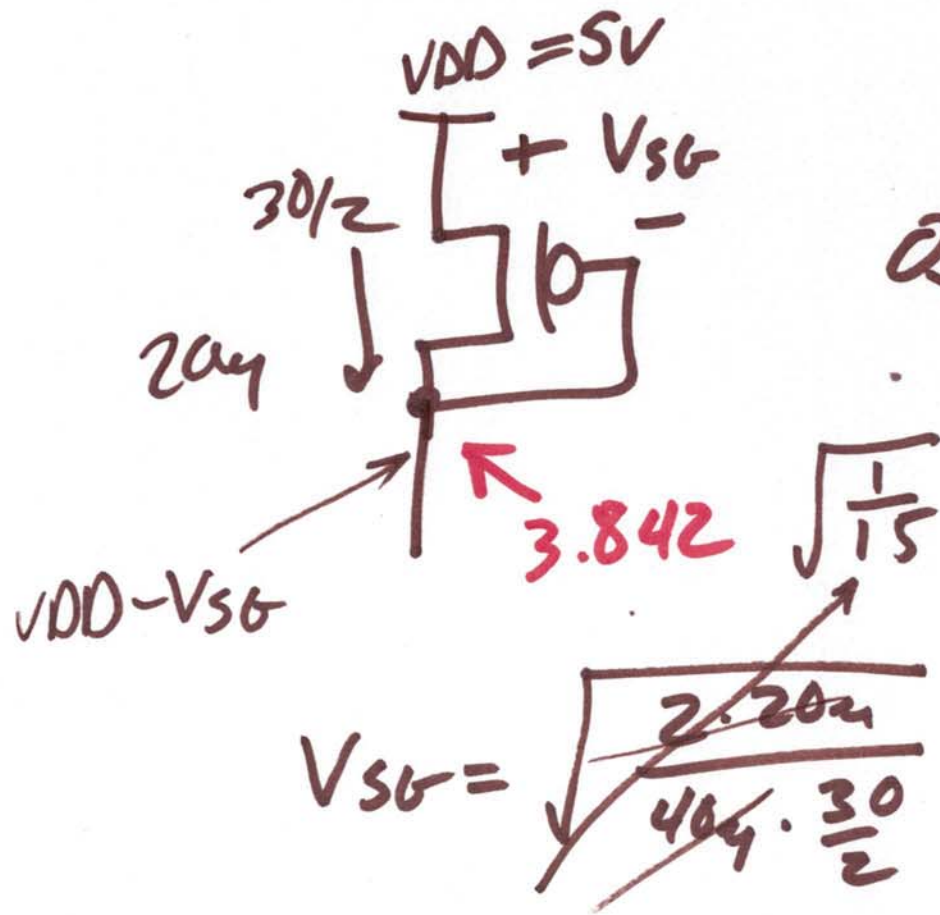

3)

AC small-signal

R_{eff}

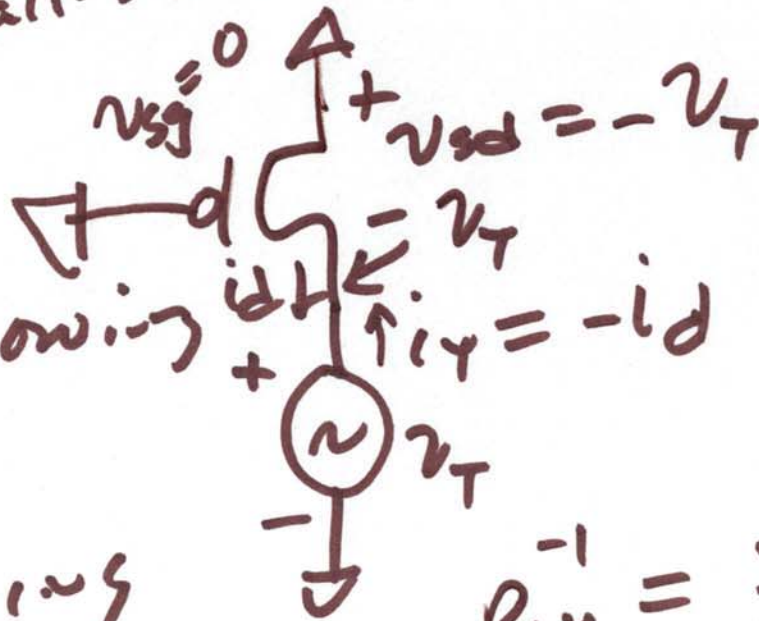

Not showing

DC


biasing

triode

$$I_D = K_P \frac{W}{L} \cdot \left((V_{GS} - V_{TH}) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$R_{eff}^{-1} = \frac{\partial I_D}{\partial V_{SD}} = K_P \frac{W}{L} \left((V_{GS} - V_{TH}) - V_{DS} \right) \cdot \frac{\partial V_{GS}}{\partial V_{SD}}$$

$$V_{GS} \ll V_{DS}$$

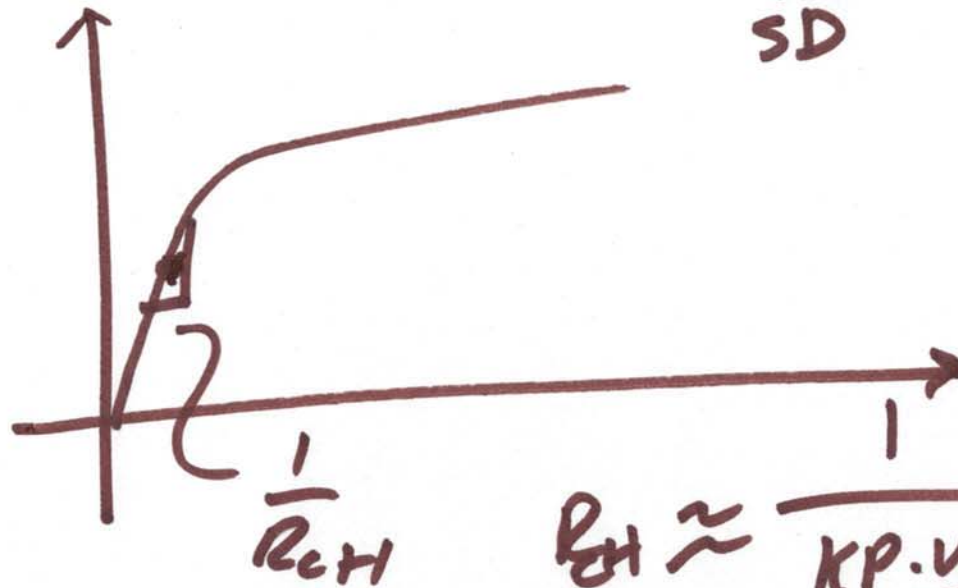

$$R_{eff} \approx \frac{1}{K_P \frac{W}{L} (V_{GS} - V_{TH}) + V_{DS}}$$

$$R_{CH}^{-1} = \frac{\delta i_D}{\delta v_{OS}} = \frac{-\delta i_V}{-\delta v_V} =$$

$$R_{CH}^{-1} = \frac{\delta i_D}{\delta v_{OS}} = \frac{\delta}{\delta v_{OS}} \left(K_P \cdot \frac{W}{L} \left((v_{GS} + v_{DS} - V_{THN})^2 \cdot v_{DS} \right) \right)$$

$v_{OS} \ll v_{DS}$


$$= K_P \cdot \frac{W}{L} (v_{GS} - V_{THN}) \cdot v_{DS} - \frac{K_P \cdot W}{L} v_{DS}^2$$

$v_{OS, SAT} = \frac{v_{DS}}{2}$

$$R_{CH} \approx \frac{1}{K_P \cdot \frac{W}{L} (v_{GS} - V_{THN})}$$

v_{DS} is small

5)

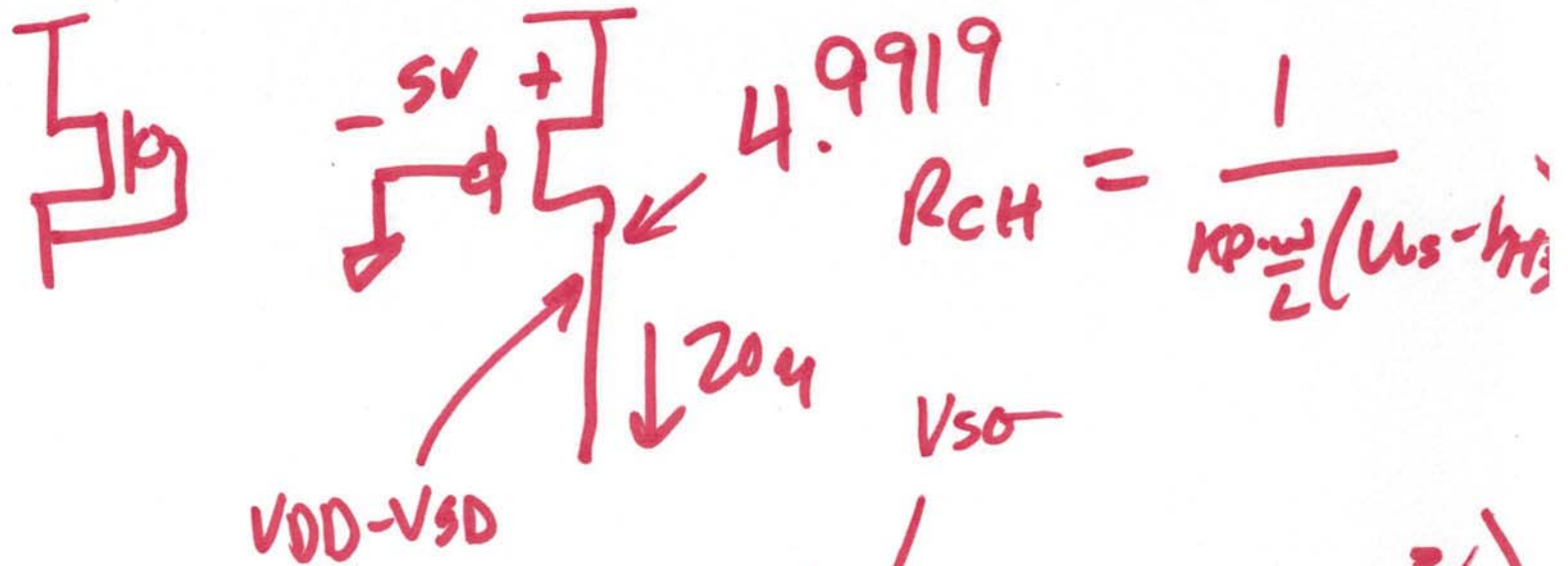

$$20\mu = 40\mu \cdot \frac{30}{2} \left((5 - 0.9) V_{SD} - \frac{V_{SD}^2}{2} \right)$$

$$V_{SD} = \frac{1}{30 \cdot 4.1} = 8.1\mu V$$