


EE420/ELG620

Analog IC Design Lecture 5

$$R_{eff} = \frac{1}{\frac{K_P \cdot W}{L} (V_{GS} - V_{TH})}$$

30/2 - pmos
10/2 - nmos

Feb. 5, 2020

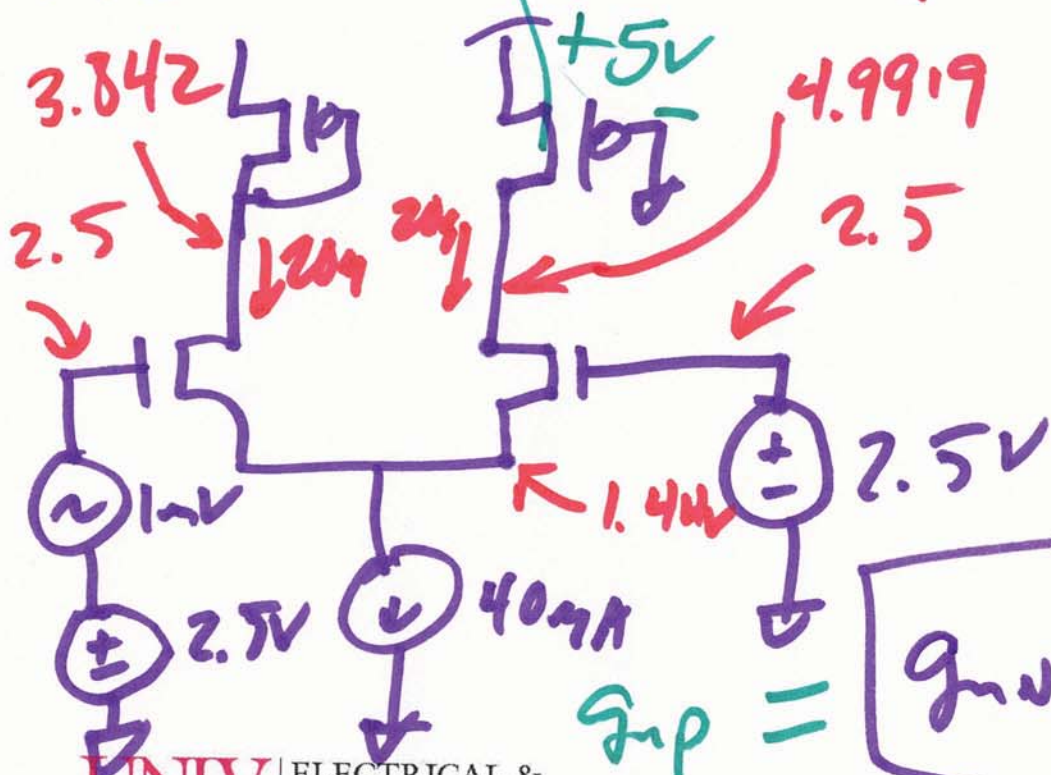

$$g_{mN} = \sqrt{2\beta_N I_D}$$

$$= \sqrt{2K_P \cdot \frac{W}{L} I_D}$$



$$= \sqrt{2 \cdot 120 \mu A \cdot \frac{10}{2} \cdot 20 \mu V}$$

$$g_{mN} = 150 \mu A/V$$


$$\sqrt{24000} \sqrt{\frac{A^2}{V}}$$

$$R_{CH} = \frac{1}{K_P \frac{W}{L} (V_{SG} - V_{THP})} = \frac{1}{404 \cdot \frac{30}{2} (4.1)}$$

$$R_{CH} = 406.55 \Omega$$

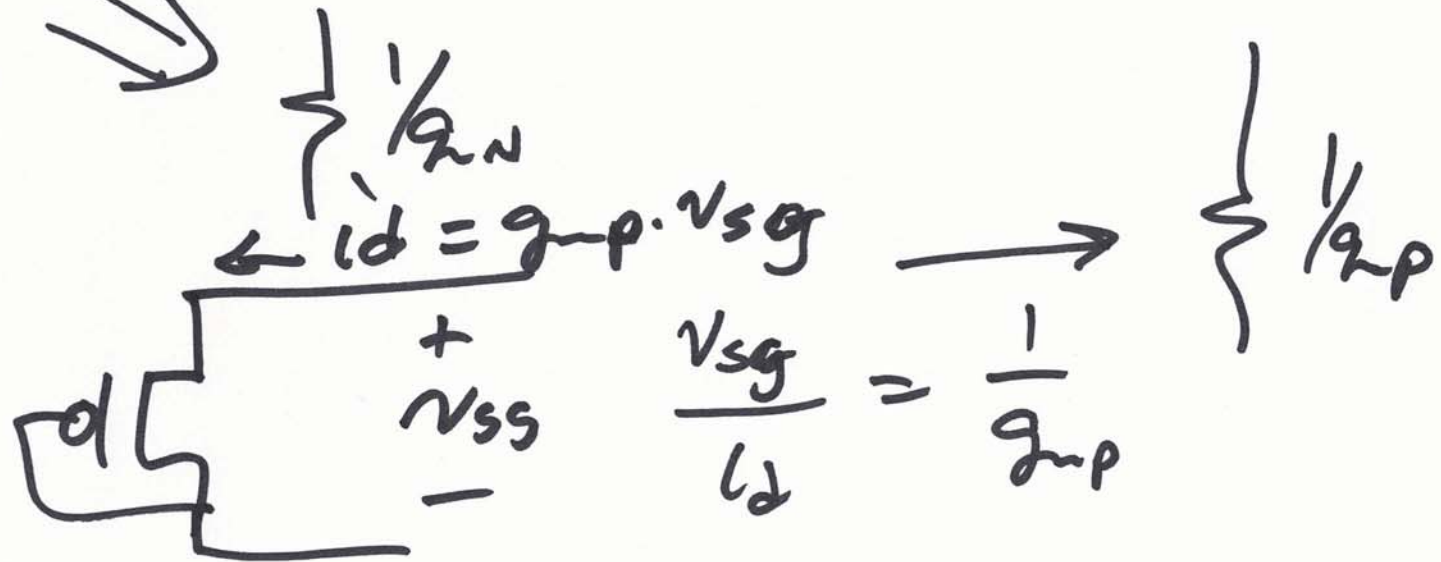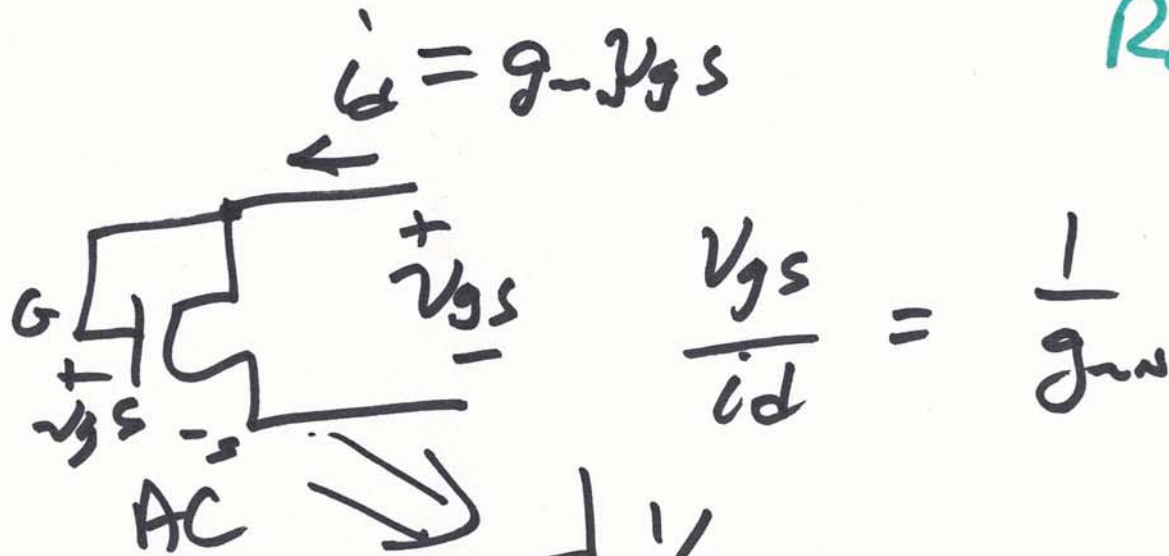

2)

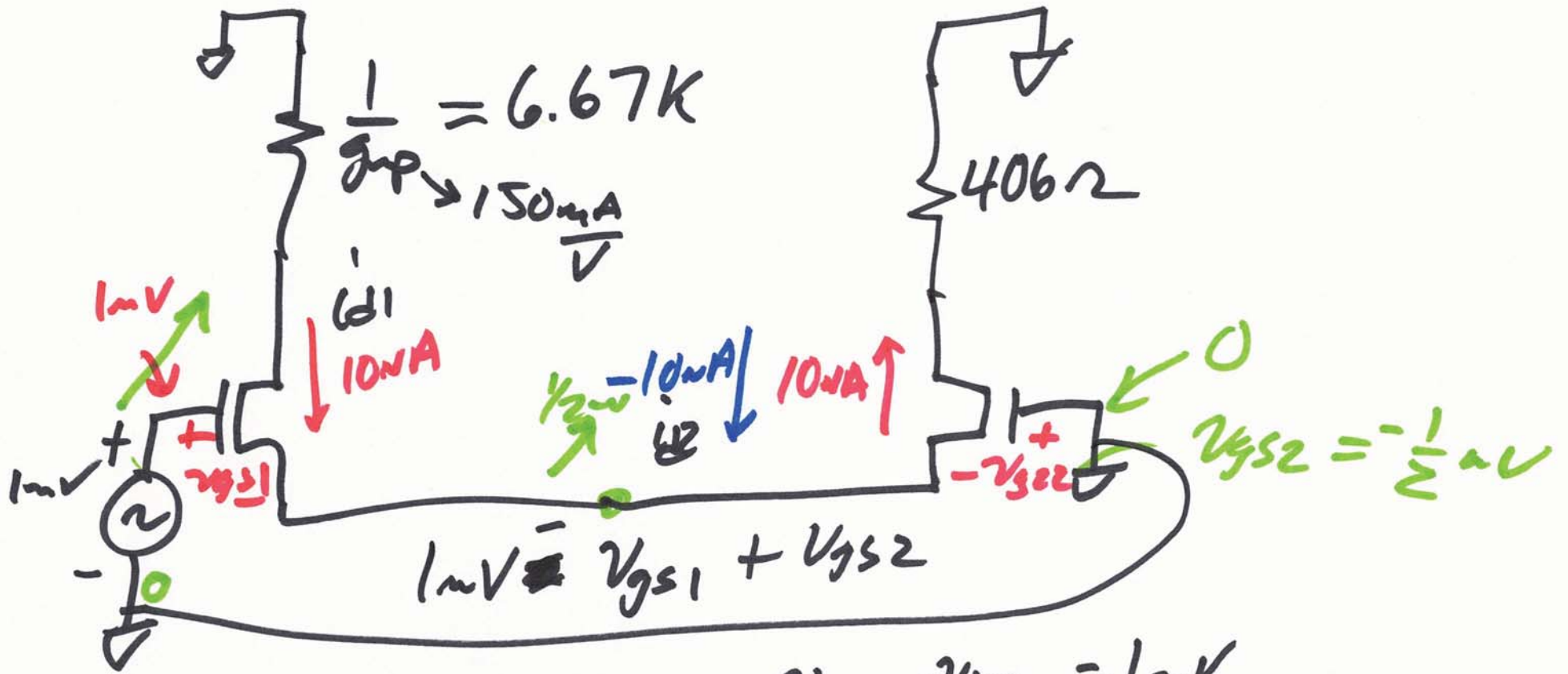

ACKKT

$$2i_{d1} = g_m \cdot 1 \mu\text{V}$$

$$i_{d1} = g_m \cdot \frac{1 \mu\text{V}}{2} = g_m \cdot V_{gs1}$$

$$V_{gs2} = -\frac{1}{2} \mu\text{V}$$

$$V_{gs1} - V_{gs2} = 1 \mu\text{V}$$


$$\frac{i_{d1}}{g_m} - \frac{i_{d2}}{g_m} = 1 \mu\text{V}$$

$$i_{d1} - i_{d2} = g_m \cdot 1 \mu\text{V}$$


$$i_{d1} = -i_{d2}$$


~~2i_{d1}~~

3)

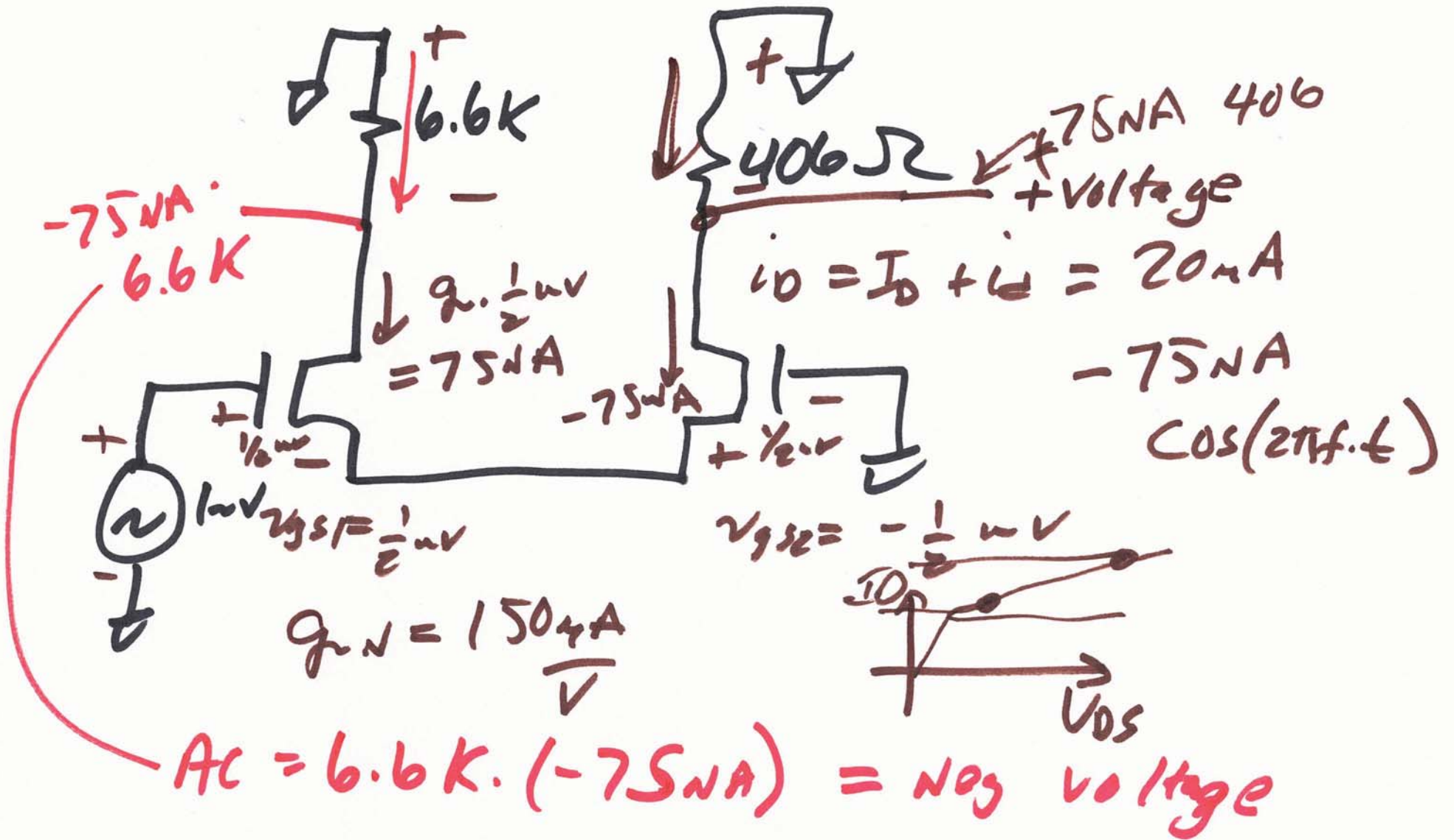

4)

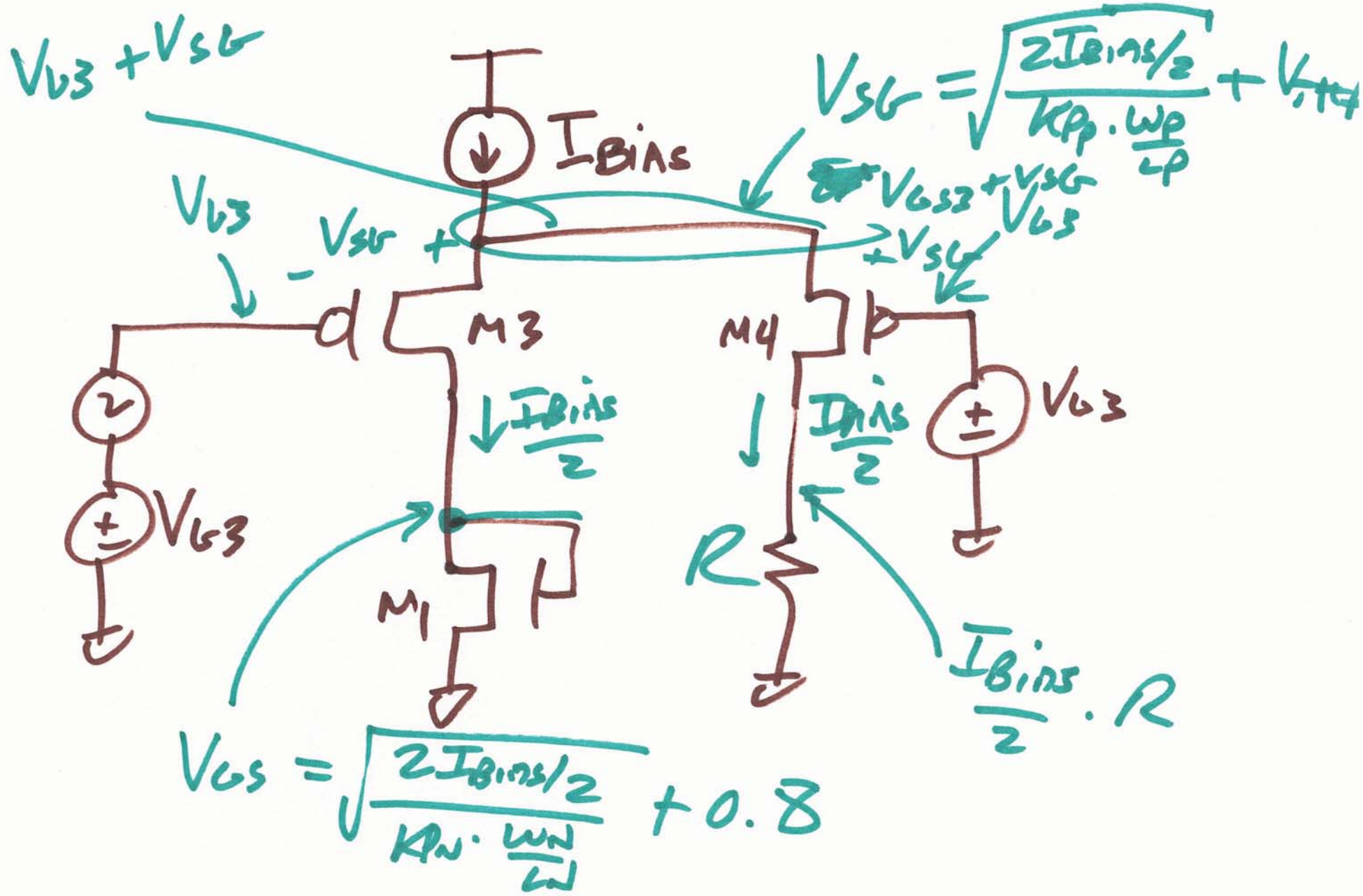

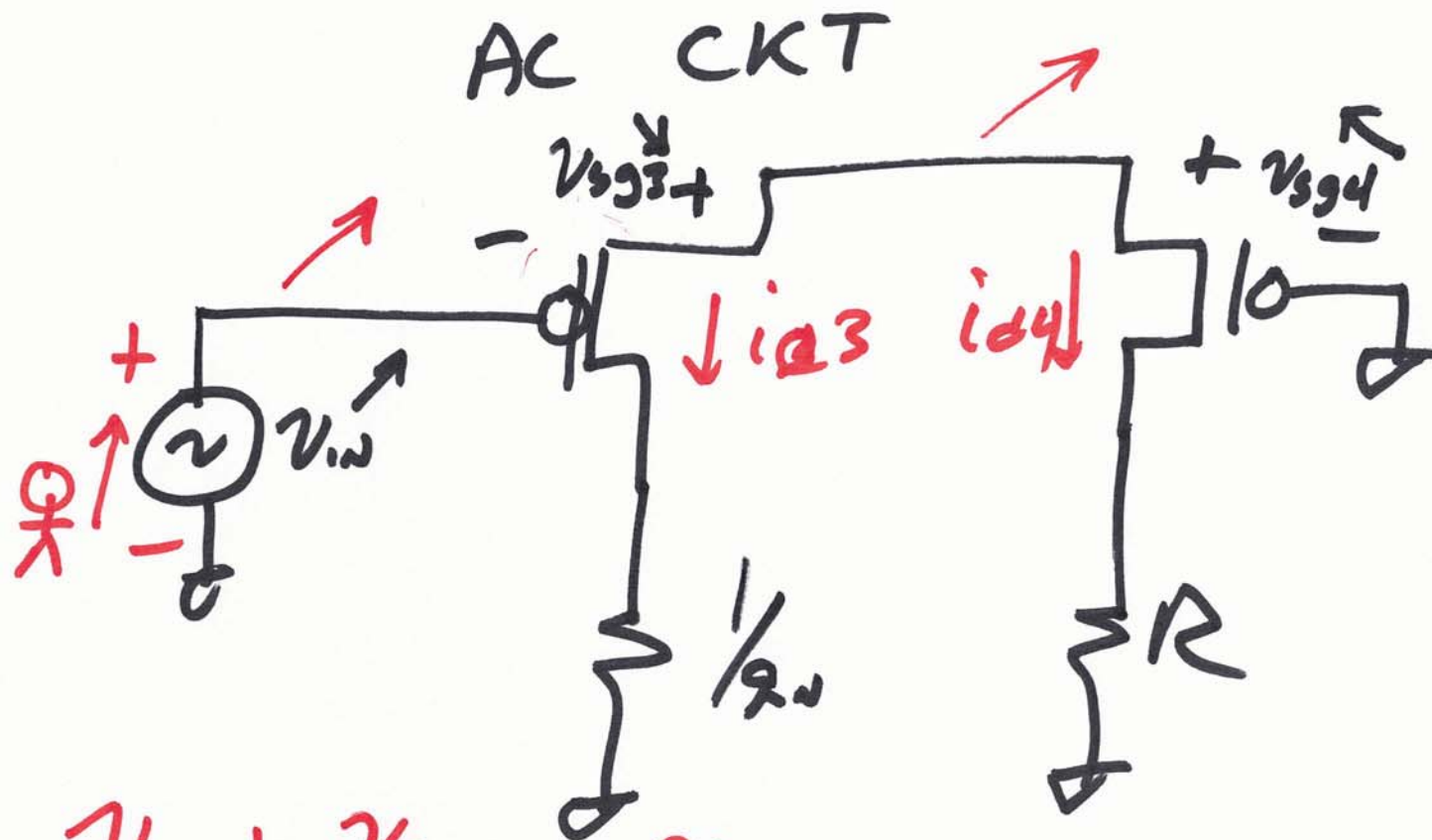

$$v_{in} + v_{gs3} - v_{gs4} = 0$$

$$v_{in} = v_{gs4} - v_{gs3} \rightarrow v_{gs4} = -v_{gs3}$$

$$i_{d3} = -i_{d4} \quad v_{gs3} = -v_{gs4}$$

6)