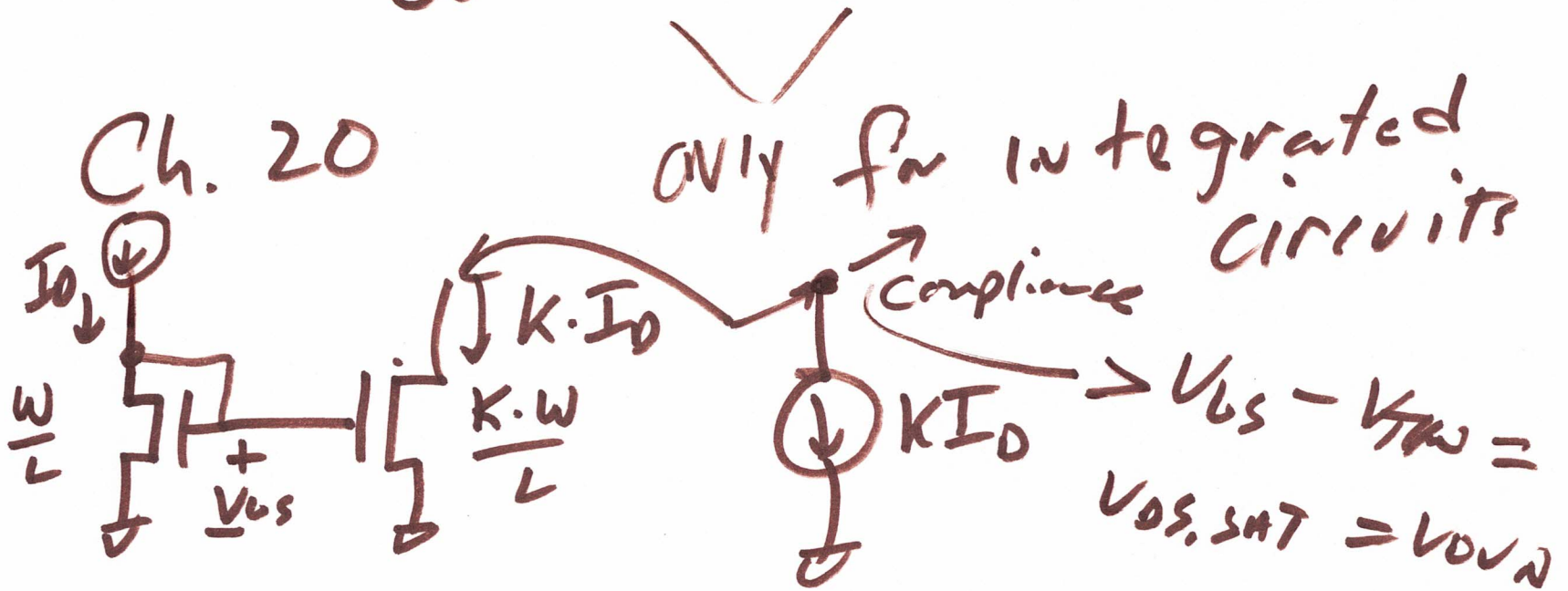


EE 420 / ELG 620 Analog IC Design


Feb. 12, 2020

Lecture 7

CURRENT MIRRORS



1)

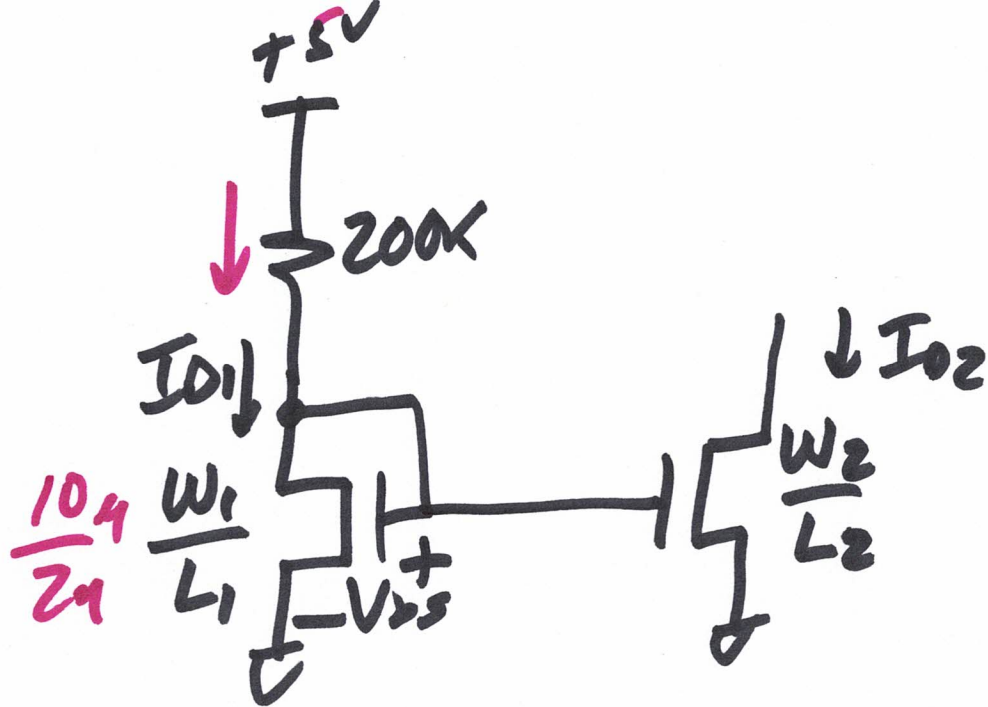

$$\frac{5 - V_{DS}}{200k} = \frac{120\mu \cdot 10}{2} \frac{10}{2} \cdot \frac{1}{2} \cdot (V_{DS} - 0.8)^2$$

$$\frac{I_{D1}}{I_{D2}} = \frac{\frac{K_P}{2} \frac{W_1}{L_1} (V_{DS} - V_{TH})^2}{\frac{K_P}{2} \frac{W_2}{L_2} (V_{DS} - V_{TH})^2}$$

$$= \frac{W_1/L_1}{W_2/L_2}, L_1 = L_2 \rightarrow \frac{W_1}{W_2}$$

2)

$$\frac{5 - V_{GS}}{200k} = 30\mu (V_{GS} - 0.8)^2$$

$$0.2 \cdot 10^6$$


$$5 - V_{GS} = 60 (V_{GS}^2 - 1.6V_{GS} + 0.64)$$

$$5 - V_{GS} = 60V_{GS}^2 - 96V_{GS} + 38.4$$


$$0 = 60V_{GS}^2 - 95V_{GS} + 33.4$$

$$NO < V_{TH} = V_{GS}^2 - 1.58V_{GS} + 0.56$$

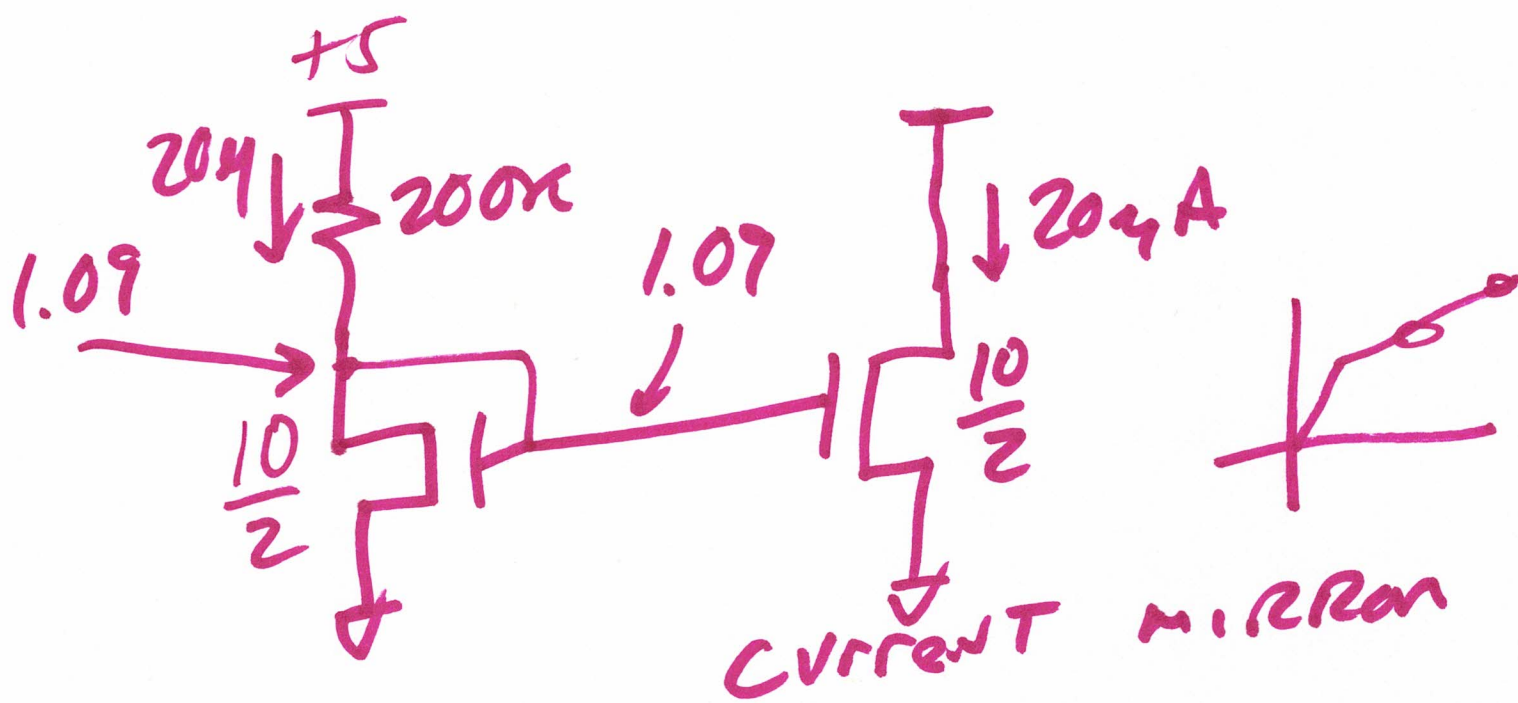
$$1.09, .49 \quad V_{GS} = \frac{1.58 \pm \sqrt{2.5 - 2.24}}{2}$$



$$\frac{5 - 1.07}{200k} \approx 204A$$

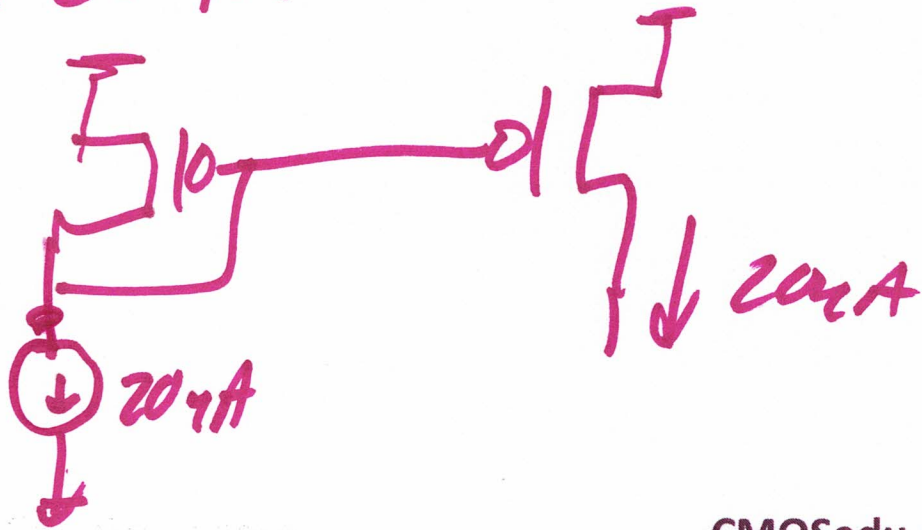

4)

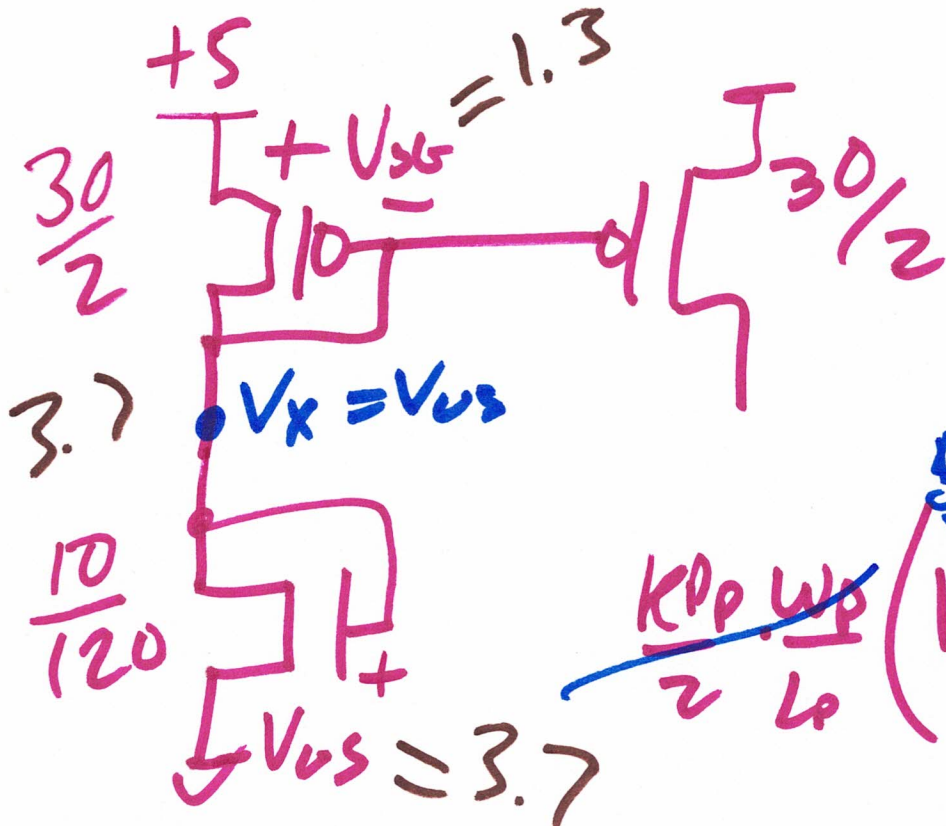

$$5 = V_{SG} + V_{GS}$$

$$\sqrt{\frac{2I_0}{k_{np} \frac{W_p}{L_p}}} + 0.9 + \sqrt{\frac{2I_0}{k_{pn} \frac{W_n}{L_n}}}$$

$$\frac{k_{np} \frac{W_p}{L_p}}{2} (5 - V_x - V_{TAP})^2 =$$

$$\frac{k_{pn} \frac{W_n}{L_n}}{2} (V_x - V_{THN})^2$$

$$I_0 = \frac{120 \mu A/V^2 \cdot 10}{2 \cdot 120} (3.7 - 0.5)^2$$

$$= \boxed{42 \mu A = I_0}$$

5)

$$\frac{40 \mu\text{A}/\sqrt{2}}{2} \cdot 15 (5 - V_x - 0.9)^2$$

$$\frac{120 \mu\text{A}}{2} \cdot \frac{10}{120} (V_x - 0.8)^2$$

$$\frac{300 \mu\text{A}}{\sqrt{2}} (4.1 - V_x)^2 = \frac{5 \mu\text{A}}{\sqrt{2}} (V_x - 0.8)^2$$

$$60 (4.1 - V_x)^2 = (V_x - 0.8)^2$$


$$7.7 (4.1 - V_x) = V_x - 0.8$$

$$31.76 - 7.7 V_x = V_x - 0.8$$

$$V_x = 3.7\text{V}$$

CMOSedu.com

Threshold voltage mismatch

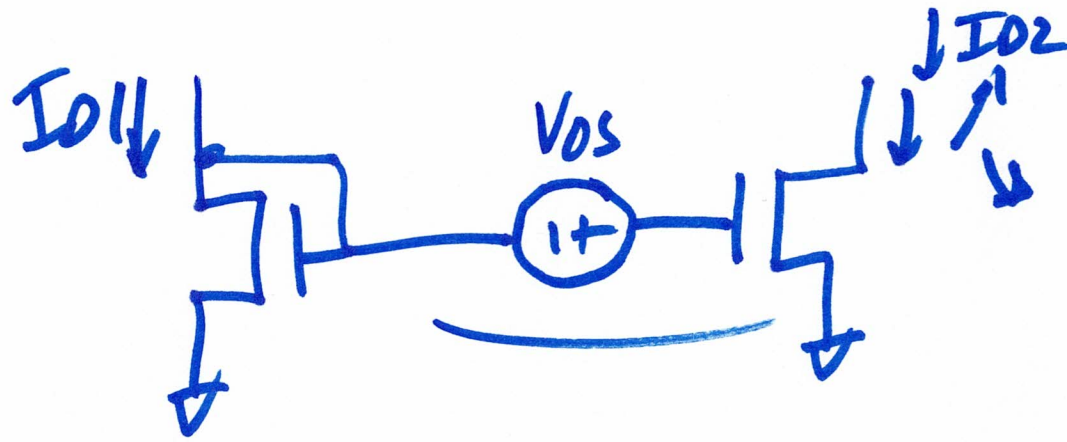

$$\frac{I_{D2}}{I_{D1}} =$$