

Quiz #15 EE 420/ECG 620 Spring 2020 Name: _____

Open book and closed notes.

Show your work for credit and place a box around each of your answers.

1. Estimate the input capacitance of the following circuit. Show your work for credit. (5 points)

