

Quiz #17 EE 420/ECG 620 Spring 2020 Name: \_\_\_\_\_

Open book and closed notes.

Show your work for credit and place a box around each of your answers.

1. Estimate the DC and AC voltages on the sources of M1/M2. Also estimate the DC and AC voltages on Vout. (5 points)

