

Quiz #19 EE 420/ECG 620 Spring 2020 Name: \_\_\_\_\_

Open book and closed notes.

**Show your work for credit and place a box around each of your answers.**

1. Show how to determine the AC gain of the PMOS diff-amp in Fig. 22.37. Be very clear and consistent with your labeling. (5 points)