

Open book and closed notes.

Show your work for credit and place a box around each of your answers.

1. Plot the IV curve for the following circuit? (4 points)

