Open book and closed notes.

Show your work for credit and place a box around each of your answers.

For the 1 um book process used below: $V_{THN} = 800 \text{ mV}$, $V_{THP} = 900 \text{ mV}$, $KP_n = 120 \text{ uA/V}^2$, and $KP_p = 40 \text{ uA/V}^2$.

1. What is the DC voltage on the drain of M7? Calculate the DC and AC currents in M5. (5 points)

