

EE 421 / ECG 621

Dec. 4, 2013

Lecture 27

Review for Final

Parameters from SPICE
level 3

Level 3

VTO VSG VSD
2 pmos

2 pmos

$$C_{ox} = \frac{C_{ox} \cancel{A_{ox}}}{A_{ox}}$$

$\swarrow$ KP
 TOX T


$$I_0 = \frac{K_P}{2} \cdot \frac{\omega}{L} (V_{GS} - V_{th})^2$$

$$I_0 = \frac{K_P}{2} \cdot \frac{\omega}{L} (V_{GS} - V_{THN})$$

300N


600~ VTO
0.64

↓
VTO

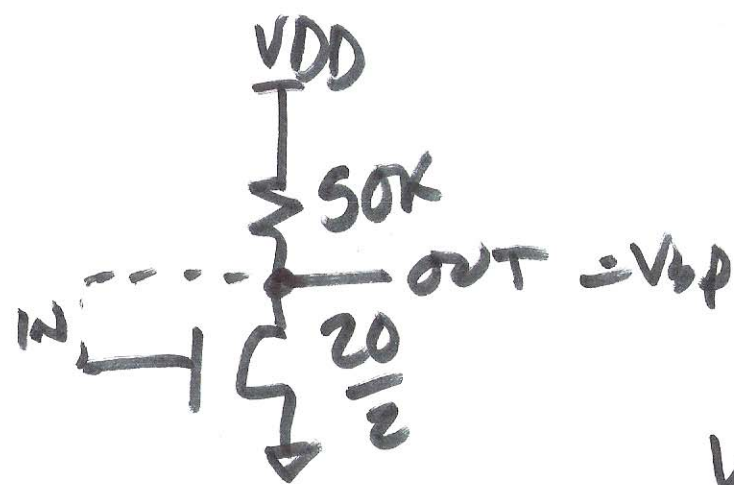



V_{sp} , V_{th} , V_{ol}
state assumptions
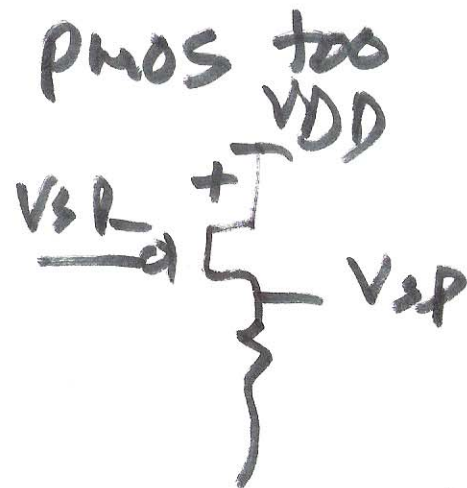
$$\frac{V_{DD} - V_{sp}}{50k} = \frac{20}{Z} \cdot \frac{K_P}{2} (V_{sp} - \underbrace{V_{th}}_{V_{TO}})^2$$



$$V_{sg} = V_{DD} - V_{sp}$$

Calculate R_N , R_N' , C_{ox}

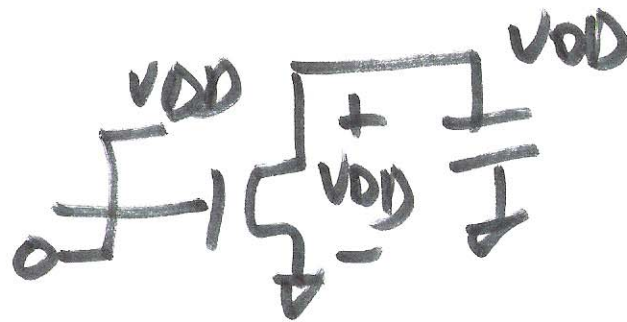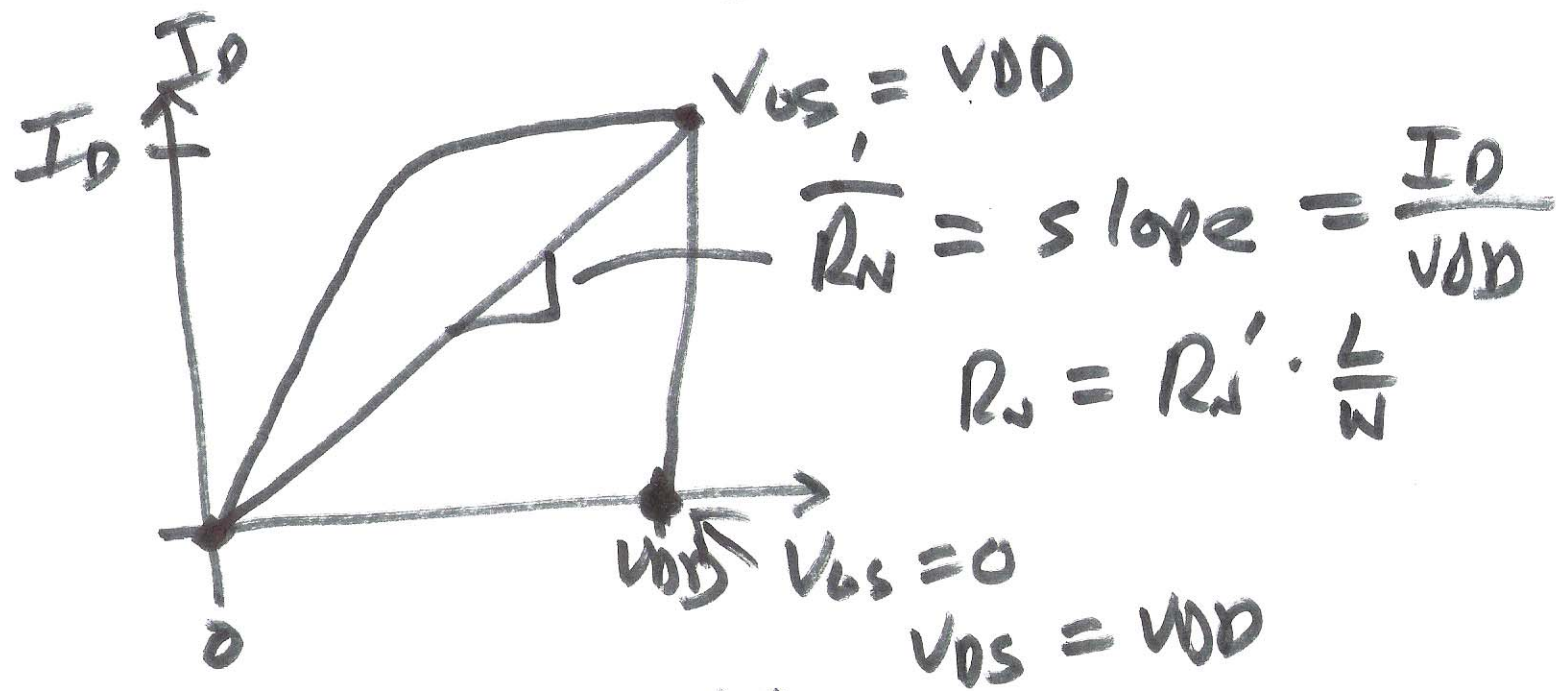


$$R_N = \frac{V_{DD}}{\frac{K_P}{2} \cdot \frac{W}{L} (V_{DD} - V_{THN})^2}$$

pmos
too

$$R_N' = \frac{V_{DD}}{\frac{K_P}{2} (V_{DD} - V_{THN})^2}$$

CMOSedu.com

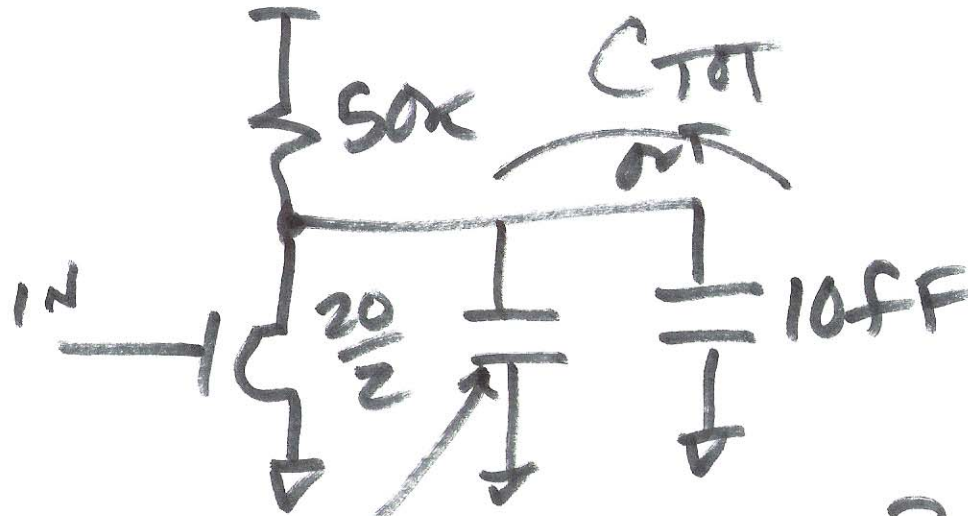

$$t_{pHL} = ? = 0.7 R_N C_{TOT}$$


$$C_{ox} =$$

$$t_{pLH} = ? = 0.7 \cdot 50x C_{TOT}$$


$$W \cdot L \cdot C'_{ox} \cdot (\text{Scale})^2$$

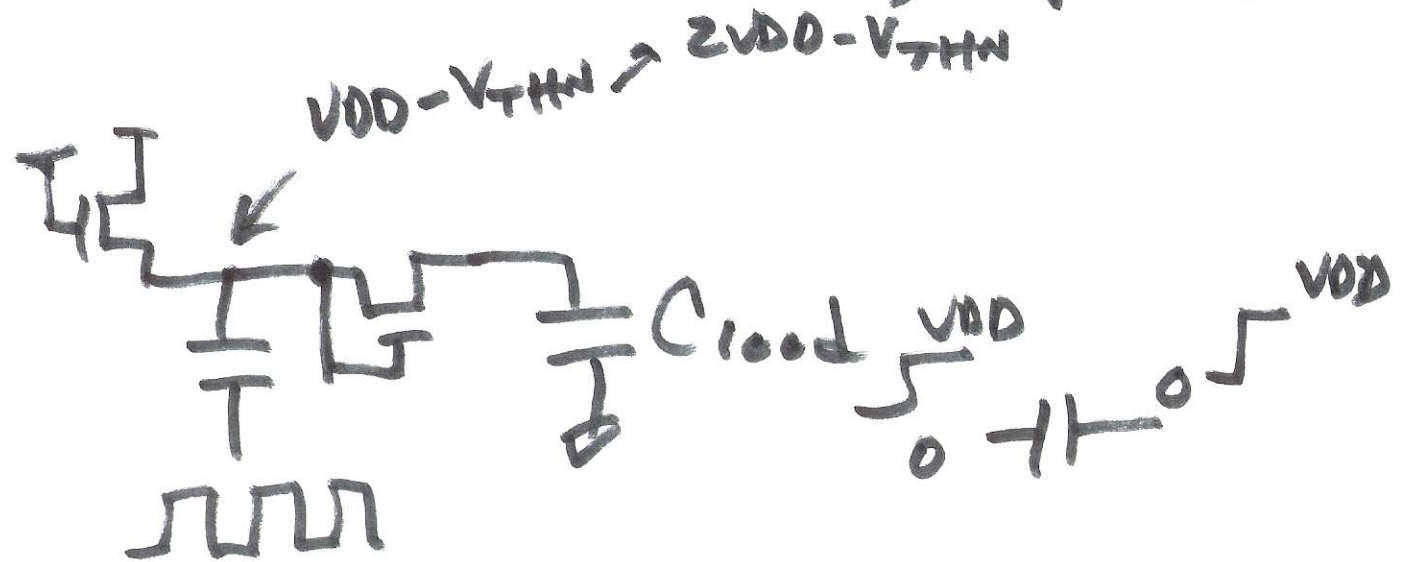4)


Sketch a ^{self-starting} pos. charge pump



Sketch a ^{NEG.} charge pump

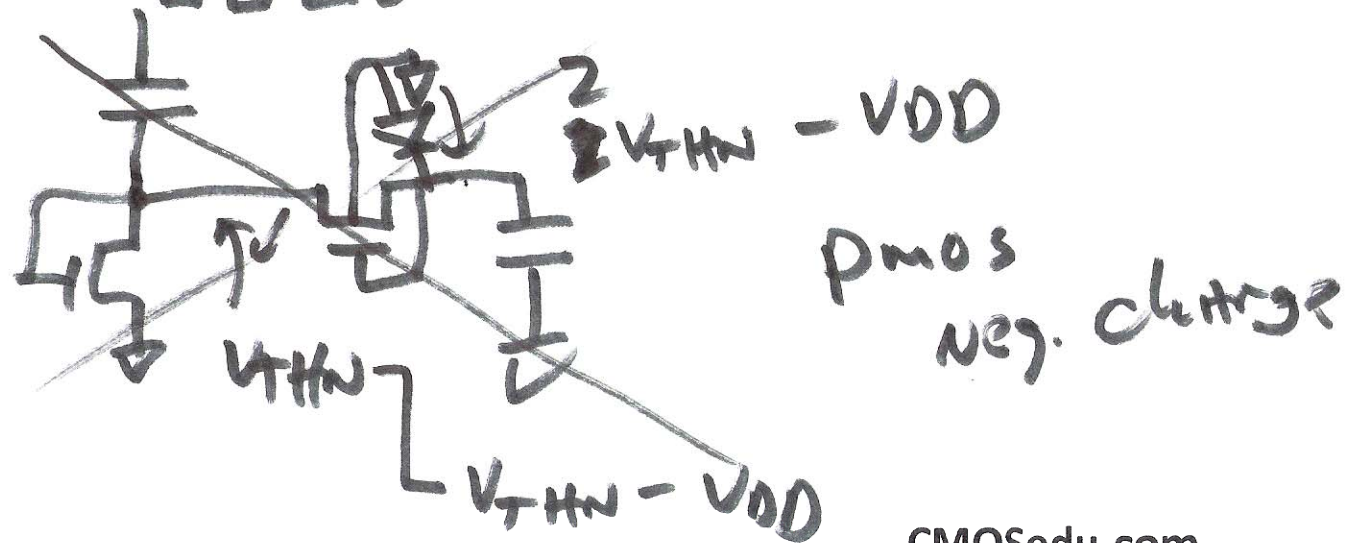

Estimate delays

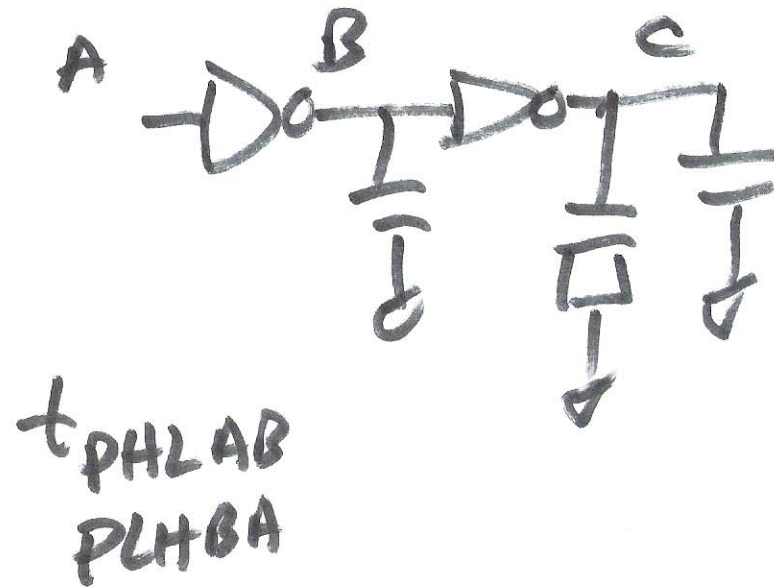

Sketch the schematic of an edge triggered D-FF




$$\bar{A}B + \bar{B}A = \text{XOR}$$

$$A + CB$$



$$\overline{A \cdot B}$$

Layout $\rightarrow$ Schematic



Poly1-Poly2 CAP

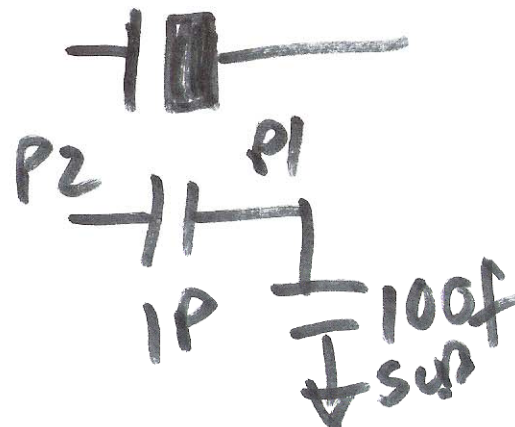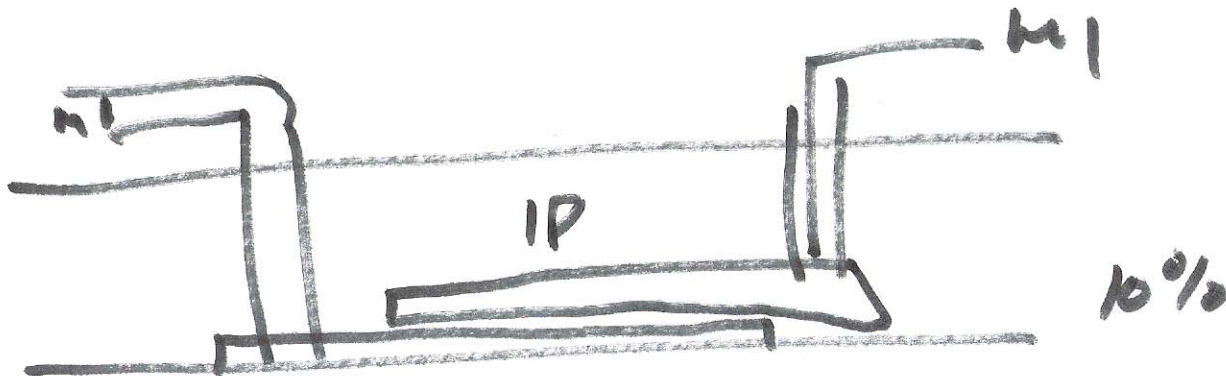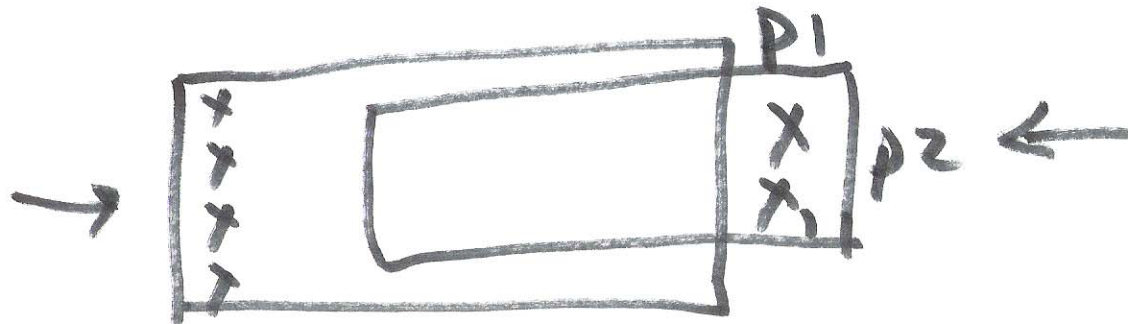

10%

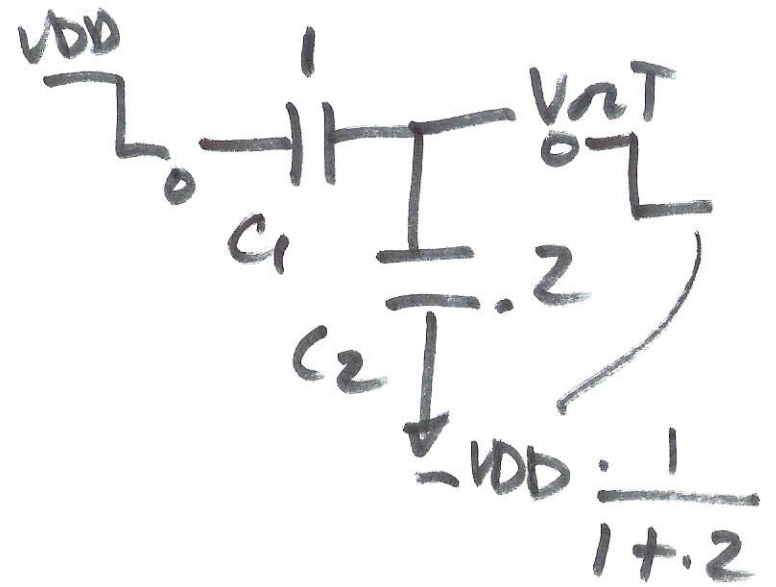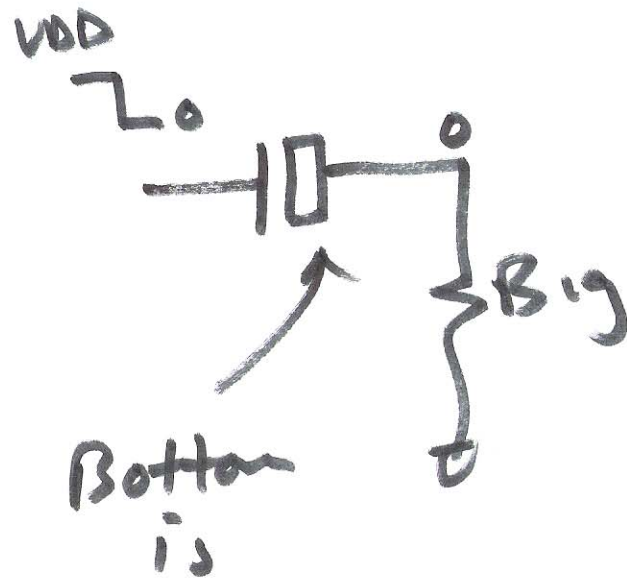

20% of desired

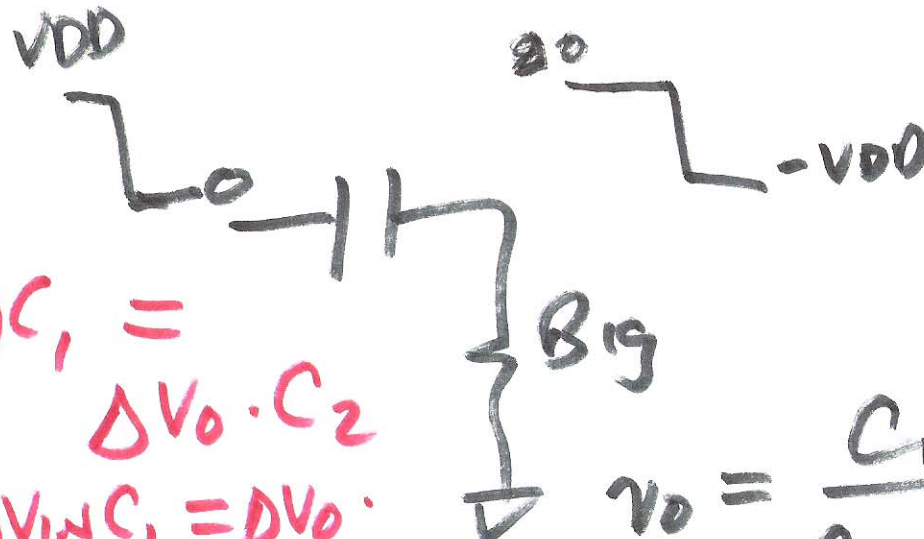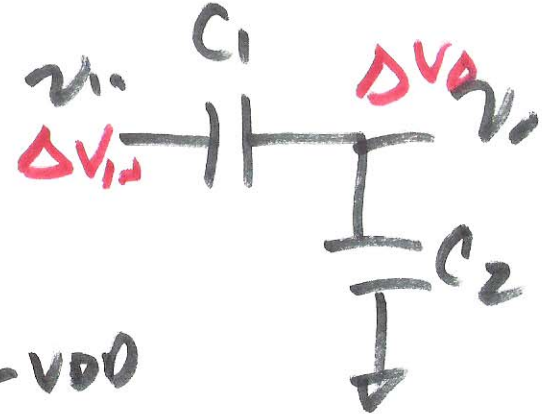



$$(\Delta V_{in} - \Delta V_{out})C_1 = \Delta V_{out} \cdot C_2$$

$$\Delta V_{in} C_1 = \Delta V_{out} (C_1 + C_2)$$

$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{C_1}{C_1 + C_2}$$

$$v_o = v_{in} \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + \frac{1}{j\omega C_1}}$$
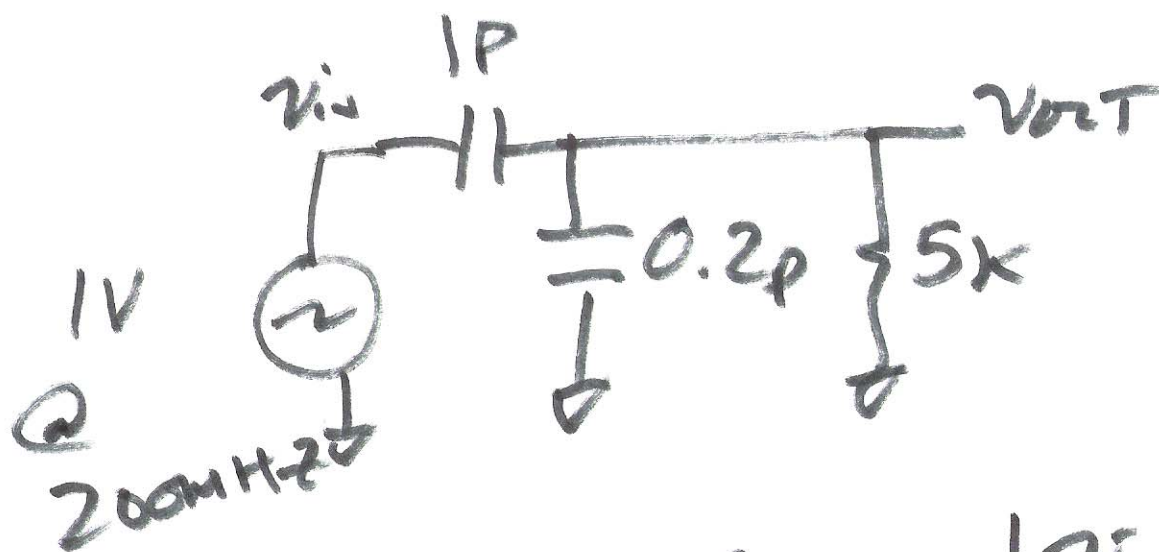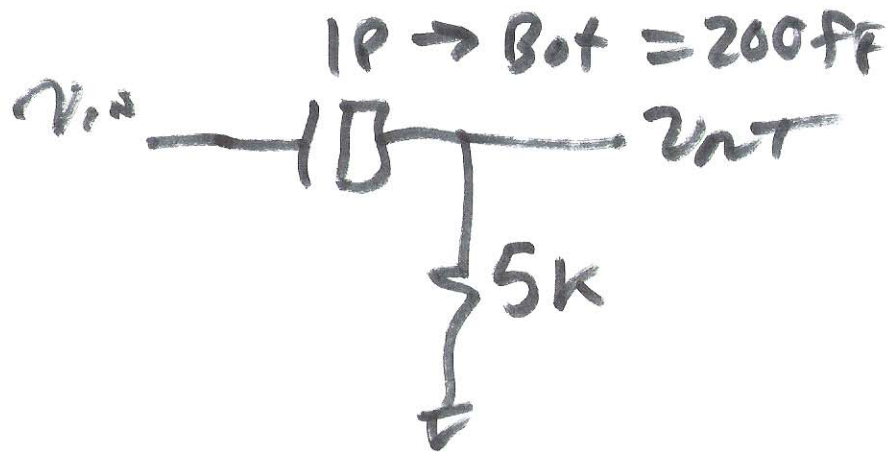
$$\frac{v_o}{v_{in}} = \frac{C_1}{C_1 + C_2}$$




plot
 $\left| \frac{v_{out}}{v_{in}} \right|$ v. f
 $\angle \frac{v_{out}}{v_{in}}$ v. f
 Bode plot

Sketch v_{out} & v_{in}
 on the same plot
 || $\angle \rightarrow t_d$

a)

Switching point voltage

$$S \cdot A + \bar{S} \cdot B = z$$

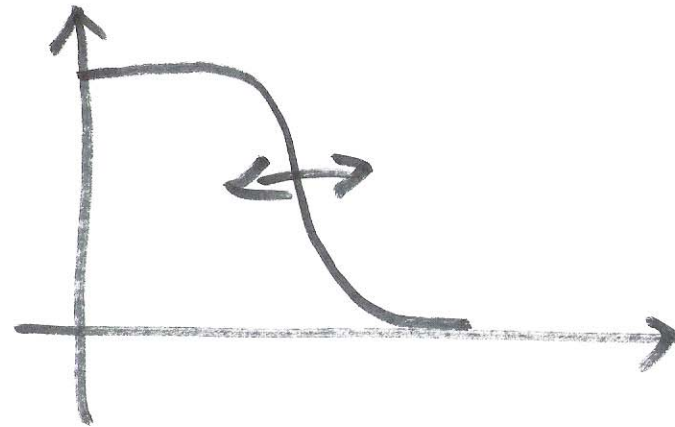

power diss.

on & off currents
& how relate to power


$$\begin{array}{l}
 \begin{array}{c}
 2V \\
 \updownarrow \\
 \text{PMOS} \\
 \updownarrow \\
 0 \\
 \updownarrow \\
 \text{NMOS} \\
 \updownarrow \\
 0
 \end{array}
 \end{array}$$

$$I_{on, P} = \frac{1 \mu A}{4 \mu s}$$

$$I_{off, N} = 0.5 \mu A / \mu s$$

$$\frac{1 \mu A \cdot 10 \cdot 0.3 \mu s}{4 \mu s} = 3 \mu W$$

$$\underline{\underline{6 \mu W}}$$

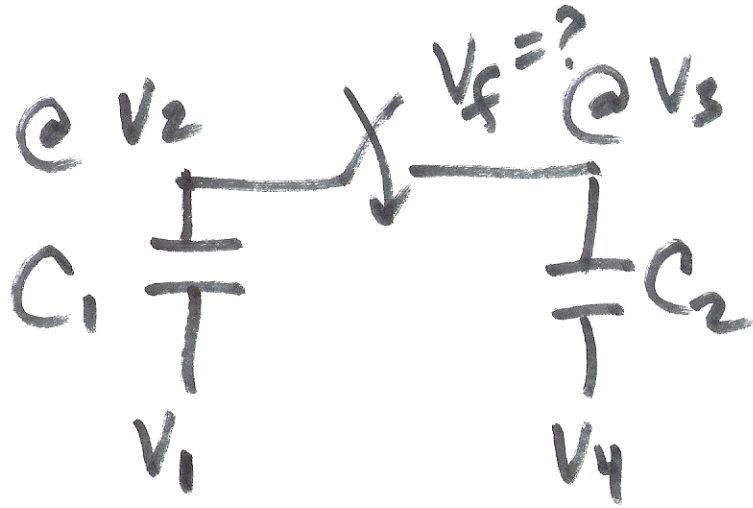

$$C_1(V_2 - V_1) + C_2(V_3 - V_4) =$$

$$\cancel{C_1(V_2 - V_1) + C_2(V_3 - V_4)} \quad C_1(V_f - V_1) + C_2(V_f - V_4)$$

$$V_f = \frac{C_1 V_2 + C_2 V_3}{C_1 + C_2} = V_f (C_1 + C_2)$$