


Lecture 14

OCT. 13, 2014

Review for mid-term

From ch. 1


Sketch V_{in} & V_{out} v.t

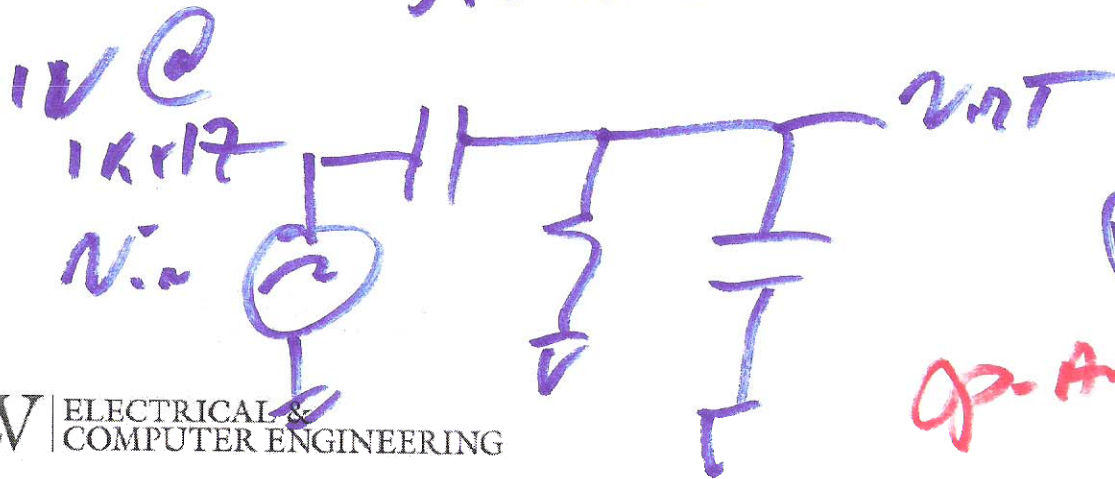

Bode plot


Op-Amps

Ch. 2

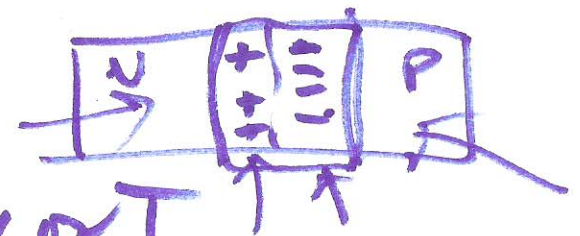


N-well

layout
Sheet Resistance

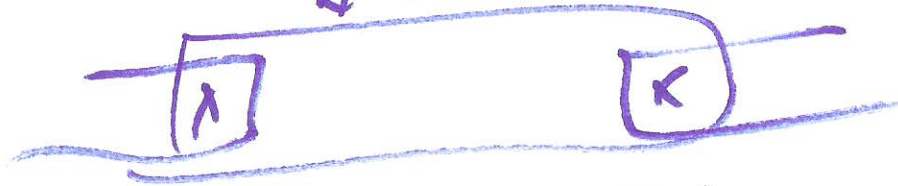

Depletion C

Distributed RC

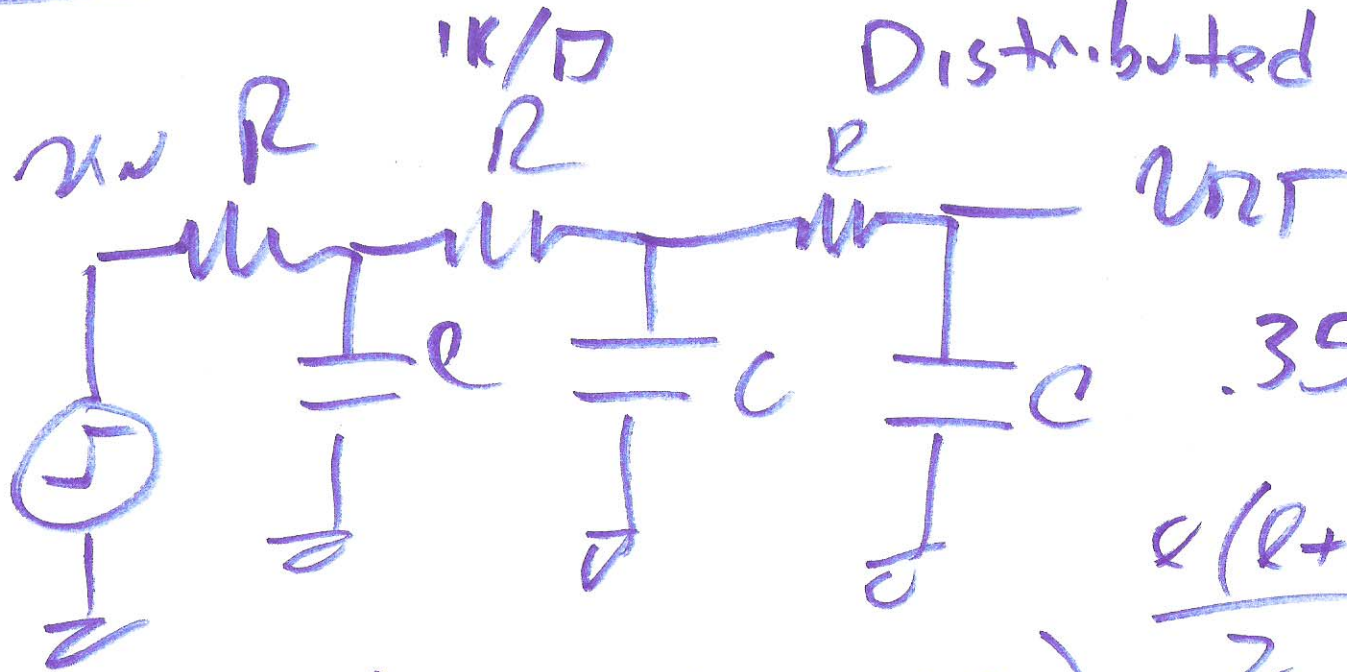





$$.35 RC l^2$$

$$\frac{l(l+1)}{2} \approx \frac{l^2}{2}$$

$$0.7(RC + 2RC + 3RC)$$

l big

2)

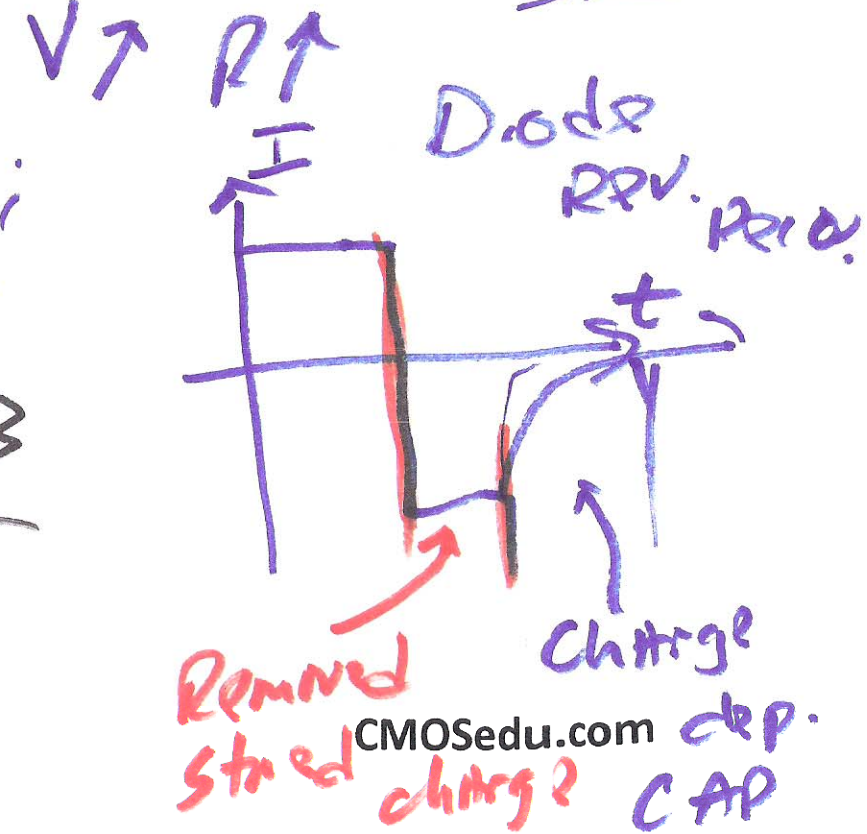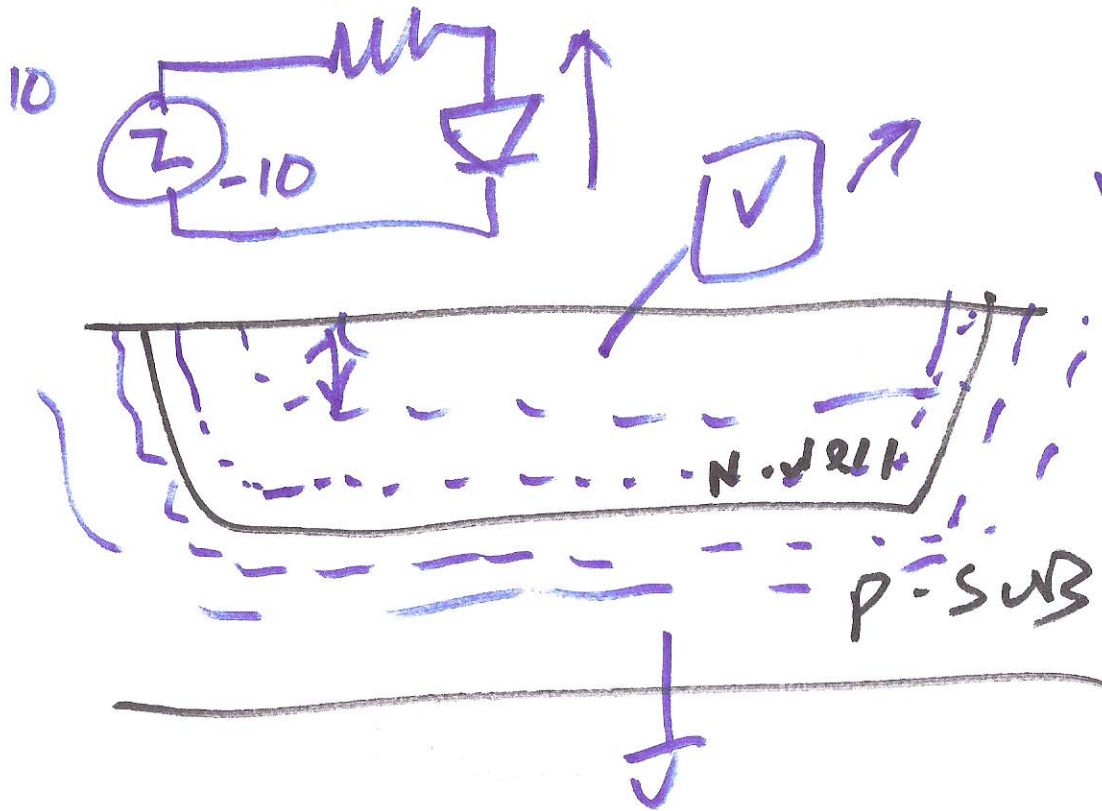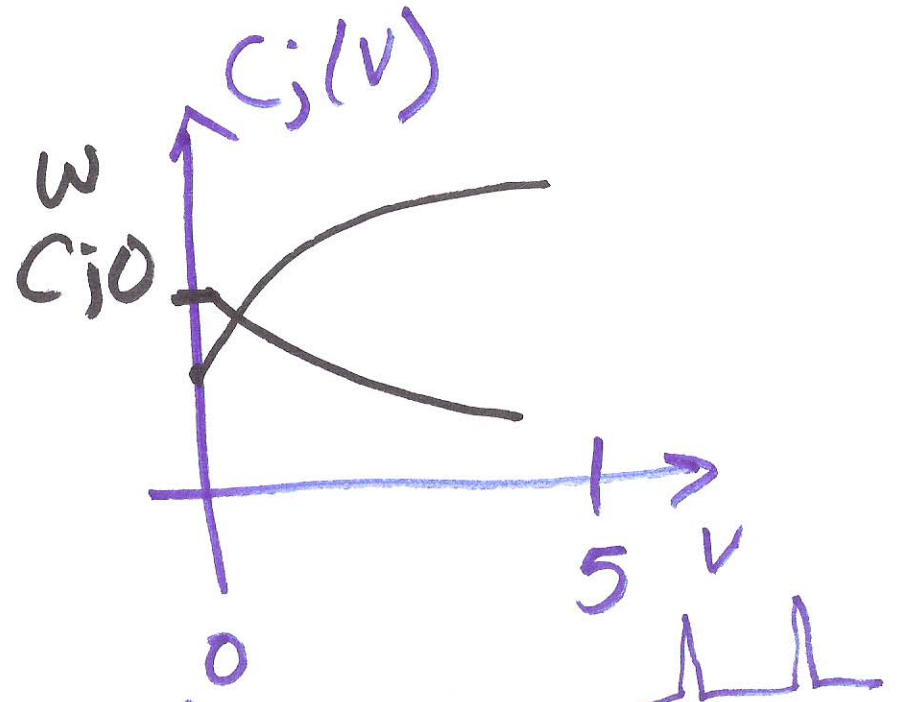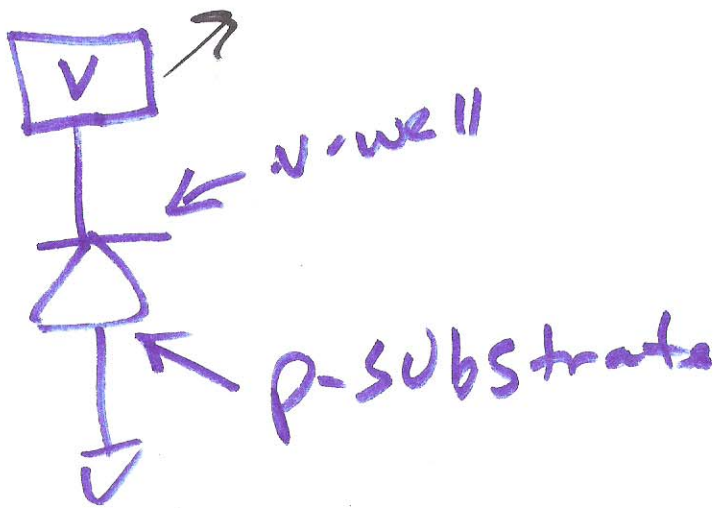

3)

Ch. 3


Metal layers

Layout VIA
NGL

Electromigration

Power Supply Decoupling

Sheet resistance

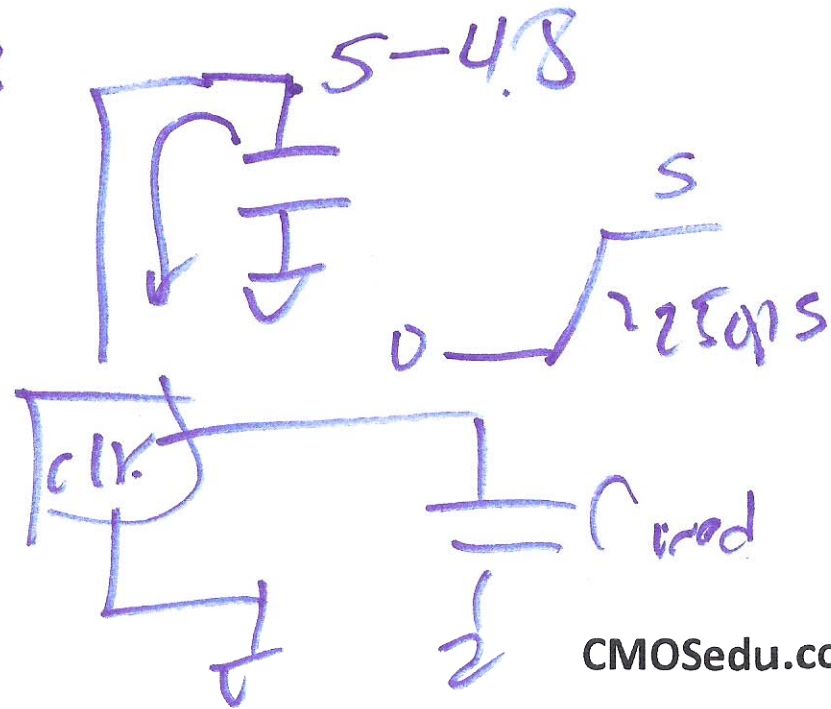

4)


Ch. 4

poly-poly



Active & poly

Hi-Res.

LAYOUTS

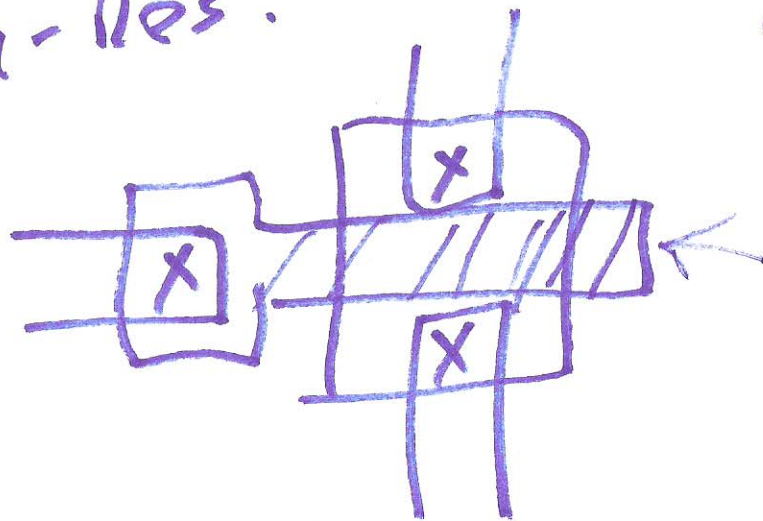


poly

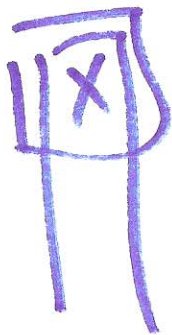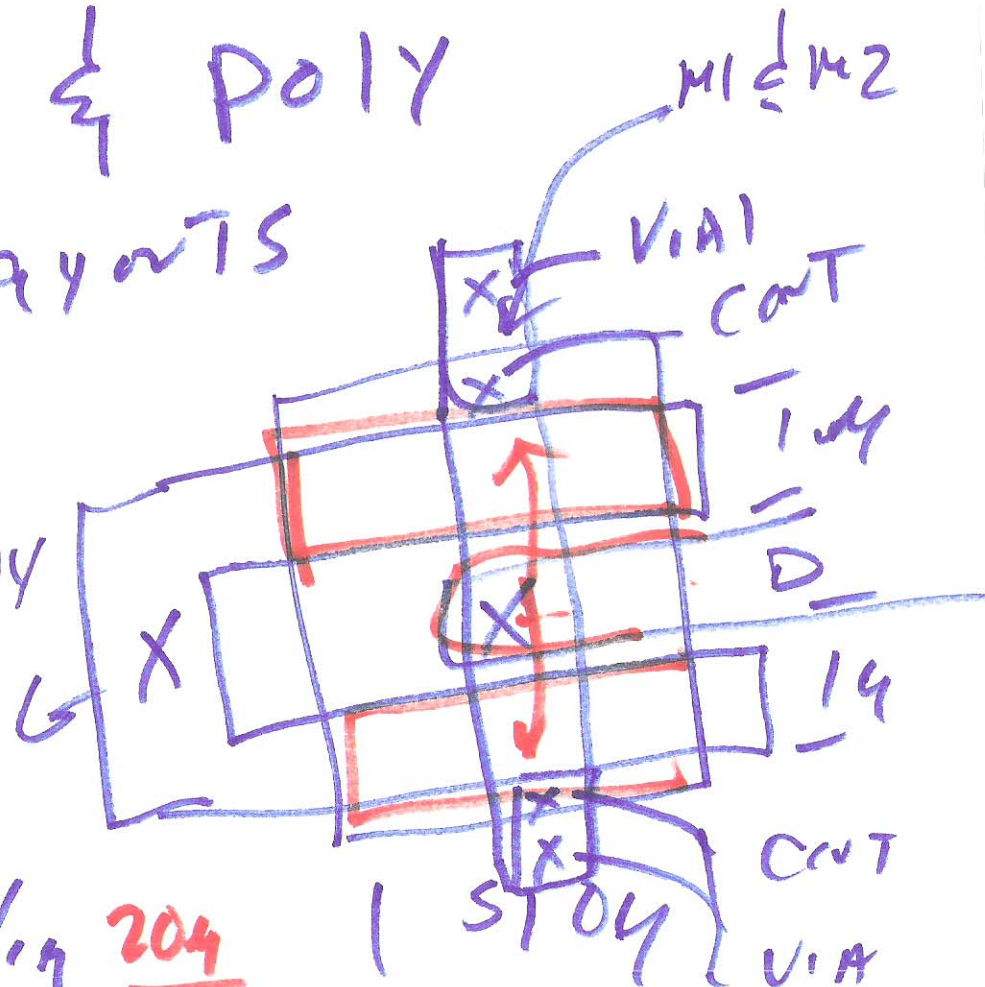

$$D = 10\mu / 14 \quad M=2 \quad \frac{204}{14}$$

5)

MOSFET CAPACITANCES

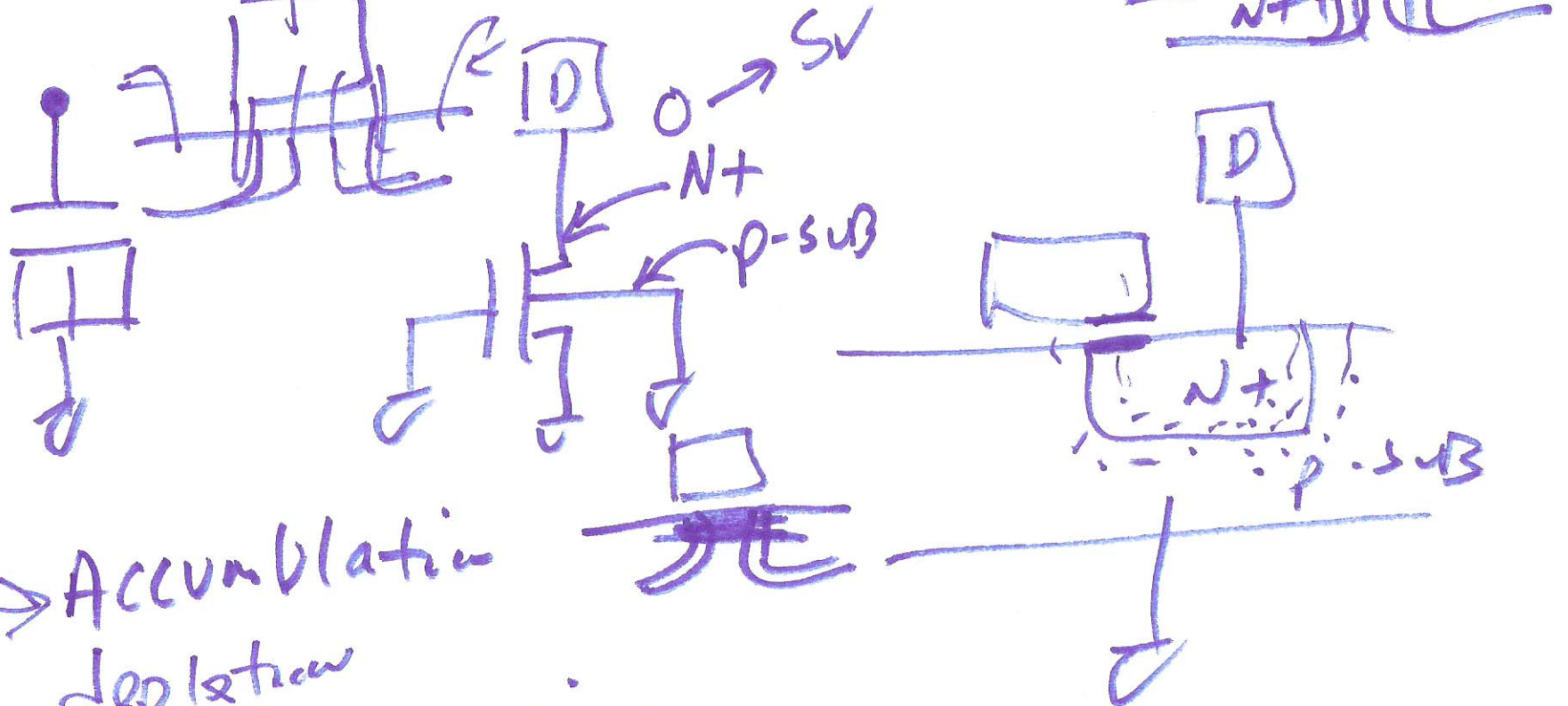


Accumulation
depletion
Strong inversion


Lateral diffusion

OVERLAP C

6)

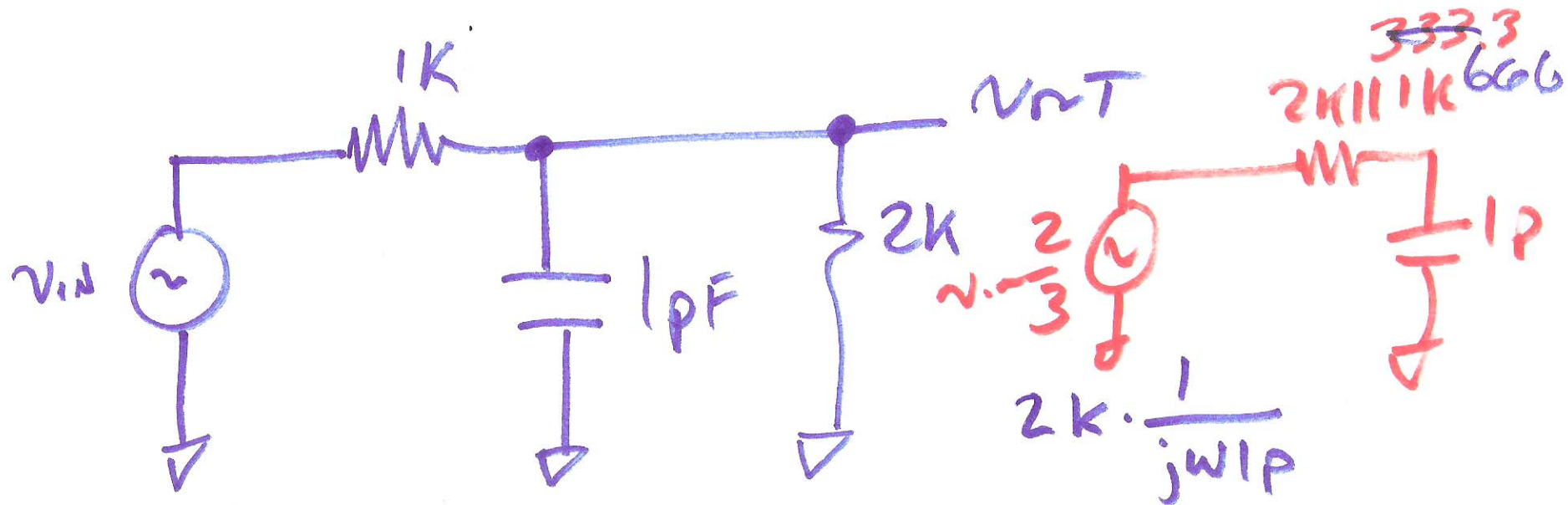
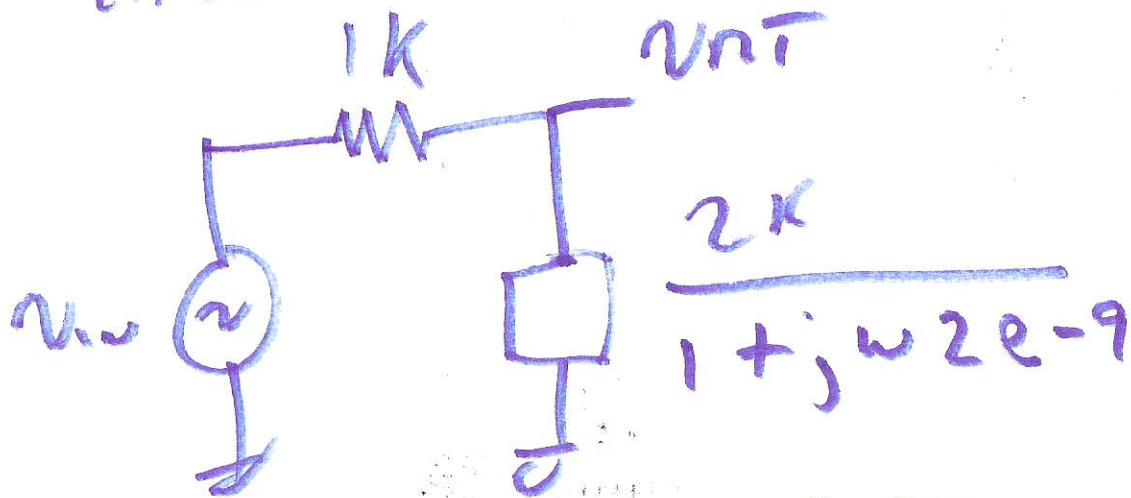
$$\frac{1}{2\pi \cdot 666 \cdot 10^{-12}}$$



$$\frac{2k}{1 + j\omega 2e-9}$$

$$\frac{2k \cdot \frac{1}{j\omega 1p}}{2k + \frac{1}{j\omega 1p}}$$

$$v_{nt} = v_w \cdot \frac{\frac{2k}{1 + j\omega 2e-9}}{\frac{2k}{1 + j\omega 2e-9} + 1k}$$

$$\frac{v_{nt}}{v_w} = \frac{2k}{2k + 1k + j\omega 2e-9}$$

$$\frac{V_{out}}{V_{in}} = \frac{2k + j0}{3k + j\omega 2e-6}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\sqrt{(2k)^2 + (0)^2}}{\sqrt{(3k)^2 + (2\pi f 2\mu)^2}} = \frac{2k}{\sqrt{(3k)^2 + (2\pi f 2\mu)^2}}$$

$$\theta = \frac{t_d}{T} \cdot 360^\circ$$


$$= t_d \cdot f \cdot 360 \angle \frac{V_{out}}{V_{in}} = \tan^{-1} \frac{0}{2k} - \tan^{-1} \frac{2\pi f 2\mu}{3k}$$

$$= \frac{t_d}{T} \cdot 2\pi$$

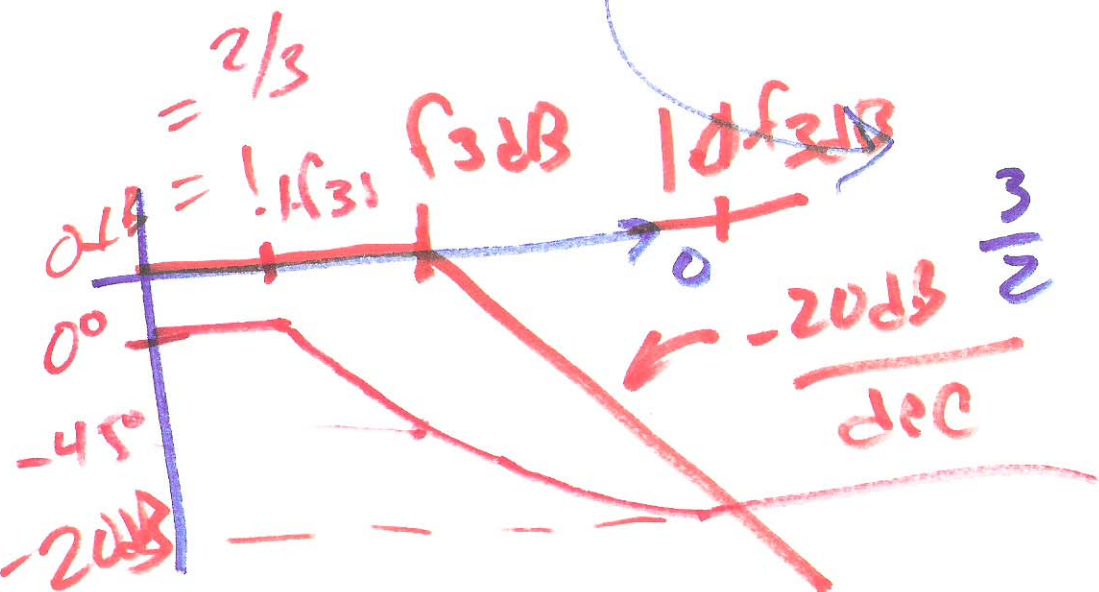8)

$$\frac{v_{out}}{v_{in}} = \frac{1}{\frac{3}{2} + j\omega 1N}$$

$$= \frac{1}{\frac{3}{2}} \cdot \frac{1}{1 + j\omega \frac{2}{3}N}$$





$$\frac{3}{2} = 2\pi f_{3dB} \cdot \frac{1}{3}N$$

$$f_{3dB} = \frac{1}{2\pi 1N \cdot \frac{2}{3}}$$


$$= \frac{1}{2\pi \cdot 666 \cdot 10^{-9}}$$

$$= \frac{1}{2\pi \cdot 666 \cdot 10^{-12}}$$

9)

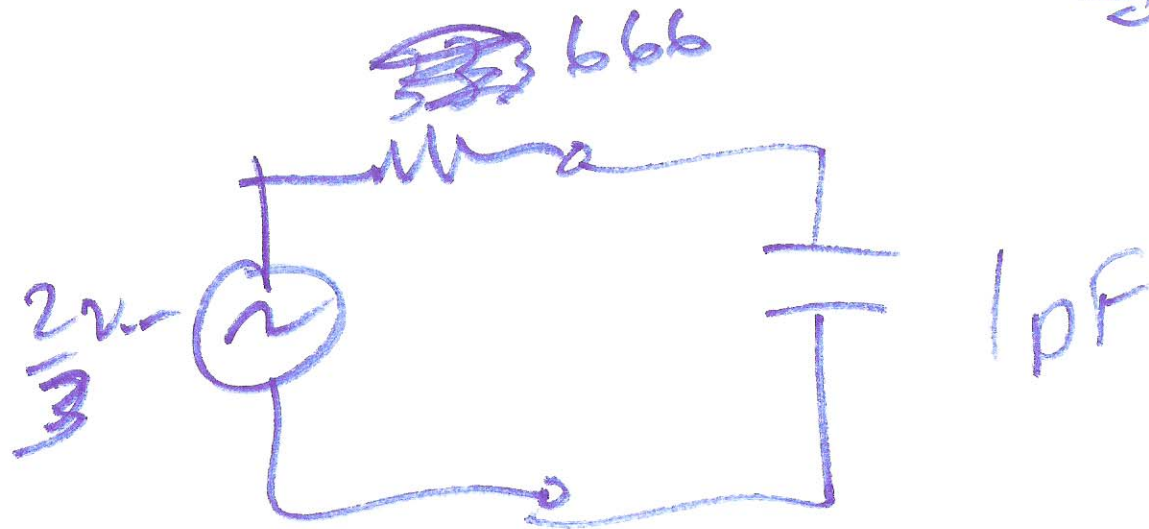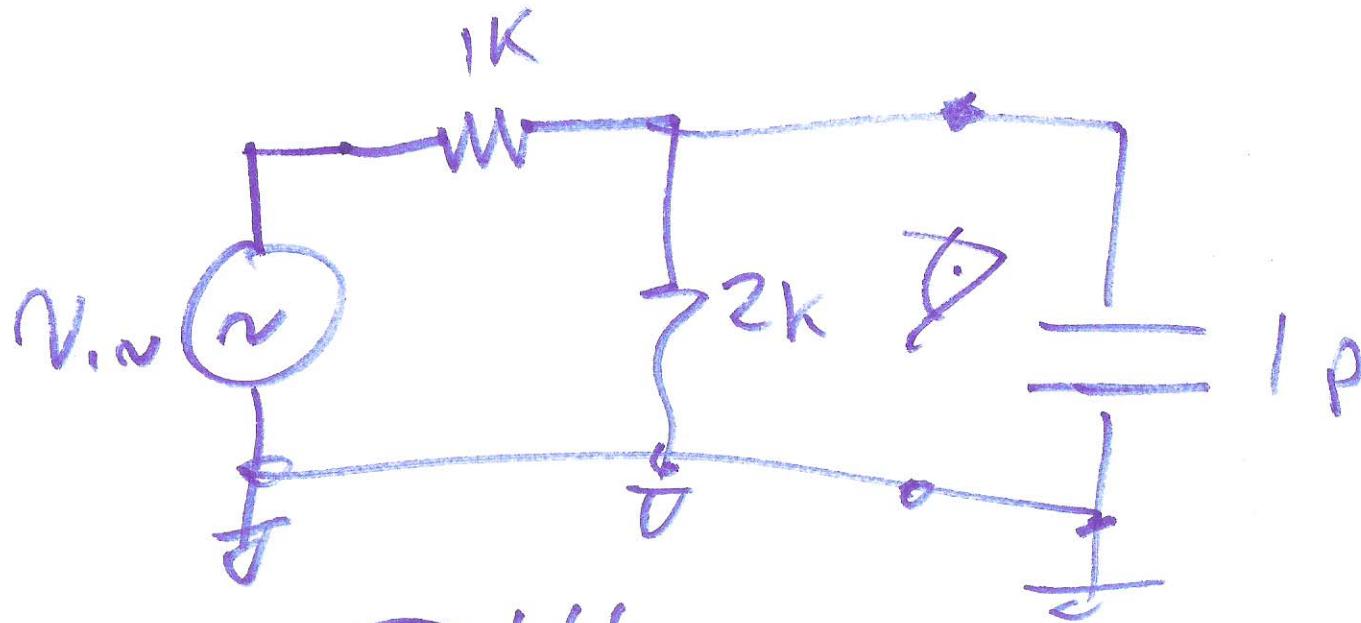

10)

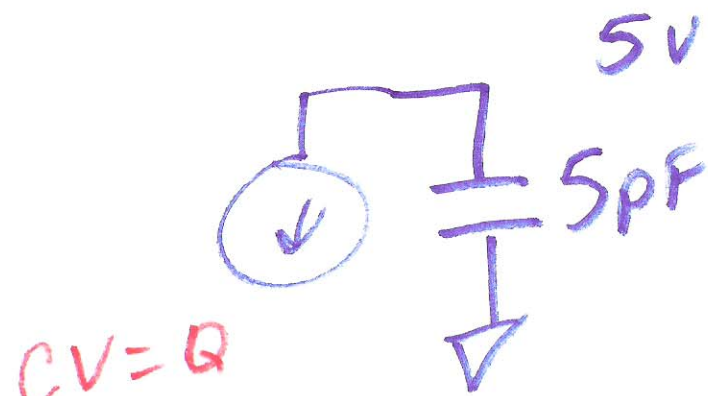

$$CV = Q$$

$$I = C \frac{dV}{dt}$$

$$I = C \frac{dV}{dT}$$

$$1) Q = CV = 25pC$$


2) How current flows to discharge in 25ps?

$$Q = CV = 25pC \frac{1A \cdot 25ps}{1N}$$

$$I = 5p \cdot \frac{5}{25ps} = \underline{\underline{1A}}$$

$$0.2V \cdot C = 25pC$$
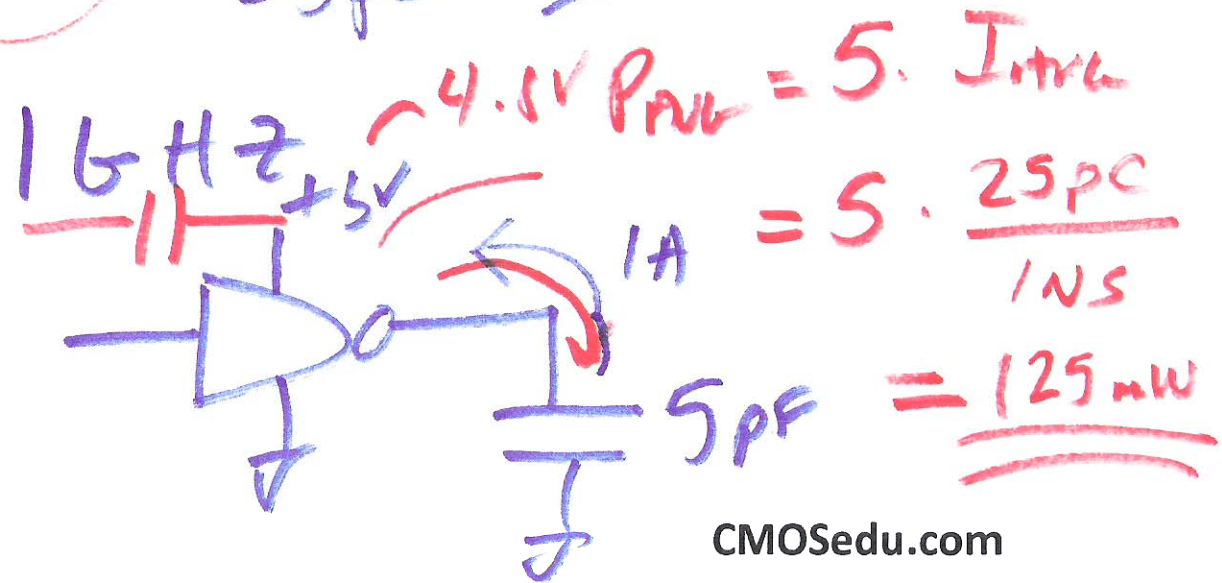
$$C = \frac{25p}{0.2} = \underline{\underline{125pF}}$$



11)