
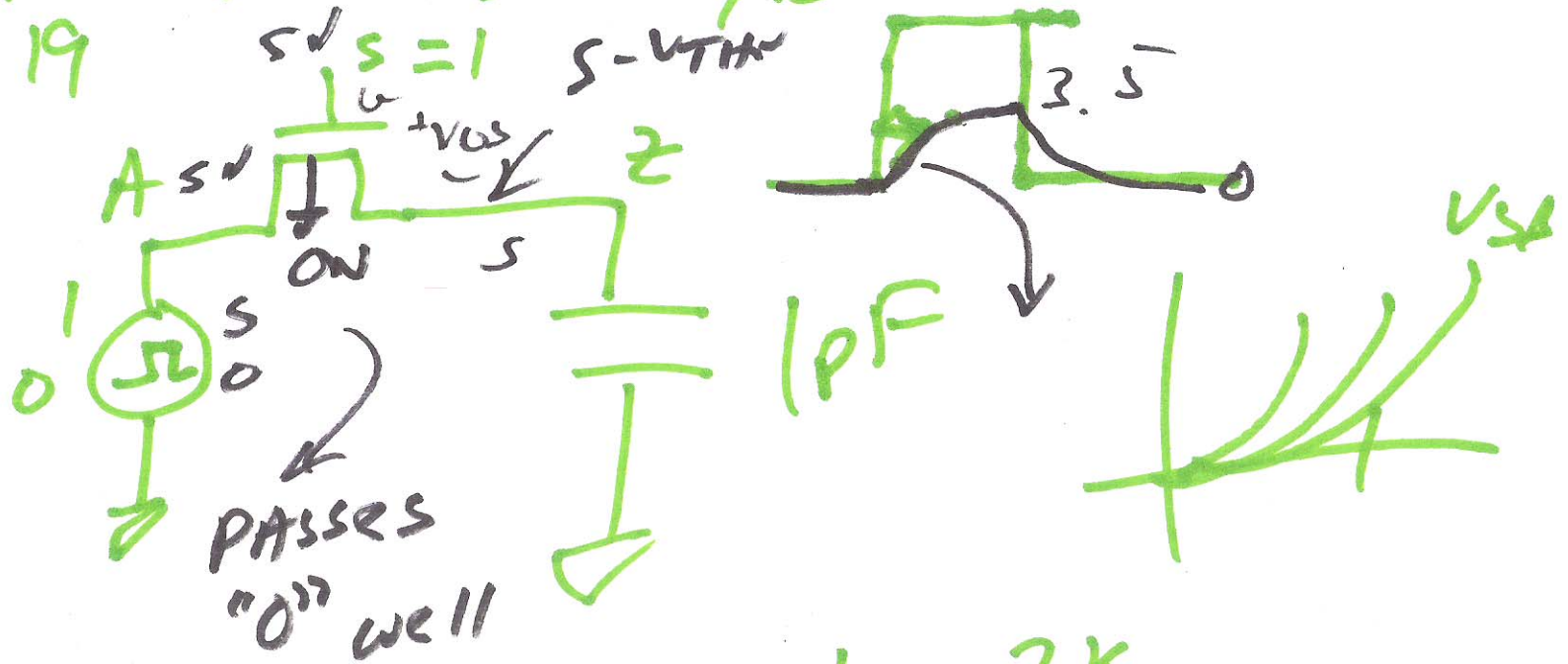



OCT. 29, 2014  
Lecture 19

EE421/EECG62

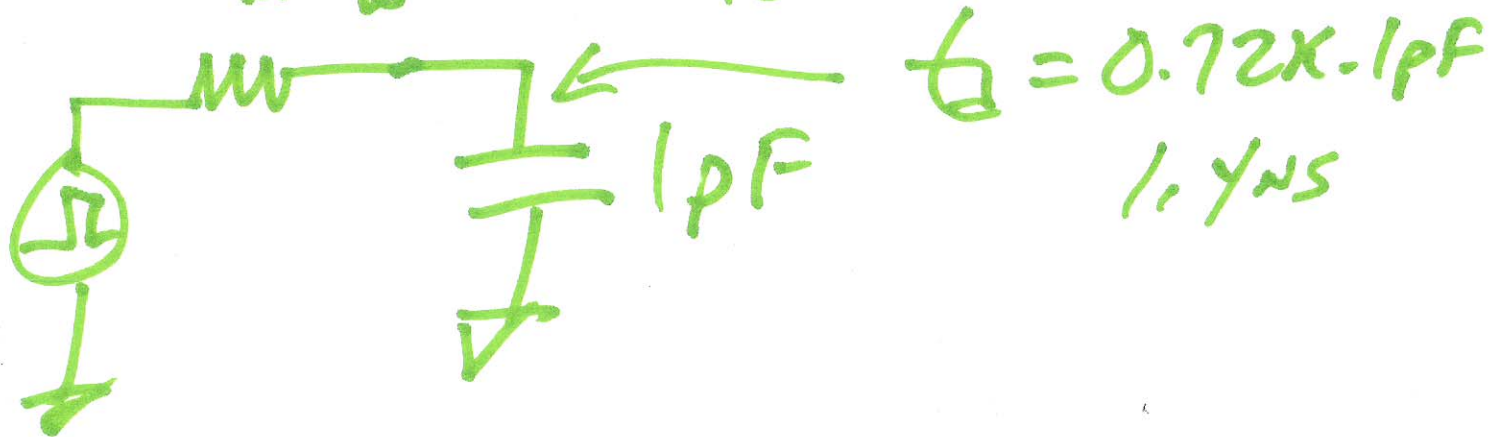

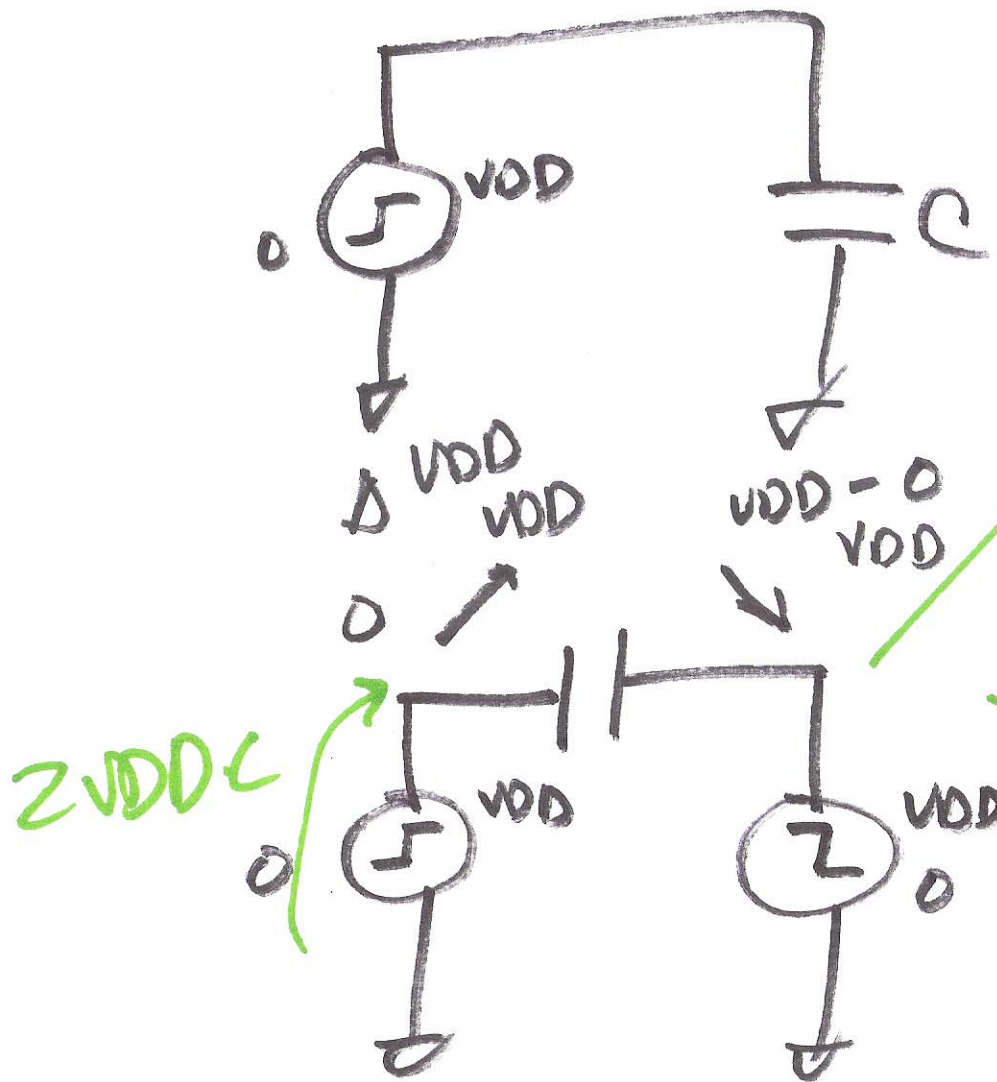
$$R_d \cdot \frac{C}{\omega} = 20k \cdot \frac{1}{10} = 2k$$





$$Q = C \cdot V_{DD}$$


~~$V_{DD} \cdot \frac{1}{2}$~~

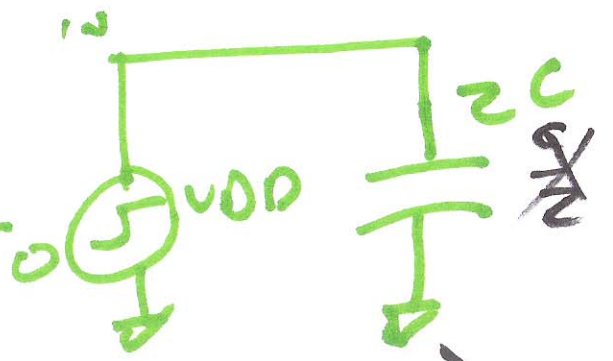




$$Q = C (V_{DD} - V_{DD})$$

$2V_{DD}$



$$Q = 2V_{DD} \cdot C$$

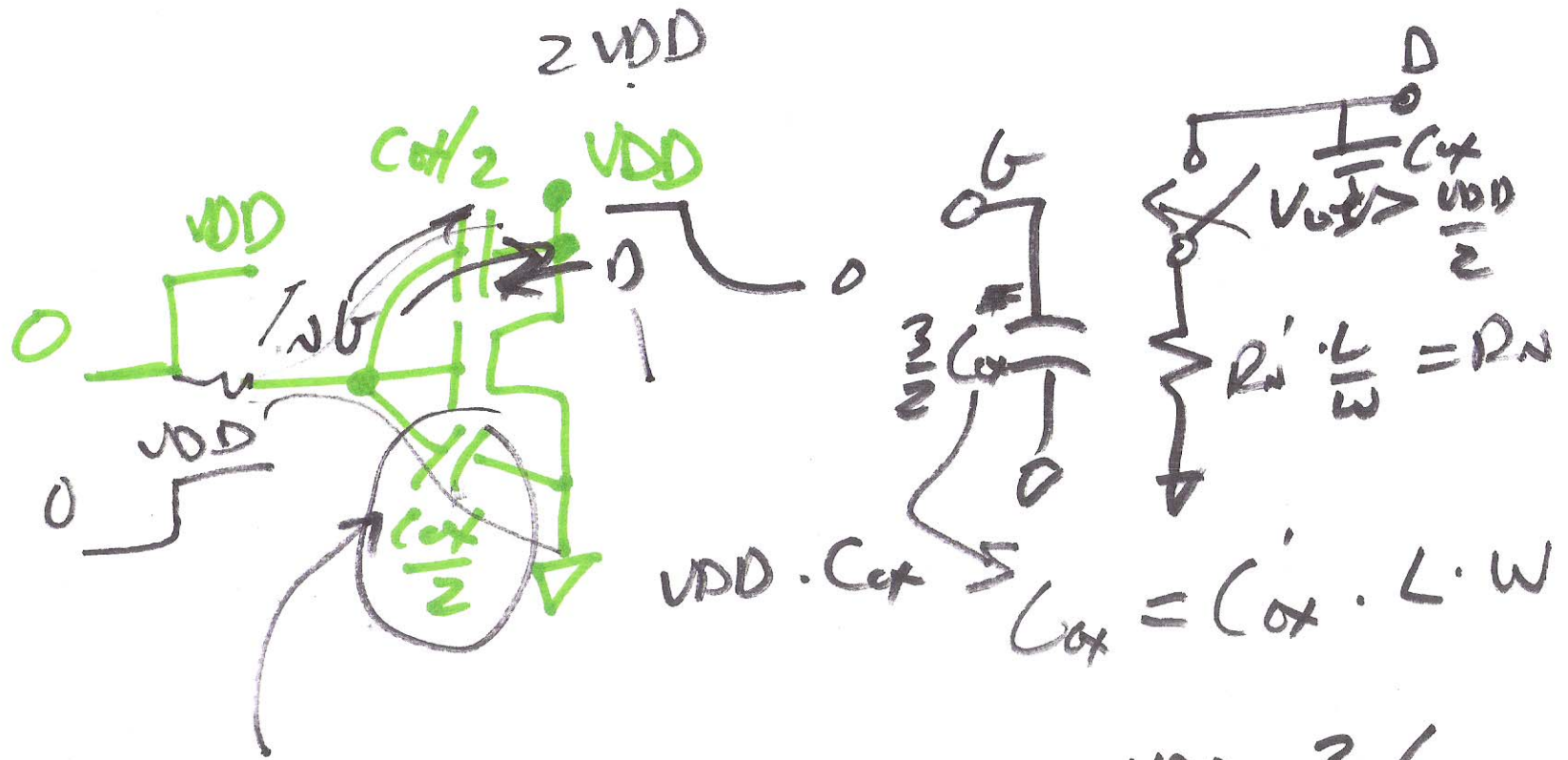
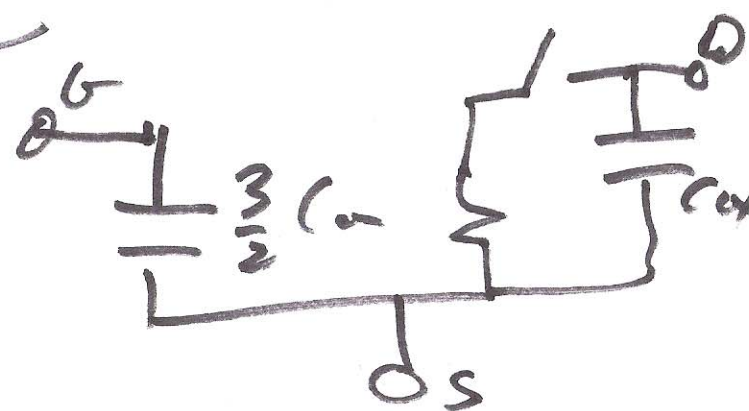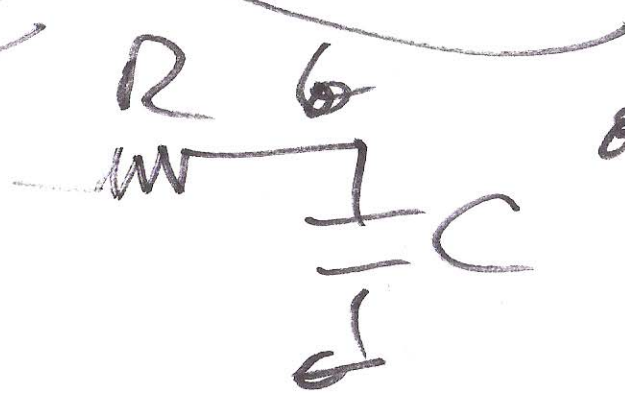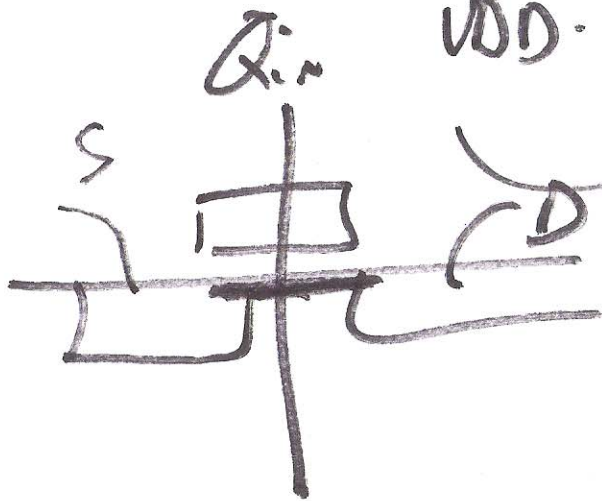
$$V_{DD} \cdot \frac{C_{ox}}{2} + V_{DD} - 2 \cdot \frac{C_{ox}}{2} = V_{DD} \cdot \frac{3}{2} C_{ox}$$


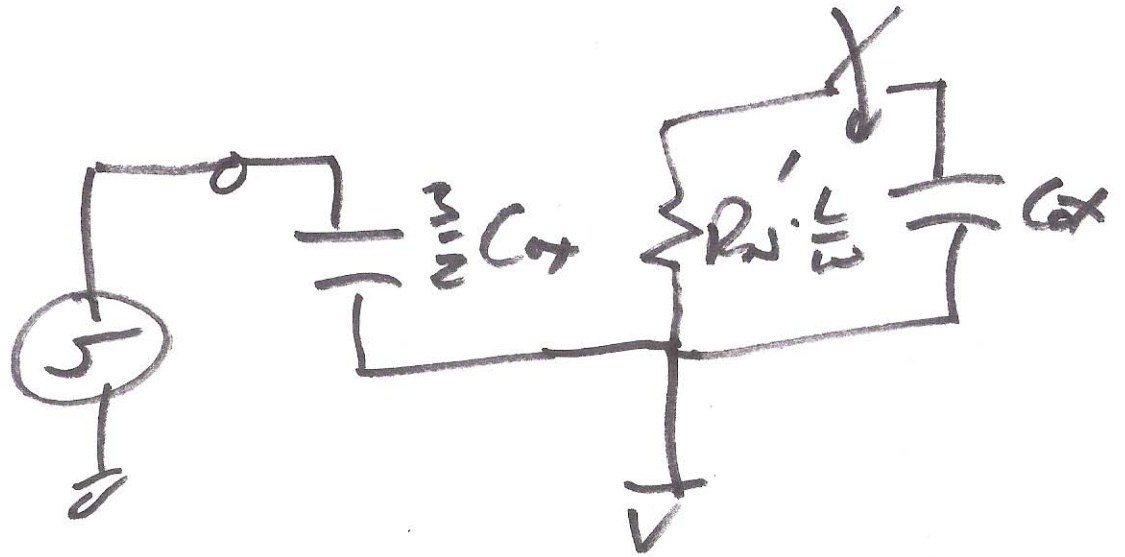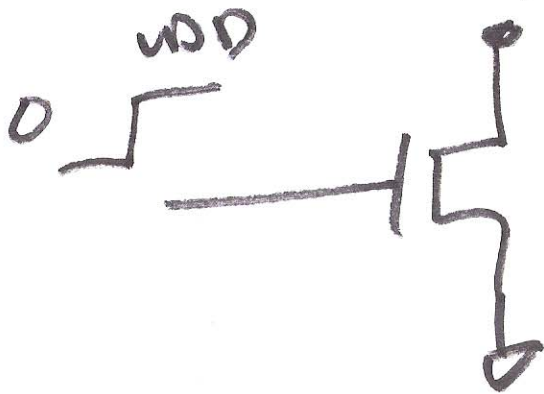
# Process characteristic initially time constant at VDD



$$\tau_N = R_N \cdot C_{ox} = R_N' \cdot \frac{L}{w} \cdot C_{ox} \cdot w \cdot L$$

$$= \frac{V_{DD}}{\frac{\mu_n C_{ox}}{2} (V_{DD} - V_{THN})^2} \cdot L^2 \cdot C_{ox}'$$

For high-speed  
 $L \rightarrow$  small  
 $\mu_n \Rightarrow$  Dis  
 $V_{DD} \rightarrow$  Big

4)