

EE 421 / ECG 621



Digital IC

Design


NOV. 2, 2015

Lecture 19


4 to 1 MUX/DEMUX

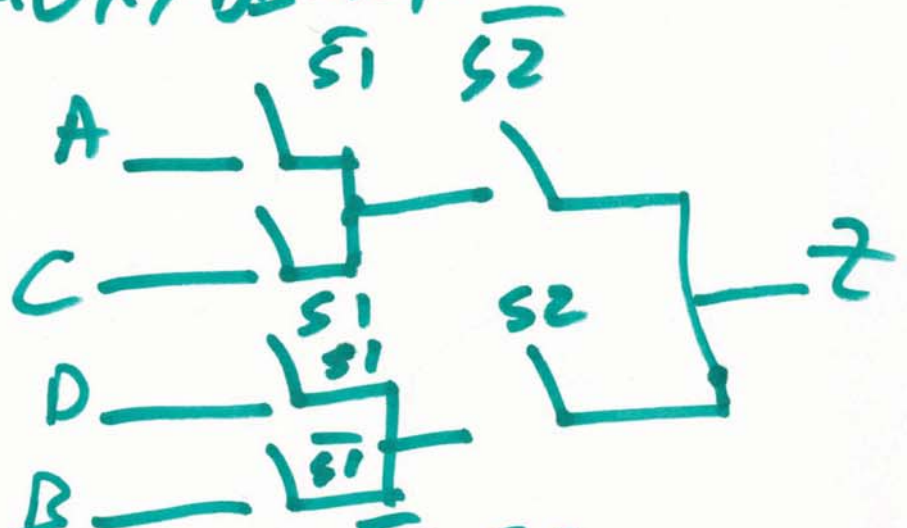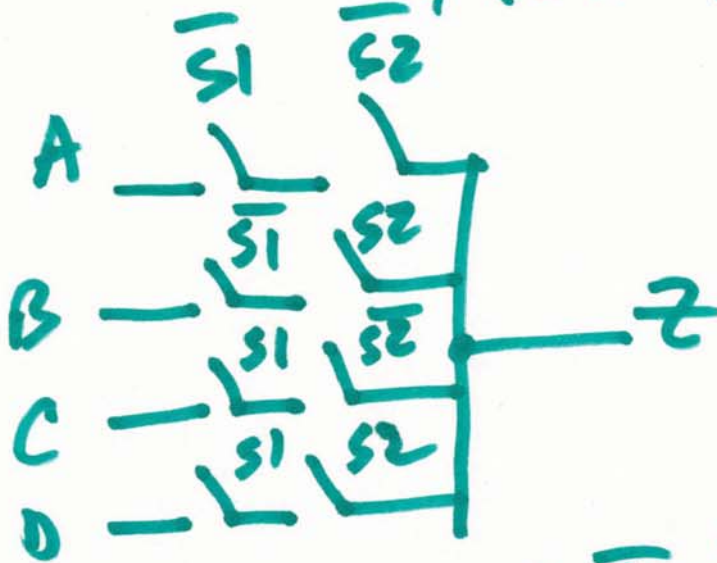

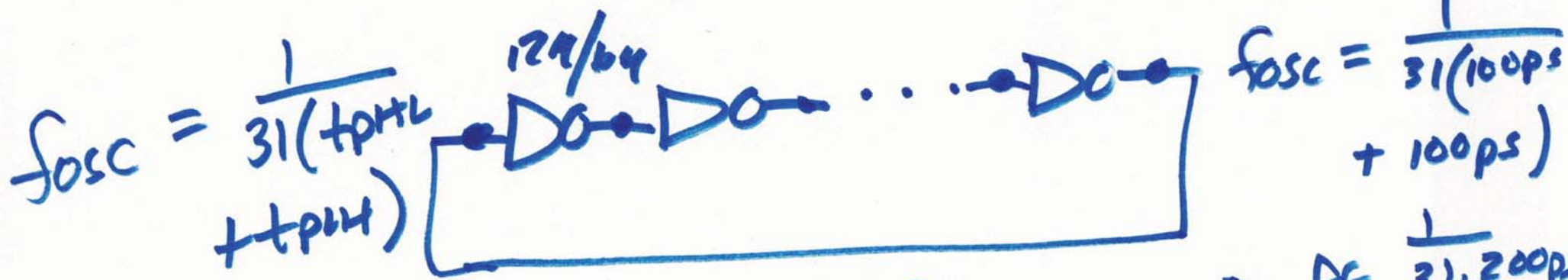
$$Z = A \cdot \bar{S}_1 \cdot \bar{S}_2 + B \cdot \bar{S}_1 \cdot S_2 + C \cdot S_1 \cdot \bar{S}_2 + D \cdot S_1 \cdot S_2$$





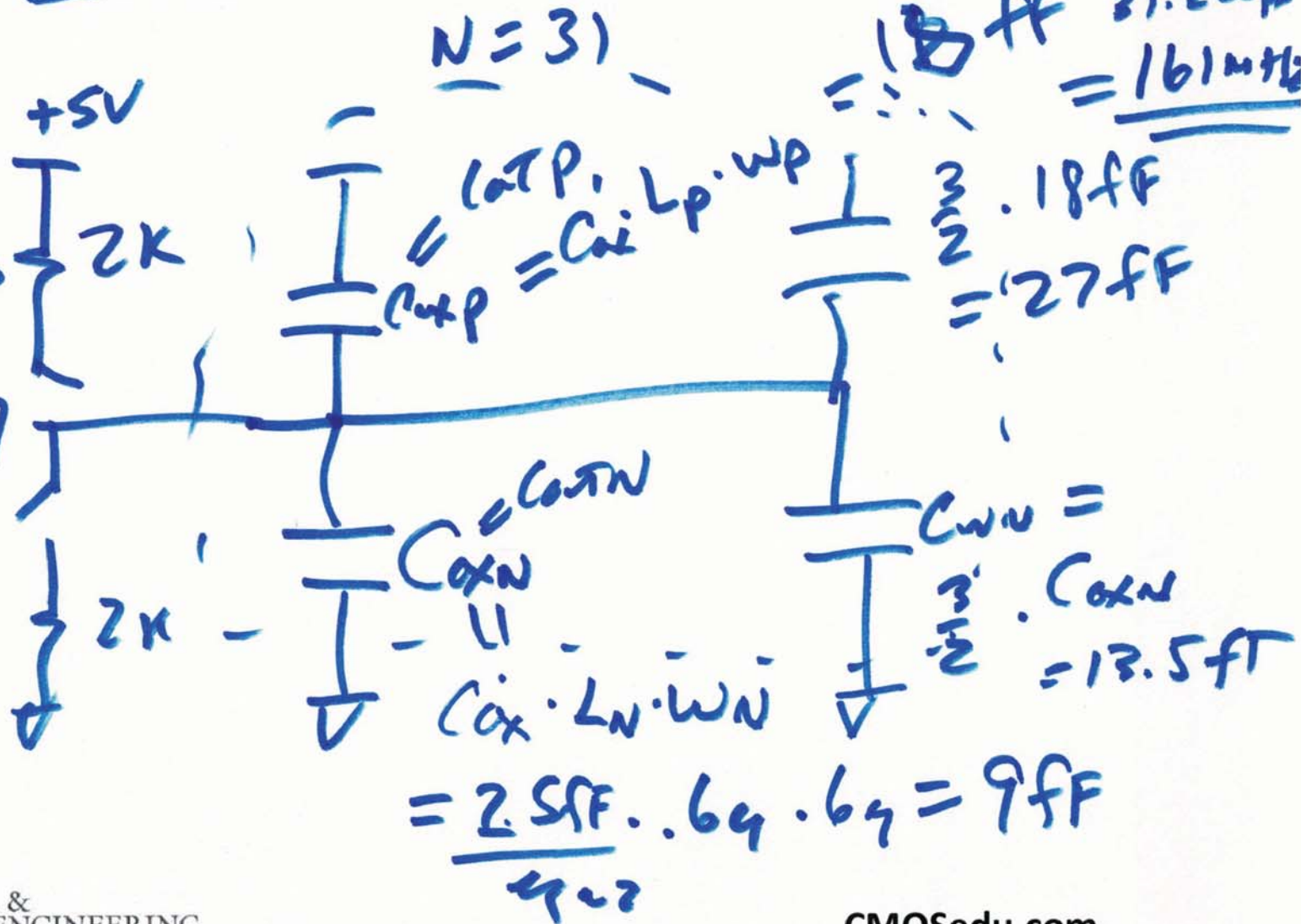$t_{PHL} = t_{PLH}$
 $= 0.7$
 $= 2k \cdot 67.5fs$
 $= 135ps \cdot 0.7$
 $\approx 100ps$




2)

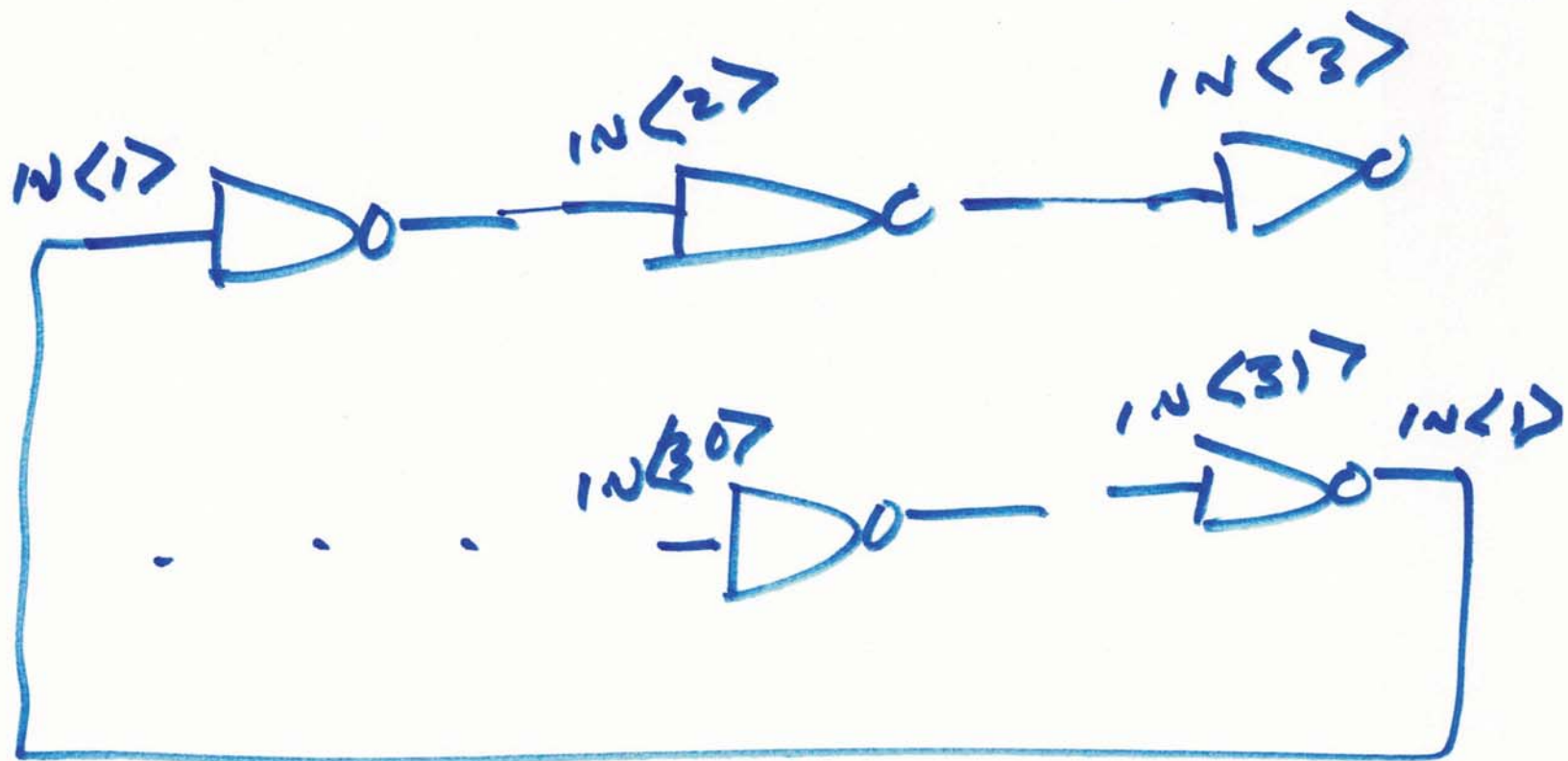

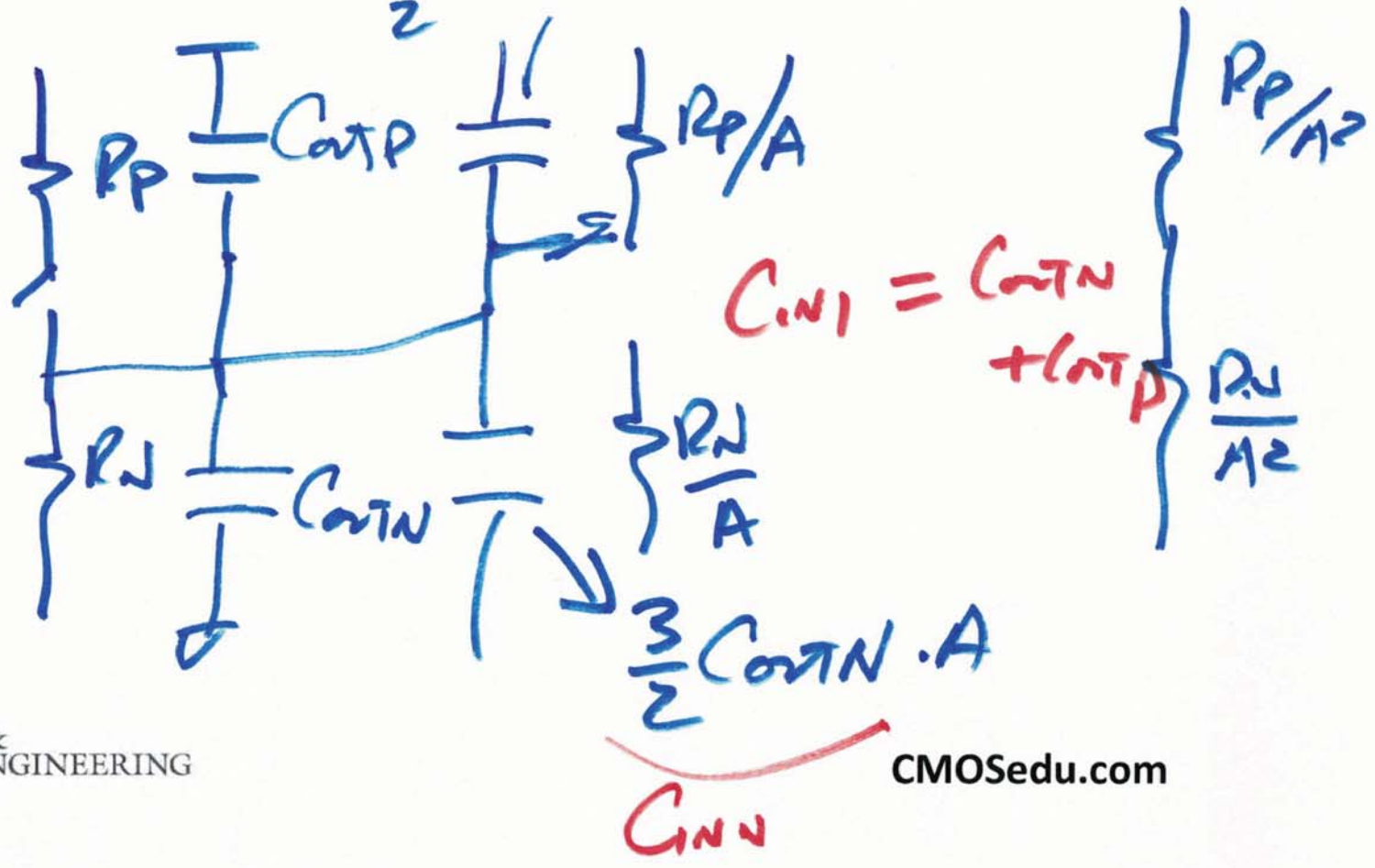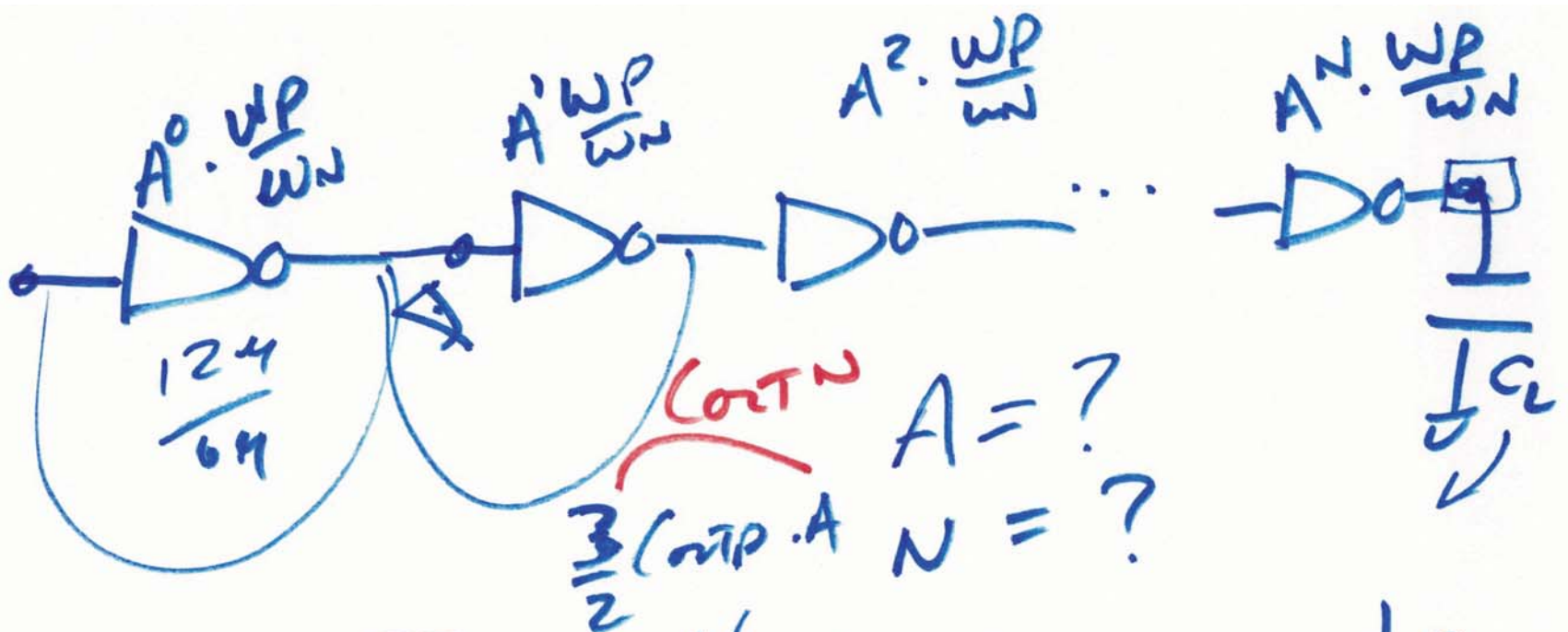

4)

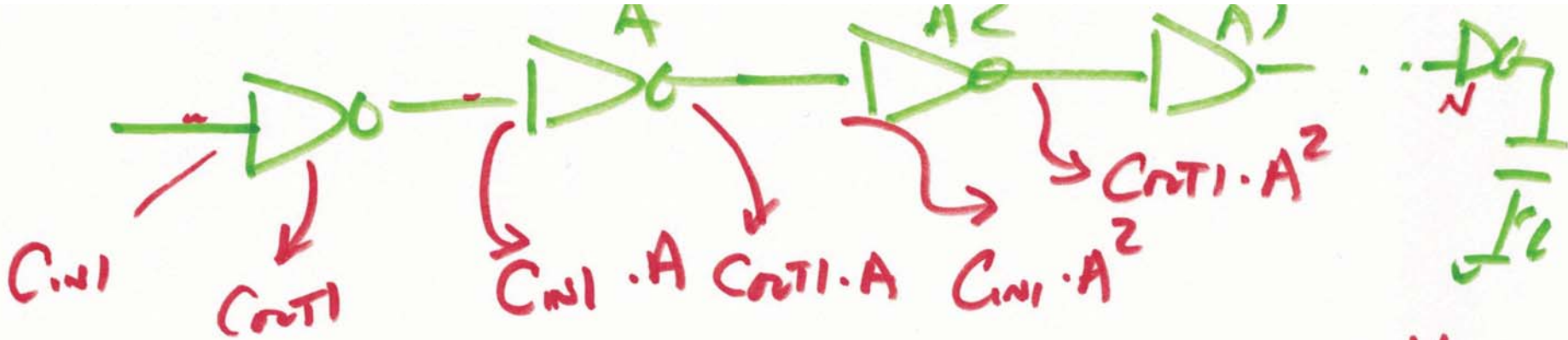

$$C_L = C_{in} A^N, \quad A = \left(\frac{C_L}{C_{in}} \right)^{1/N}$$

$$t_{PHL} + t_{PLH} = 0.7 \sum_{k=1}^N (\tau_{n1} + \tau_{p2}) (C_{out1} + A C_{in1})$$

$$N = \ln \frac{C_{load}}{C_{in1}}$$

$$\underline{\underline{A = e \Rightarrow 2.718}}$$

5)