

EE 421 / ECG 621


Lecture 13

OCT. 12, 2016

Digital IC Design

Midterm on Monday

Chs. 1-6

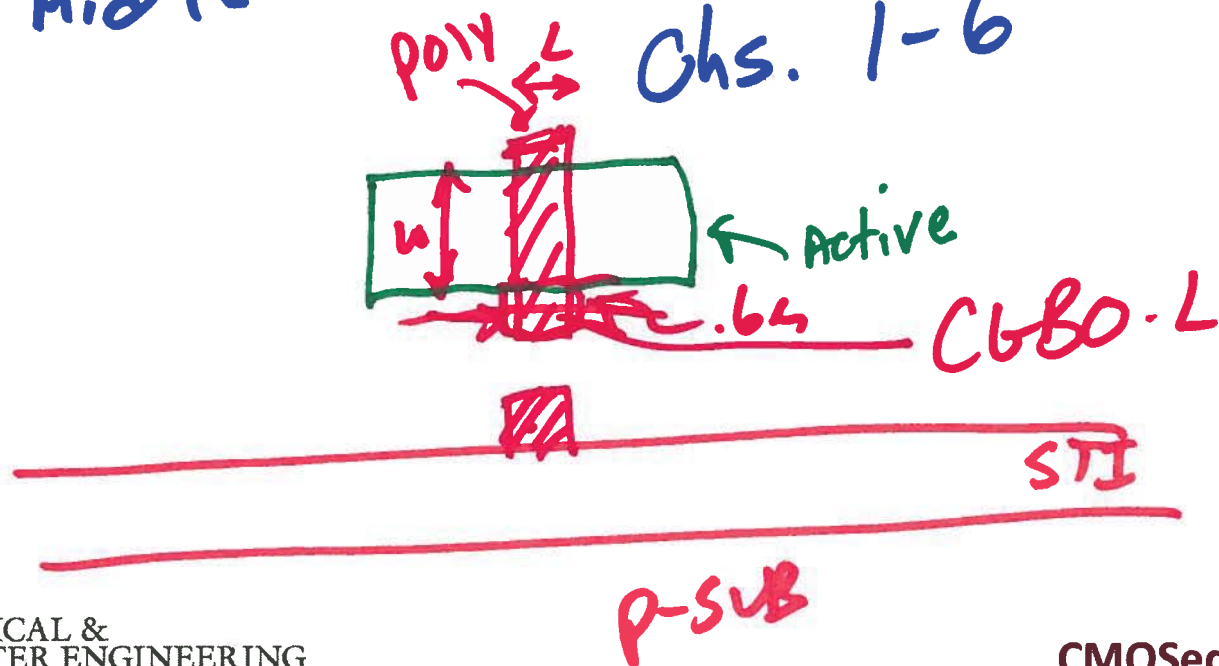

1)

$$Q'_I(y) = C'_{ox} (V_{GS} - V(y) - V_{THN})$$

$V_{GS} = V_{GS} - V_{THN} \quad Q'_I(y) = 0$




$$V_{DS, SAT} = V_{GS} - V_{THN}$$

$$V(0) = 0$$


$$V(L) = V_{DS}$$

QUIZZES
 H.W. problems (additional) → Also look
 the ones
 not assigned
 End chapter problems

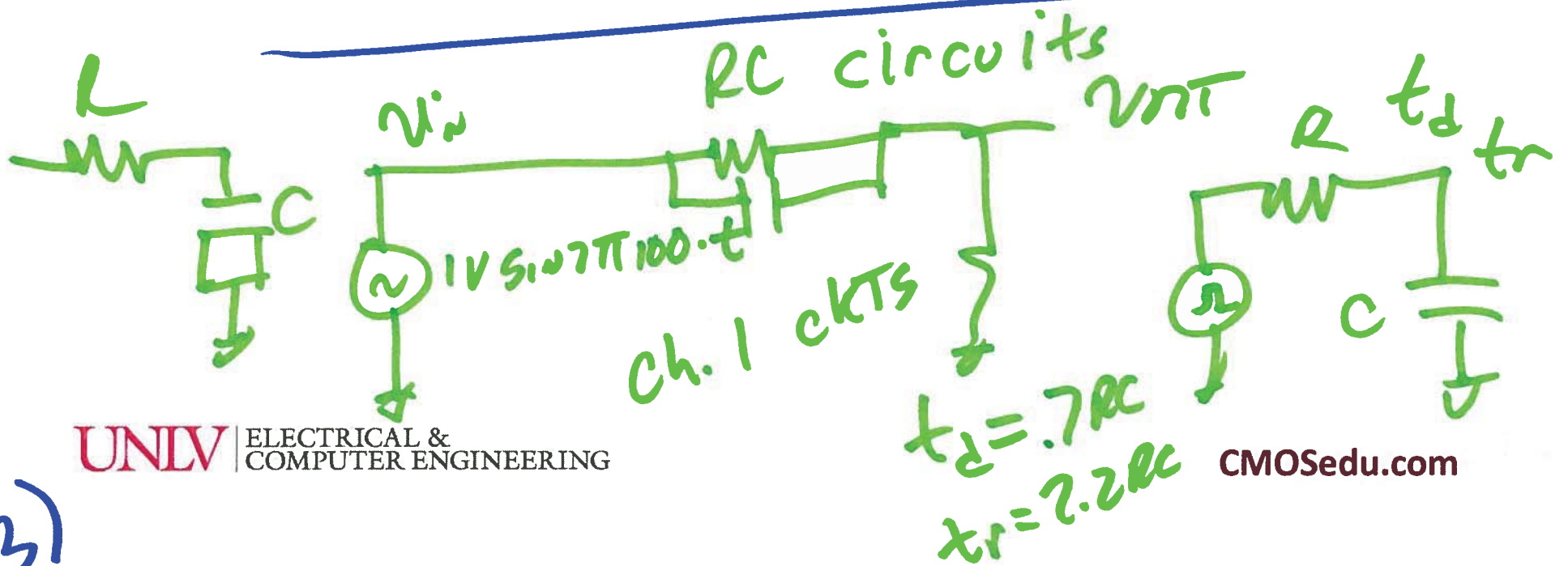Chs. 1-6
 Basic layout / PTAP / NPTAP / P-select / P-active / CC / Metal 1
 Unit cells



3)

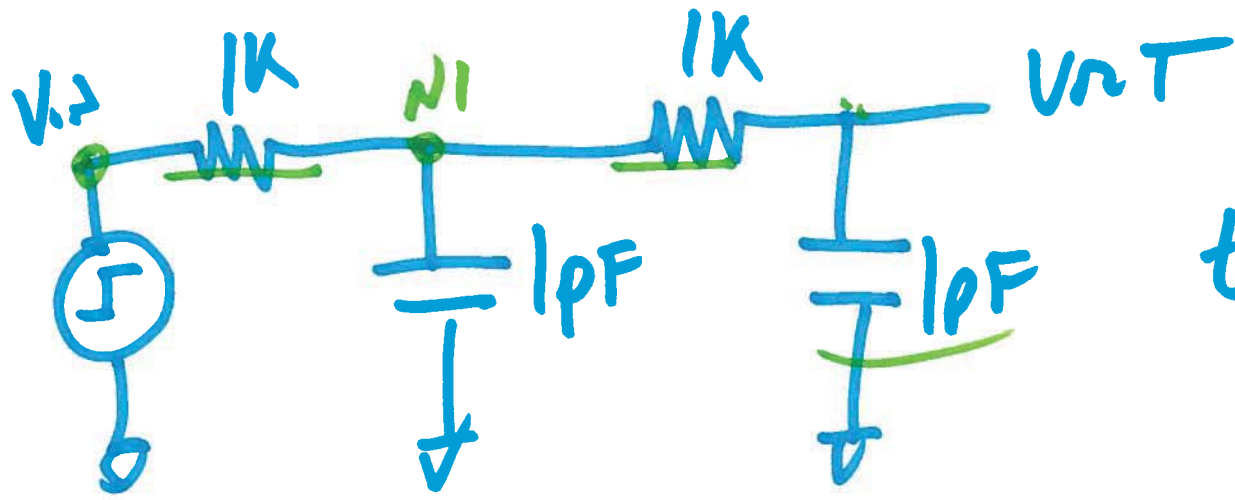


$$t_d = 0.35 \cdot 1k \cdot 1pF \cdot 2^2$$

$$0.35 \cdot 1k \cdot 2^2$$


$$t_d = \underbrace{0.7 \cdot 1k \cdot 1pF}_{V_{in} \rightarrow N1} + \underbrace{0.7 \cdot (1k + 1k) \cdot 1pF}_{V_{in} \rightarrow \text{output}}$$

$$= 0.7 \cdot 1pF \cdot (3k)$$

4)

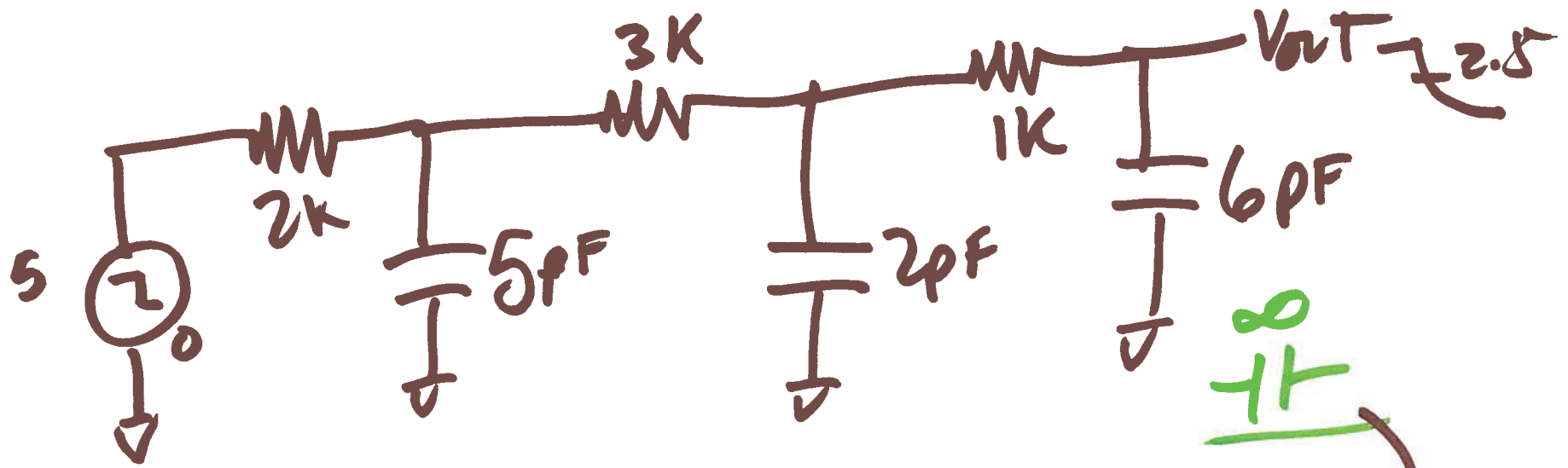
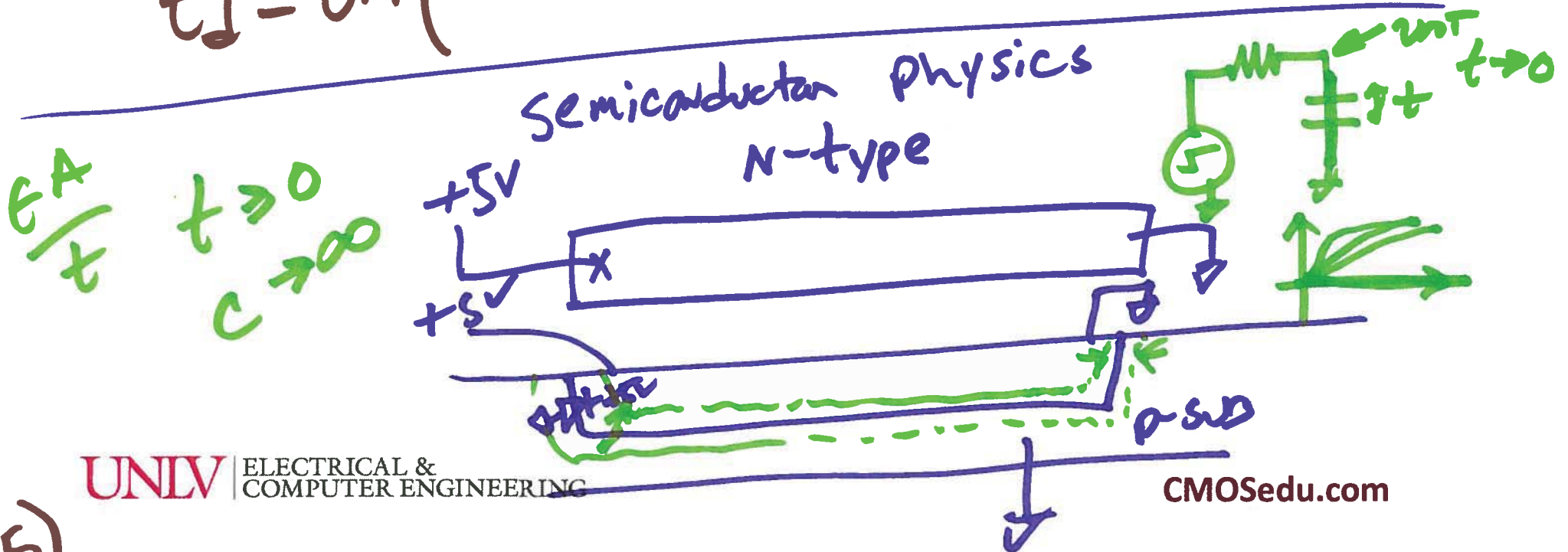
$$t_d = 0.7(2k \cdot 5pF + 5k \cdot 2pF + 6k \cdot 6pF)$$



5)


diode reverse recovery

Sheet resistance $\begin{cases} \text{N-well} \\ \text{poly} \\ \text{N+} \\ \text{metal 1} \end{cases}$

1,000 μm long piece of metal 1
0.9 μm wide. the sheet $R = 0.152/\square$
suppose it's loaded every $1\mu\text{m}$ with
a 1pF cap what is the delay through
the metal line?
calculate ~~trans~~ C values

67

Ground bounce
power supply

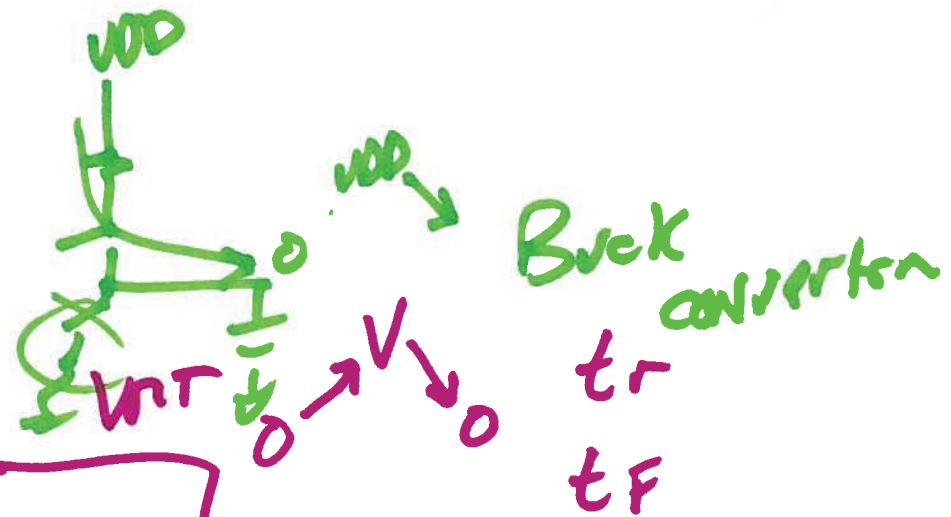


$$Q = CV$$

$$I_{avg} = \frac{Q}{T_{clk}}$$

$$P_{avg} = I_{avg} \cdot V$$

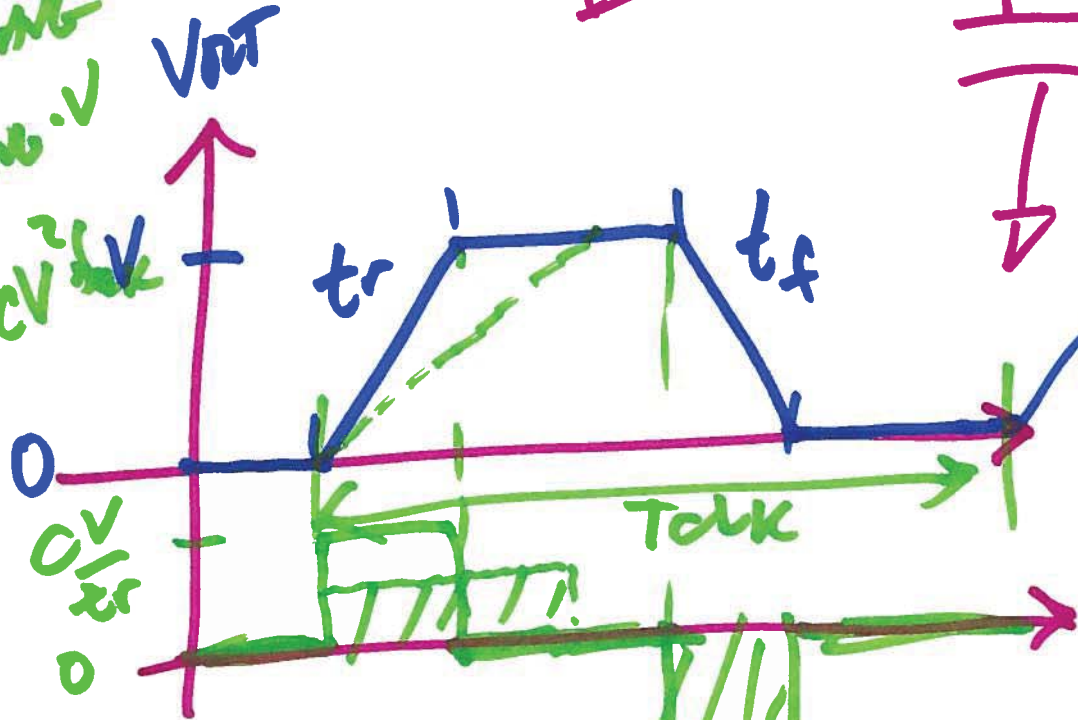
$$\frac{CV^2}{T_{clk}} = CV \frac{V}{T_{clk}}$$



$$I = C \frac{dV}{dt}$$

$$= C \cdot \frac{V}{tr}$$

$$-C \cdot \frac{V}{tf}$$

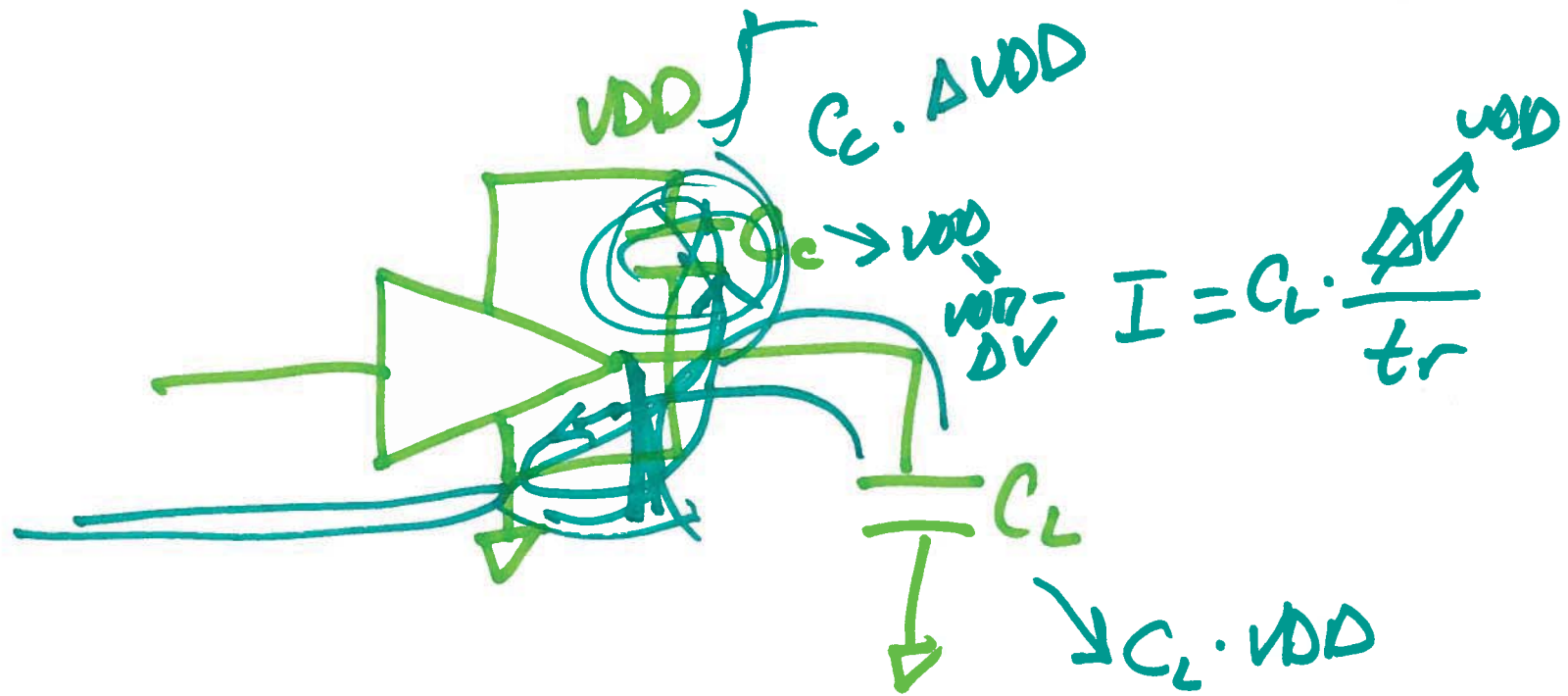

$$C_c \cdot \Delta V_{DD} = C_L \cdot V_{DD}$$

$$\Delta V_{DD} = \frac{C_L \cdot V_{DD}}{C_c}$$

$$C_c = \frac{C_L \cdot V_{DD}}{\Delta V_{DD}}$$