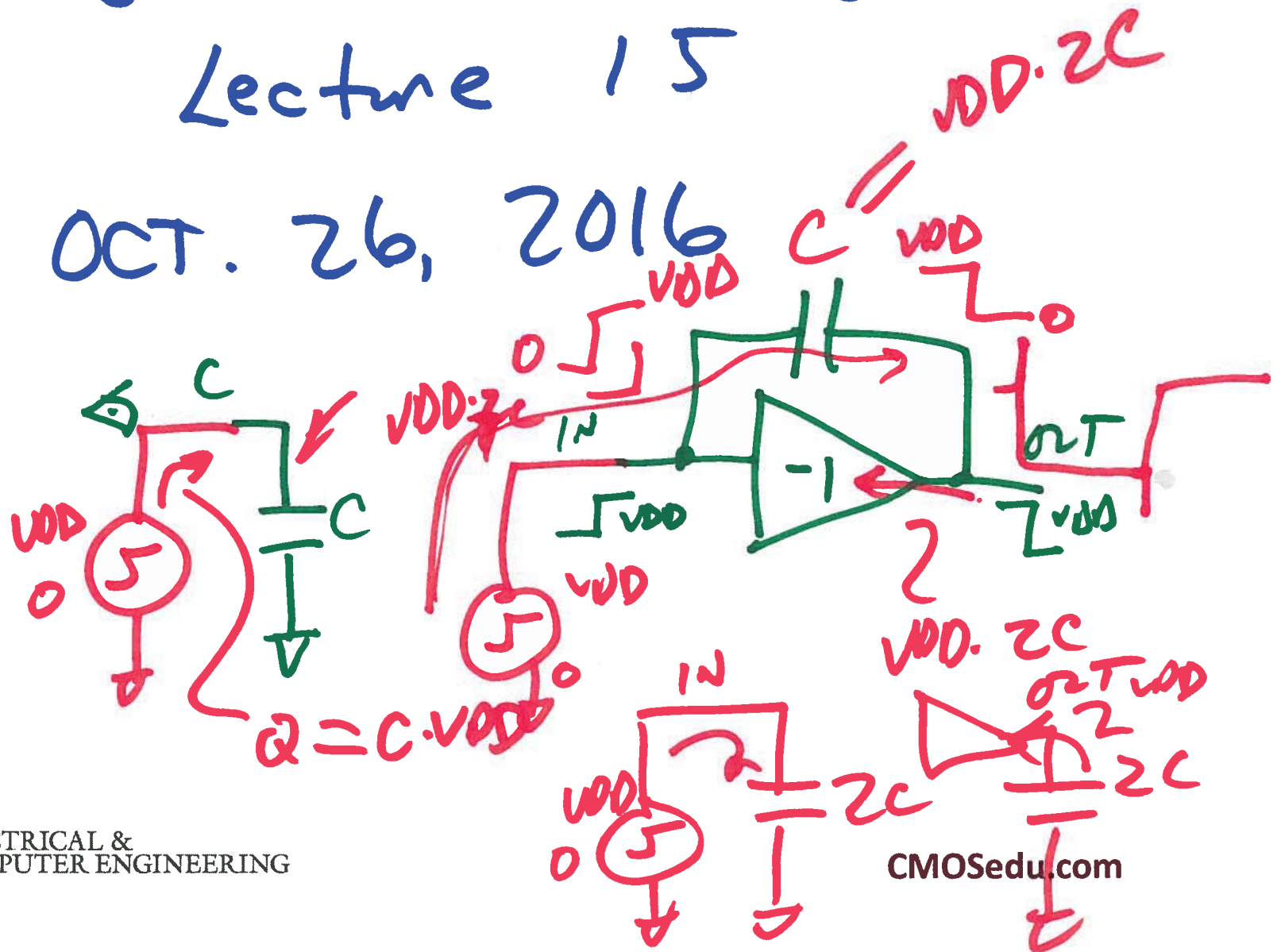


EE 421 / ECG 621


# Digital IC Design

## Lecture 15


OCT. 26, 2016



$$C V = Q$$

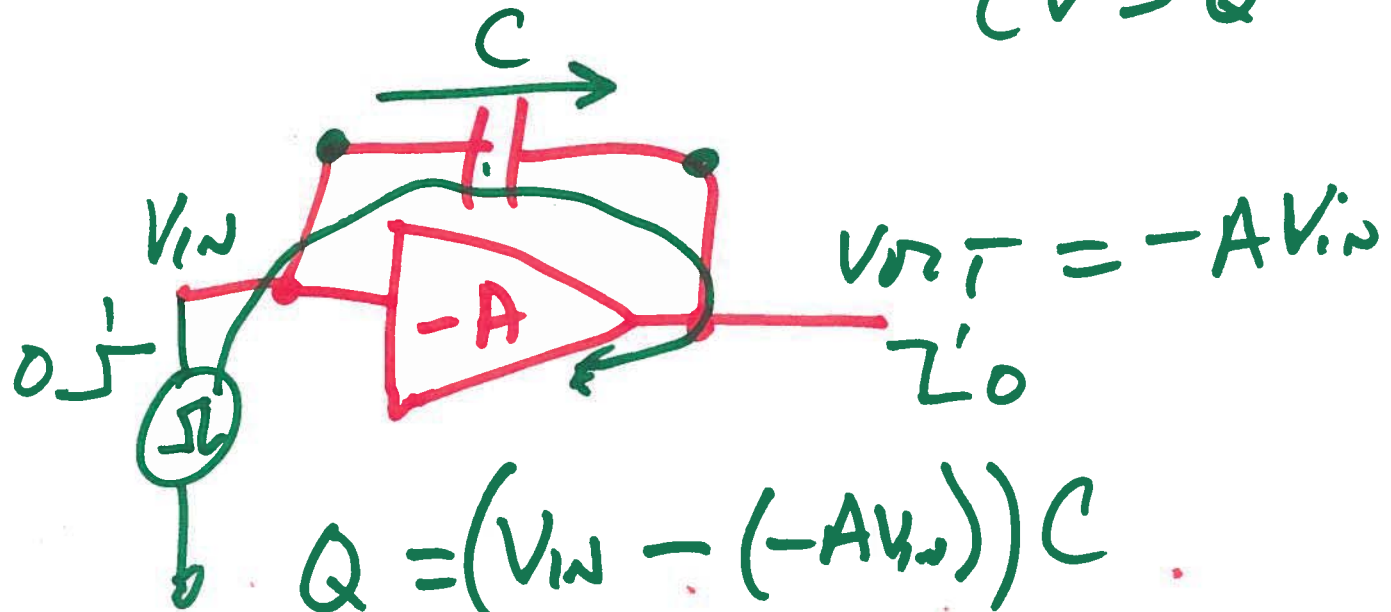


$$Q = (V_{in} - (-A V_{out})) C$$

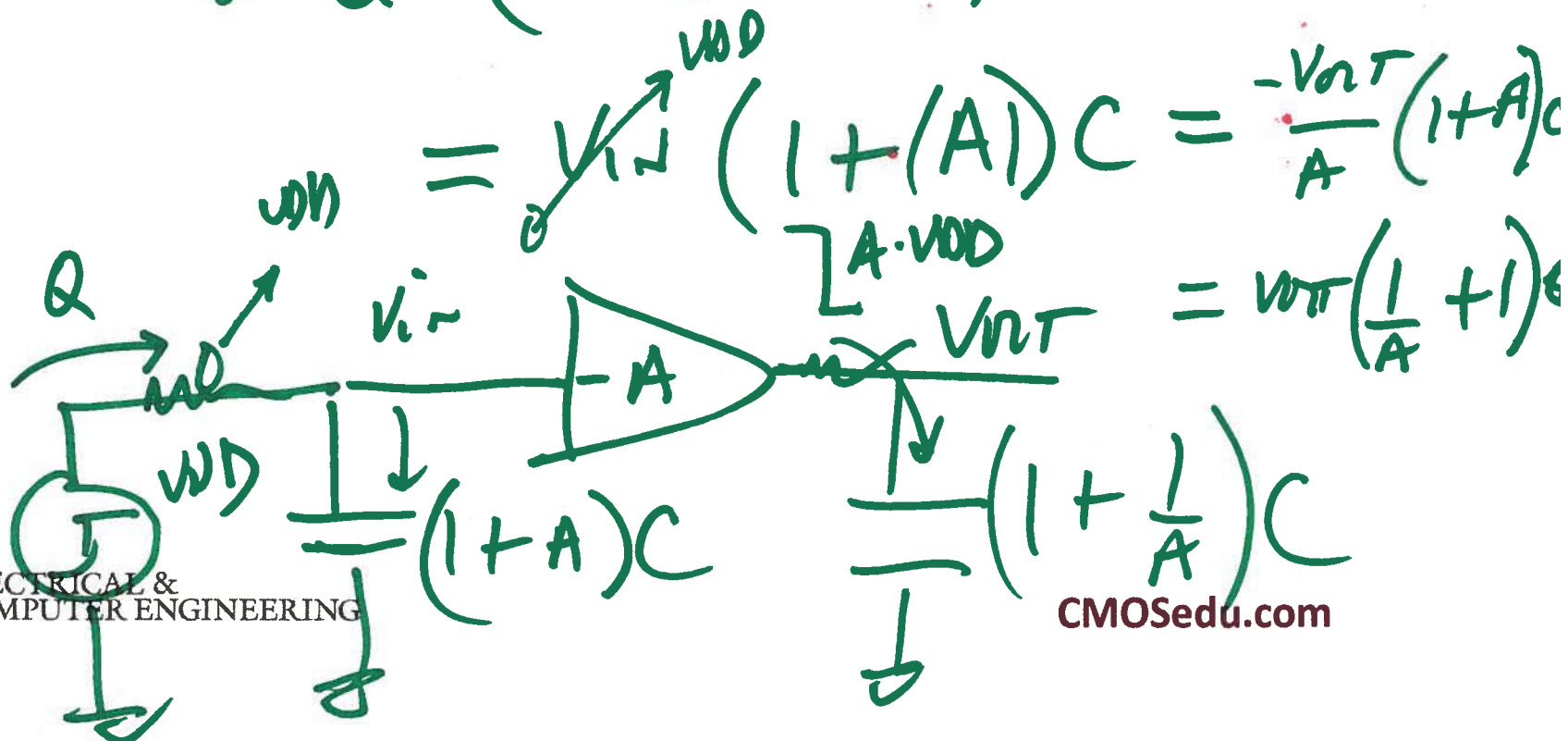


$$Q = V_{in} (1 + A) C = \frac{-V_{out}}{A} (1 + A) C$$

$$A \cdot V_{out} = V_{out} \left( \frac{1}{A} + 1 \right) C$$



2)

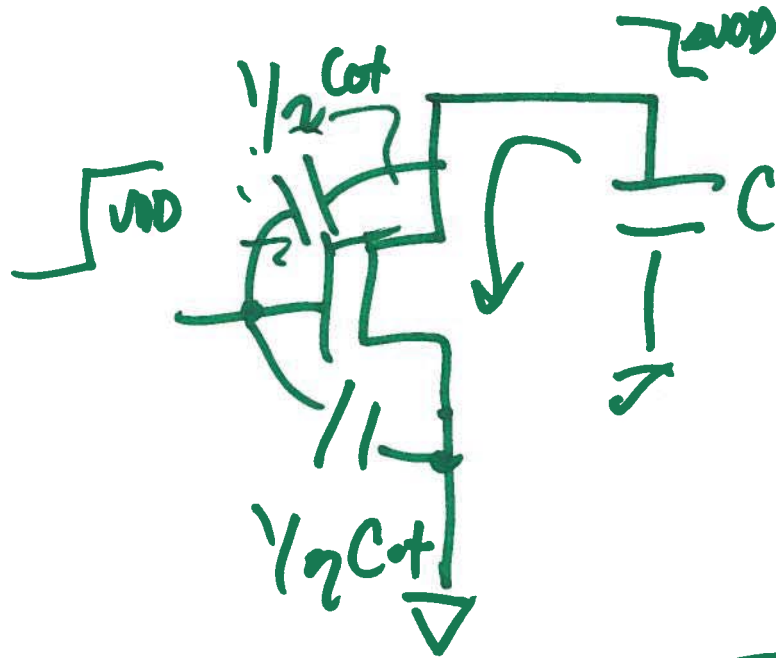

$$C_{ox} = C'_{ox} \cdot W \cdot L$$

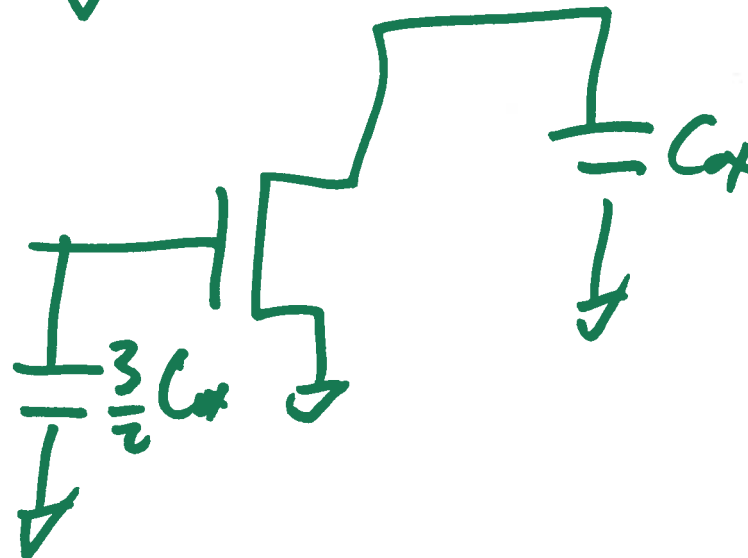

3)

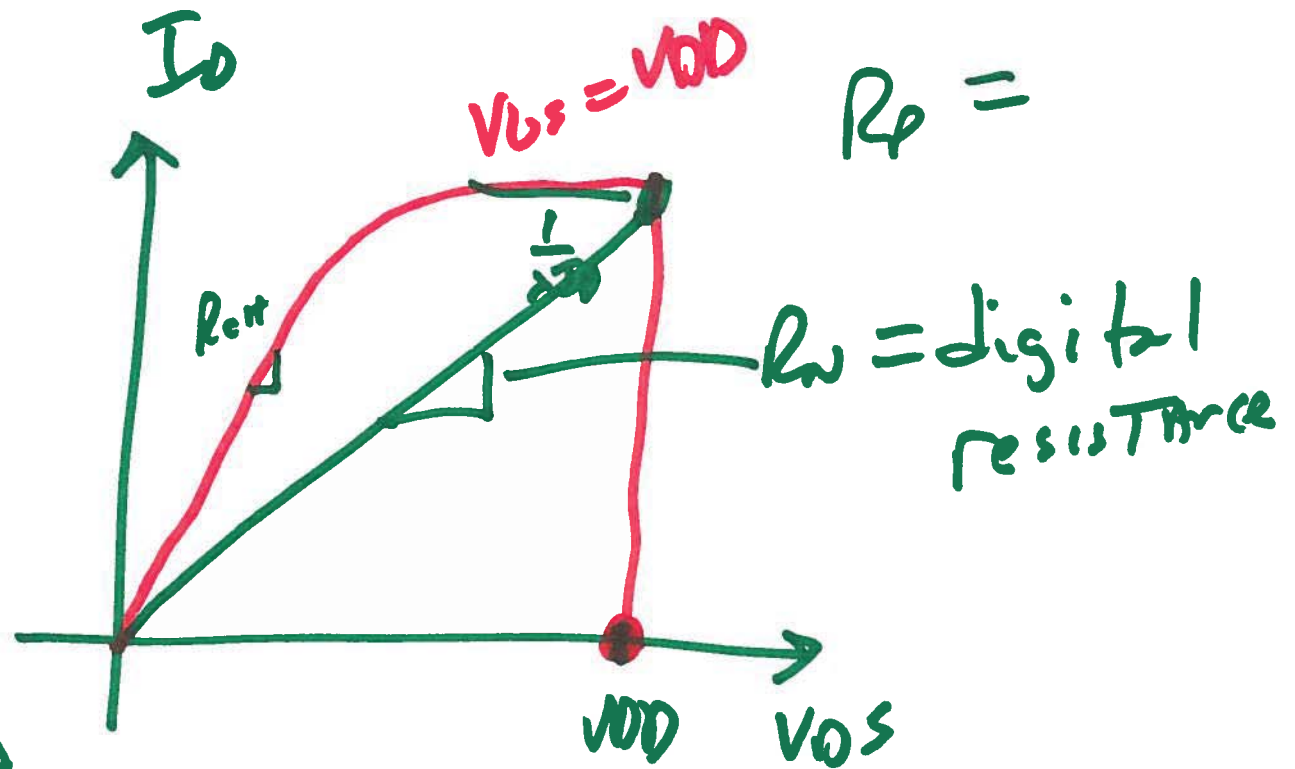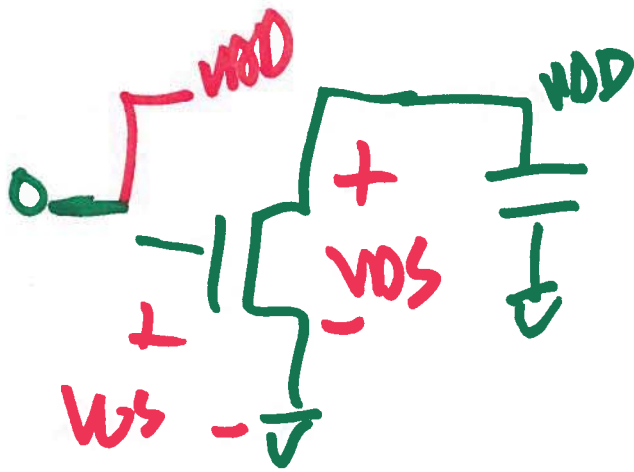


$$R_L = R_n' \cdot \frac{0.6}{6} = \frac{5}{2.5 \mu\text{A}}$$

$$R_n' = \frac{50}{2.5 \mu\text{A}} = 20 \text{ k}\Omega$$


$$\frac{V_{DD}}{I_D} = \frac{V_{DD}}{\frac{K_P \cdot W}{2 \cdot L} (V_{DD} - V_{TH})^2}$$

$$R_L = R_n' \cdot \frac{L}{W}$$

4)

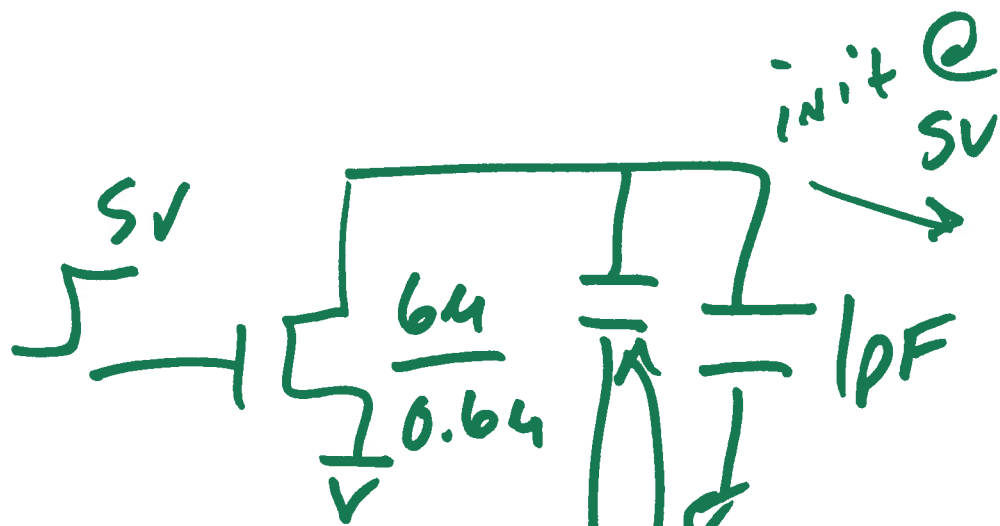

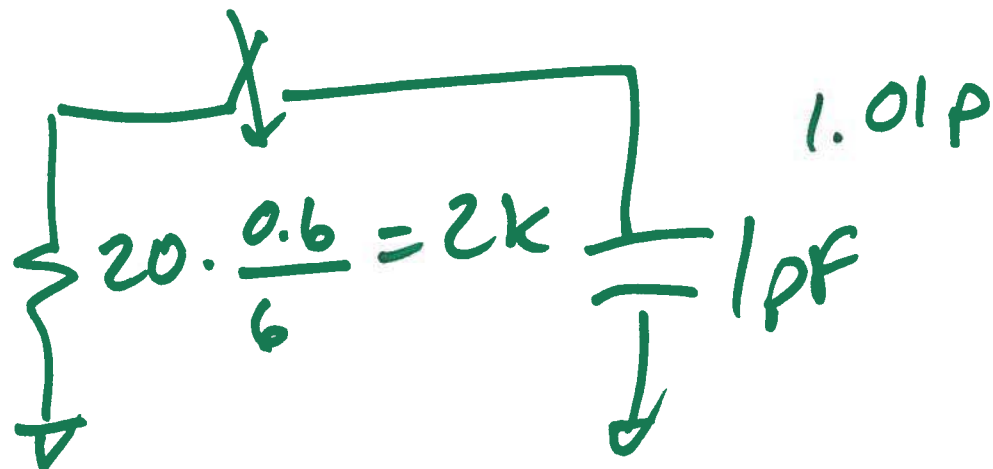
$2.5 \text{ fF}$   
 $\cdot 6 \cdot 6$   
 $3.6 \cdot 2.5$   
 $\text{fF}$   
 $\approx 10 \text{ fF}$




$$\tau = 2 \text{ ns}$$



$$t_d = 1.4 \text{ ns}$$

5)

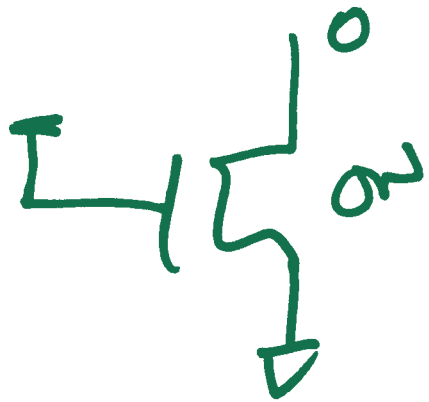


NMOS → passes a 0 well

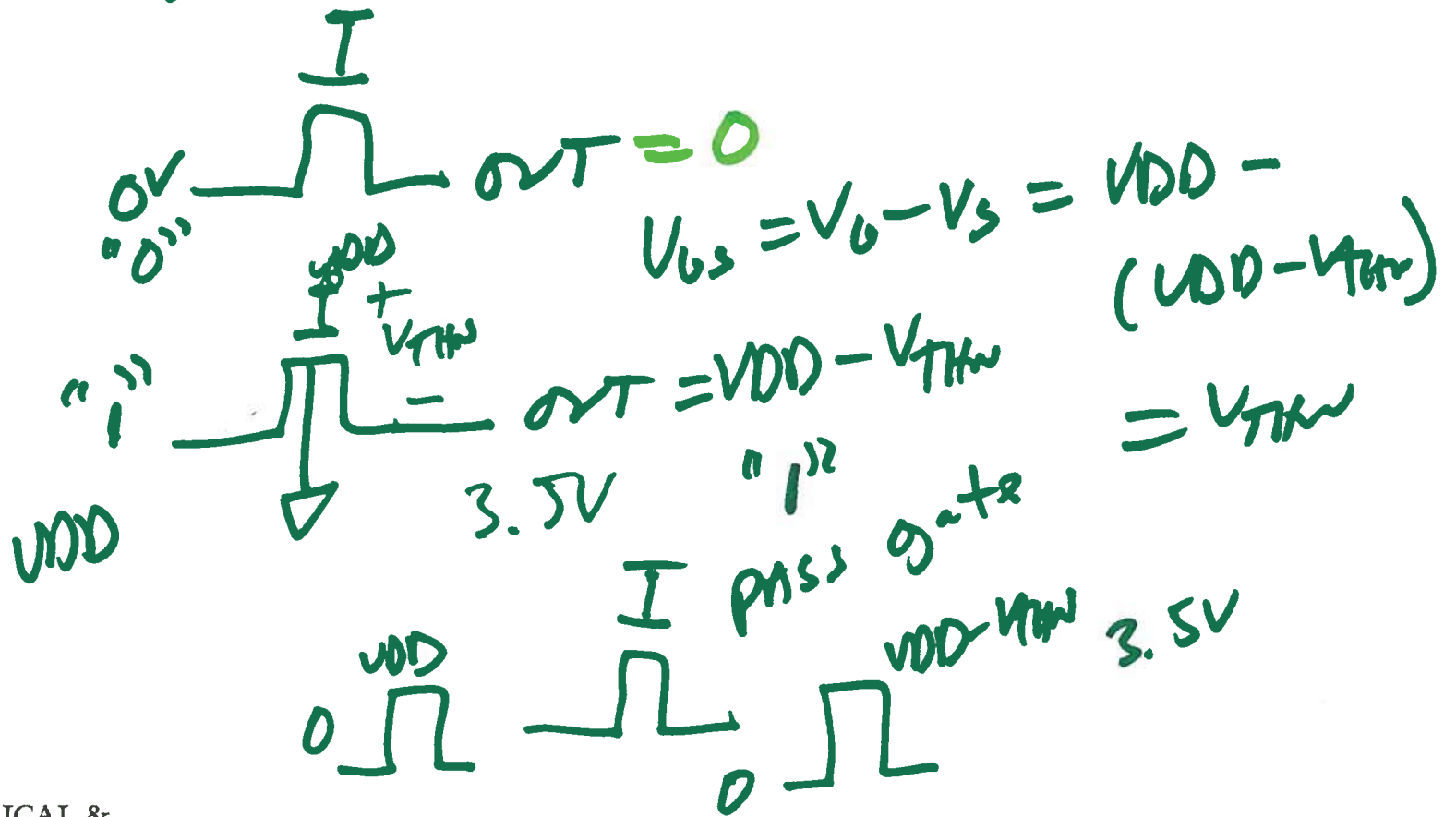

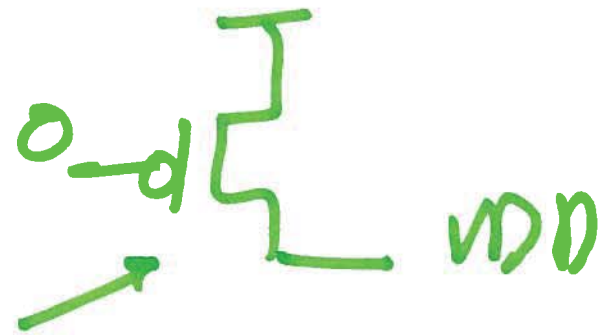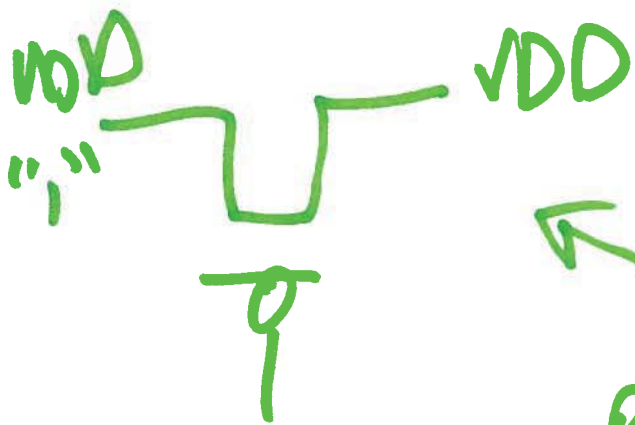



PASS gate

PMOS passes a 1 well

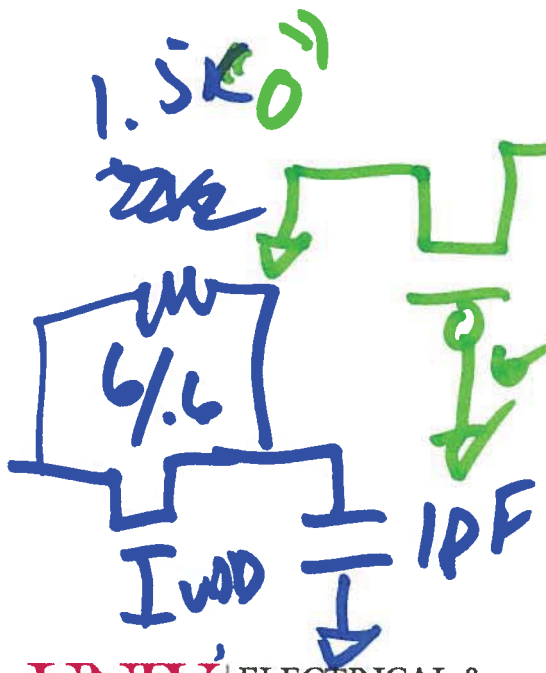


$OUT = V_{THP}$   
 $V_{SL} = V_{THP}$

$Z = A \cdot S + B \cdot \bar{S}$

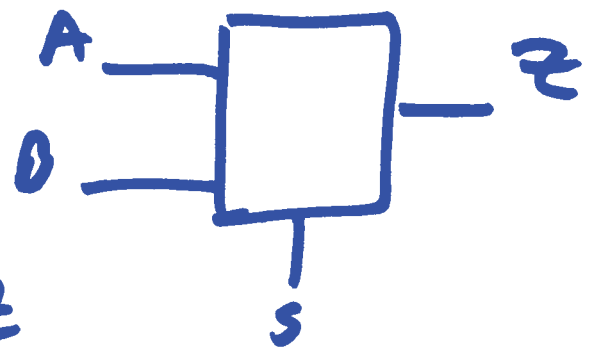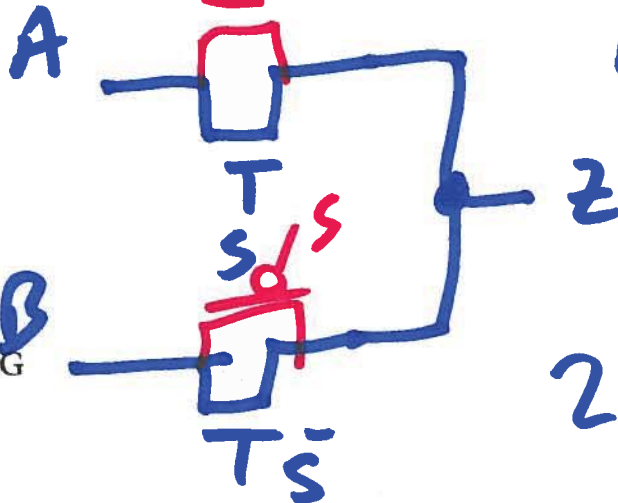

2 to 1 MUX

# Transmission GATE (TG)

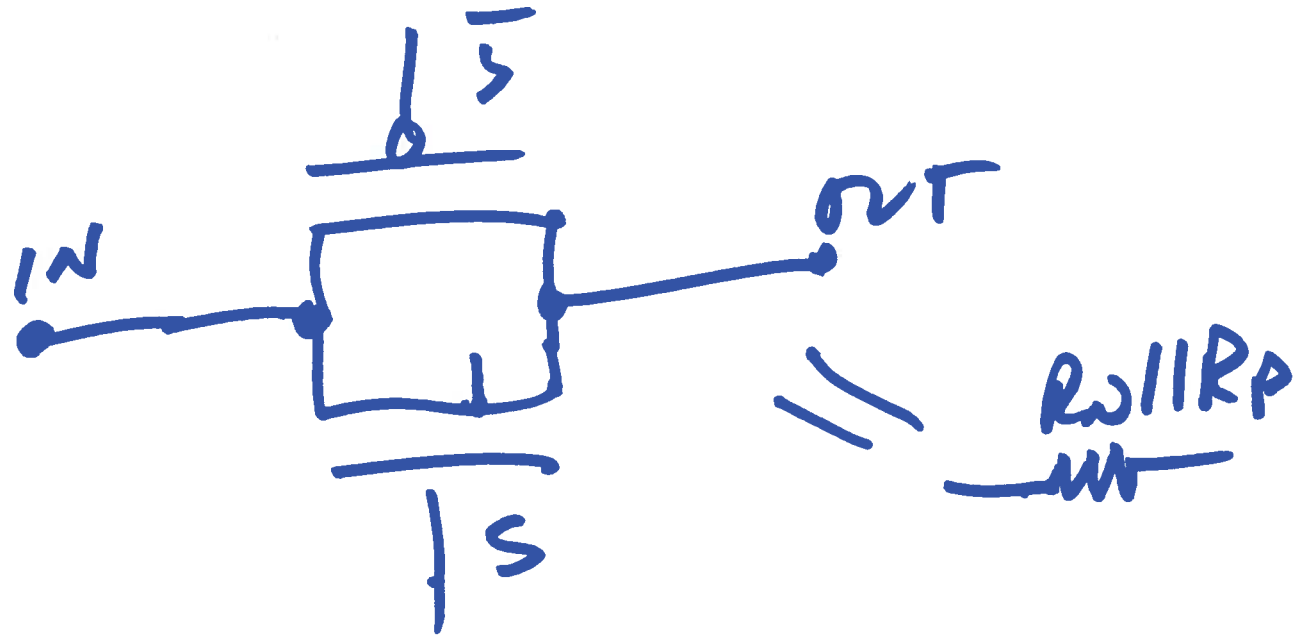

8)



Quiz 8 – EE 421/ECG 621 Digital Electronics and Digital IC Design, Fall 2016

NAME: KEY

Open book and notes.  
Show your work for credit!

- Below is the output filter and associated equations we derived in Lecture 14 for the Buck switching power supply. Assuming the inductor value remains at 625 uH how would the operation of the circuit change if the load current decreases to 1 mA? Increases to 100 mA? (hint: the frequency of the input has to change, change to what? Calculate it.) How does the duty cycle of the input change if the input swings from 0 to 5 and the output is 2.5 V. (5 points)


$$D = \frac{1}{2}$$

$$V_{out} = D \cdot V_{DD}$$

$$\frac{V_{DD} - V_{out}}{L} = \frac{I_{max} - I_{in}}{DT}$$

$$\frac{0 - V_{out}}{L} = \frac{I_{max} - I_{in}}{(1-D)T}$$

$$I_{avg} = \frac{I_{max} + I_{in}}{2}$$

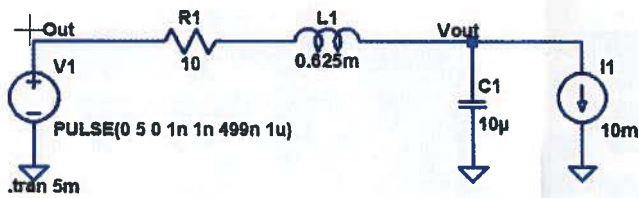

for 100uA  
Assume  $\rightarrow$  if

$$I_{max} = 110\mu A \quad \& \quad I_{min} = 90\mu A$$

$$\text{Then } T = \frac{625\mu \cdot 20\mu A}{2.5V \cdot \frac{1}{2}} = 104s, \quad \underline{\underline{f = 100kHz}}$$

for 1mA  
Assume  $\rightarrow$  if

$$I_{max} = 1.1mA \quad \& \quad I_{min} = 0.9mA$$

$$\text{Then } T = \frac{625\mu \cdot 0.2\mu A}{2.5V \cdot \frac{1}{2}} = 100ns$$

$$\underline{\underline{f = 10MHz}}$$

Duty cycle doesn't change. Stays  $\frac{1}{2}$