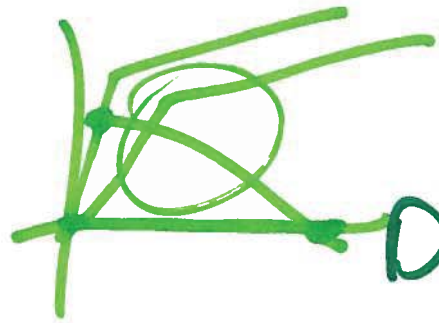


Lecture 16



EE 421 / ECE 621

Digital IC Design

$$R_p = R_p' \cdot \frac{L}{W}$$



180H/0.64
10/31/16

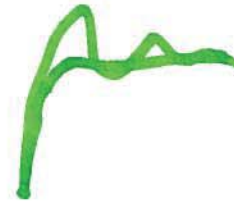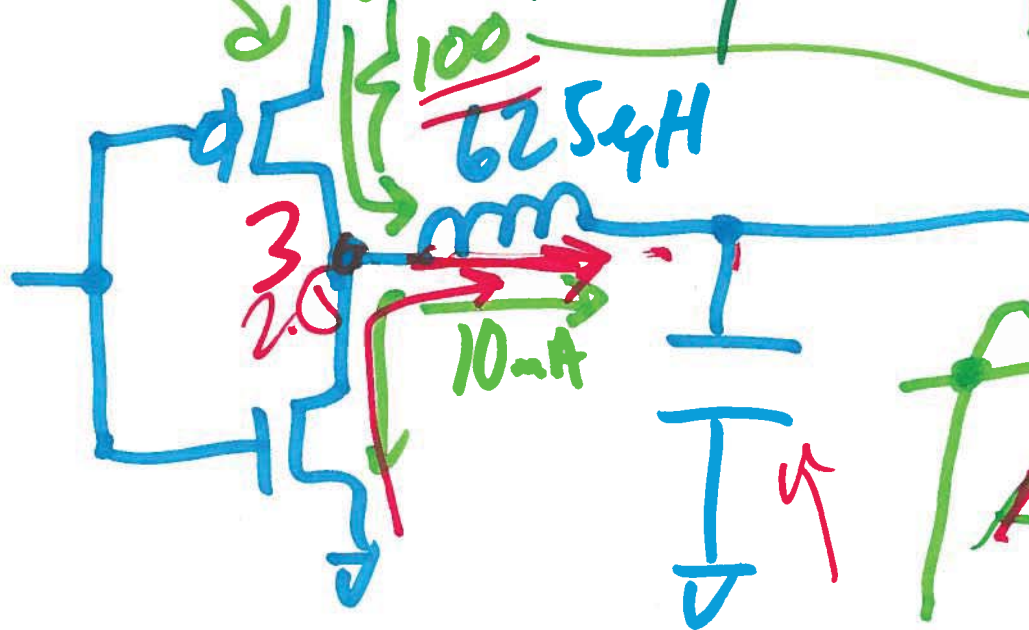


$$R_p' = 30k$$


$$100 = 30k \cdot \frac{L}{W} \quad 0.64$$

$$W = \frac{30k \cdot 0.64}{100}$$

$$= 300 \cdot 0.64 = 180$$

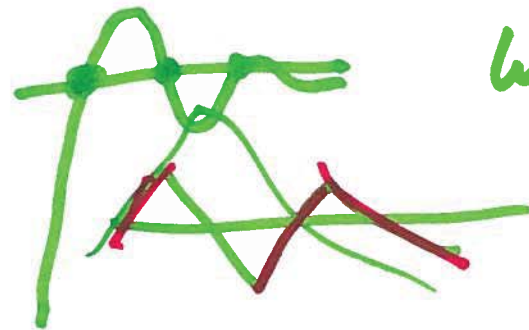

11)

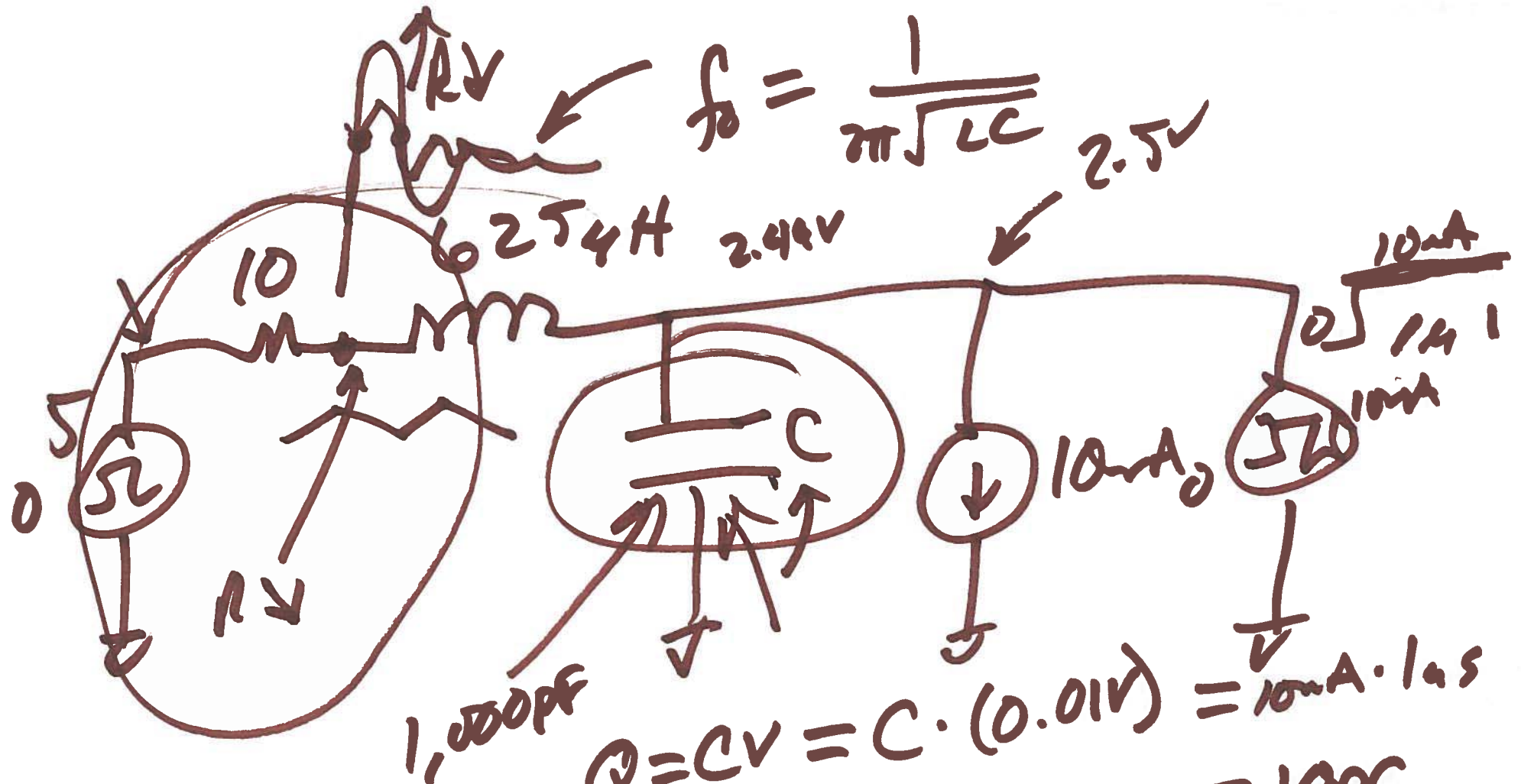

$$f_0 = \frac{1}{\pi \sqrt{LC}}$$


1,000 pF

$$Q = CV = C \cdot (0.01V) = 10nA \cdot 1ns = 10pC$$


$$10nA \cdot t_r$$

$$C = \frac{10pC}{0.01} = 1000pF$$

2)

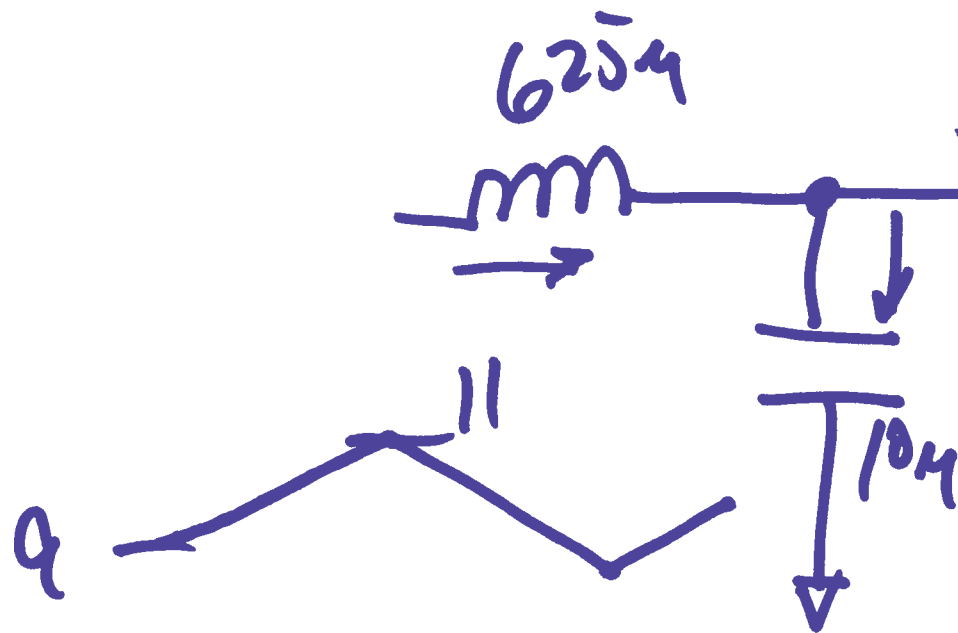

2500.05
2.49995

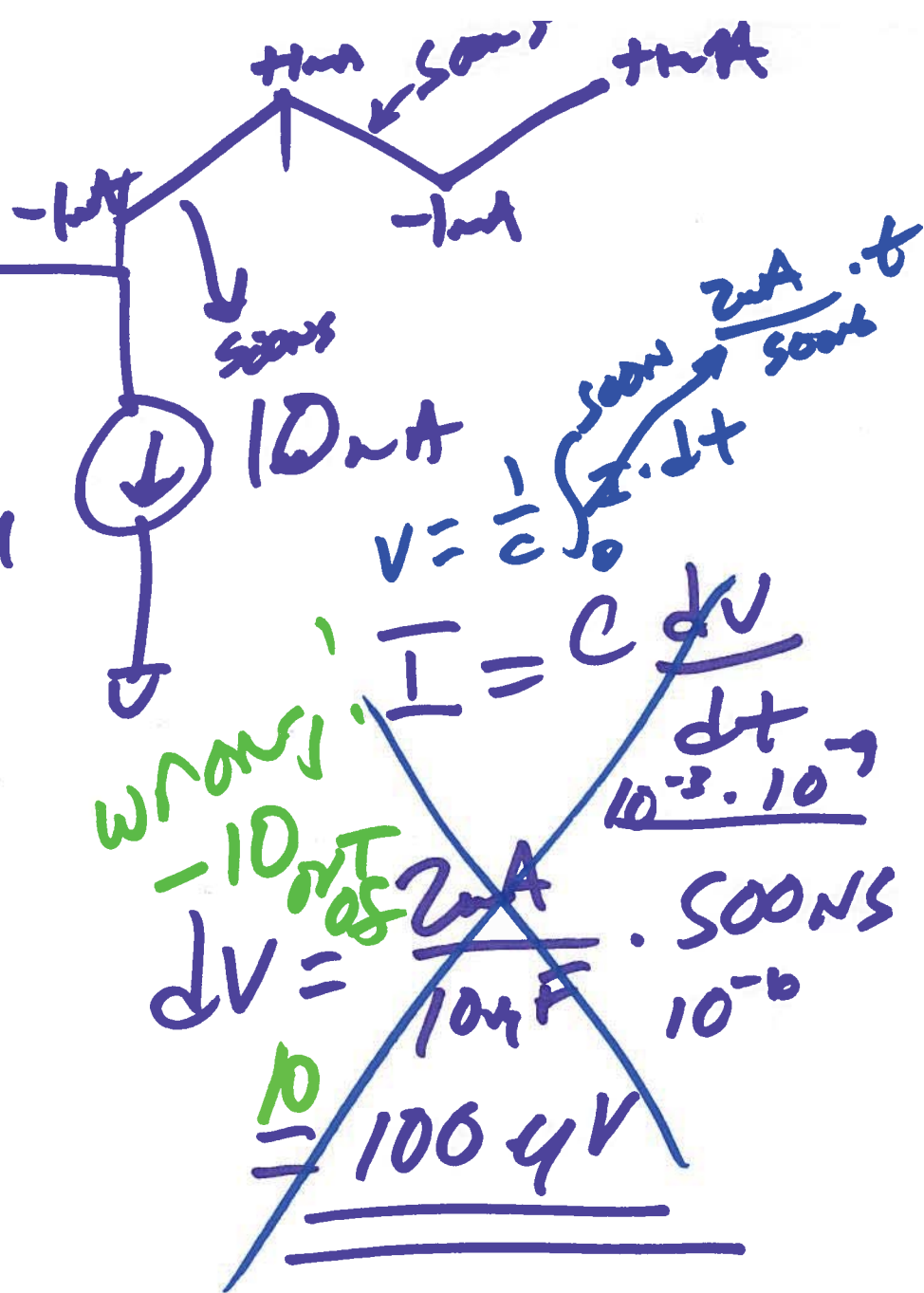



3)

$$\Delta V = \frac{L}{10\mu} \int_0^{500\text{ns}} \frac{2\mu\text{A}}{500\text{ns}} \cdot t \cdot dt$$



$$\frac{1}{10\mu} \cdot \frac{2\mu\text{A}}{500\text{ns}} \left(\frac{t^2}{2} \right) \Big|_0^{500\text{ns}}$$

$$\Delta V = \frac{1}{10\mu} \cdot \frac{2\mu\text{A} \cdot 500\text{ns}}{2}$$
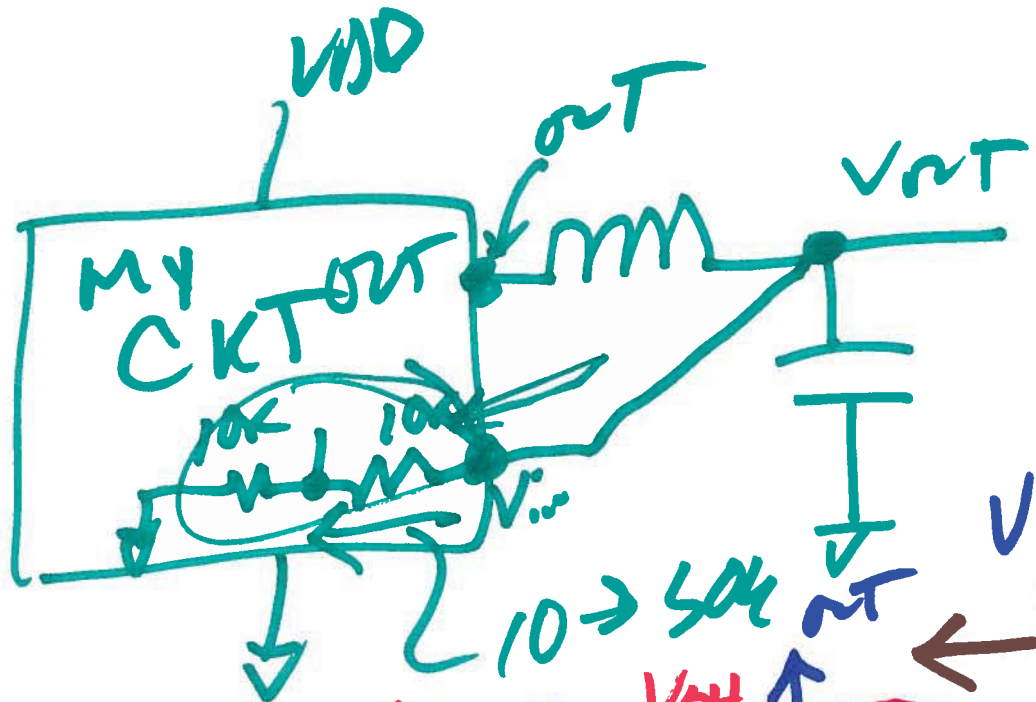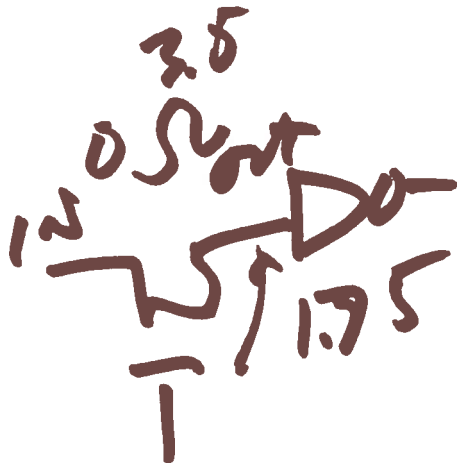
$$= \frac{500\text{p}}{10\mu} = \underline{\underline{50\mu\text{V}}}$$



inverters

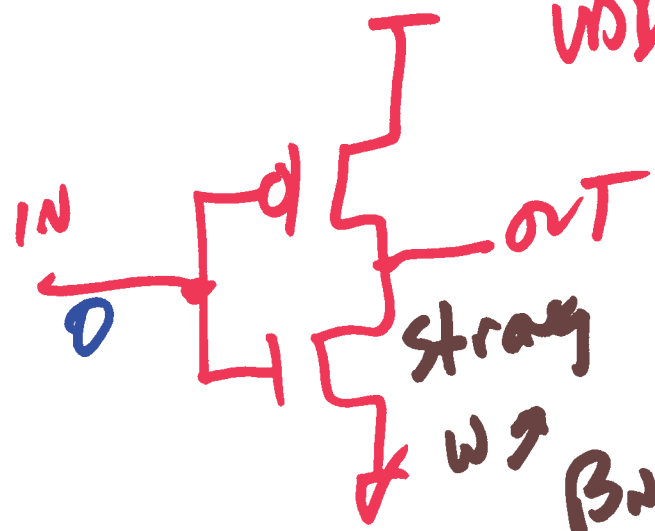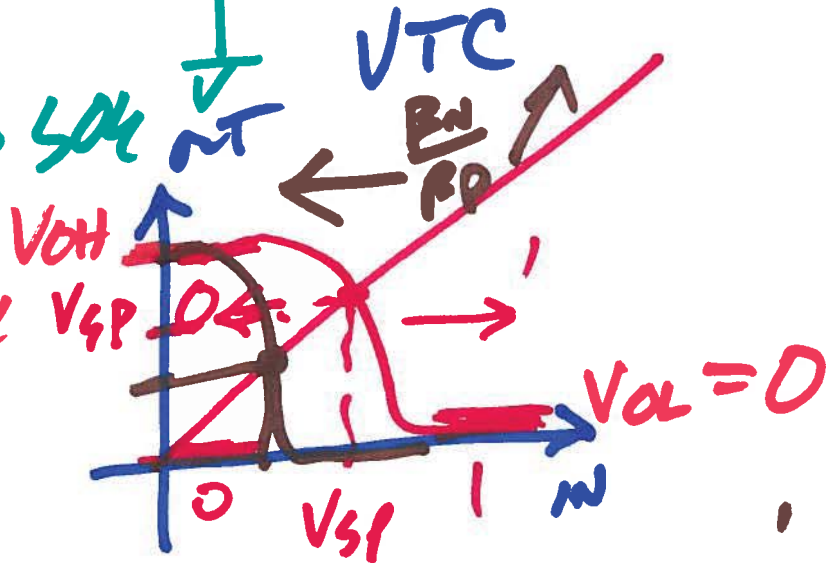

$$\beta_n = \frac{w}{L} \cdot K_P = \frac{w}{L} \mu_n \cdot C_{ox}$$

$$\sqrt{\frac{K_1}{\frac{K_{PN}}{2} \frac{W_{PN}}{L_{PN}}}} (V_{SP} - V_{THN}) = \sqrt{\frac{K_{PP} \cdot W_{PP}}{2 \cdot L_{PP}}} (V_{DD} - V_{SP} - V_{THP})$$


$$K_1 \cdot V_{SP} - K_1 \cdot V_{THN} = K_2 \cdot V_{DD} - K_2 V_{SP} - K_2 \cdot V_{THP}$$

$$V_{SP} (K_1 + K_2) = K_2 V_{DD} - K_2 V_{THP} + K_1 V_{THN}$$

$$\sqrt{\frac{K_{PP} \cdot W_{PP}}{2 \cdot L_{PP}}} (V_{DD} - V_{THP}) + \sqrt{\frac{K_{PN} \cdot W_{PN}}{2 \cdot L_{PN}}} \cdot V_{THN}$$

$$V_{SP} = \frac{\sqrt{\frac{K_{PP} \cdot W_{PP}}{2 \cdot L_{PP}}} (V_{DD} - V_{THP}) + \sqrt{\frac{K_{PN} \cdot W_{PN}}{2 \cdot L_{PN}}} \cdot V_{THN}}{\sqrt{\frac{K_{PN}}{2} \frac{W_{PN}}{L_{PN}}} + \sqrt{\frac{K_{PP} \cdot W_{PP}}{2 \cdot L_{PP}}}}$$

→

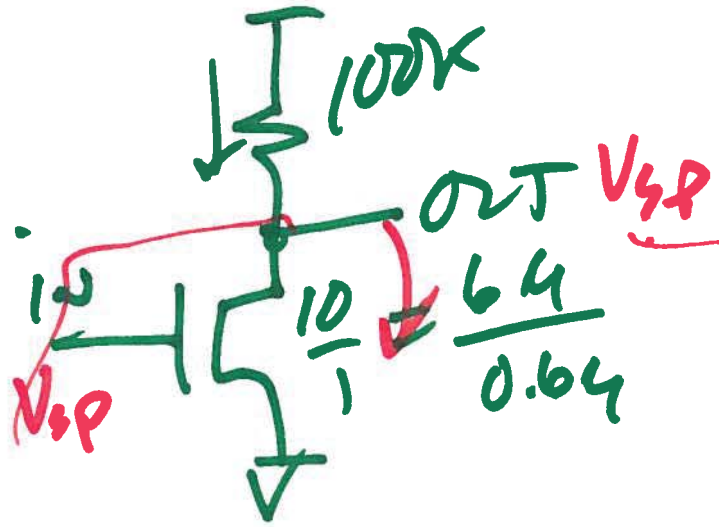

$$V_{OH} = V_{DD}$$

$$I_D = \frac{K_p \cdot C_{ox}}{2} (V_{GS} - V_{TH}) V_{SD}$$

$$\frac{V_{DD} - V_{SP}}{100\mu A} = \frac{1}{2} (V_{GS} - V_{TH}) V_{SD}$$

$$\frac{V_{DD} - V_{OL}}{100\mu A} =$$

$$K_p \cdot C_{ox} \cdot (V_{SP} - V_{TH}) V_{OL} \frac{W_n K_D}{L_n^2} (V_{SE} - V_{TH})^2$$

8)