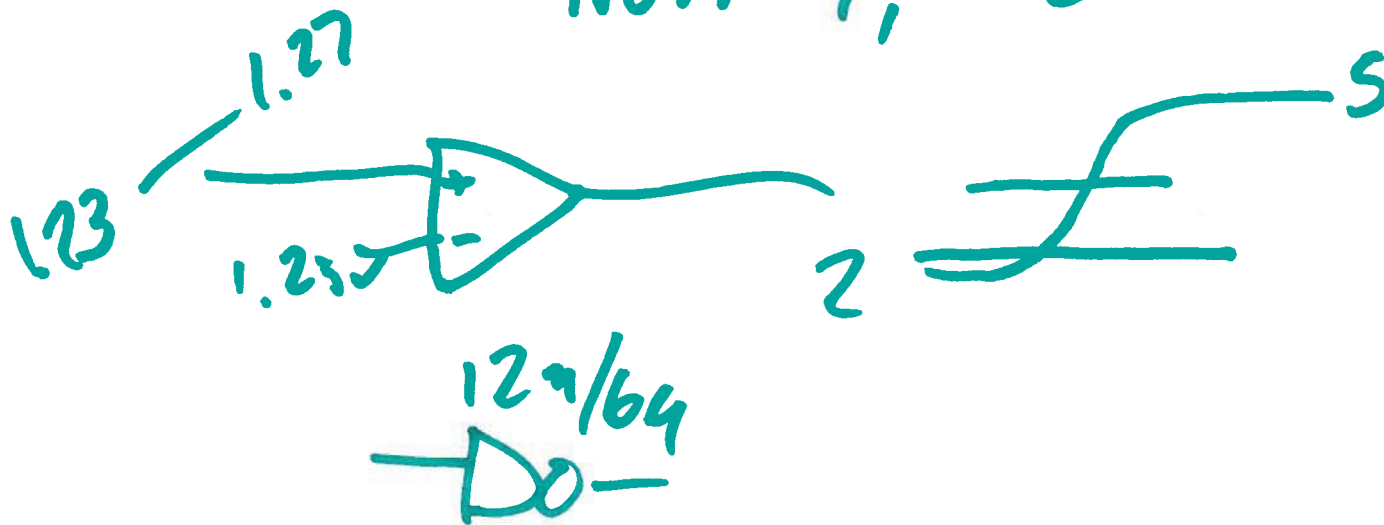




EE 421 / ECG 621

Digital IC Design

Lecture 18

NOV. 7, 2016



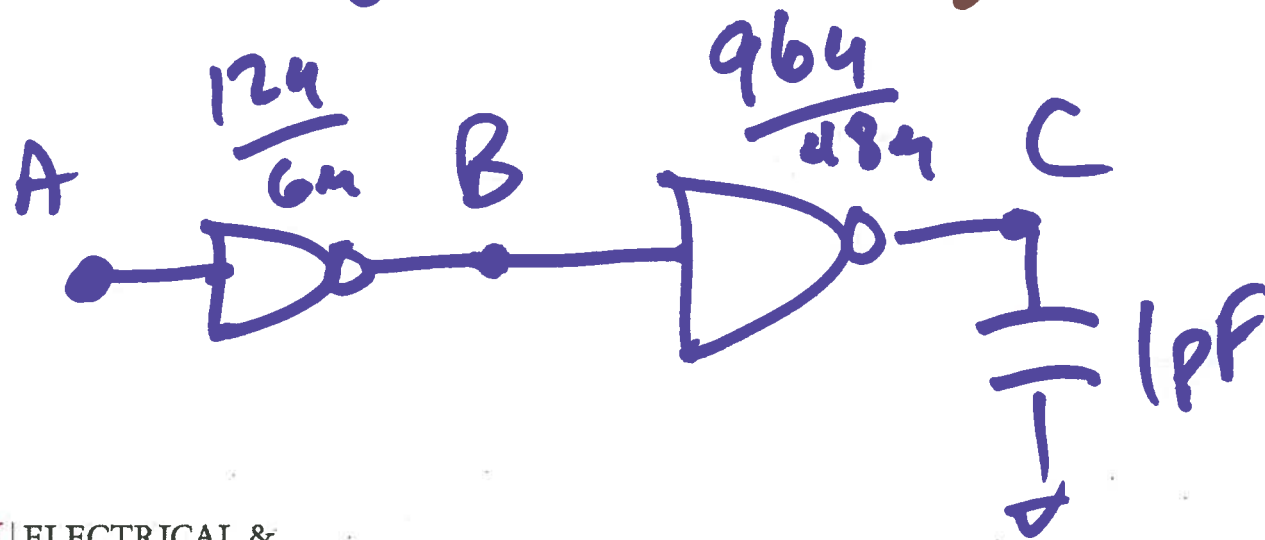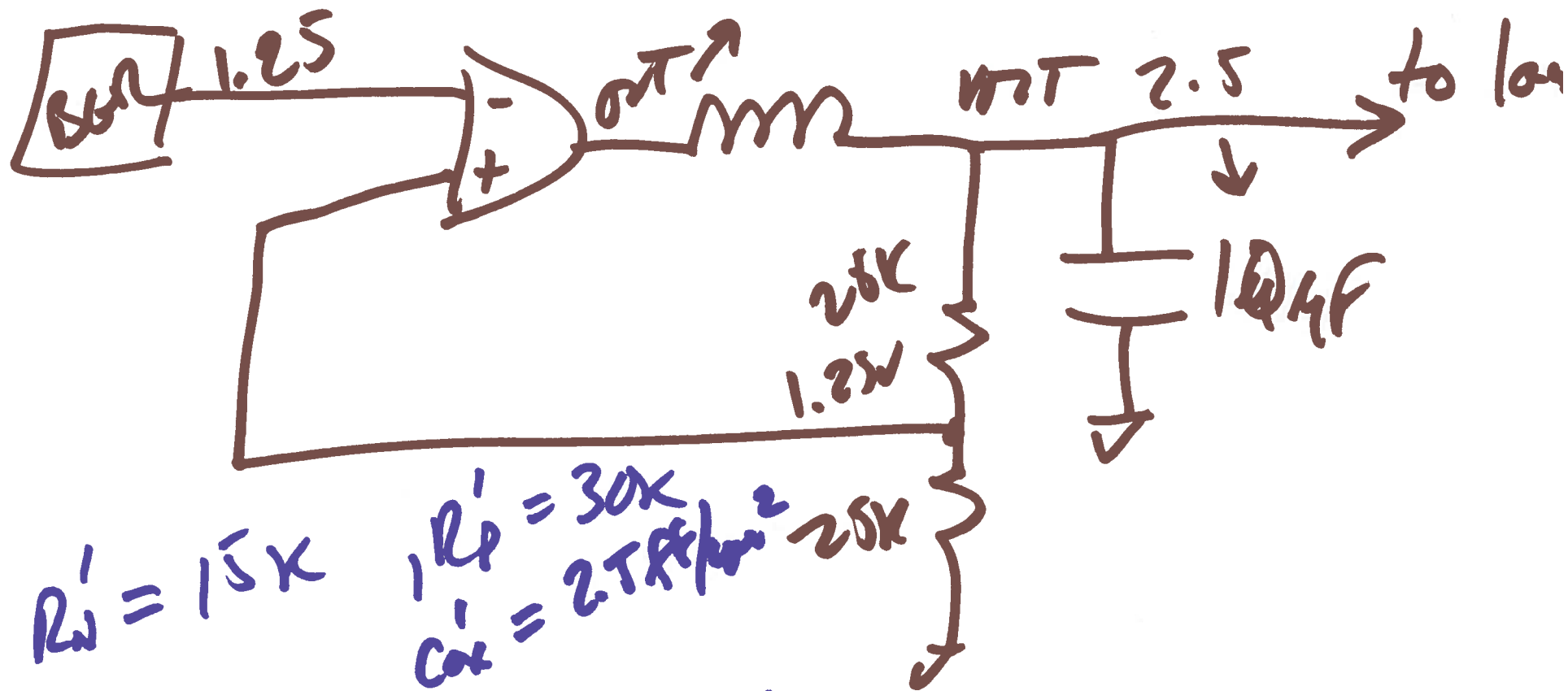




300pS

$$1k \cdot \frac{(25ff + 250ff)}{300ff} = 1.5k$$

$$15k \cdot \frac{0.6}{6} = 1.5k$$

$$30k \cdot \frac{0.6}{12} = 1.5k$$

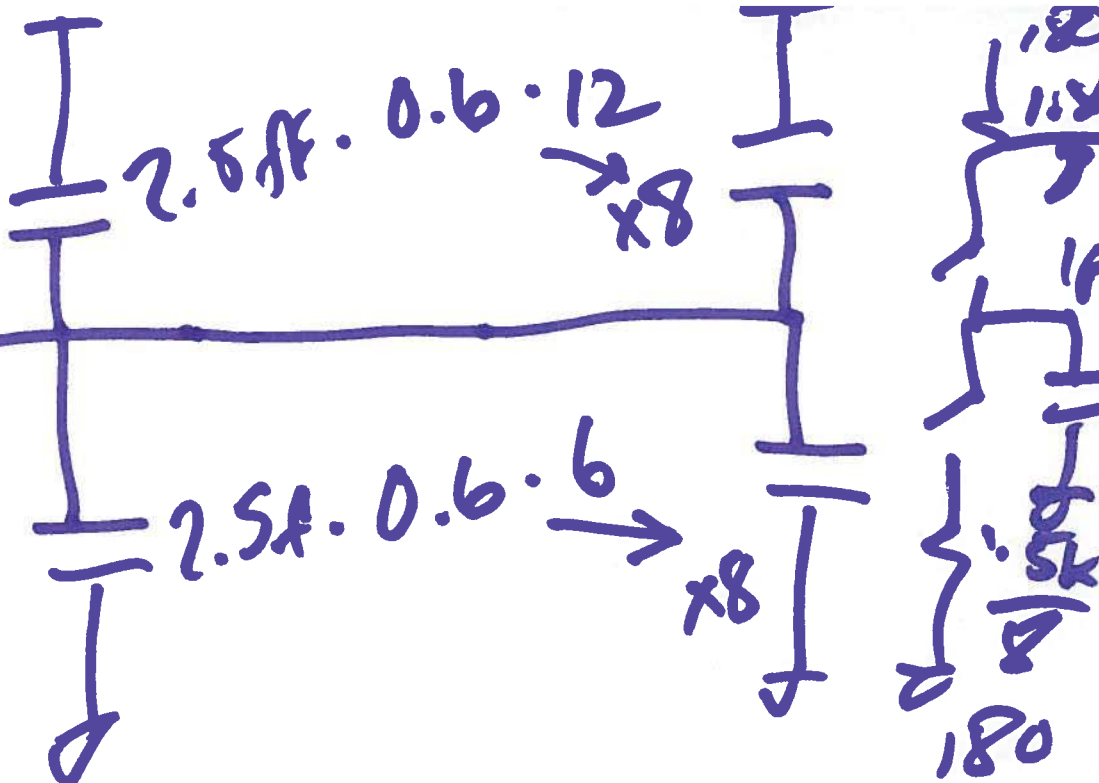


A → B

$$t_{PHL} = t_{PLH} = 1.5k \cdot .7 \left( 9 \cdot 2.5ff \cdot 0.6 \cdot (6 + 12) \right)$$

$$= 1.5k \cdot .7 \cdot \left[ (2.5ff \cdot .6 \cdot 18) + \frac{3}{2} \cdot 2.5ff \cdot .6 \cdot 18 \cdot 8 \right]$$

→ 3ns

3)

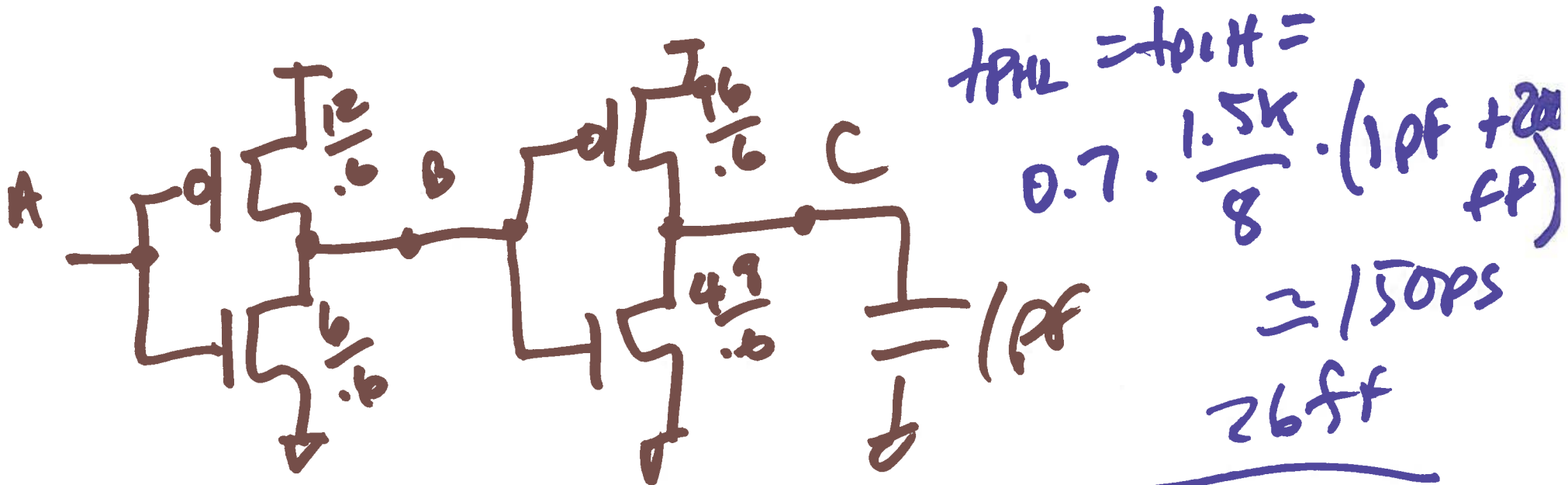

A → B


$$t_{PHL} = t_{PLH} = 0.7 \cdot \frac{1.5K}{8} \cdot (1pF + 26fF) \approx 150ps$$

$$t_{PHL} = t_{PLH} = 0.7 \cdot 1.5K \cdot \left( 2.5fF \cdot 0.6 \cdot (12+6) + \frac{3}{2} \cdot 2.5fF \cdot 0.6 \cdot (12+6) \cdot 8 \right)$$



300 fF      ≈ 380ps

4)

# NAND GATE

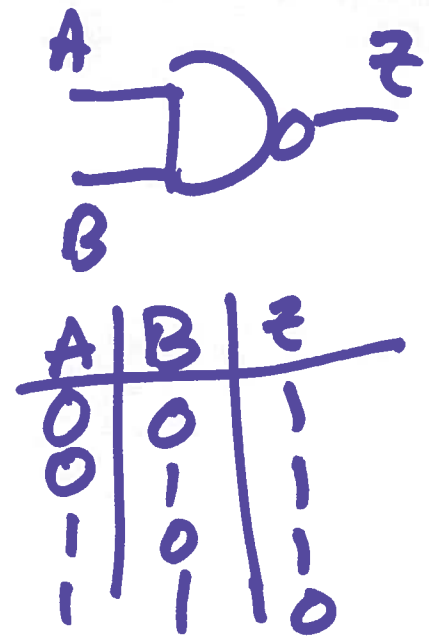


A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

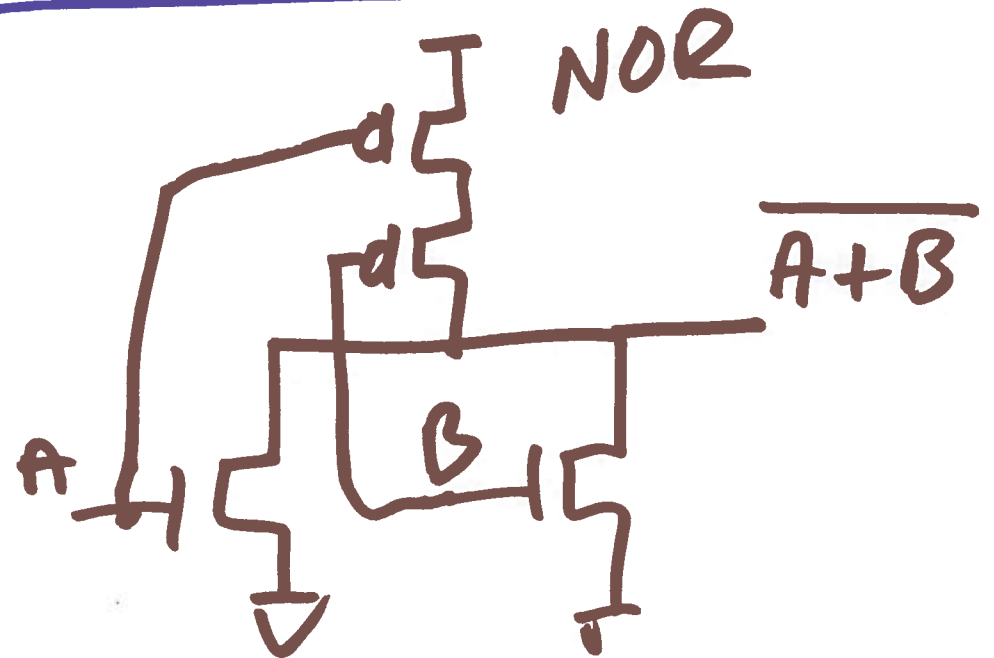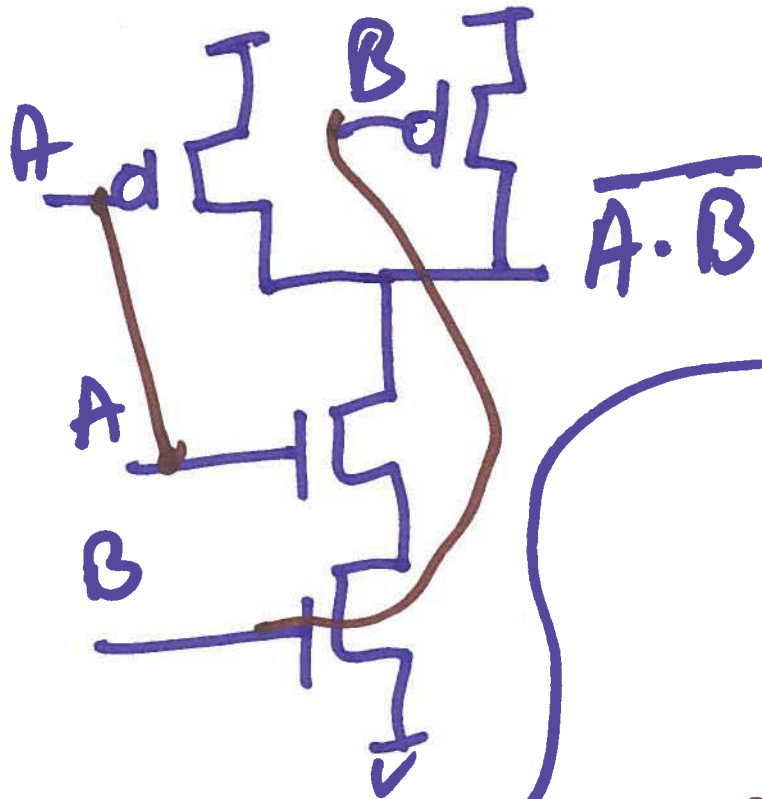

5)

# CMOS XOR

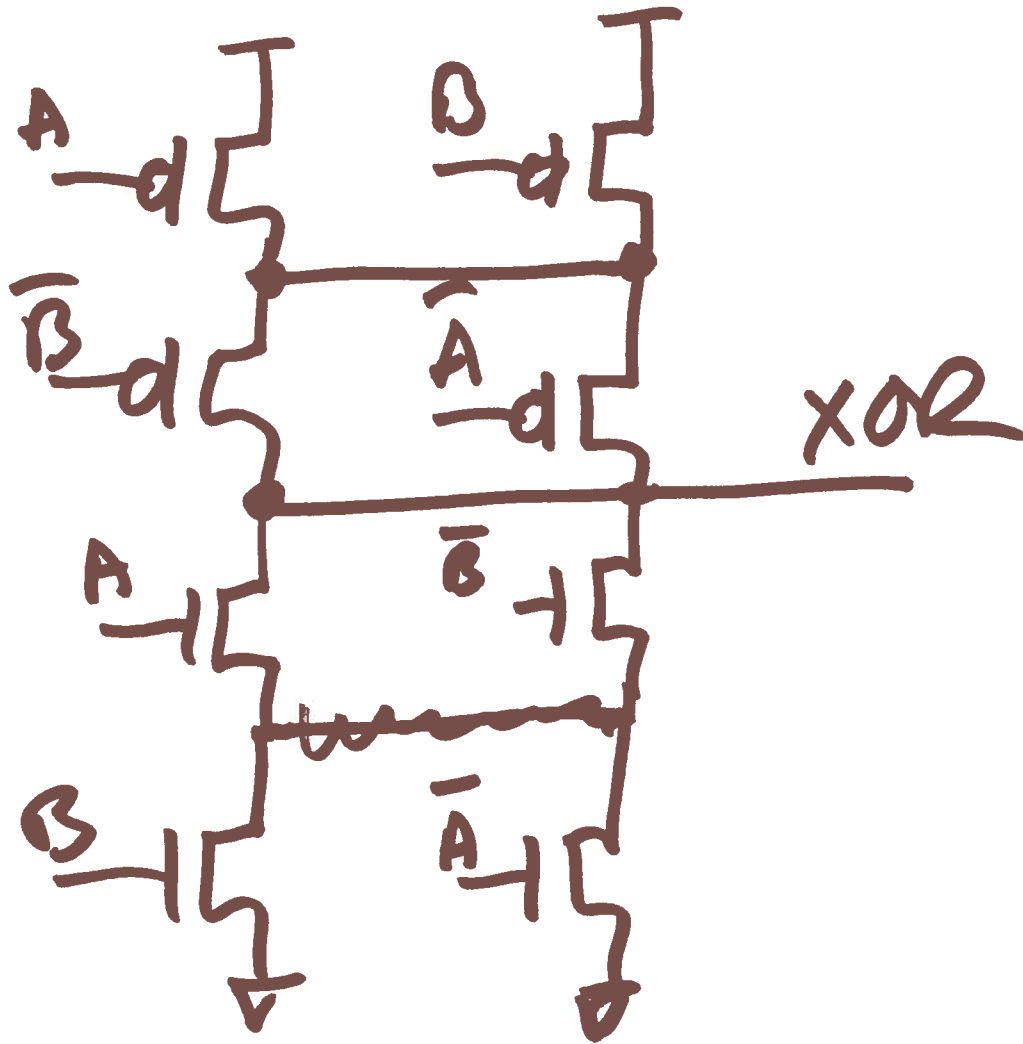

A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

$\rightarrow c$





$$z = \bar{A}B + A\bar{B}$$




$t_{PHL}$

$t_{PLH}$

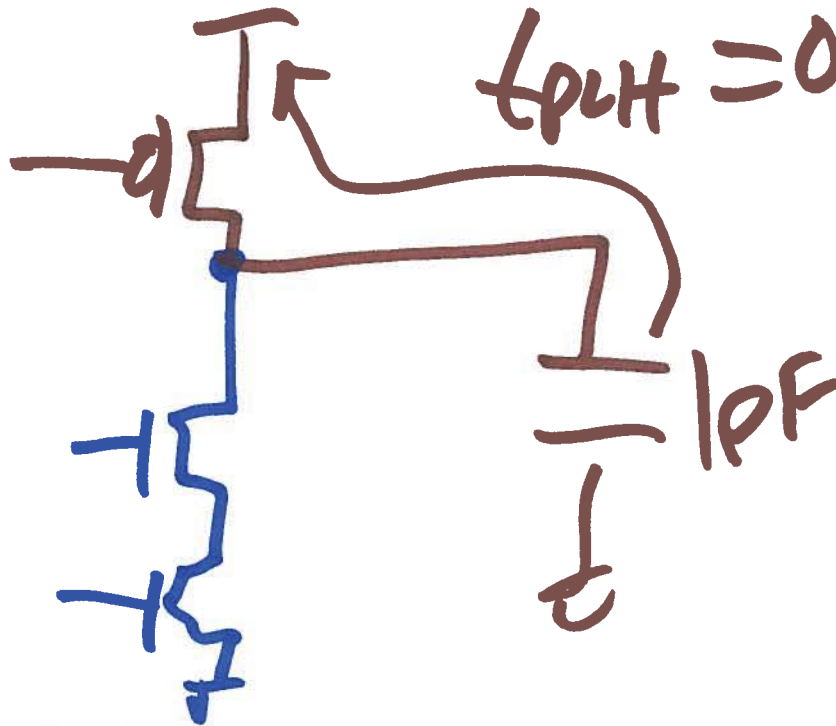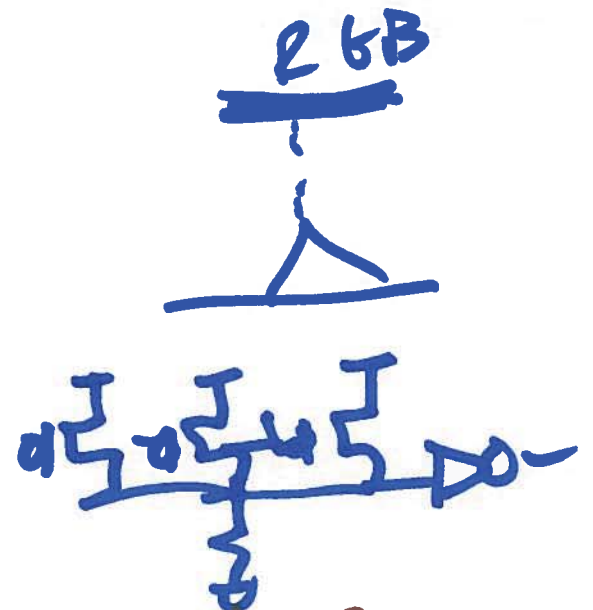


$$t_{PLH} = 0.7 \cdot R_p \cdot 1pF$$




$$t_{PHL} = 0.7 \cdot 2R_n \cdot 1pF$$

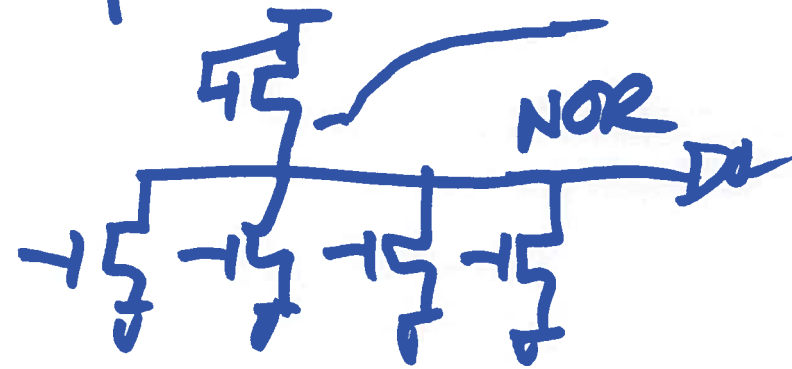

$$z = A + \bar{B}C$$

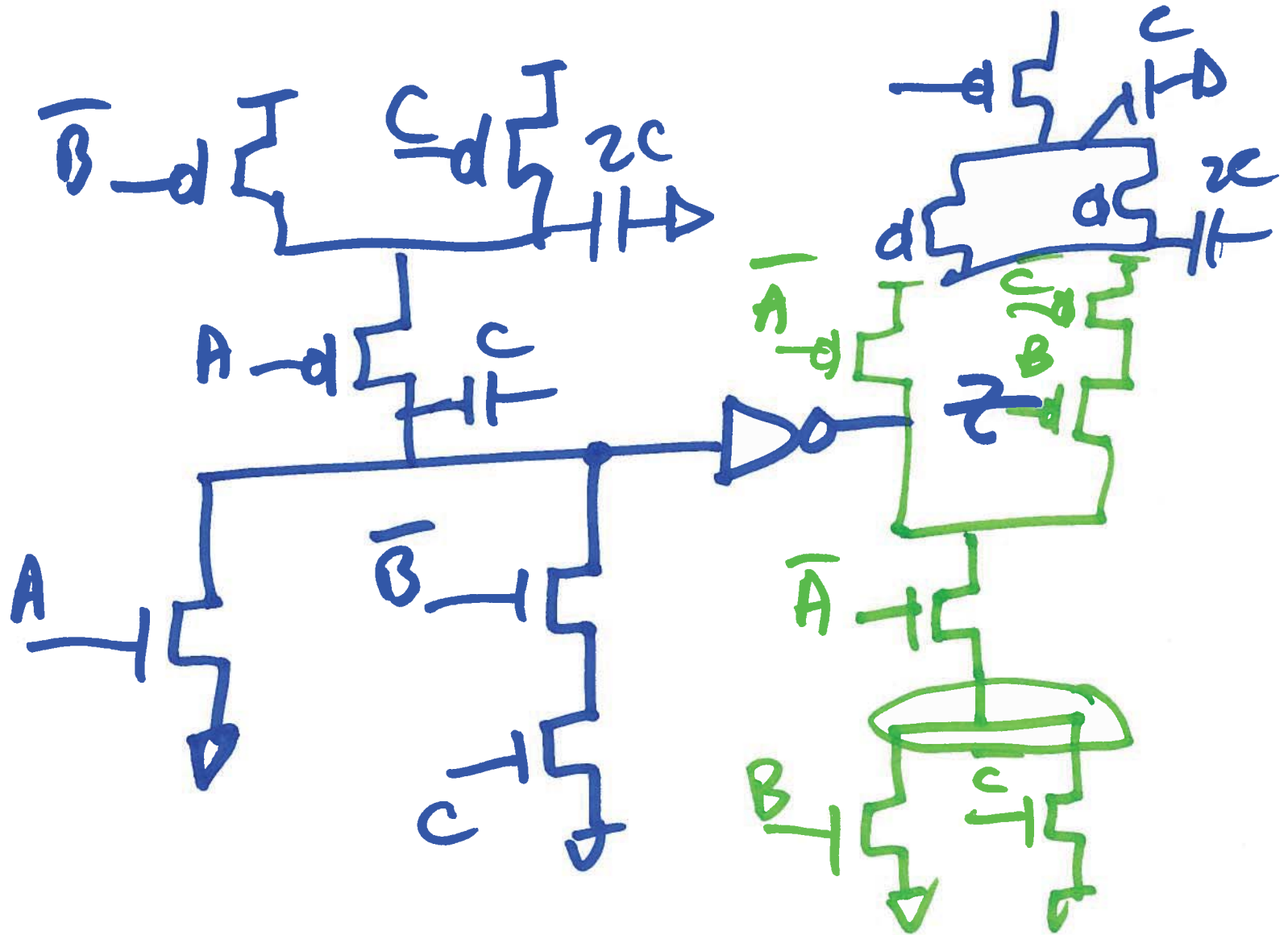



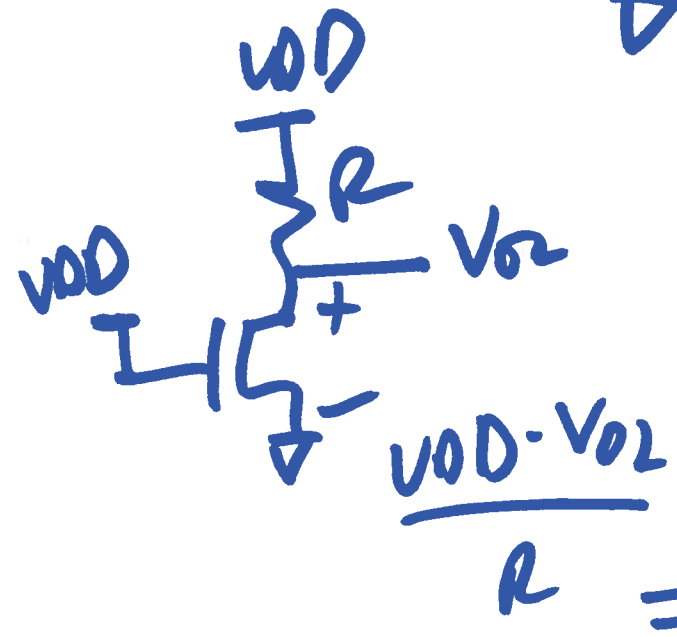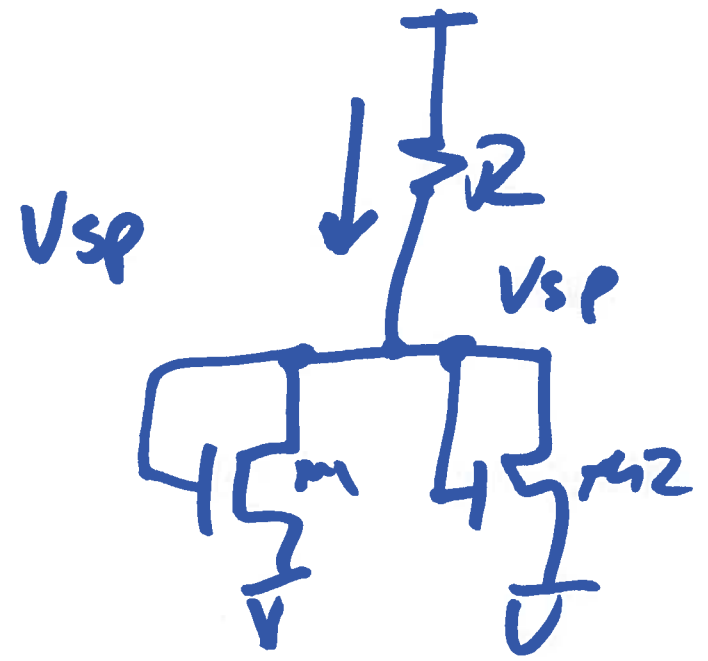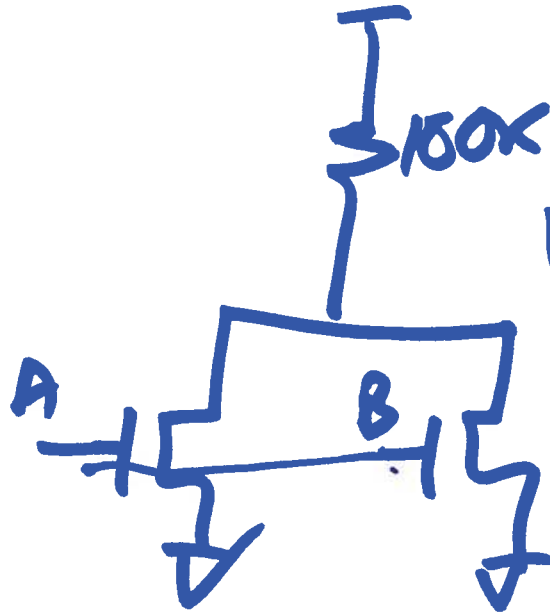

$$\frac{VDD - V_{sp}}{R} = I_{n1} + I_{n2}$$

$$\frac{VDD - V_{ol}}{R} = I_{n1} + I_{n2}$$

IN triode

$$I_{n2} = \frac{K_{n2}}{2} \frac{W}{L} (V_{gs} - V_{tn})^2$$

$V_{gs} = VDD$   
 $V_{ds} = Vol$

9)