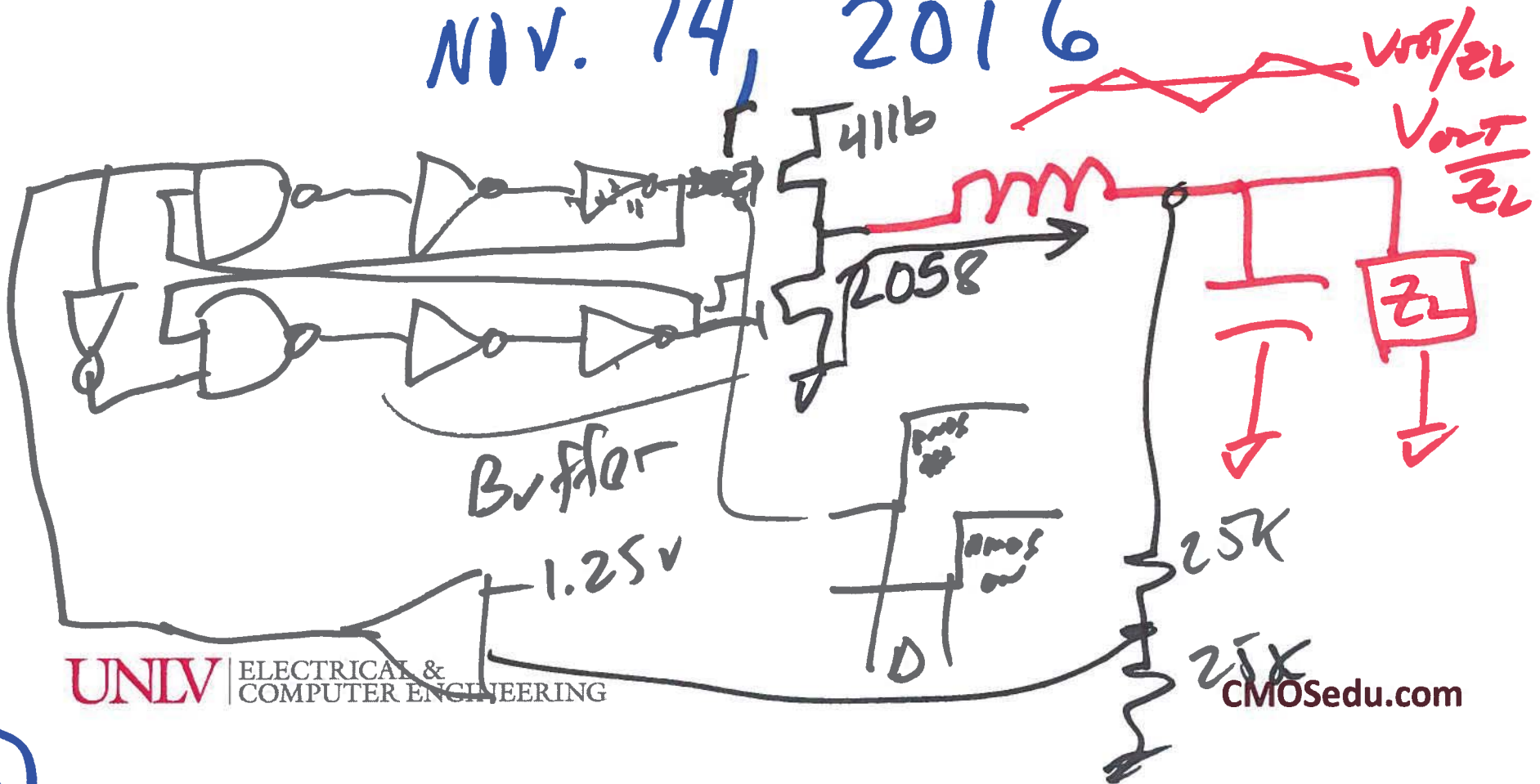




EE 421/621

Digital IC Design


Lecture 19

Nov. 14, 2016



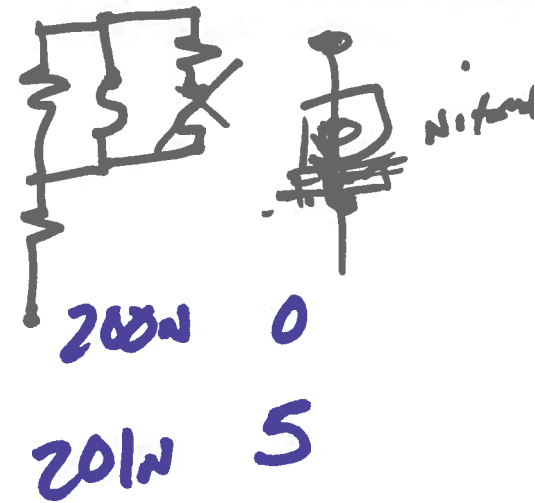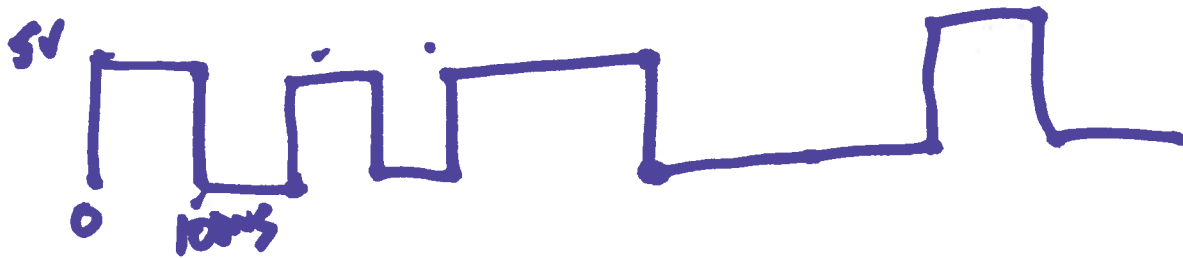


0 5 100ns 5 10ns 0 200n 0 20n 5

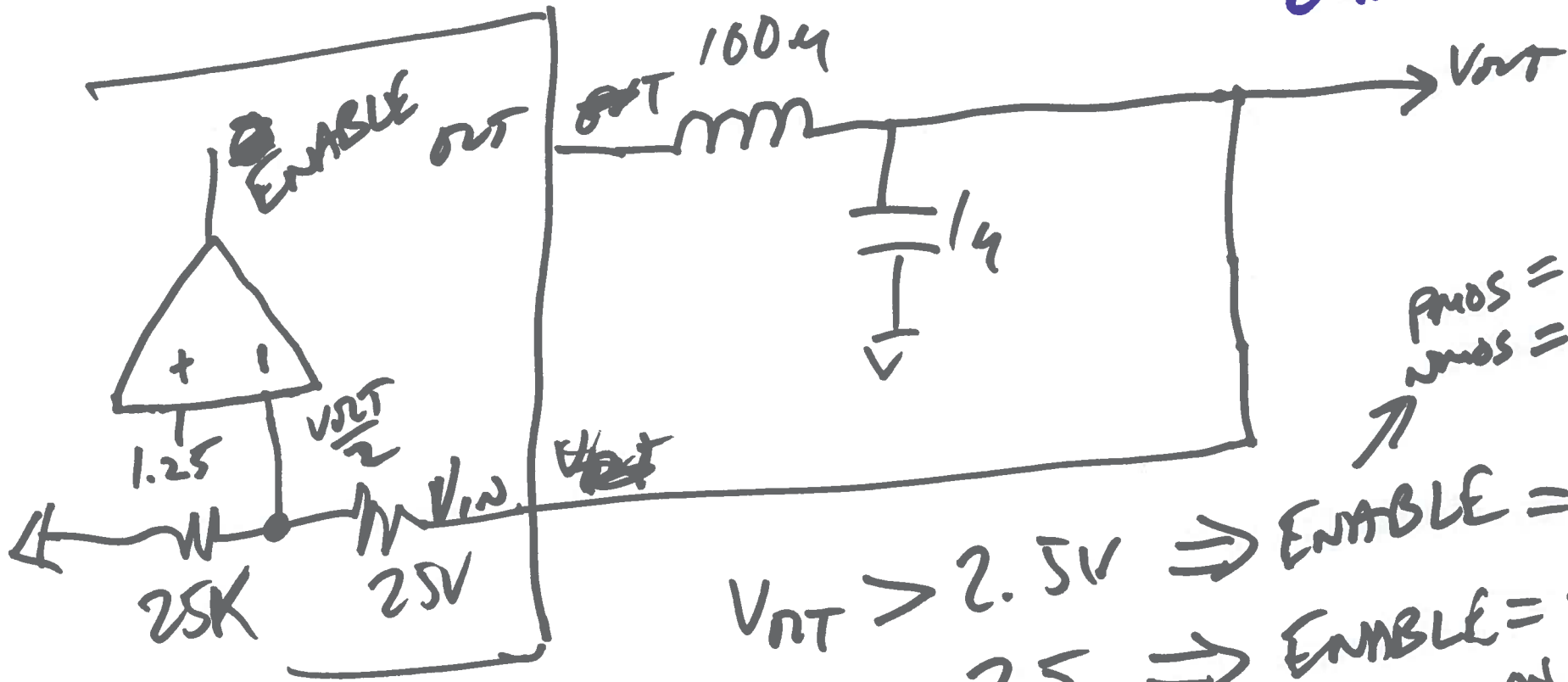

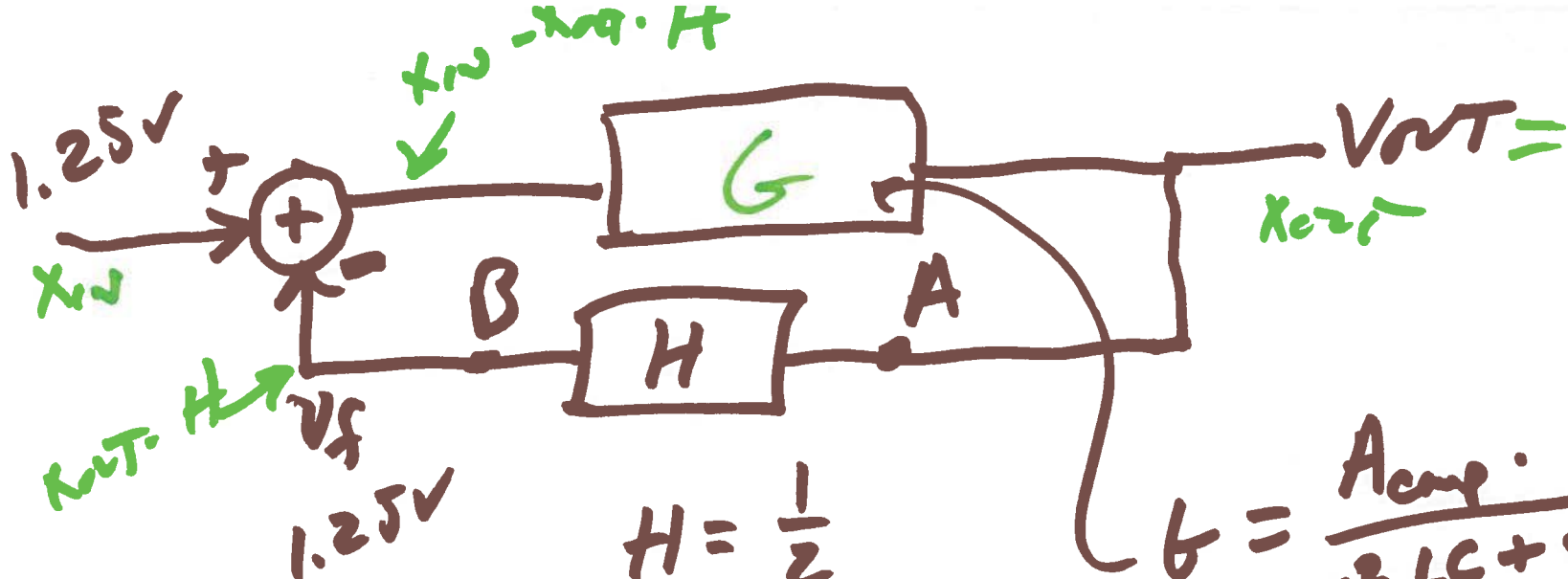
$V_{out} > 2.5V \Rightarrow \text{ENABLE} = 0$   
 $V_{out} < 2.5V \Rightarrow \text{ENABLE} = 1$   
 $\text{pmos} = \text{off}$   
 $\text{nmos} = \text{on}$   
 $\text{pmos} = \text{on}$   
 $\text{nmos} = \text{off}$





$$H = \frac{1}{2}$$

$$G = \frac{A_{amp}}{s^2 LC + sRC + 1}$$

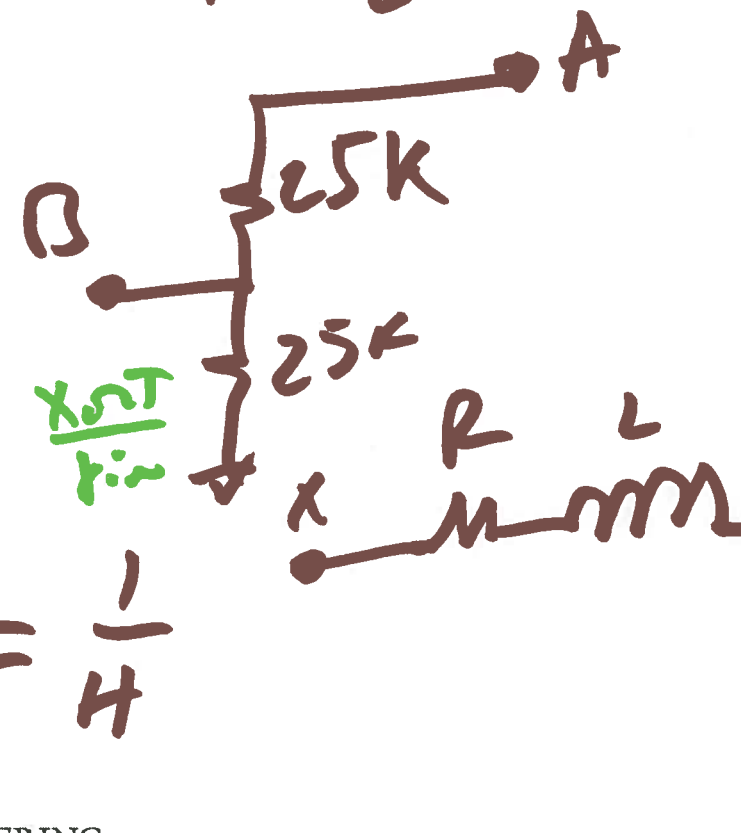


$$\frac{A}{X} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + j\omega L + R}$$

$$A_{cl} = \frac{G}{1 + GH} = \frac{x_{out}}{x_{in}}$$

$$A_{cl} = \frac{1}{\frac{1}{G} + H} = \frac{1}{H}$$


$$= \frac{1}{(j\omega)^2 LC + j\omega RC + 1}$$

3)

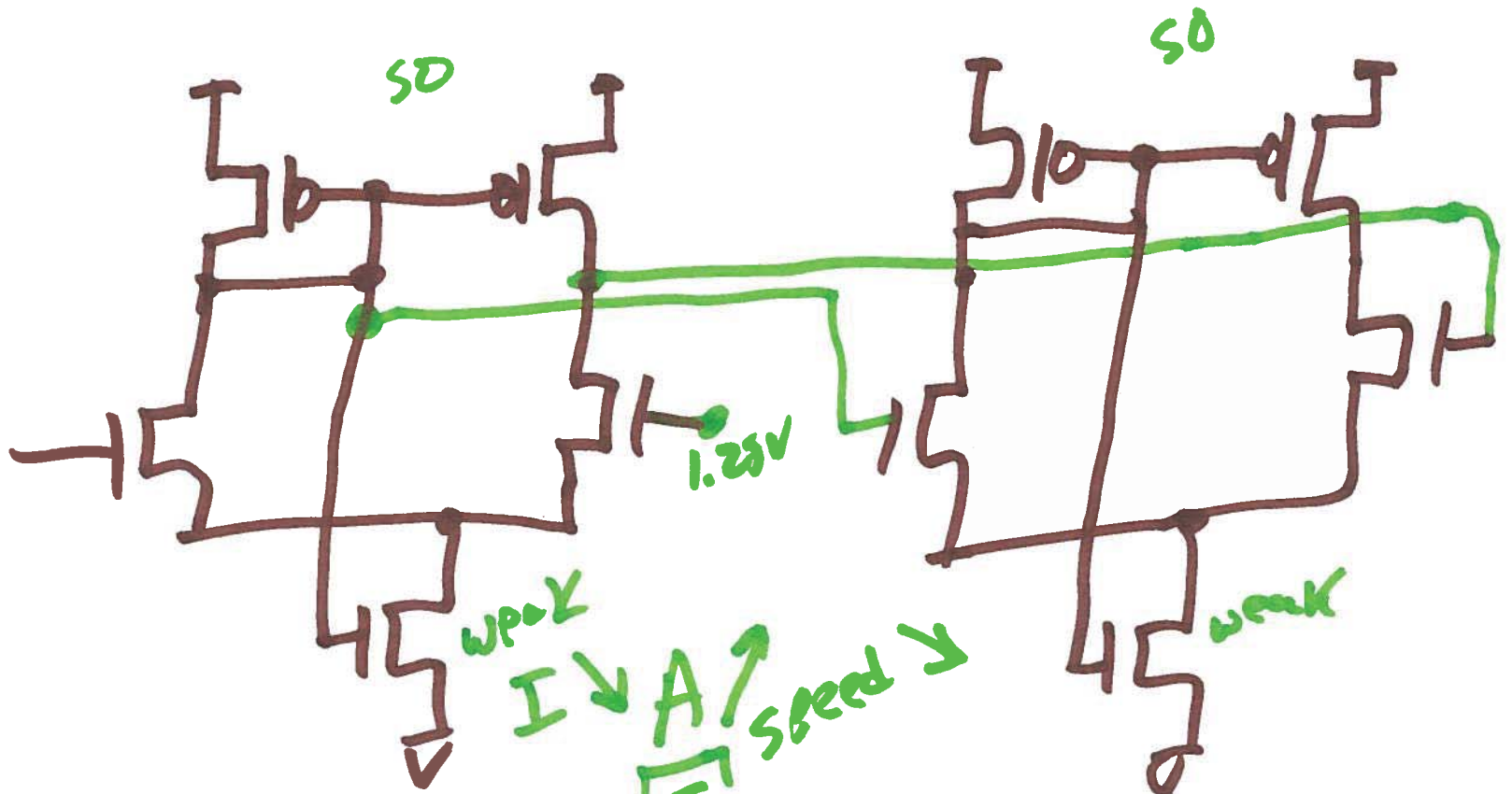


self-biased  
diff-amp

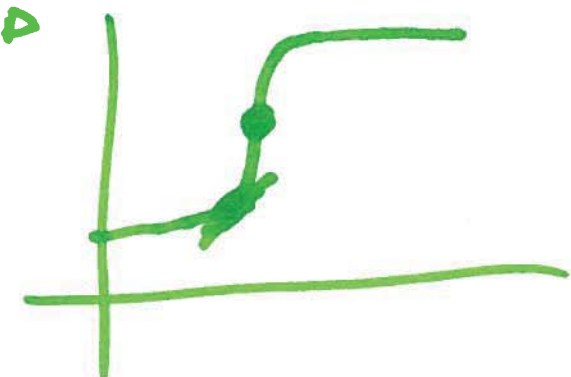$I \rightarrow A \rightarrow$  speed  $\rightarrow$   
 $\sqrt{I_D}$




4)

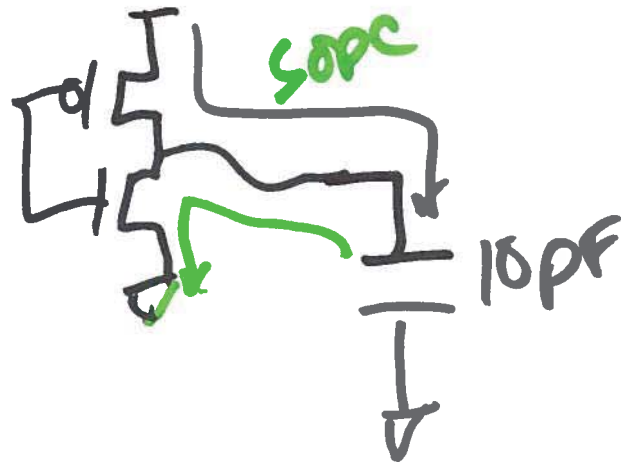

$$CV = Q = C \cdot V_{DD}$$

$$I_{avg} = \frac{50pC}{10ns} = 50nA$$
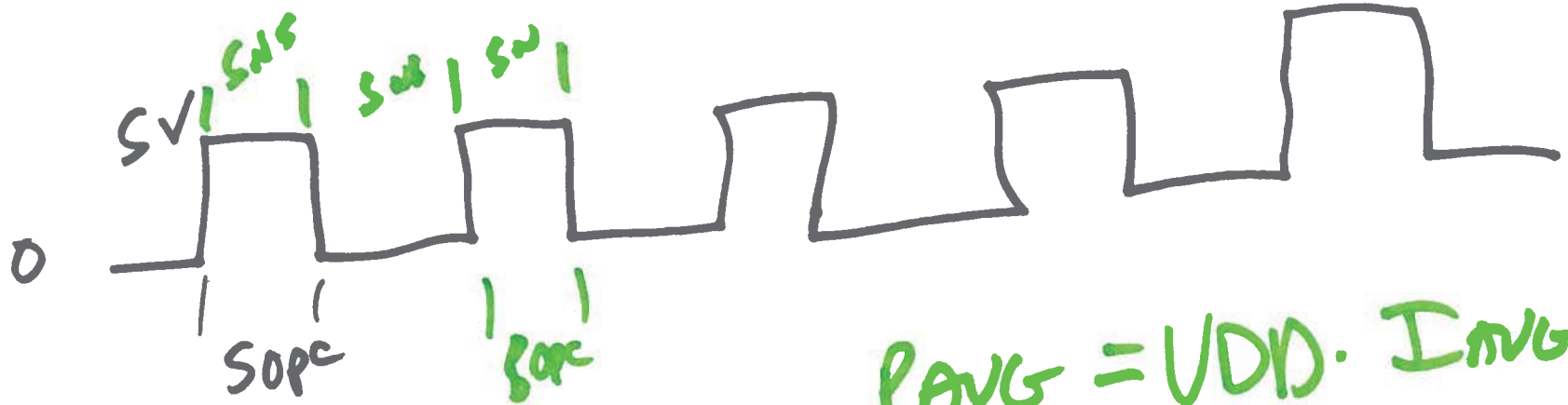
$$= \frac{CV_{DD}}{T} = C \cdot f \cdot V_{DD}$$



$$P_{avg} = V_{DD} \cdot I_{avg}$$

$$P_{avg} = C_L \cdot V_{DD}^2 \cdot f$$