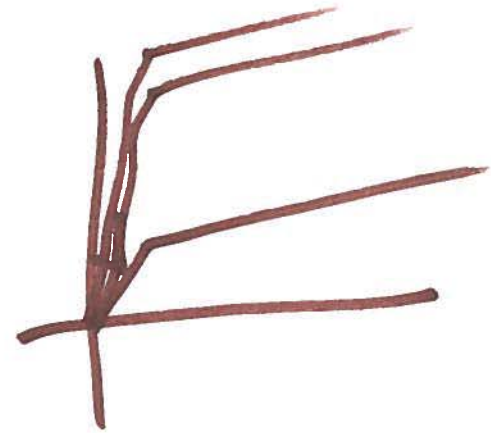


EE 421 / ECG 621

Digital IC Design

12/7/2016

Lecture 26



WANT
 $R_{in} \gg R_{out}$

))



Study for final

quizzes

Homeworks

midterm exam

project

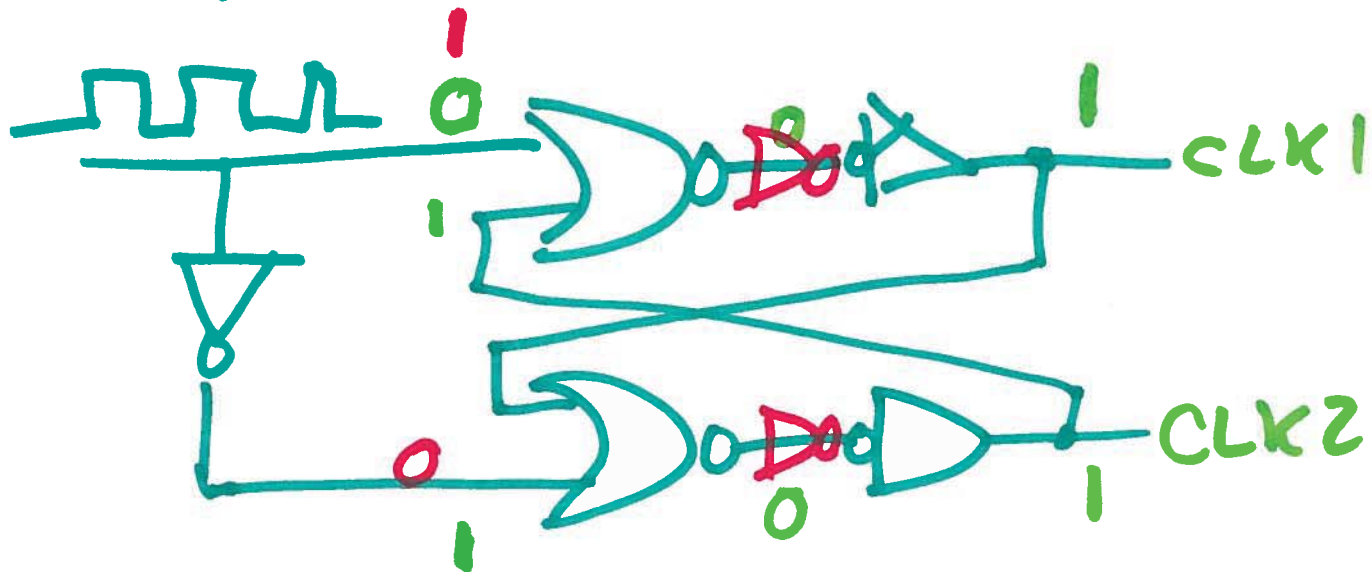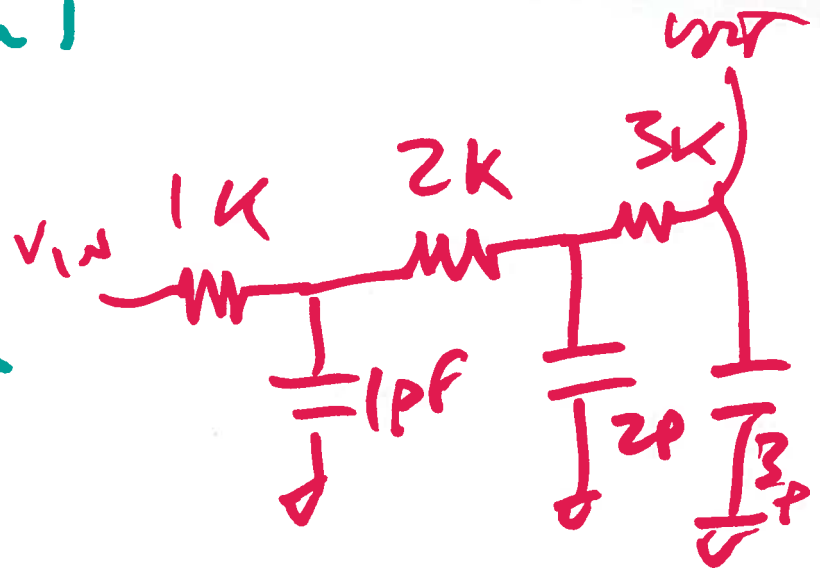

$$t_d = 0.7 \left(1k + 1p + (1k + 2k)2p + (1k + 2k + 3k)3p \right)$$





$$t_{AB} = t_{PHL} + t_{PLH} = \left(R_{in}' \cdot \frac{L}{W_{in}} + R_p' \cdot \frac{L}{W_{ip}} \right) \cdot \left[C_L + C_{ox}' \cdot L (W_{oz} + W_{pz}) \right]$$


$$0.7 \cdot \left(R_{in}' \cdot \frac{L}{W_{in}} + R_p' \cdot \frac{L}{W_{ip}} \right) \cdot \left[C_{ox}' (W_{in} L + W_{ip} \cdot L) + \frac{3}{2} C_{ox}' \cdot L (W_{zp} + W_{zn}) \right]$$

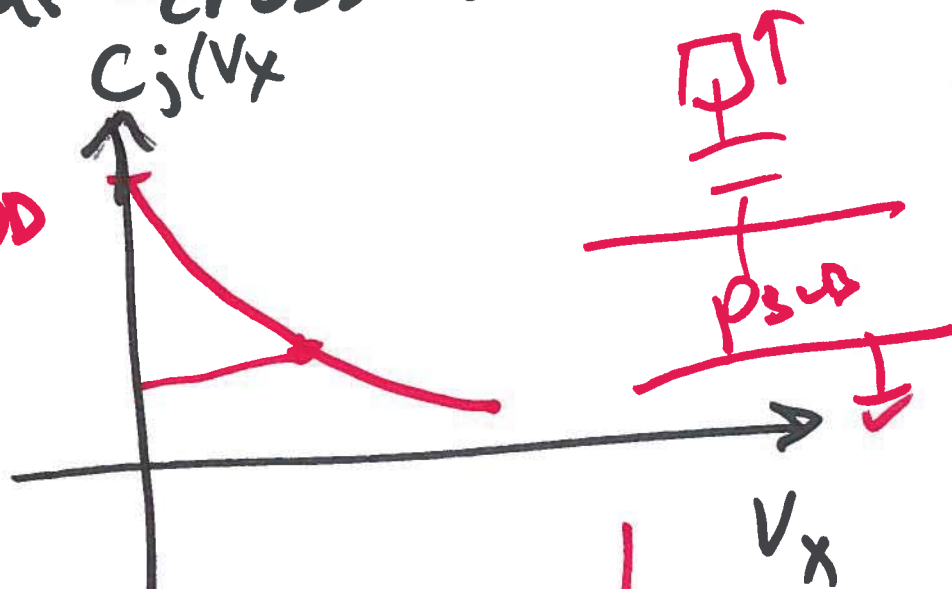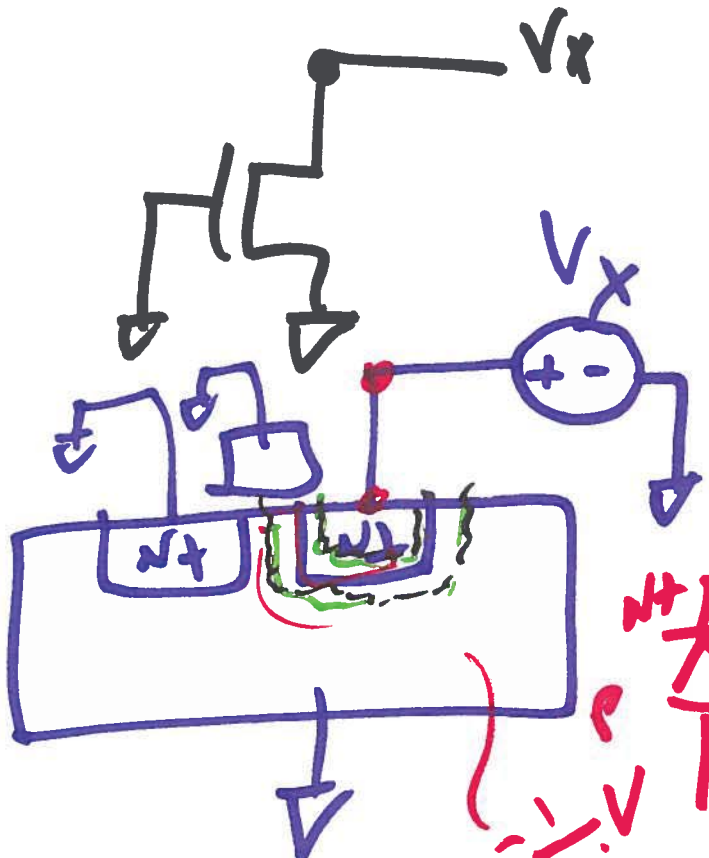3)

plot C vs. V_x for the following CKT. Sketch the cross-sectional view.






P	+	+	N
O	+	+	N
O	+	+	N

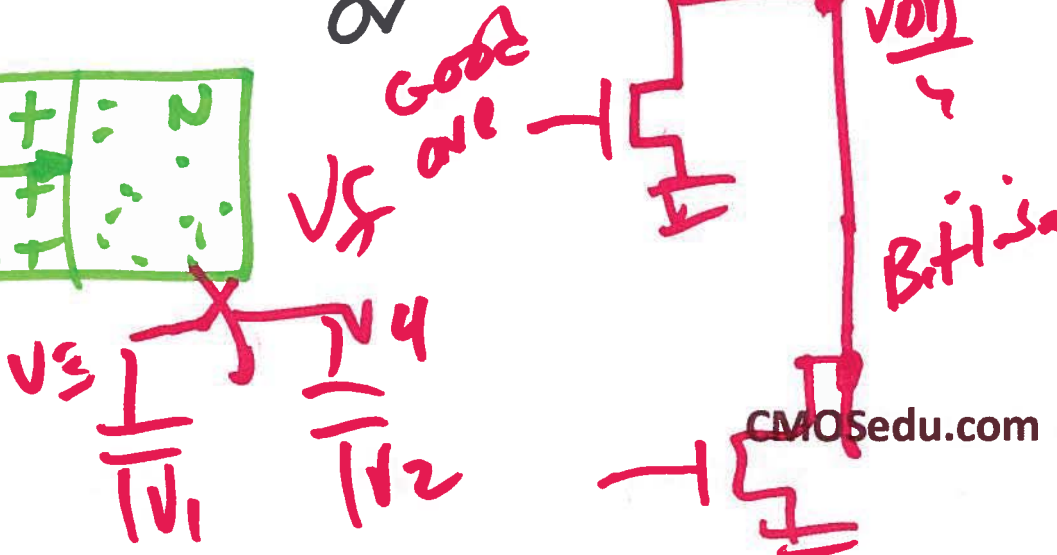

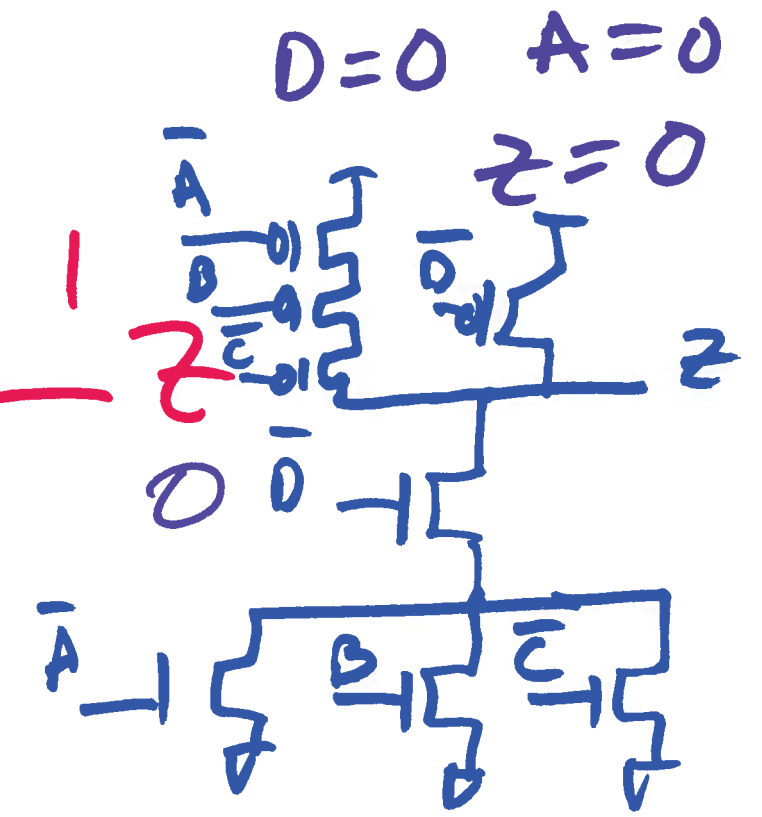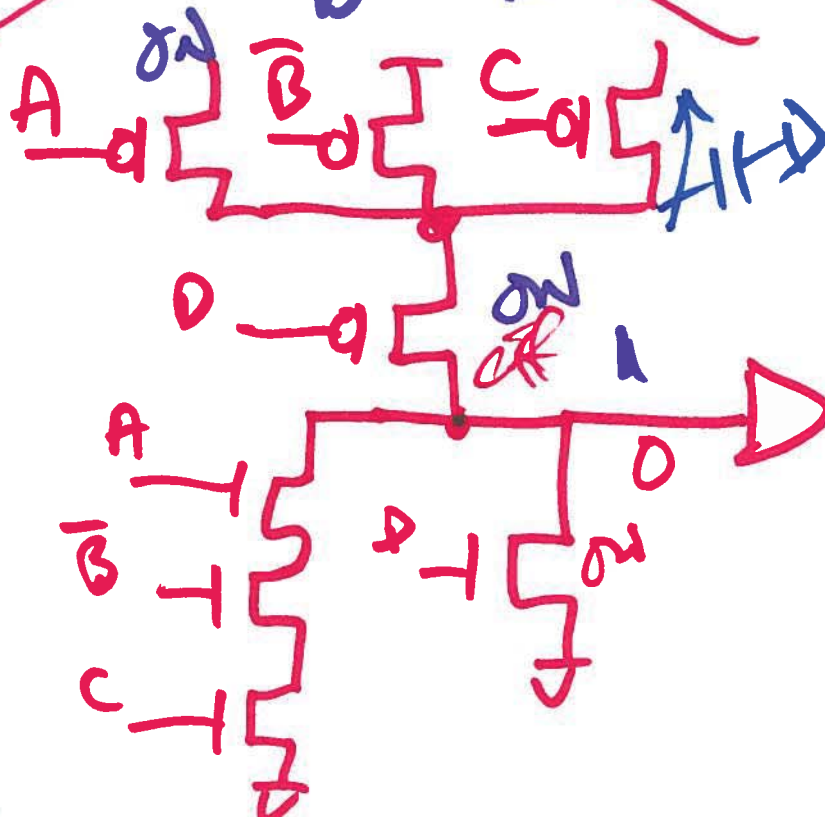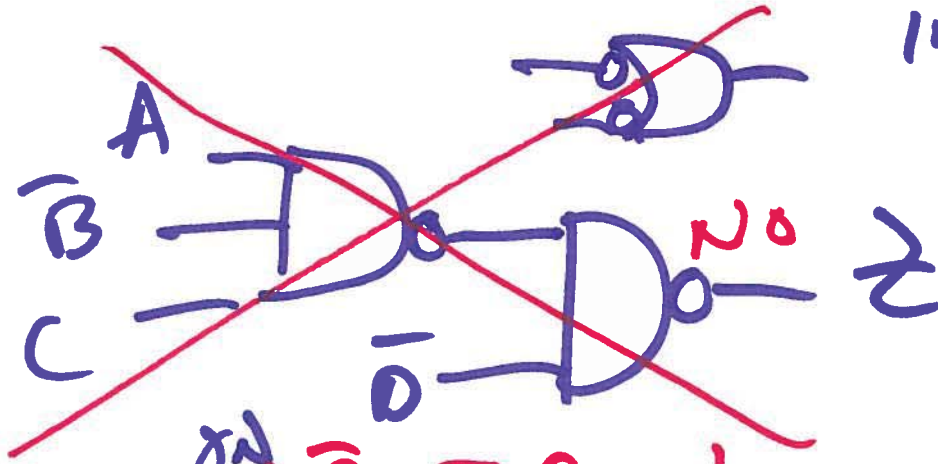4)

$$Z = A\bar{B}C + D$$


Implement a complex CMOS logic of this function



$D=0 \quad A=0$

$Z=0$


5)

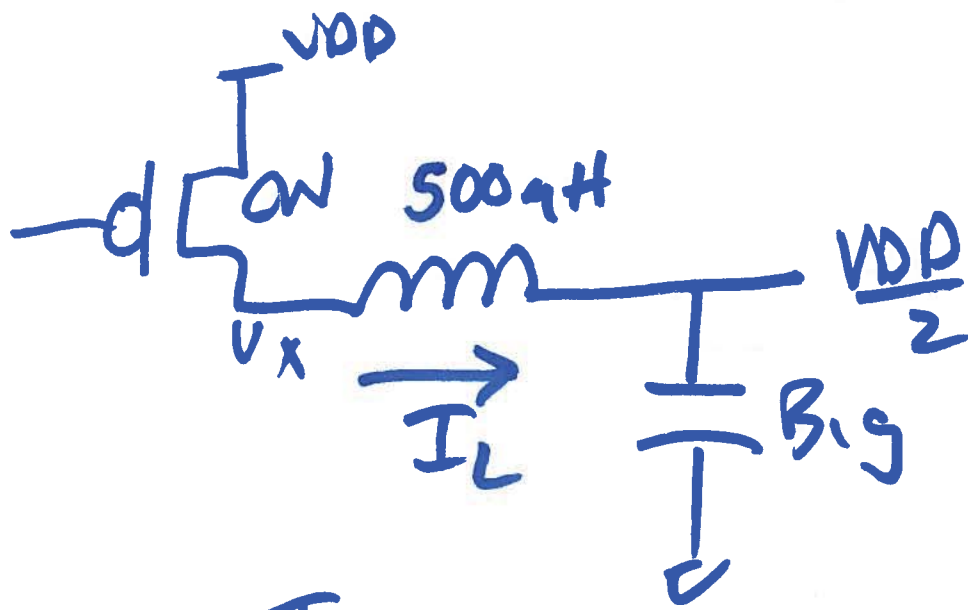

$$I = \frac{1}{L} \int_0^t v \cdot dt$$

$$\left(V_{DD} - \frac{V_{DD}}{2} \right) = \frac{V_{DD}}{2}$$

$$\frac{V_{DD}/2}{L} \cdot t$$

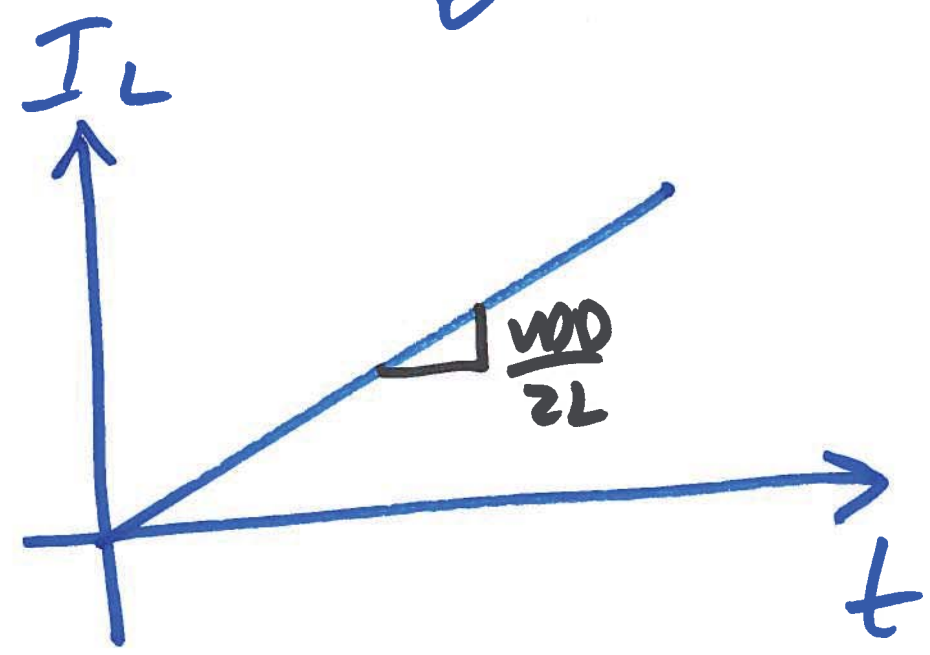

6)