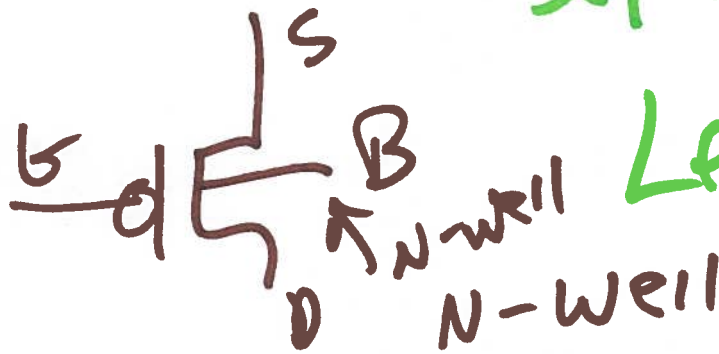


EE 421/ECG 621


CMOS Digital IC Design



September 7, 2016

Lecture 3



Resistor  
diode  
Body pins

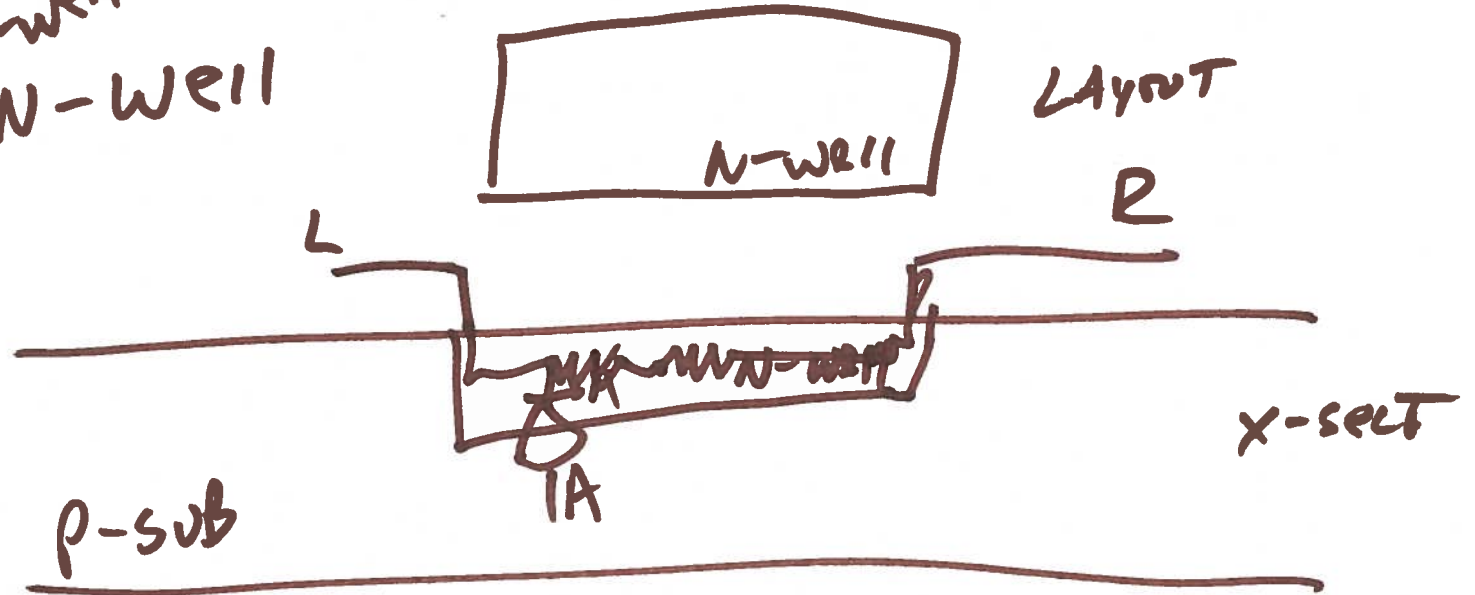

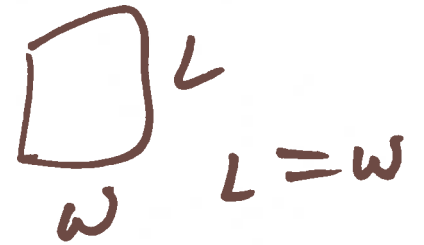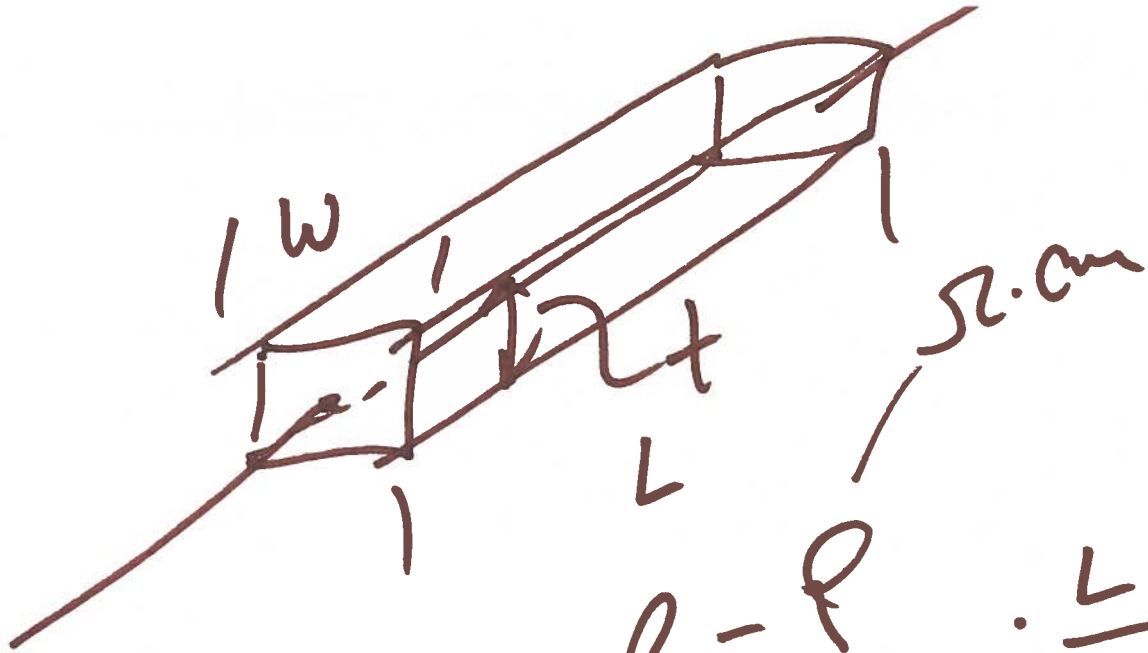

$$R = \frac{\rho}{t} \cdot \frac{L}{w}$$

sheet  
resistance  
 $\frac{\Omega}{\square}$

2)



$p.n = n_i^2$

$n = n_D \cdot 2$


$p = \frac{n_i^2}{n_D}$

$N_{Si} = 5 \times 10^{20} \frac{\text{Atoms}}{\text{cm}^3}$


$N_D = 10^{16} \frac{\text{Atoms}}{\text{cm}^3}$

depleted

$C = \epsilon \cdot \frac{A}{t}$

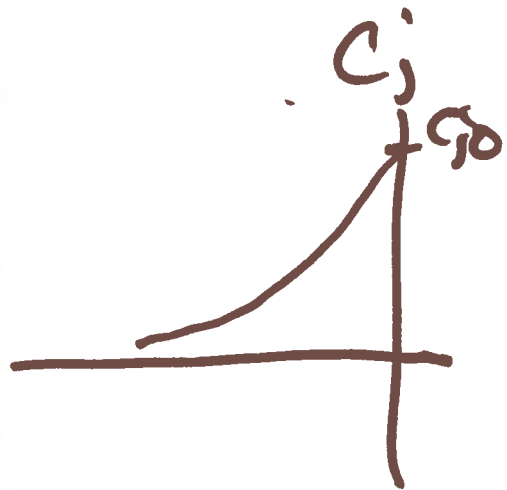

3)

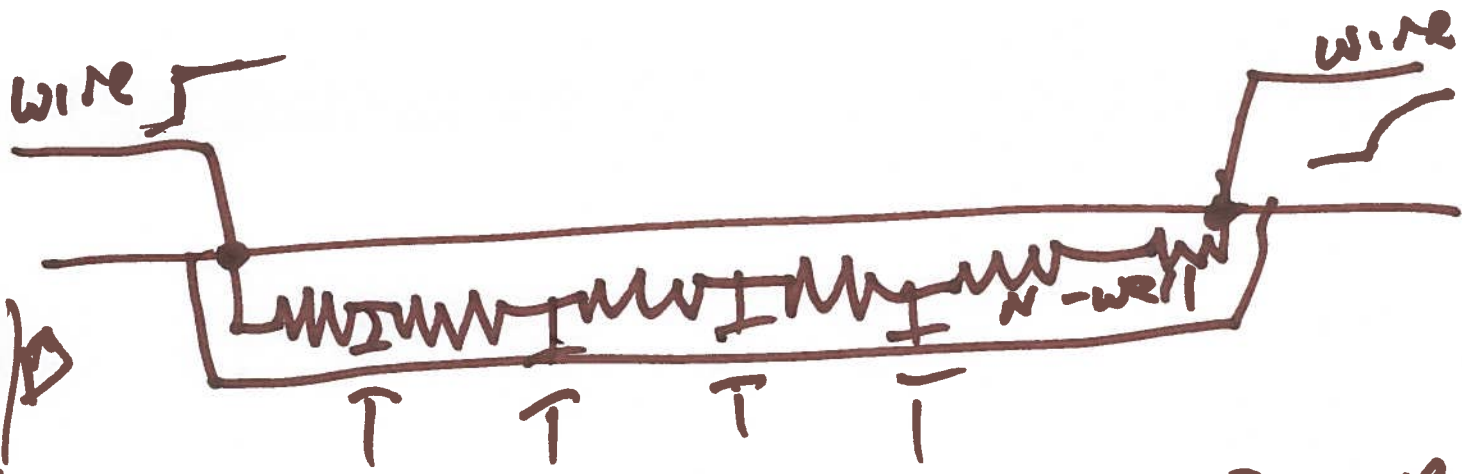

900 fF/□

900 fF

900 fF

# of squares CS ↓

$$\frac{600}{3} = 200 \text{ squares}$$

$$R_{\square} = 800 \Omega/\square$$


$$C_{dep} = 100 \text{ fF}/\mu\text{m}^2$$

- $a = 10^{-18}$
- $f = 10^{-15}$
- $p = 10^{-12}$
- $n = 10^{-6}$
- $y_{ox} = 10^{-6}$




$$R = 800 \Omega \cdot 200 \square = 160K \Omega$$

4)

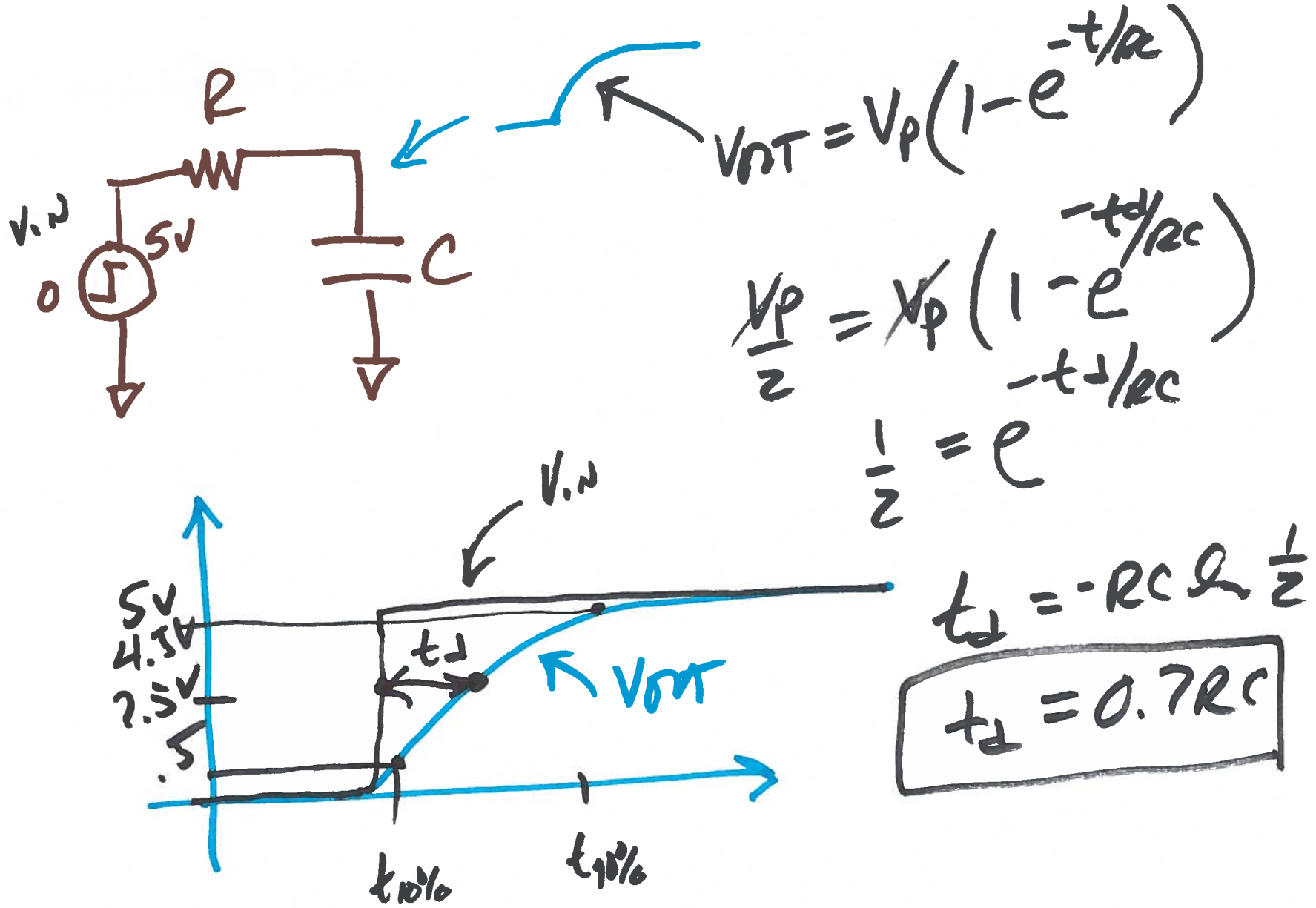

5)

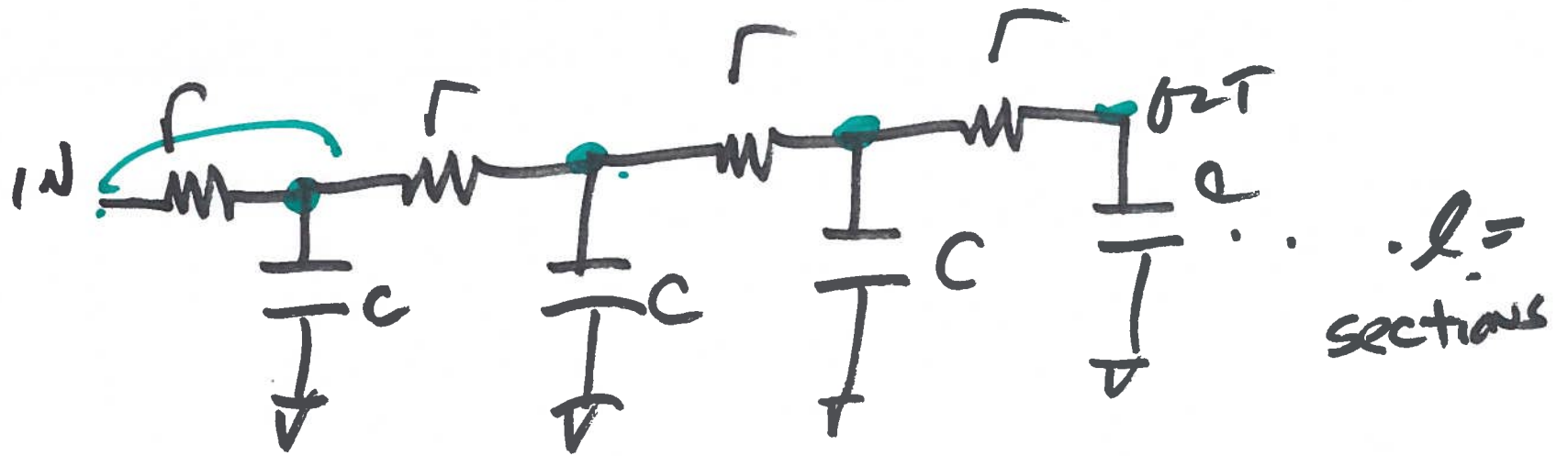

$$t_1 = 0.7rc + 0.7 \cdot 2rc +$$

$$t_2 = 0.7 \cdot \frac{l^2}{2} \cdot rc$$

$$0.7 \cdot 3rc + 0.7 \cdot 4rc$$

$$t_2 = 0.35l^2rc = 0.7rc \frac{(1+2+3+4+l)}{\frac{l^2}{2}} \approx \frac{l(l+1)}{2}$$

$$t_d = 0.35 \cdot 200^2 \cdot 800 \cdot 900 \times 10^{-18} \text{ s}$$



Stored charge



$$t_d = 10 \text{ ns}$$

