
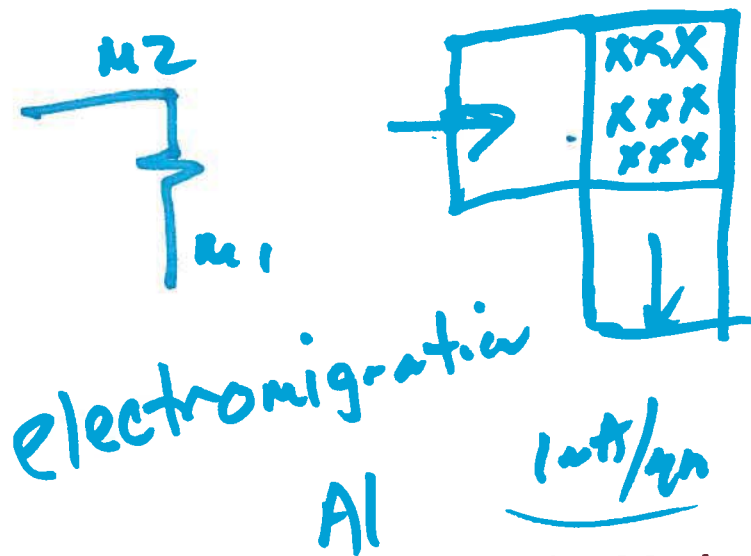



EE 421/ECG 621



Digital IC Design

Lecture 5

Sept. 14, 2016  $P = I^2R$

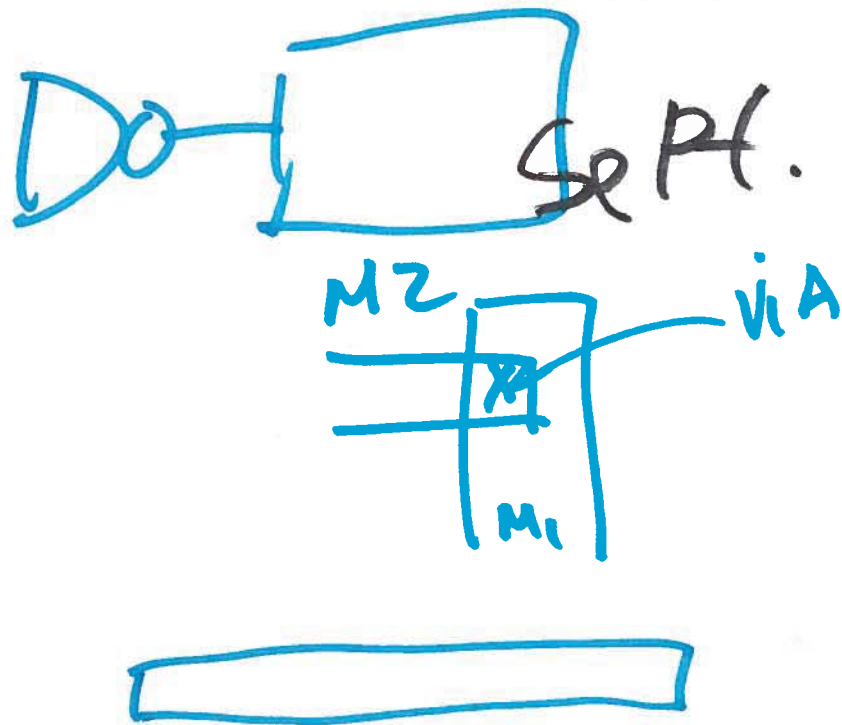


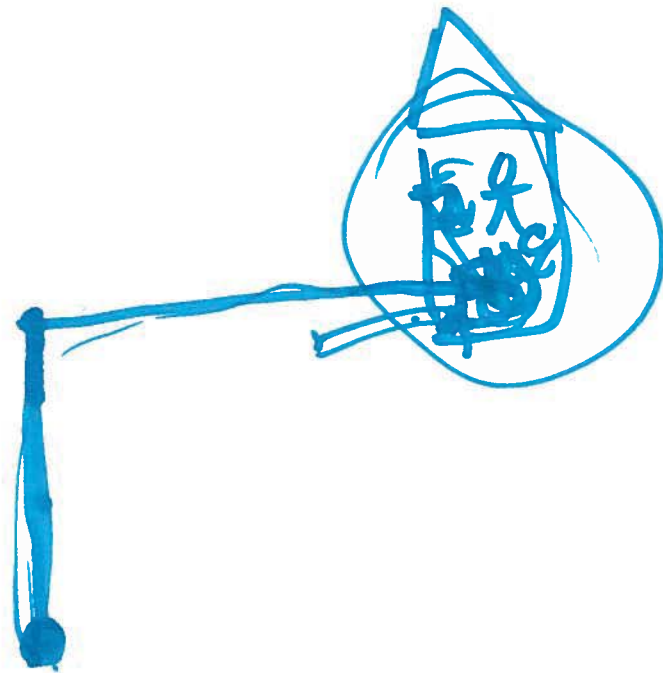

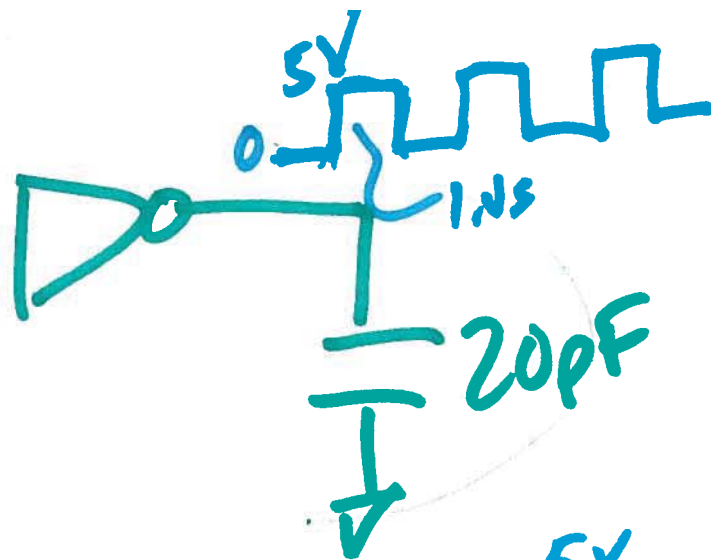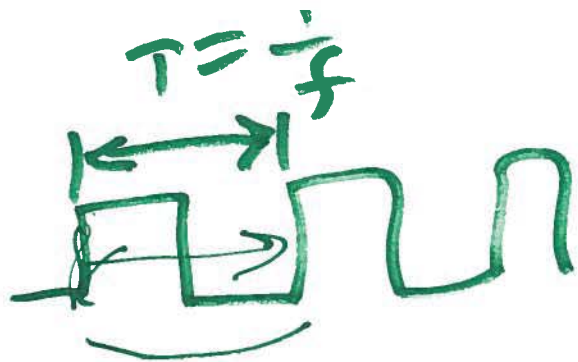

$$I = C \frac{dV}{dt} = C \cdot \frac{\Delta V}{\Delta t}$$

$$CV = Q$$

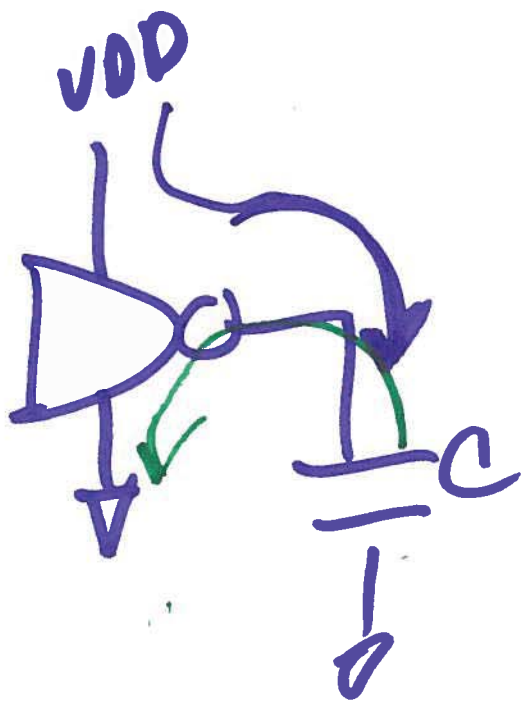

$$20\text{pF} \cdot 5 = 100\text{pC}$$

$$I_{\text{peak}} = \frac{100\text{pC}}{1\text{ns}}$$



$$= \underline{\underline{100\text{nA}}}$$



$$I_{\text{avg}} = \frac{100\text{pC}}{T} = 100\text{pC} \cdot f$$

$$C \cdot V_{DD} \cdot f$$


$$P_{\text{avg}} = V_{DD} \cdot I_{\text{avg}} = C \cdot V_{DD}^2 \cdot f$$


CMOSedu.com

$R_0 = 0.1 \mu\Omega$

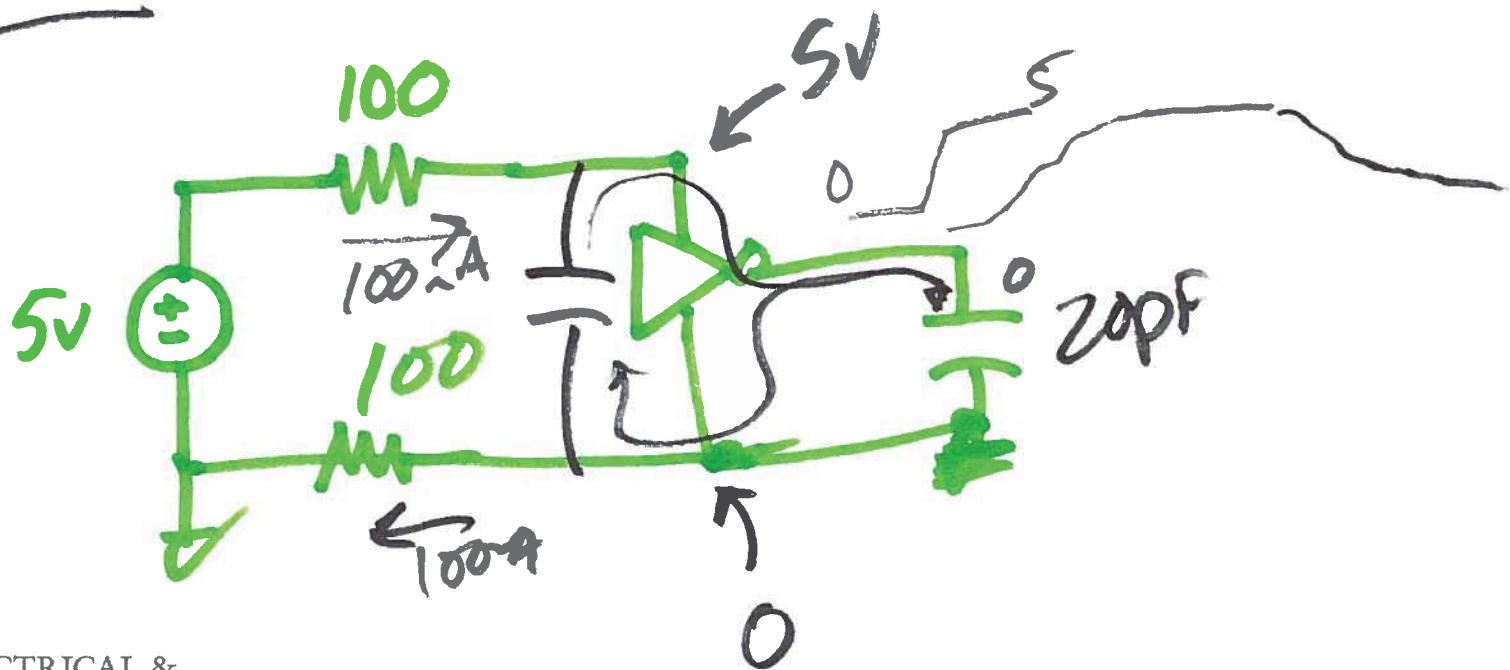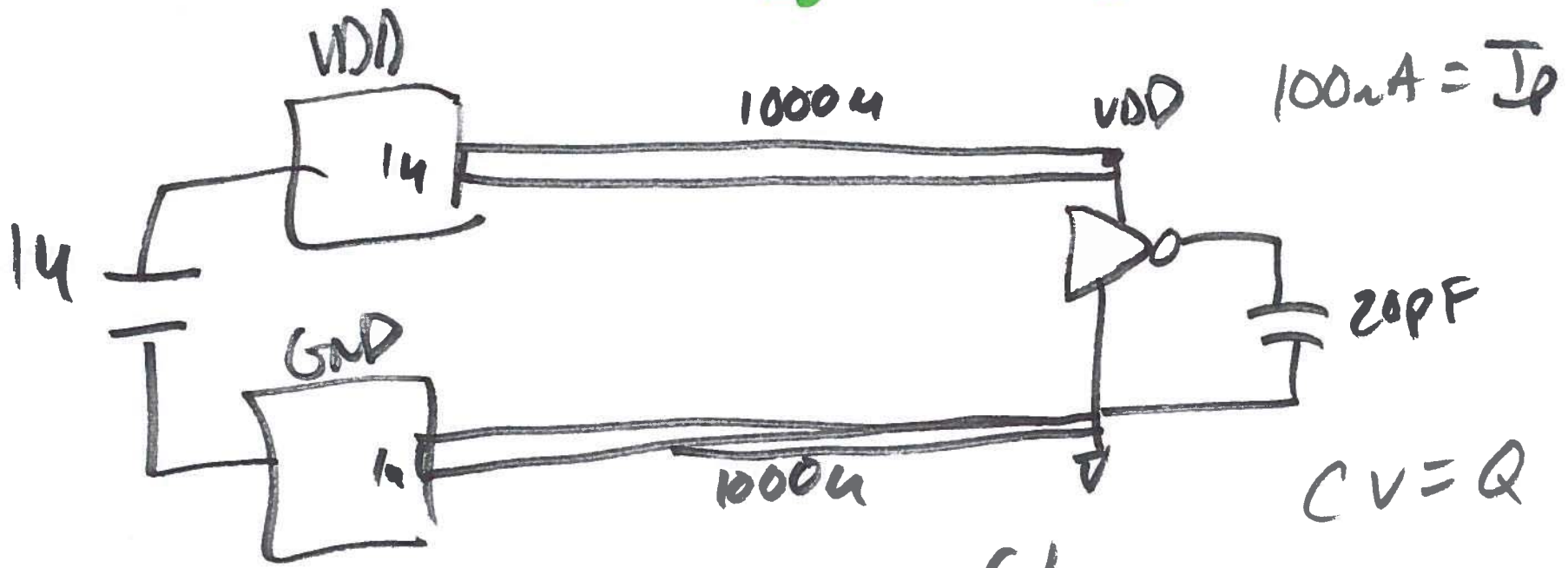

4)

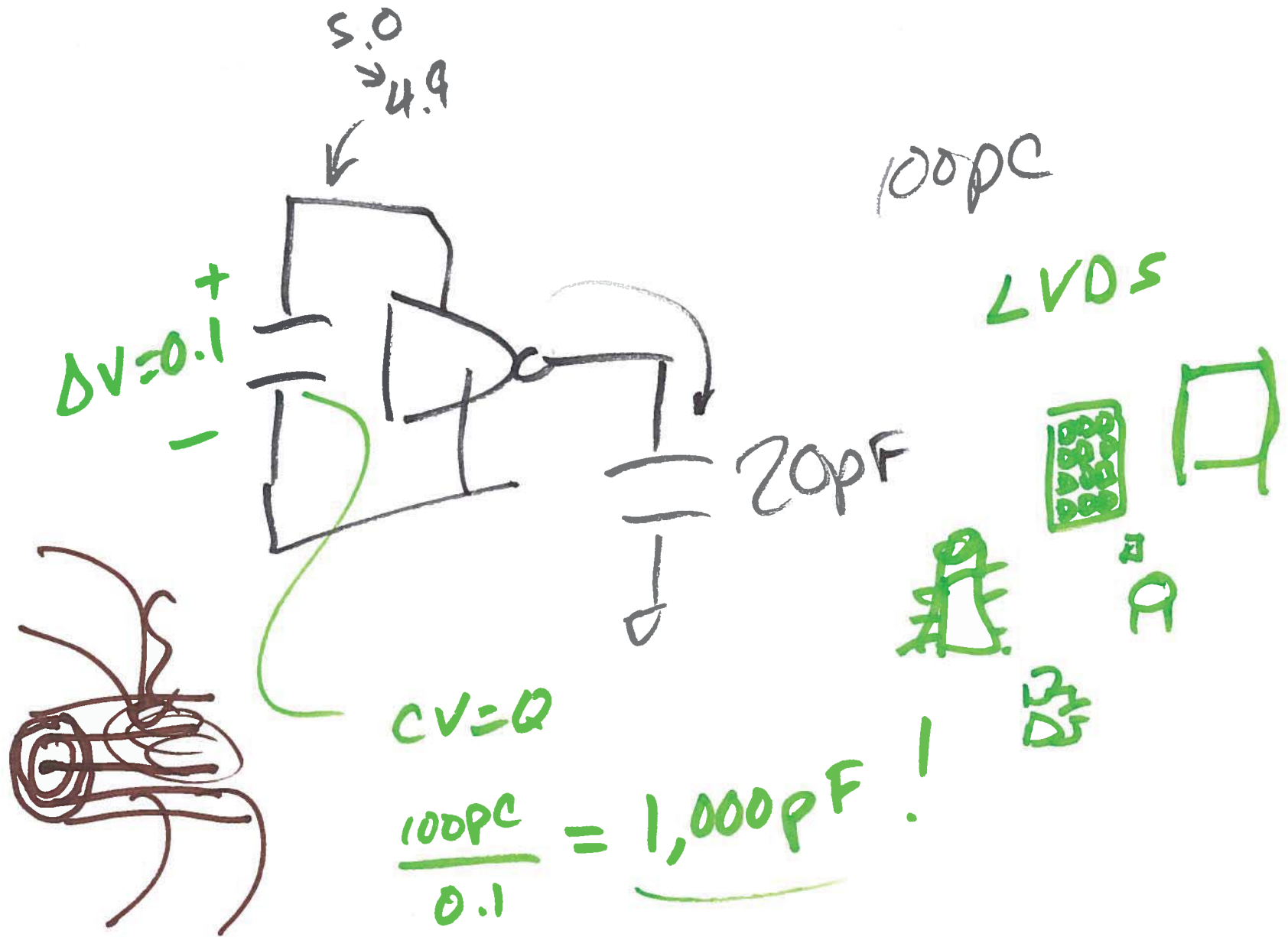

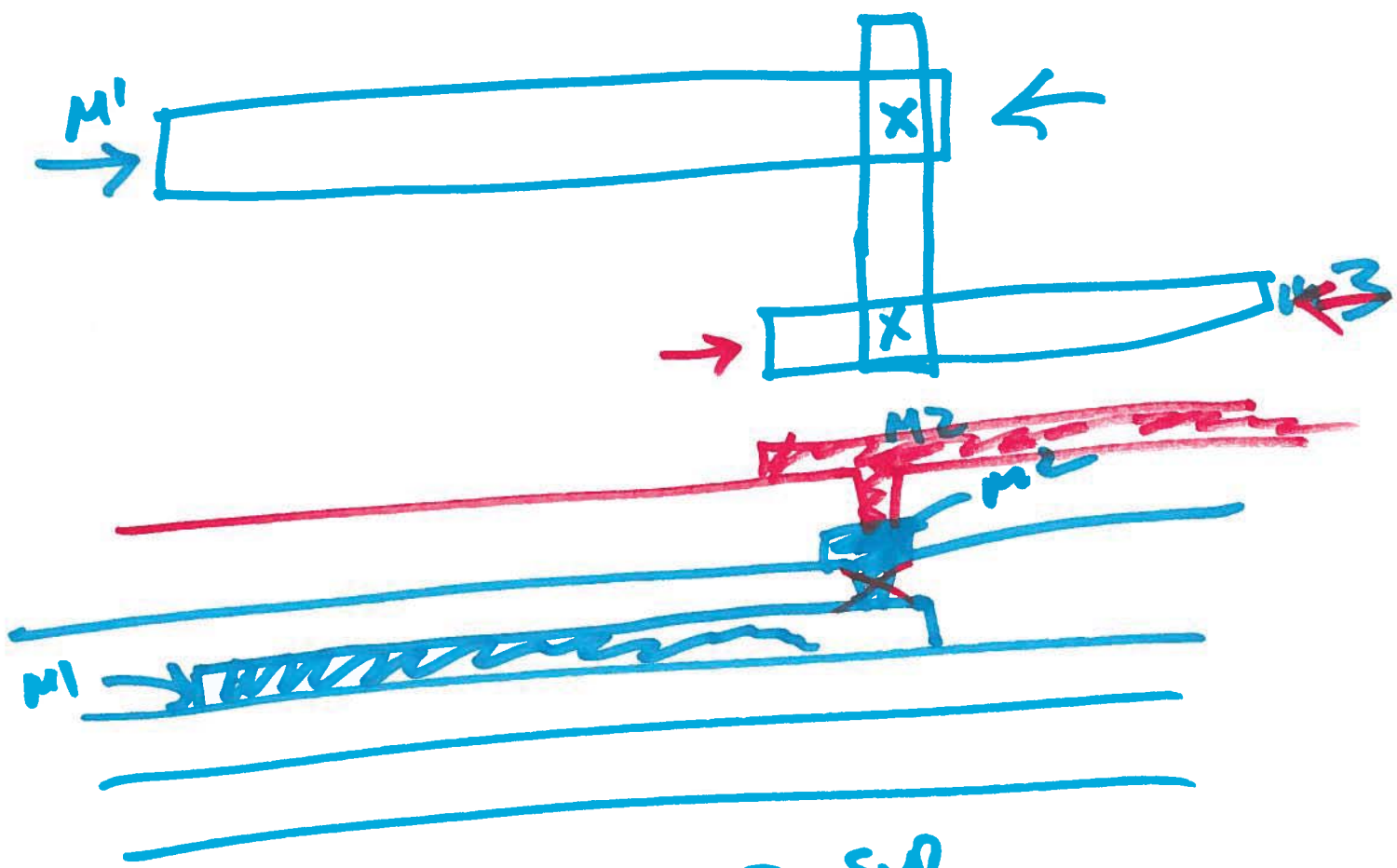

p-sub

6)