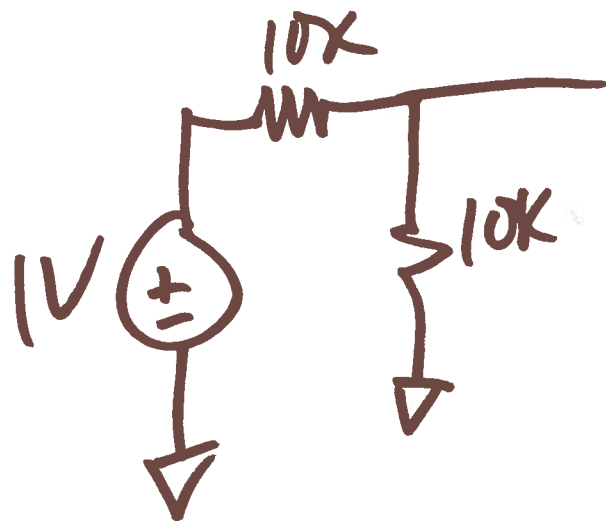


EE 421 / ECG 621

Digital IC Design


Lecture 9

Sept. 28, 2016



$$V_{out} = 1 \cdot \frac{10k}{10k + 10k} = \frac{1}{2}$$
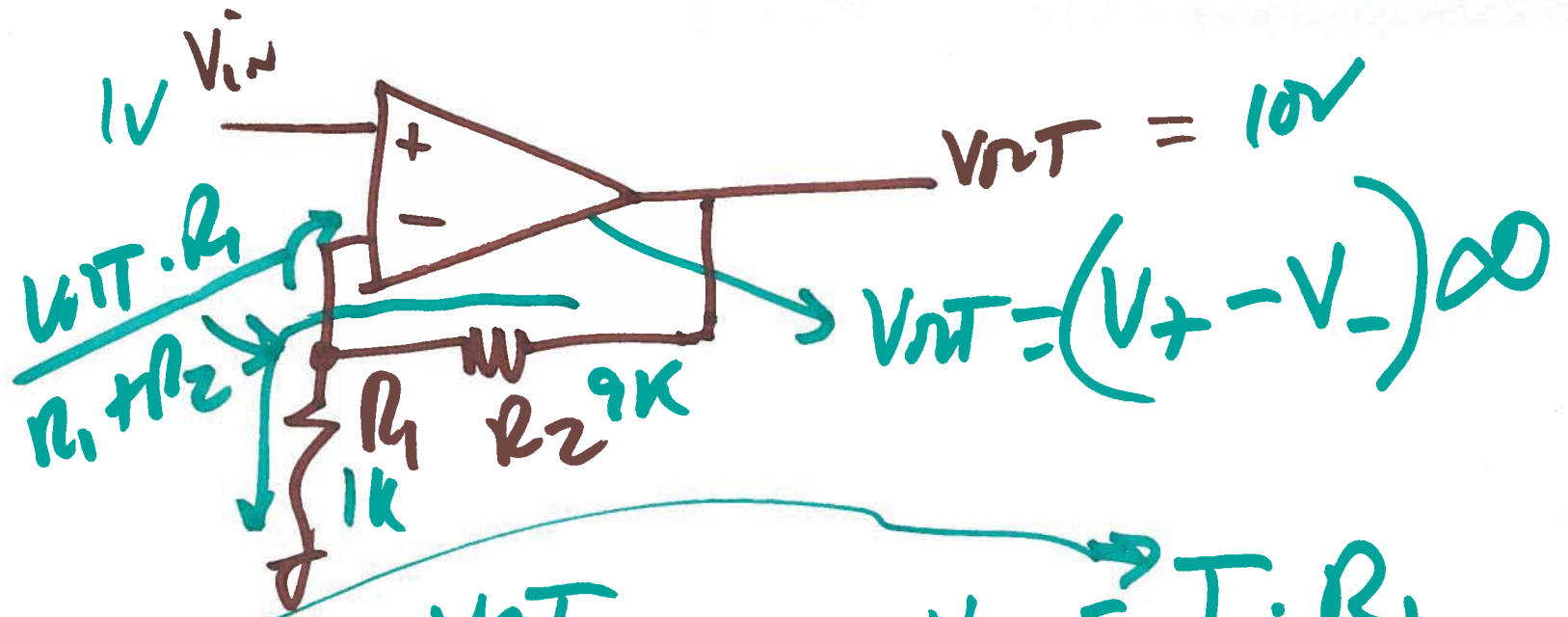
$$= 1 \cdot \frac{12k}{12k + 12k} = \frac{1}{2}$$



$$V_{out} = V_{in} \cdot \infty \frac{1 + \frac{R_1}{R_1 + R_2}}{1 + \frac{R_1}{R_1 + R_2}}$$

$$I = \frac{V_{out}}{R_1 + R_2}$$

$$V_- = I \cdot R_1$$

$$V_- = V_{out} \cdot \frac{R_1}{R_1 + R_2}$$

$$V_{out} = \left(V_{in} - \frac{V_{out} \cdot R_1}{R_1 + R_2} \right) \cdot \infty$$


$$V_{out} \left(1 + \frac{R_1}{R_1 + R_2} \cdot \infty \right) = V_{in} \cdot \infty$$

2)


$$V_{out} = V_{in} \cdot \frac{\infty}{1 + \frac{R_1 \cdot \infty}{R_1 + R_2}}$$

$$V_{out} = \frac{V_{in}}{\cancel{0} + \frac{R_1}{R_1 + R_2}} = V_{in} \cdot \left(\frac{R_1 + R_2}{R_1} \right)$$
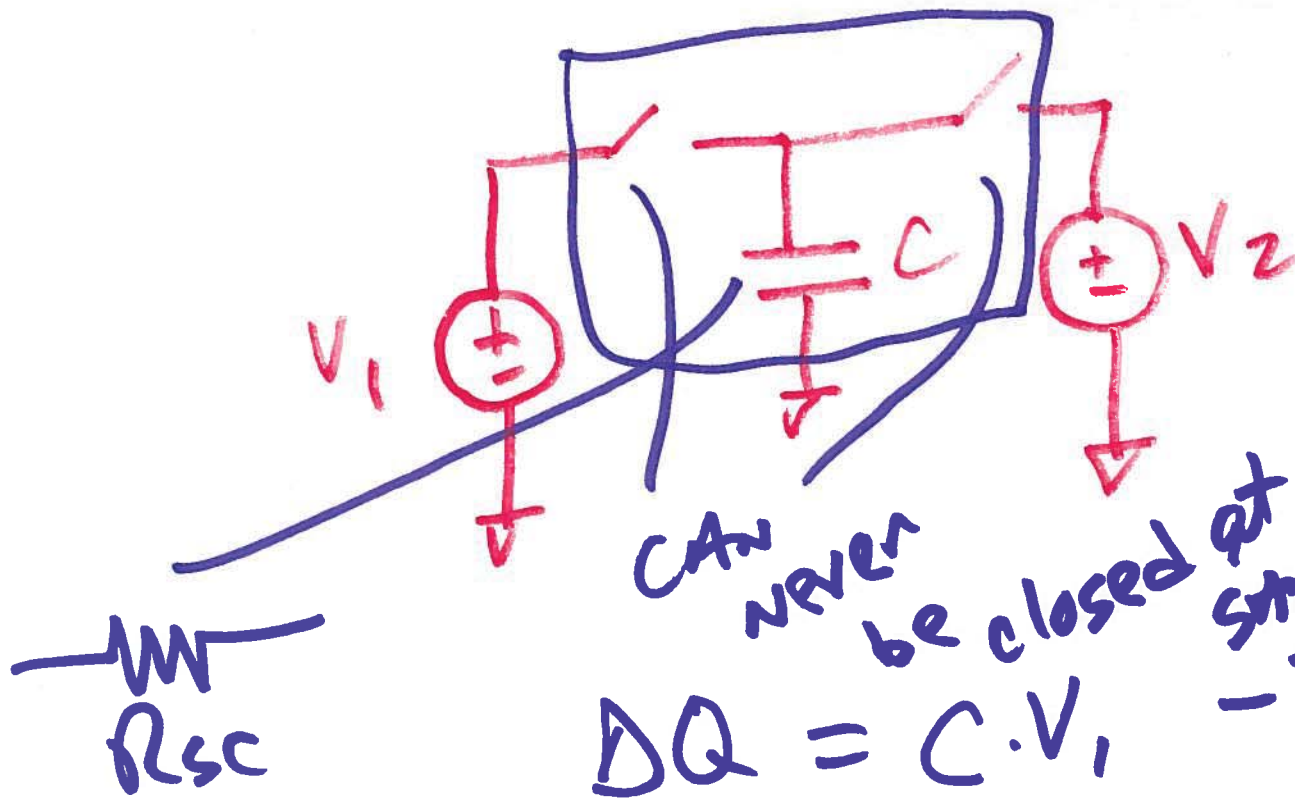
$$V_{out} = V_{in} \cdot \left(1 + \frac{R_2}{R_1} \right)$$



Switched-capacitor


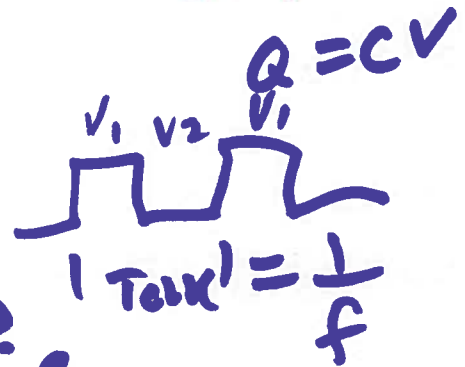


CAN NEVER be closed at same time




$$\Delta Q = C \cdot V_1 - C \cdot V_2$$

$$I_{inv} = \frac{\Delta Q}{T_{clk}} = \frac{C(V_1 - V_2)}{R_{sc} T_{clk}}$$
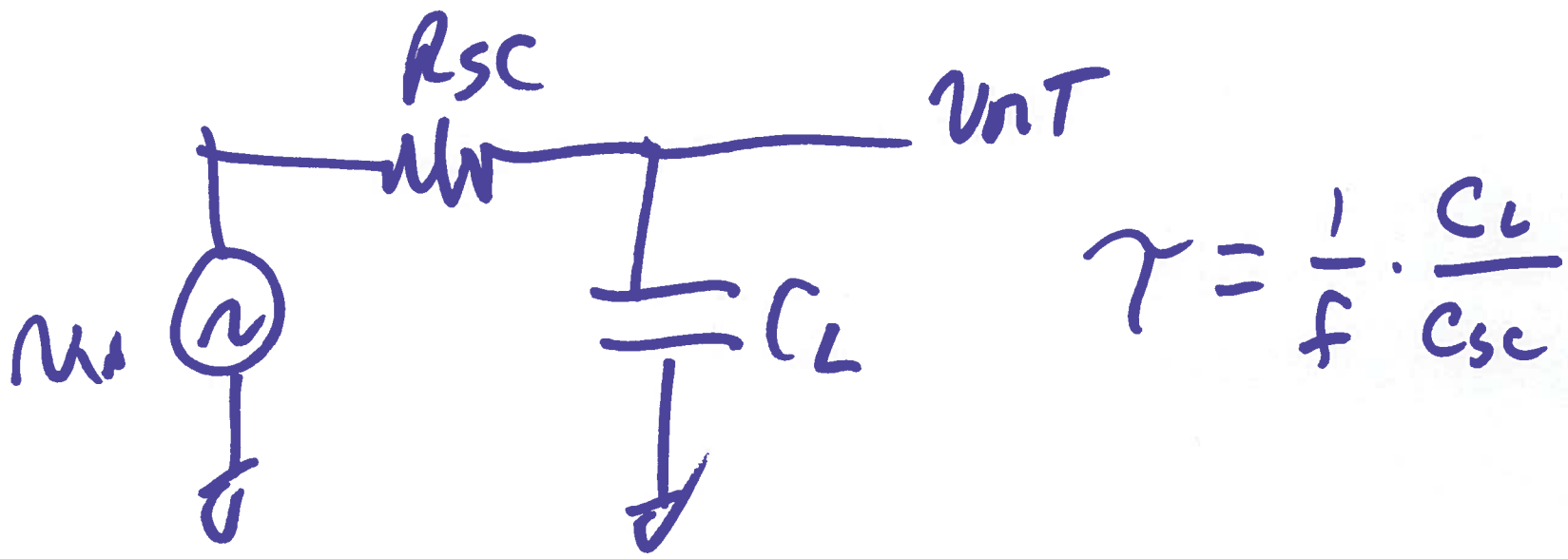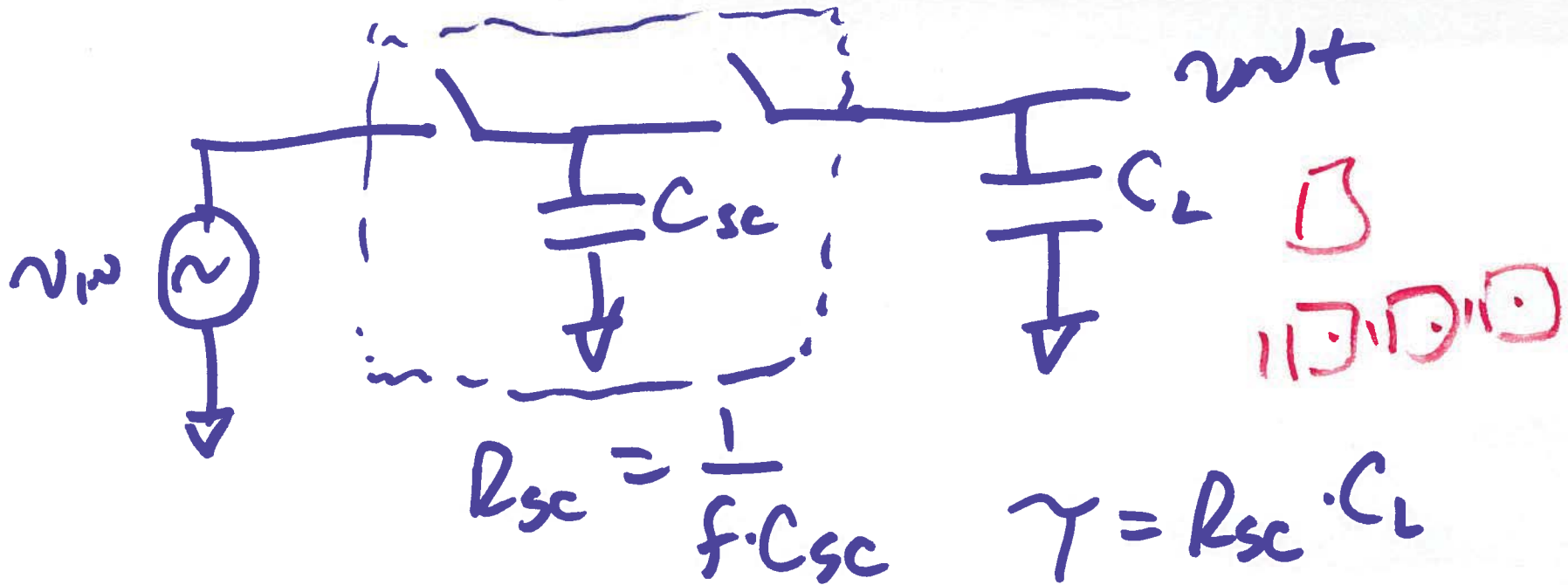
$$V_1 - V_2 = I_{inv} \cdot \frac{1}{fC} \quad \text{or} \quad fC \cdot (V_1 - V_2)$$




$$C = \frac{A \cdot \epsilon}{d}$$

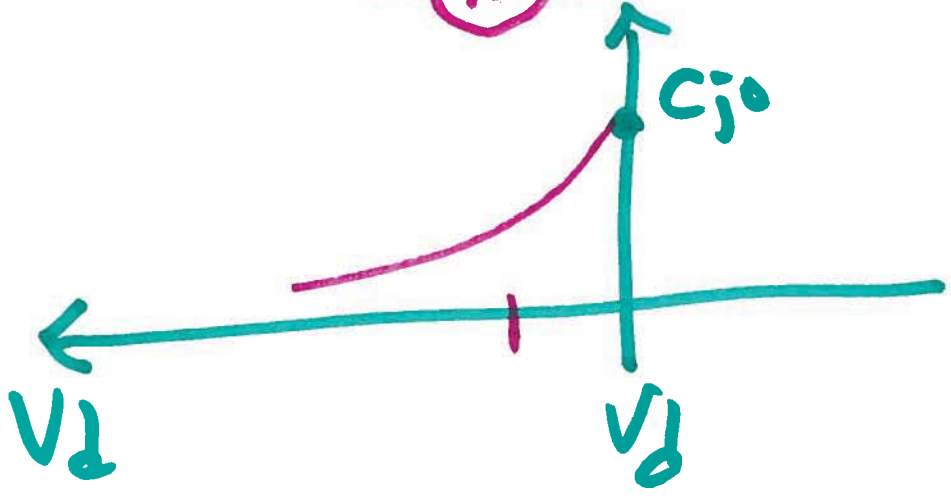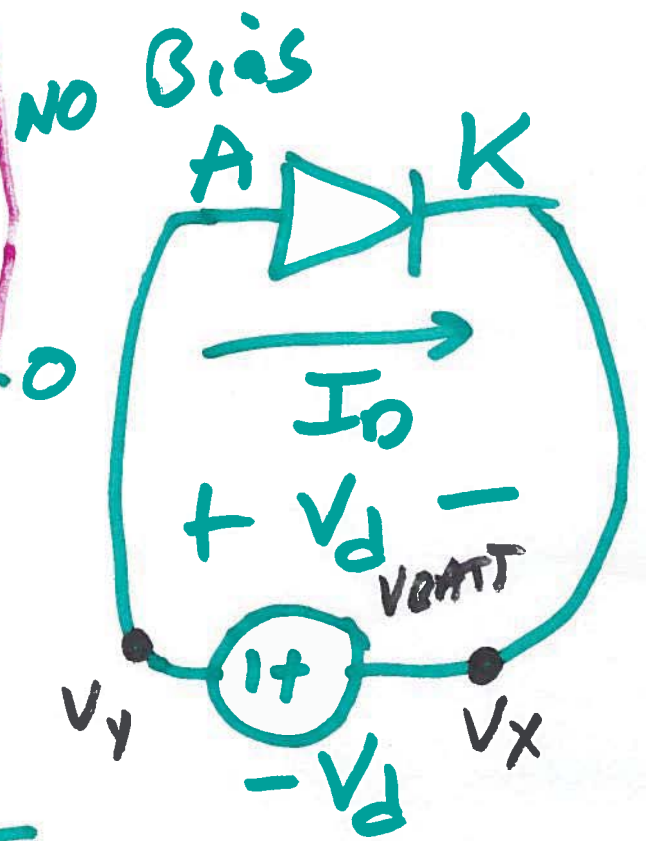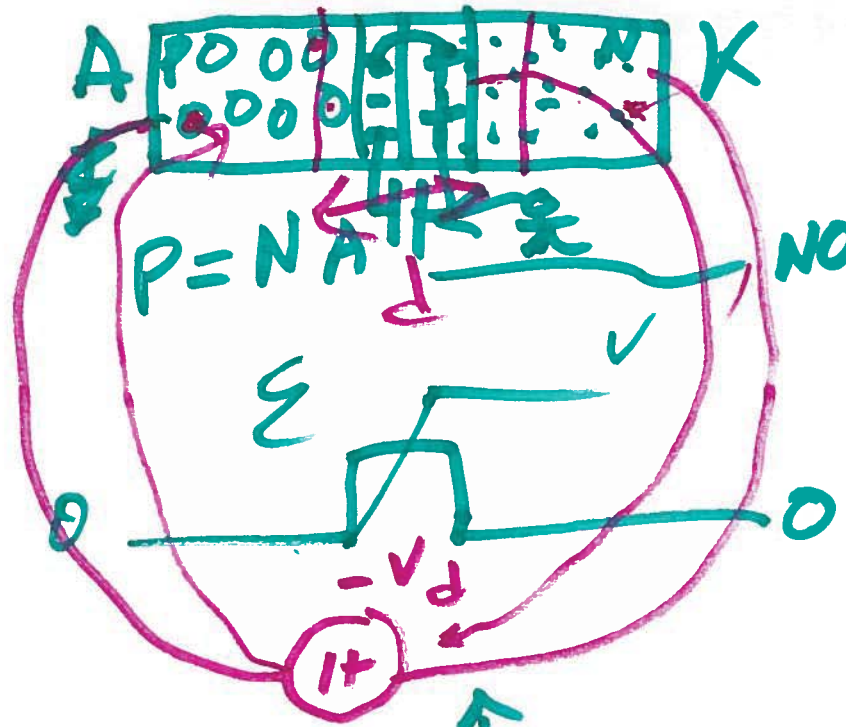

$$V_{BATT} = V_x - V_y$$

$$-V_d = V_x - V_y$$

$$V_d = V_y - V_x$$

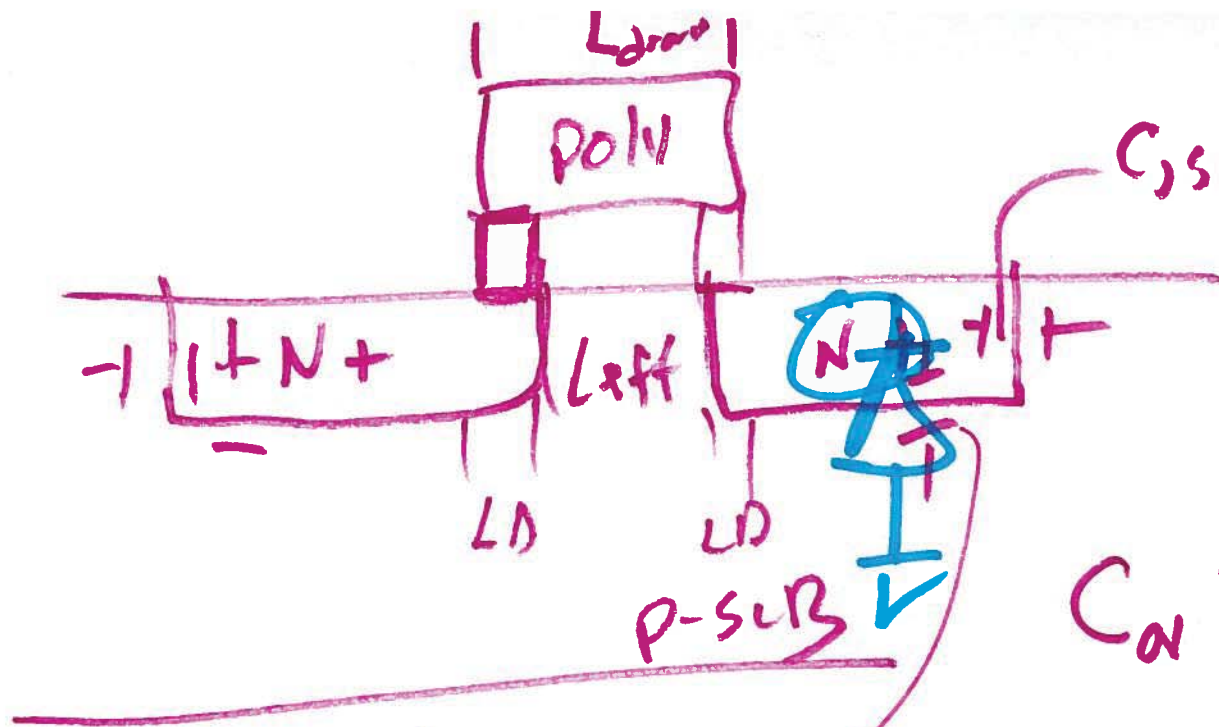



$$C_{sw} = \frac{F}{L_{eff} t_{ox}}$$

$$C_{ox} = \frac{\epsilon_{ox} \cdot L_D \cdot W}{t_{ox}}$$


CGDO
CGSO

$$C_{ox} = C_{GDO} \cdot W$$

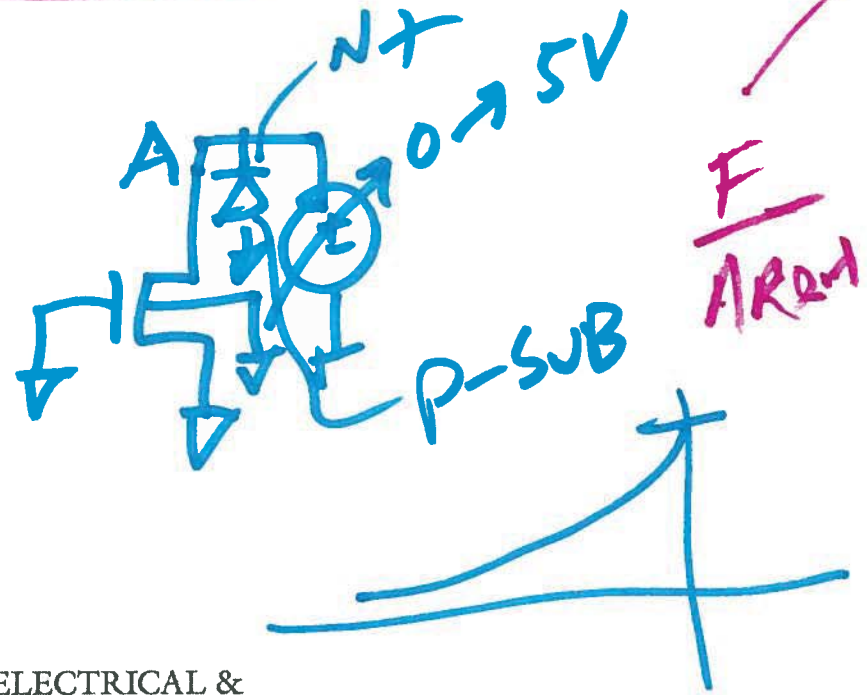

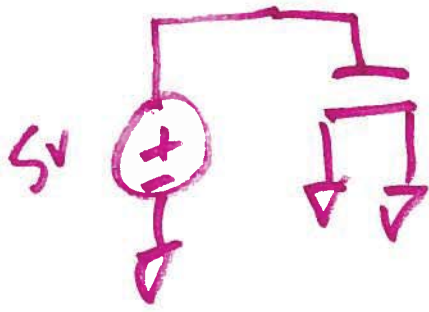


$$C = \frac{\epsilon A}{t}$$

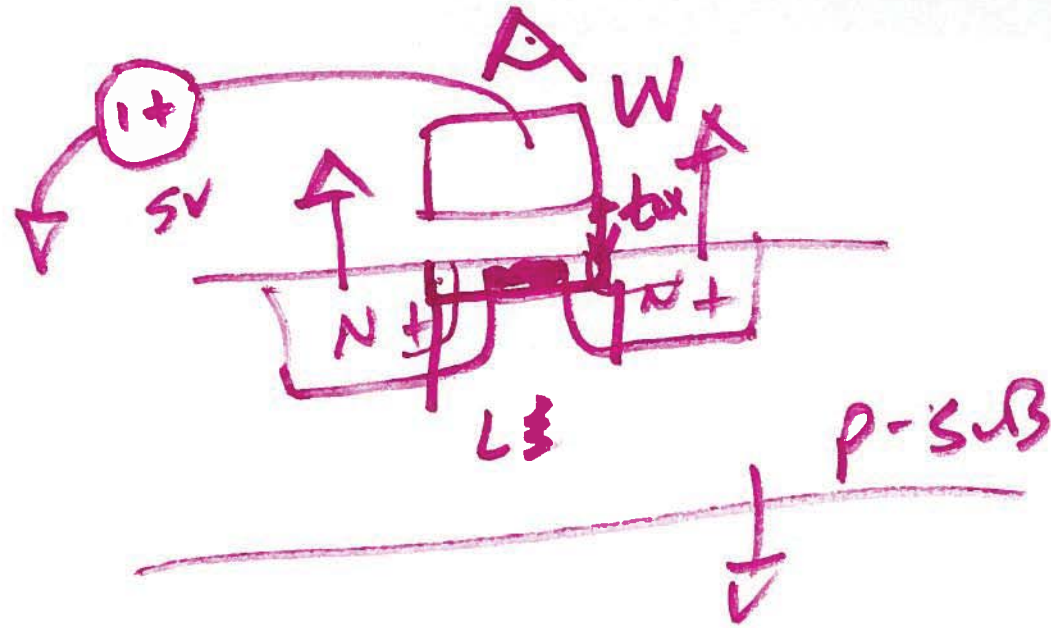

$$\frac{\epsilon_{ox}}{t_{ox}} = \frac{3.97 \cdot 8.85 \text{ aF}/\mu\text{m}}{0.0141 \mu\text{m}} \quad C'_{ox} = \frac{\epsilon_{ox} \cdot L \cdot W}{t_{ox} \cdot L \cdot W} = C'_{ox} \cdot L \cdot W$$
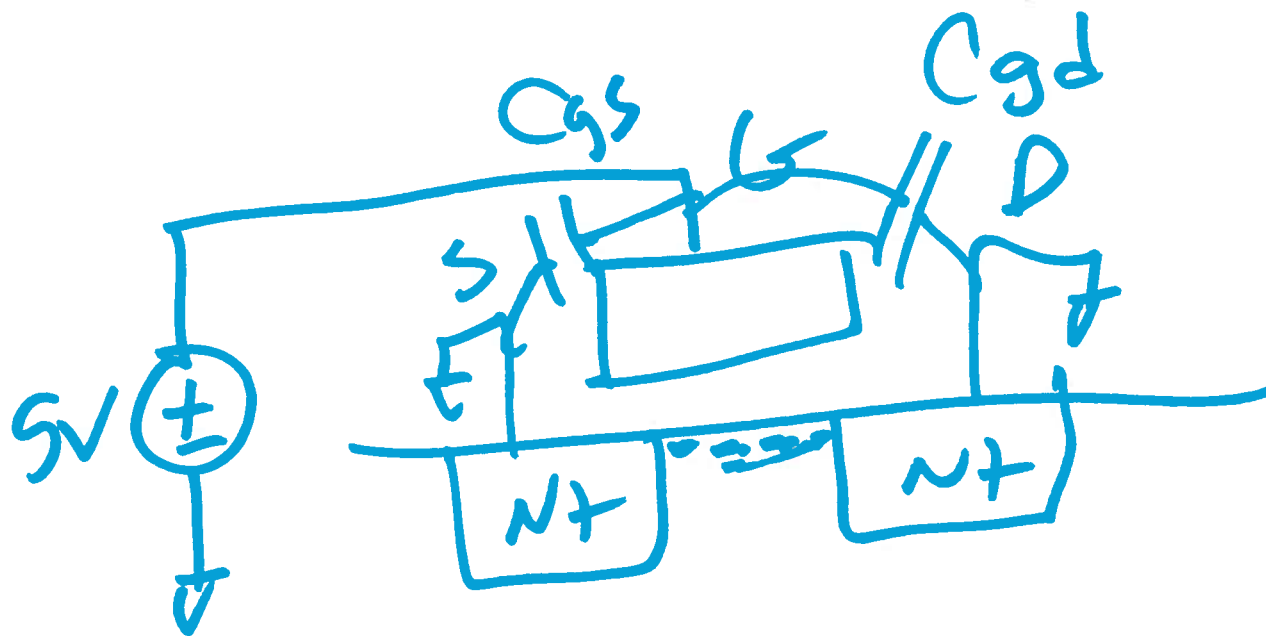
$$= 2.5 \text{ fF}/\mu\text{m}^2 \quad C'_{ox} \left(\frac{F}{\text{Area}} = \frac{F}{\mu\text{m}^2} \right)$$




p-sub

$$C_{ox} = C_{gs} + C_{gd} = C'_{ox} \cdot W \cdot L$$

$$C_{gs} = C_{gd} = \frac{1}{2} C_{ox}$$

a)

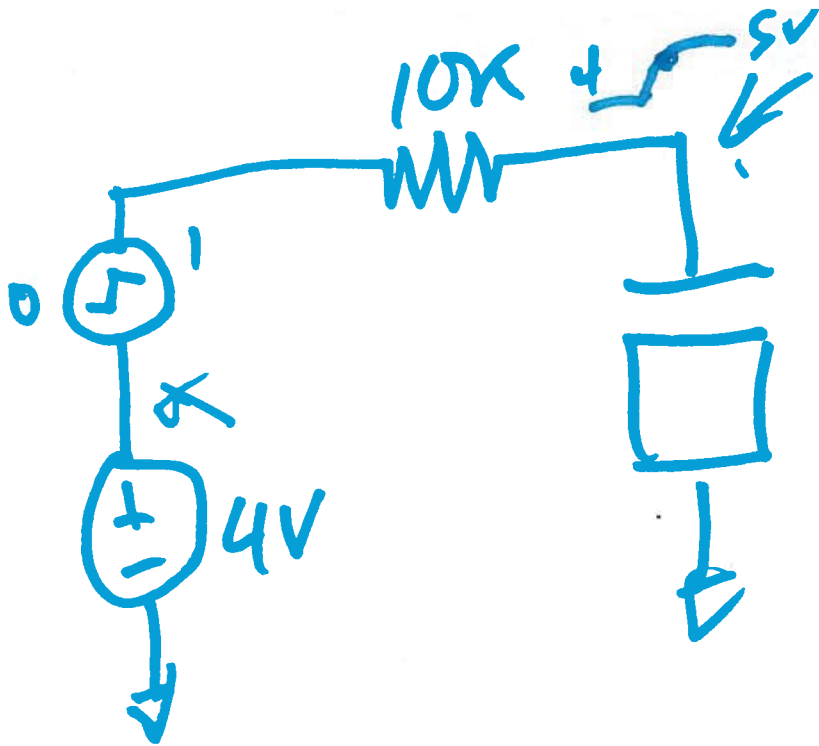

calculate and sketch


$$W \times L$$

$$100\mu \times 100\mu$$

$$W/L = \frac{100}{100}$$

$$\tau = \underline{\underline{250 \text{ ns}}}$$

$$25 \text{ pF}$$

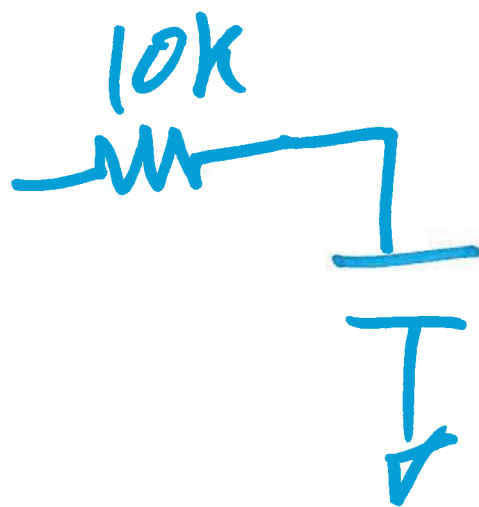

$$100 \mu \times 100 \mu \cdot \frac{2.5 \text{ pF}}{42}$$

$$0.7 \cdot \del{100} \cdot 250 \text{ ns}$$

