

$C_{in}' = 7.5 \text{ fF} / \mu\text{m}^2$  EE 421 / ECG 621


$R_p' = 40\text{k}$   
 $R_i = 20\text{k}$

NOV. 15, 2017

Lecture 22



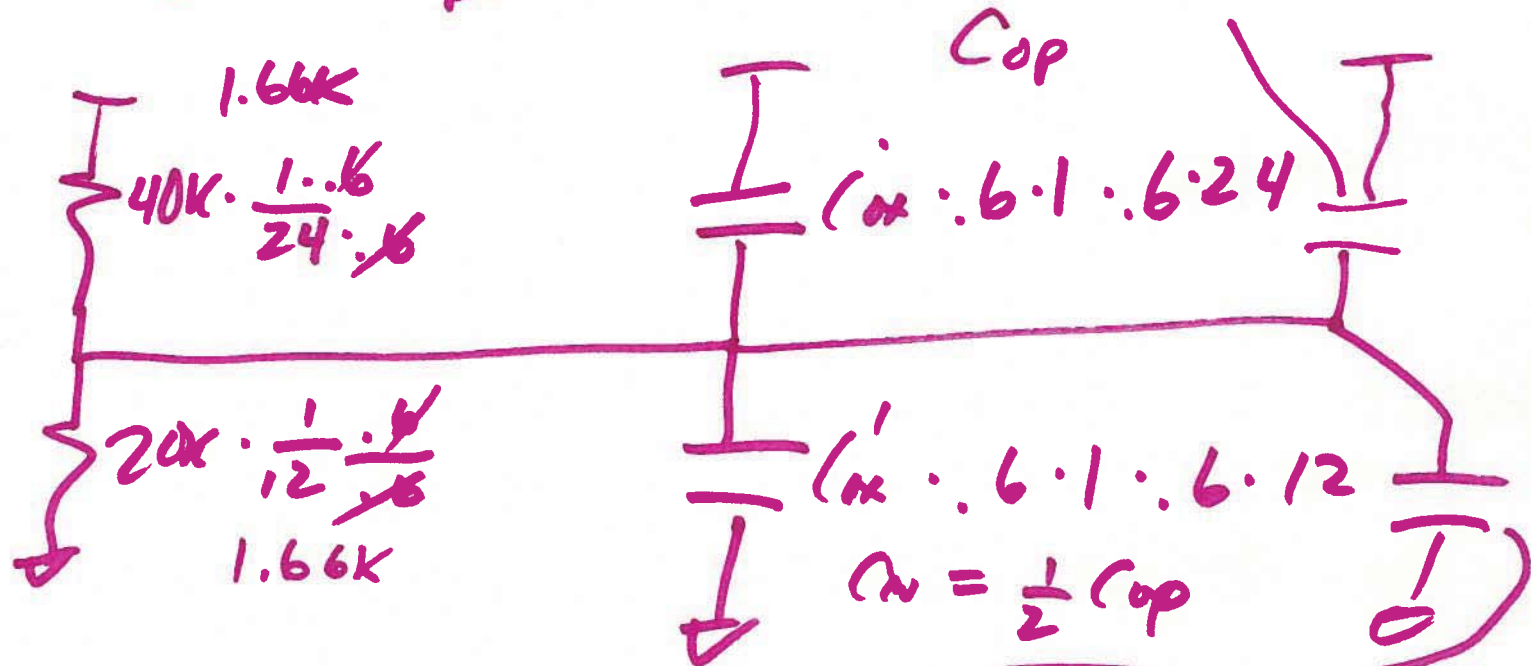$\frac{3}{2} C_{in}' \cdot 6 \cdot 1 \cdot 6 \cdot 96$



$\frac{3}{2} C_{in}' \cdot 6 \cdot 1 \cdot 6 \cdot 48$

1)

Quiz 12 – EE 421/ECG 621 Digital Electronics and Digital IC Design, Fall 2017



NAME: \_\_\_\_\_

**Open** book and closed notes.

Show your work for credit!


Assume the C5 process is used with lengths of 600 nm,  $R'_n = 20k$ ,  $R'_p = 40k$ , and  $C'_{ox} = 2.5 \text{ fF}/\mu\text{m}^2$

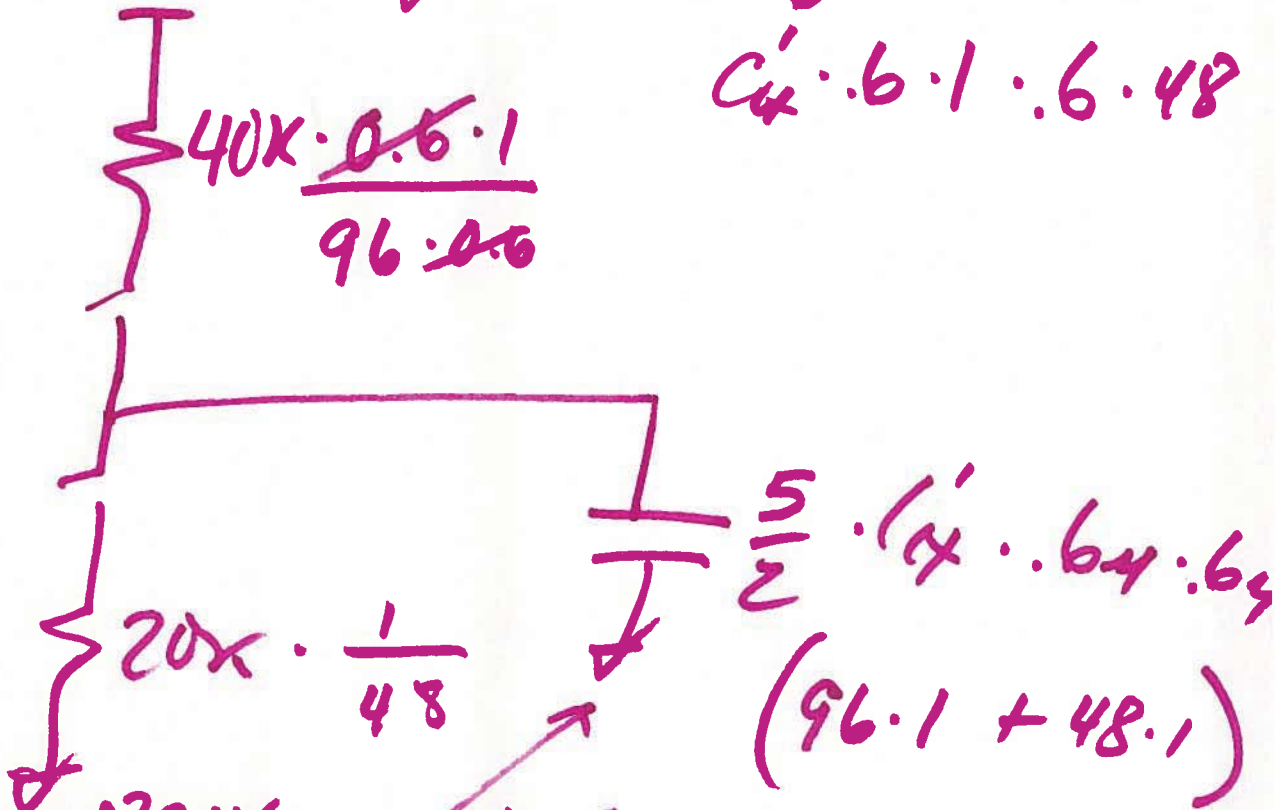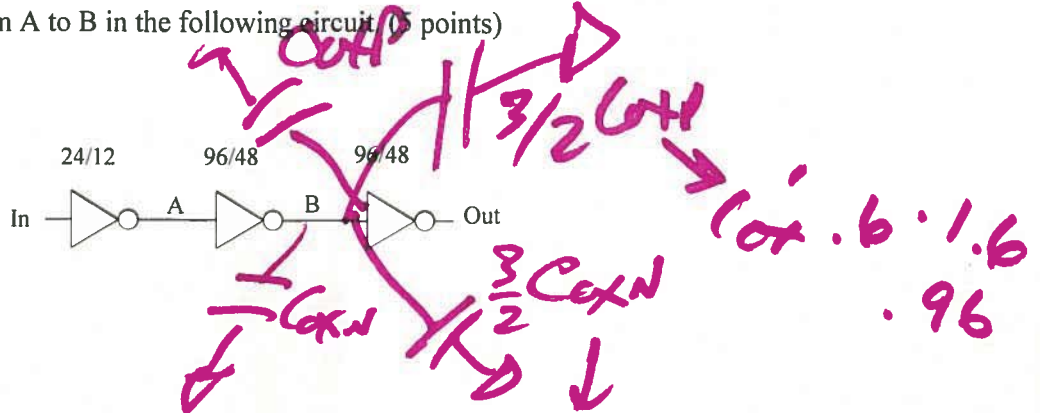1. Estimate the delay from A to B in the following circuit (5 points)




$$t_{pHL} = 0.7 \frac{20k}{48} ( )$$

$$2) t_{pLH} = 0.7 \frac{40k}{96} ( )$$

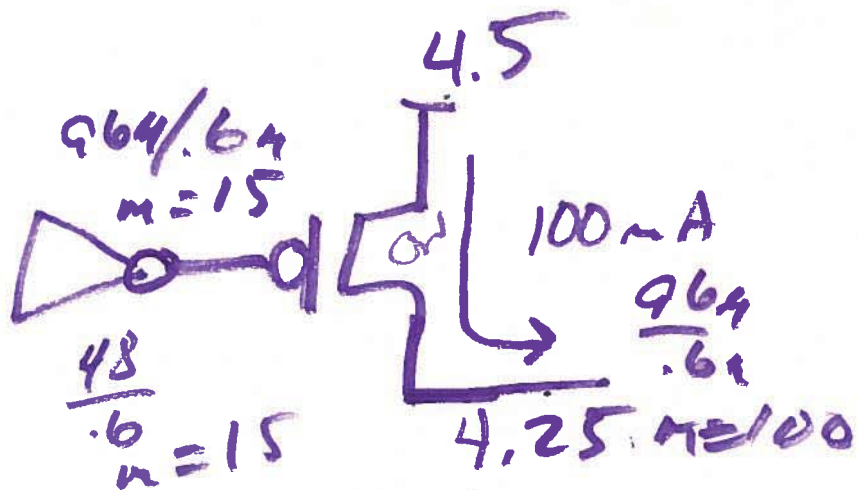

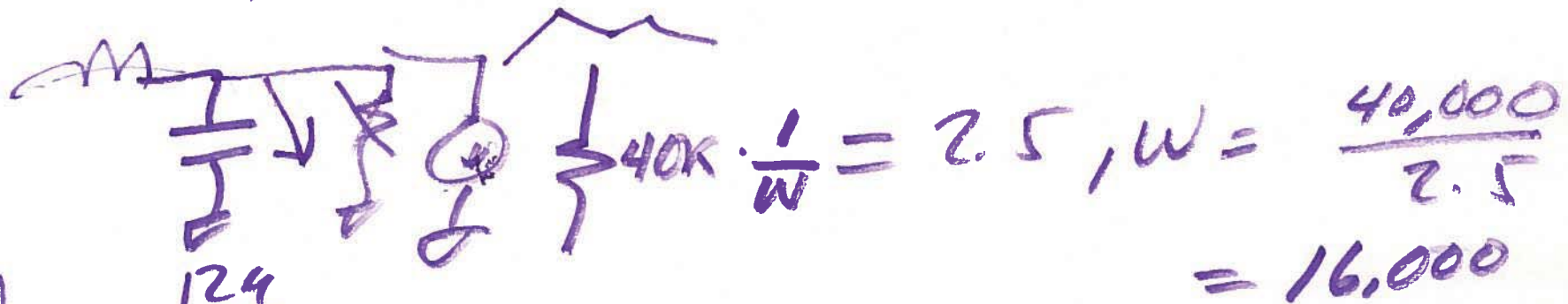
$$\frac{4.5 - 4.25}{0.1 \text{ A}} = \frac{.25}{.1} = 2.5 \Omega$$



$$40 \text{ K} \cdot \frac{1}{W} = 2.5, W = \frac{40,000}{2.5} = 16,000$$

1A  
1A

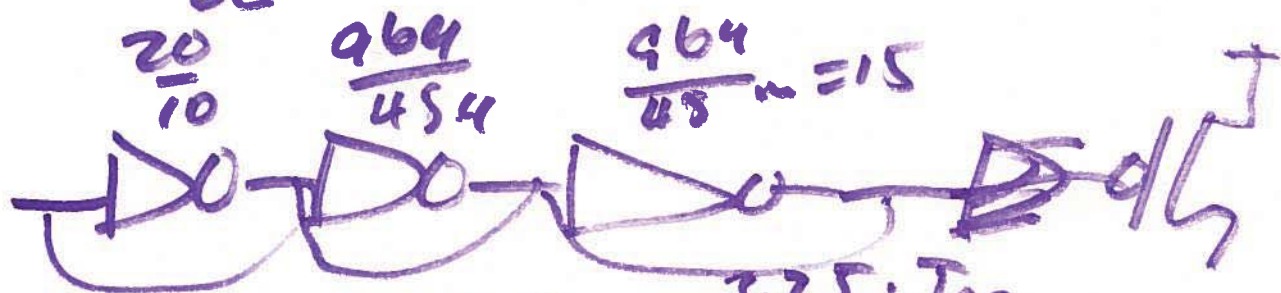

$$n=100$$



$$W=160$$

$$W=\underline{\underline{96 \mu\text{m}}}$$

$$\% \varepsilon = \frac{3.75 \cdot I_{oc}}{V_{DD} \cdot R_{ns} I(V_{DD})}$$




3)

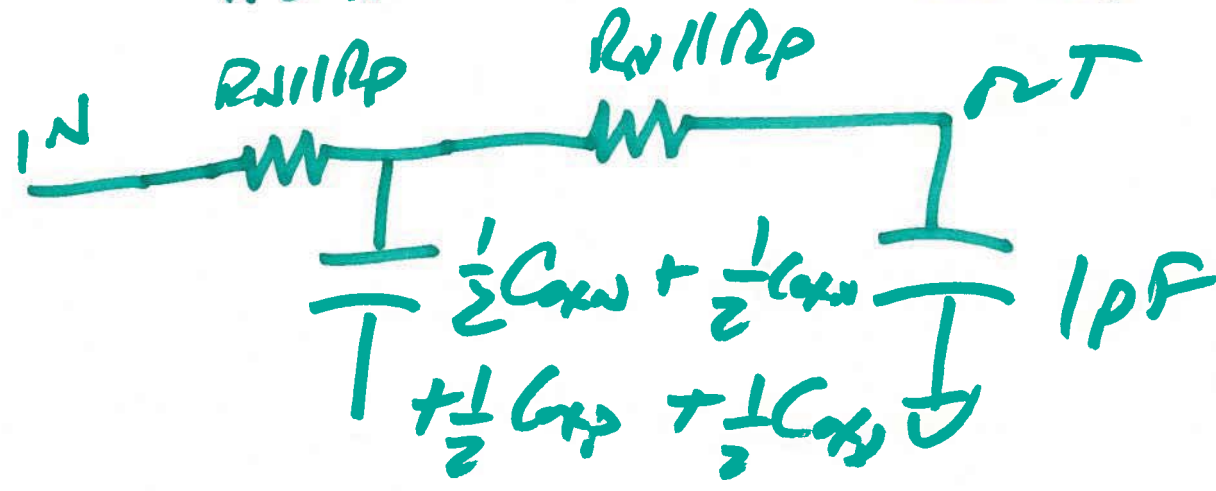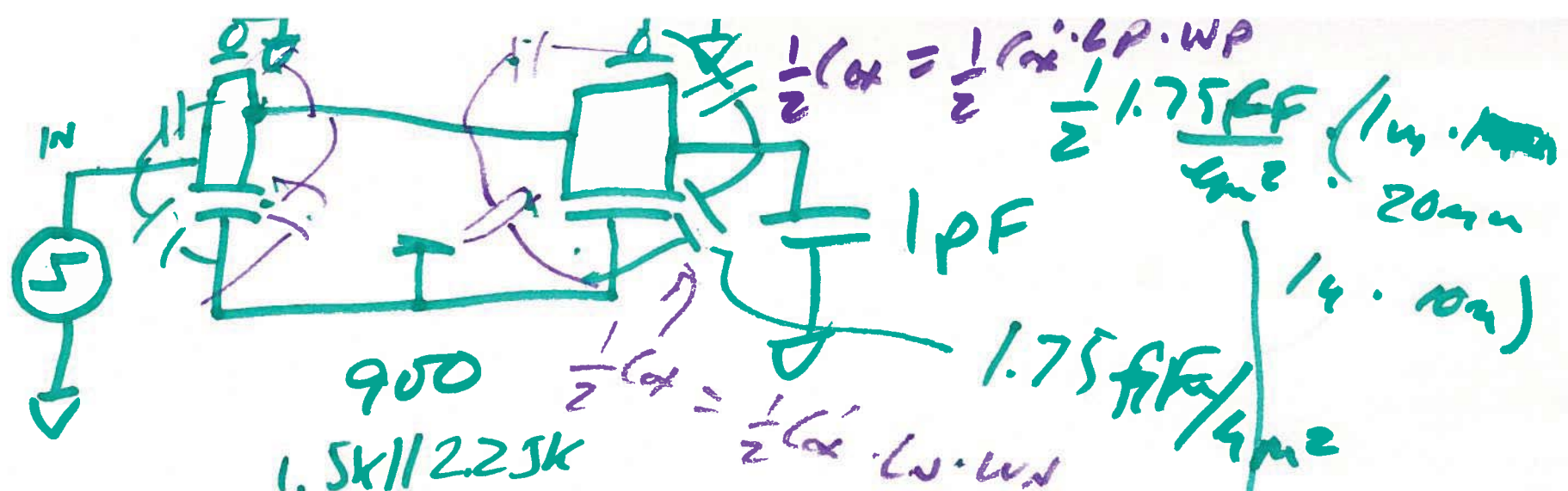

$$t_d = 0.7(900 + 900) \cdot (1pF + \dots) + 0.7 \cdot 900 \cdot (C_{oxp} + C_{oxn})$$

4)

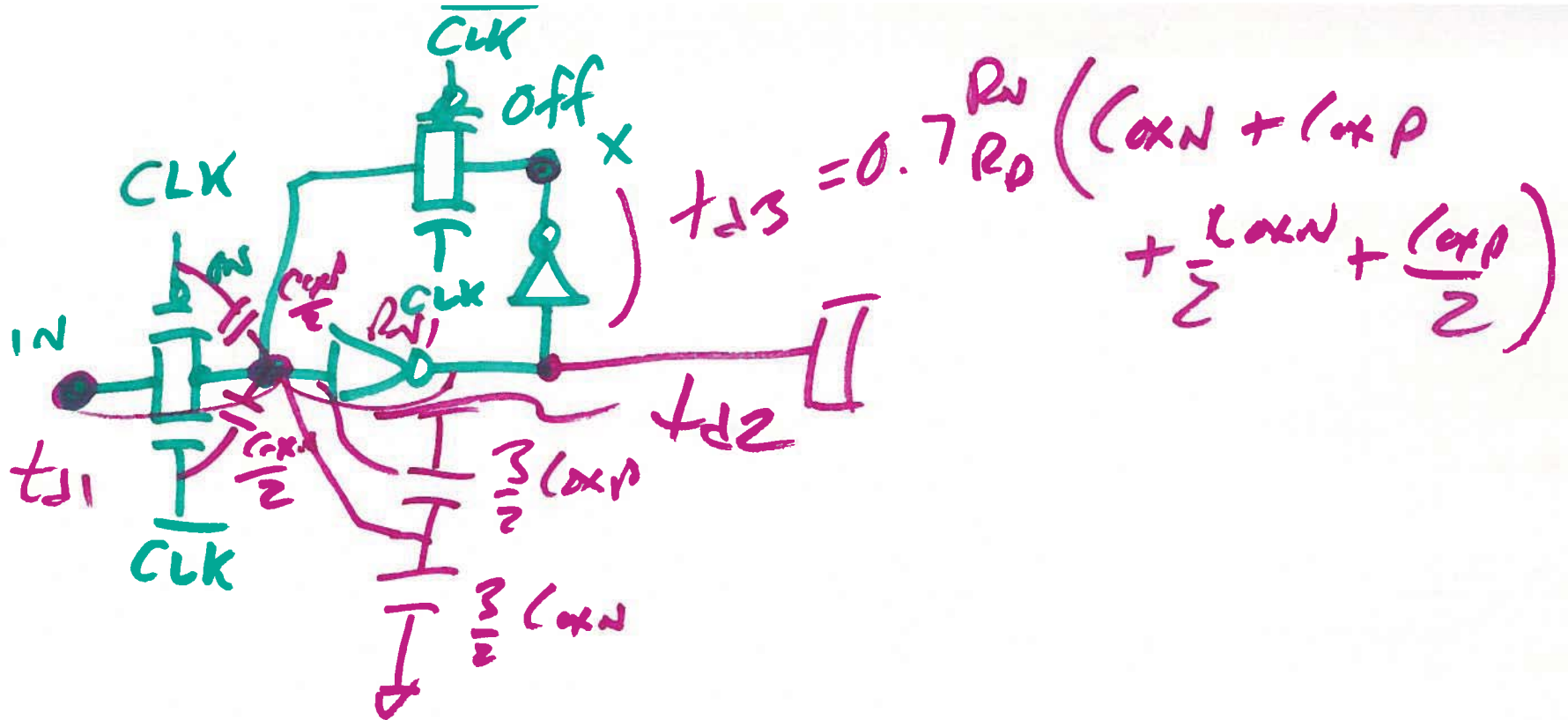



$$t_{D1} = 0.7 R_{N1} \parallel R_P \cdot \left( \frac{C_{oxP}}{2} + \frac{C_{oxN}}{2} + \frac{3}{2} C_{oxP} + \frac{3}{2} C_{oxN} \right)$$

$$t_{D2} = 0.7 R_{N1} \cdot \left( C_{oxP} + C_{oxN} + \frac{3}{2} C_{oxP} + \frac{3}{2} C_{oxN} \right)$$

PHL                      ↓  
 PLH                      R<sub>P1</sub>

$+ \frac{C_{oxN}}{2} + \frac{C_{oxP}}{2}$


5)

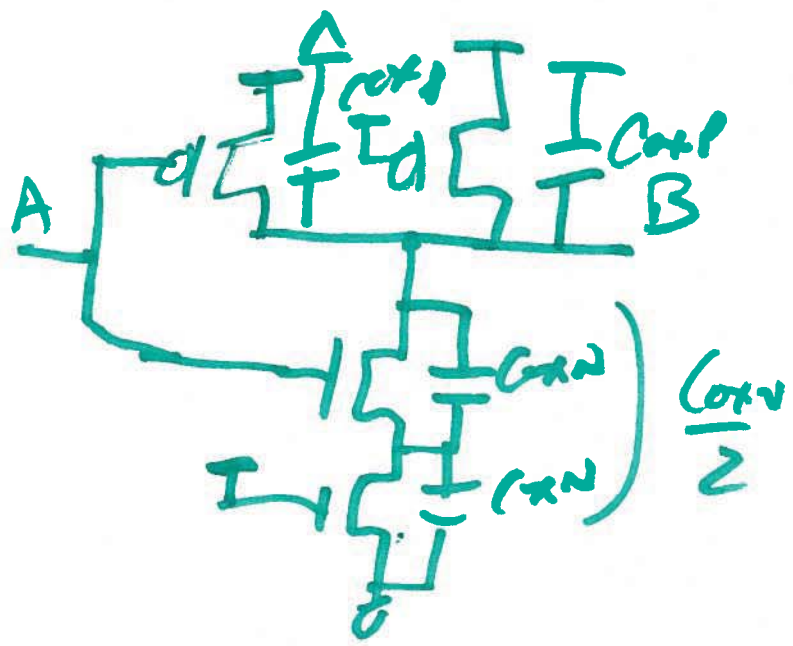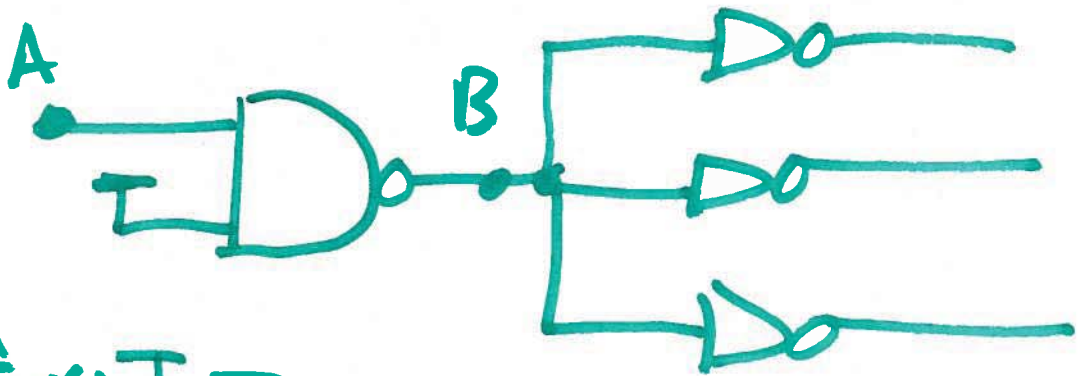

$$t_{PHL} = 0.7 \cdot 2 \cdot R_N \cdot ($$

$$t_{PLH} = 0.7 \cdot R_P \cdot (2C_{oxP} + \frac{C_{oxN}}{2} + 3 \cdot \frac{3}{2} (C_{oxP} + C_{oxN}))$$

6)

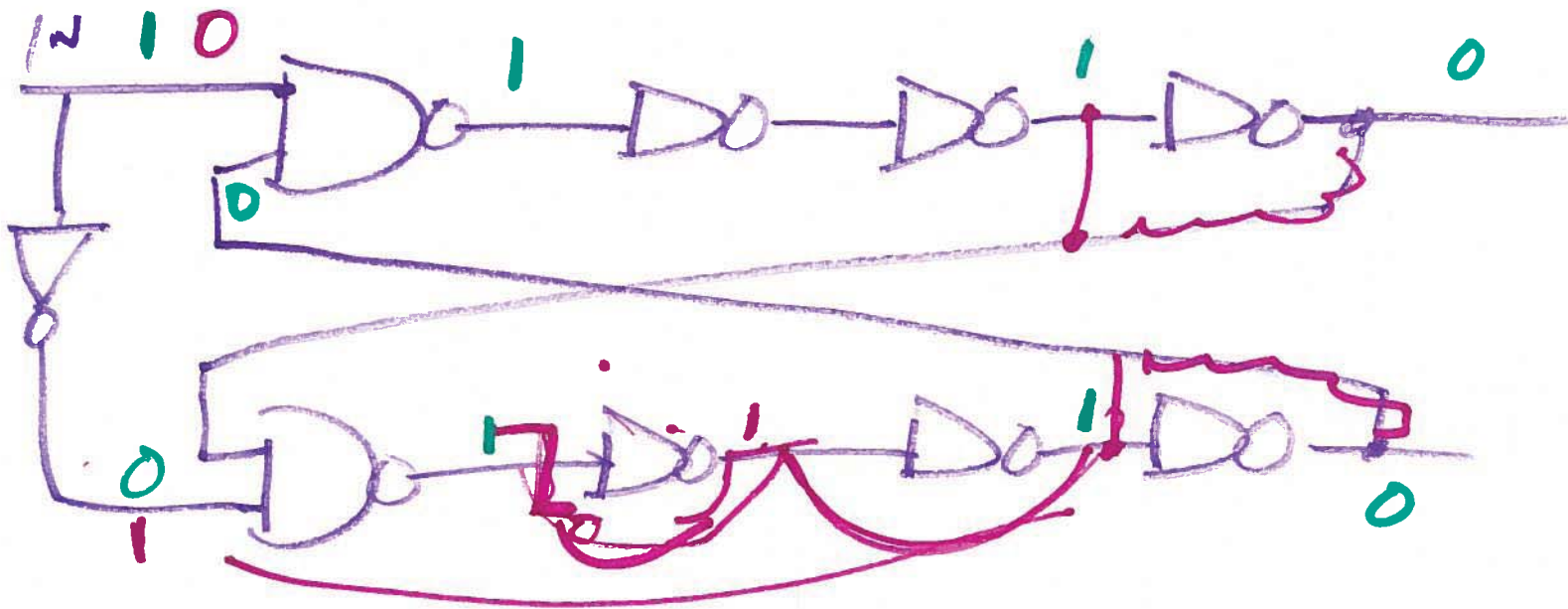

$$\begin{aligned}
 t_{PHL} &= 0.7 \cdot 2R_N \left( 2C_{out} + \frac{C_{in}}{2} + \frac{3}{2} \left( C_{in} + \frac{R_P}{R_N} C_{out} \right) \right) \\
 &+ \frac{3}{2} 0.7 R_P \cdot \left( C_{out} + C_{in} + \frac{3}{2} C_{in} + \frac{3}{2} C_{out} \right) \\
 &0.7 R_N \left( \downarrow \right)
 \end{aligned}$$