

cm/s, EE 421 / ECG 621

$$\mu_N = \frac{\text{velocity}}{\text{Electric field}}$$

v/c

Lecture 10

Sept. 26, 2018




$R(T)$



$$R = \frac{1}{q(N_A \mu_p + N_D \mu_n)}$$


electron density
of holes
hole density

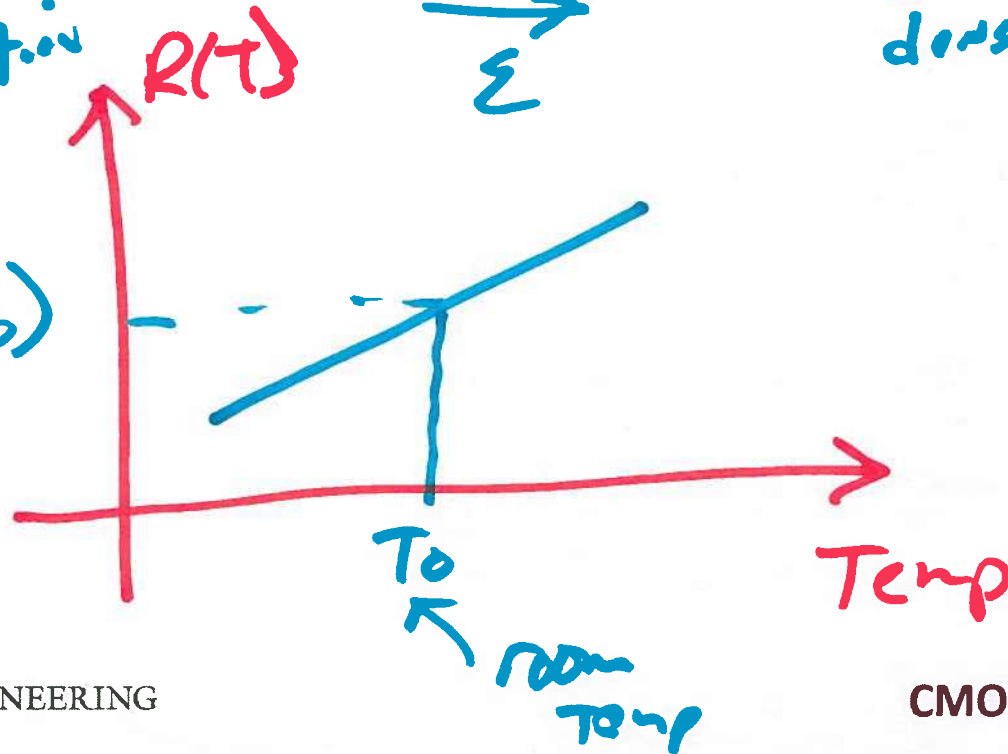$N = \text{electron concentration}$
 $= N_D \rightarrow N_i$




Si \leftarrow
No dopants

11)

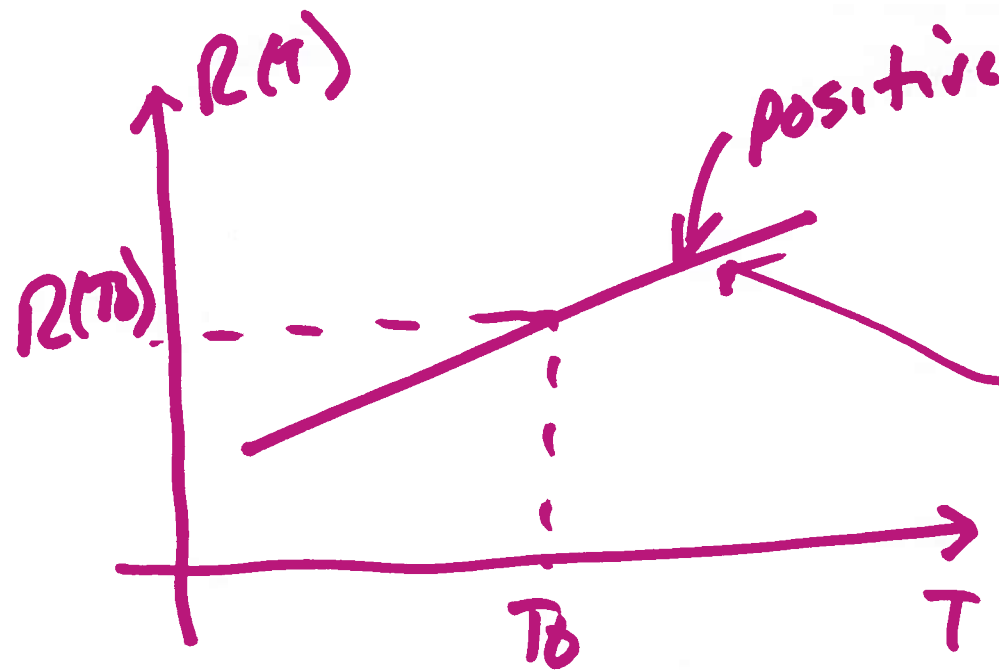


$$R(T) = R(T_0) (1 + \alpha(T - T_0))$$


$$= R(T_0) (1 + \text{TCR}(T - T_0))$$

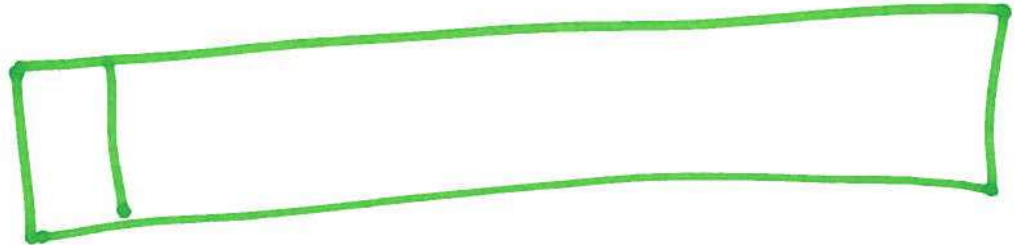



2)

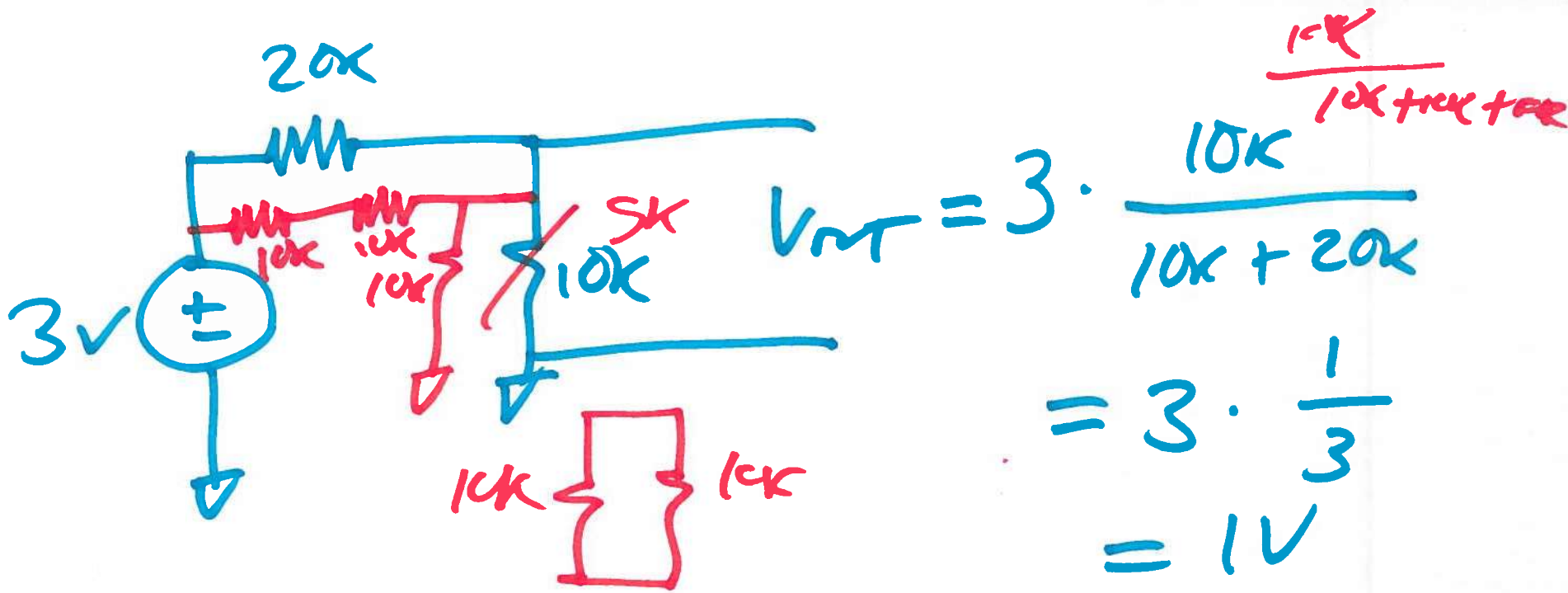

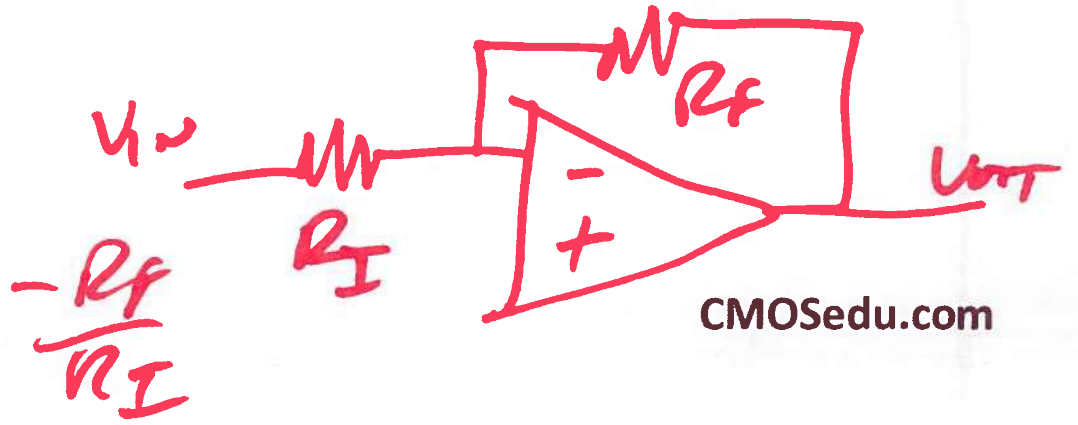$V_{out} = 3 \cdot \frac{10k (1 + \cancel{10k} (1 - 10))}{10k (1 + \cancel{10k} (1 - 10)) + \cancel{10k} (1) + 10k (1)}$
 $= 1V$





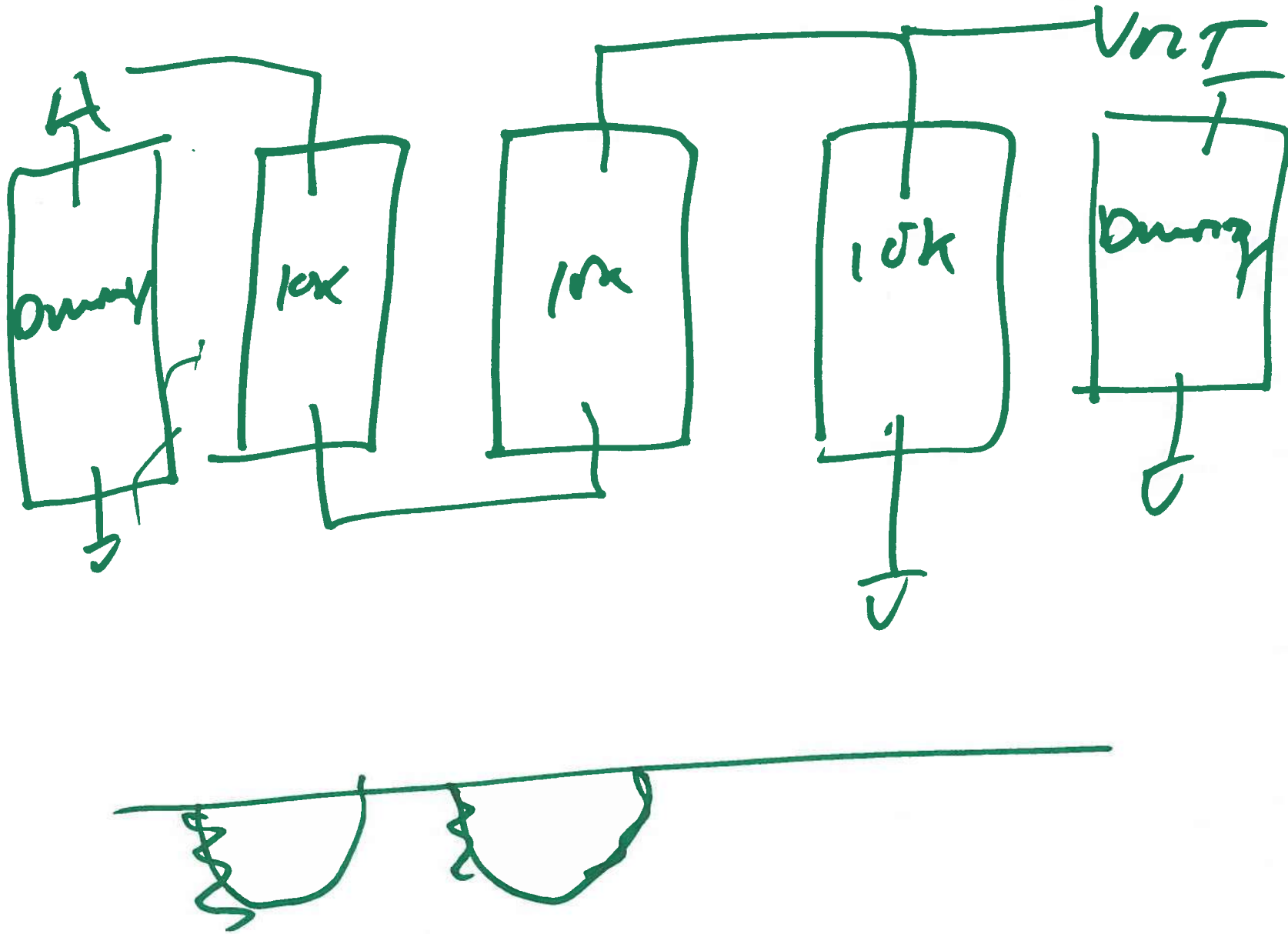

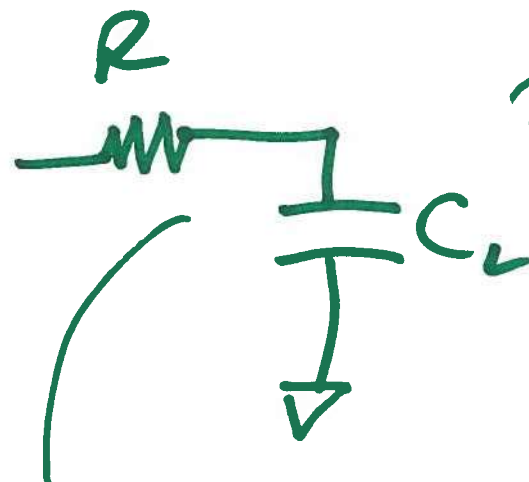

$$f_{3dB} = \frac{1}{2\pi RC_L}$$

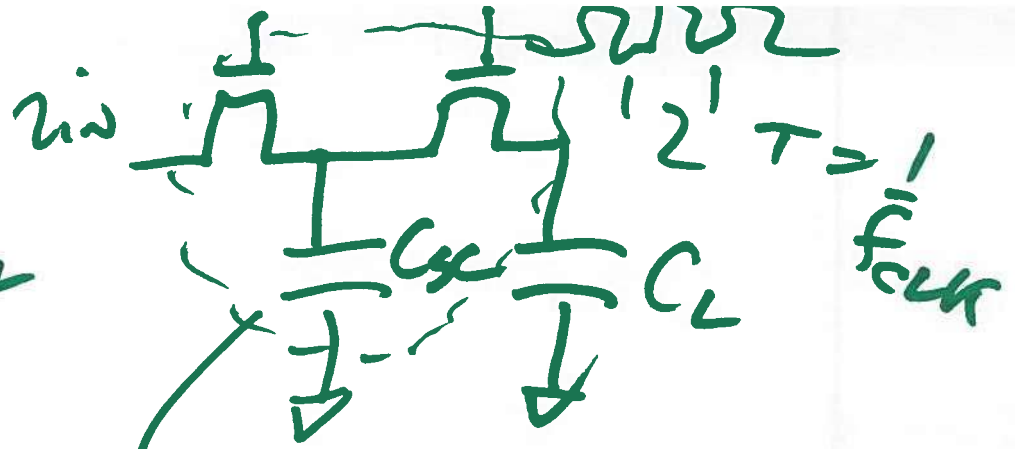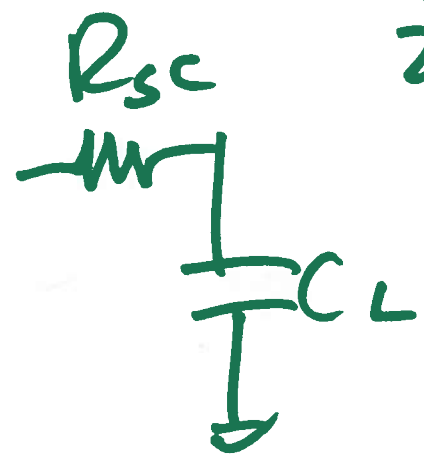
$$\frac{1}{2\pi f \cdot C_L} = \frac{R_{sc}}{f_{clk} \cdot C_{sc}}$$



Switched-Capacitor Resistor


$$R_{sc} = \frac{1}{f_{clk}}$$



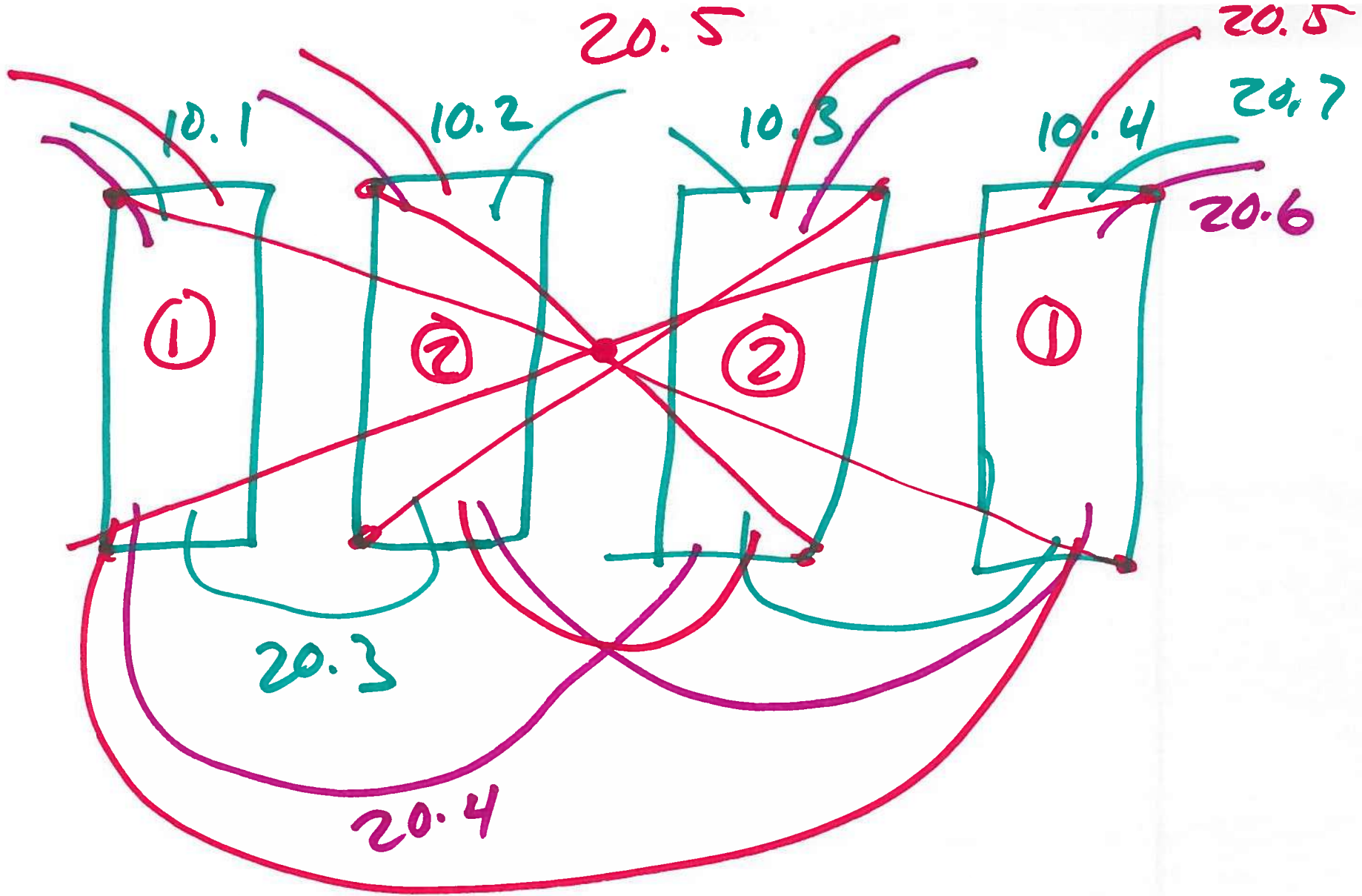


b)

$$C = \epsilon_{ox} \cdot \frac{A}{d}$$

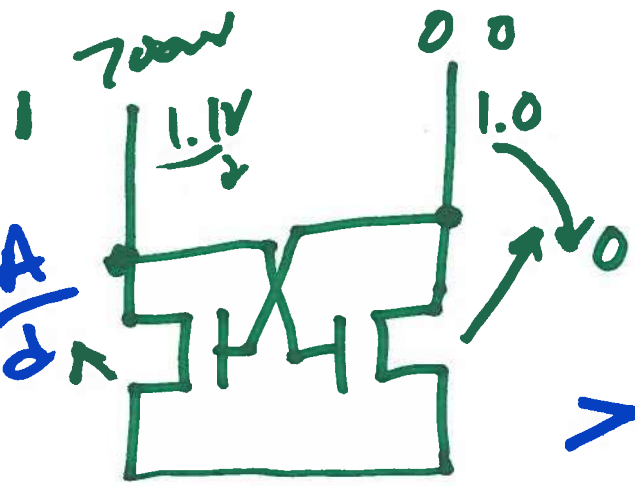

$$C = \frac{W \cdot L \cdot \epsilon_{ox}}{t_{ox}}$$

C_{ox}

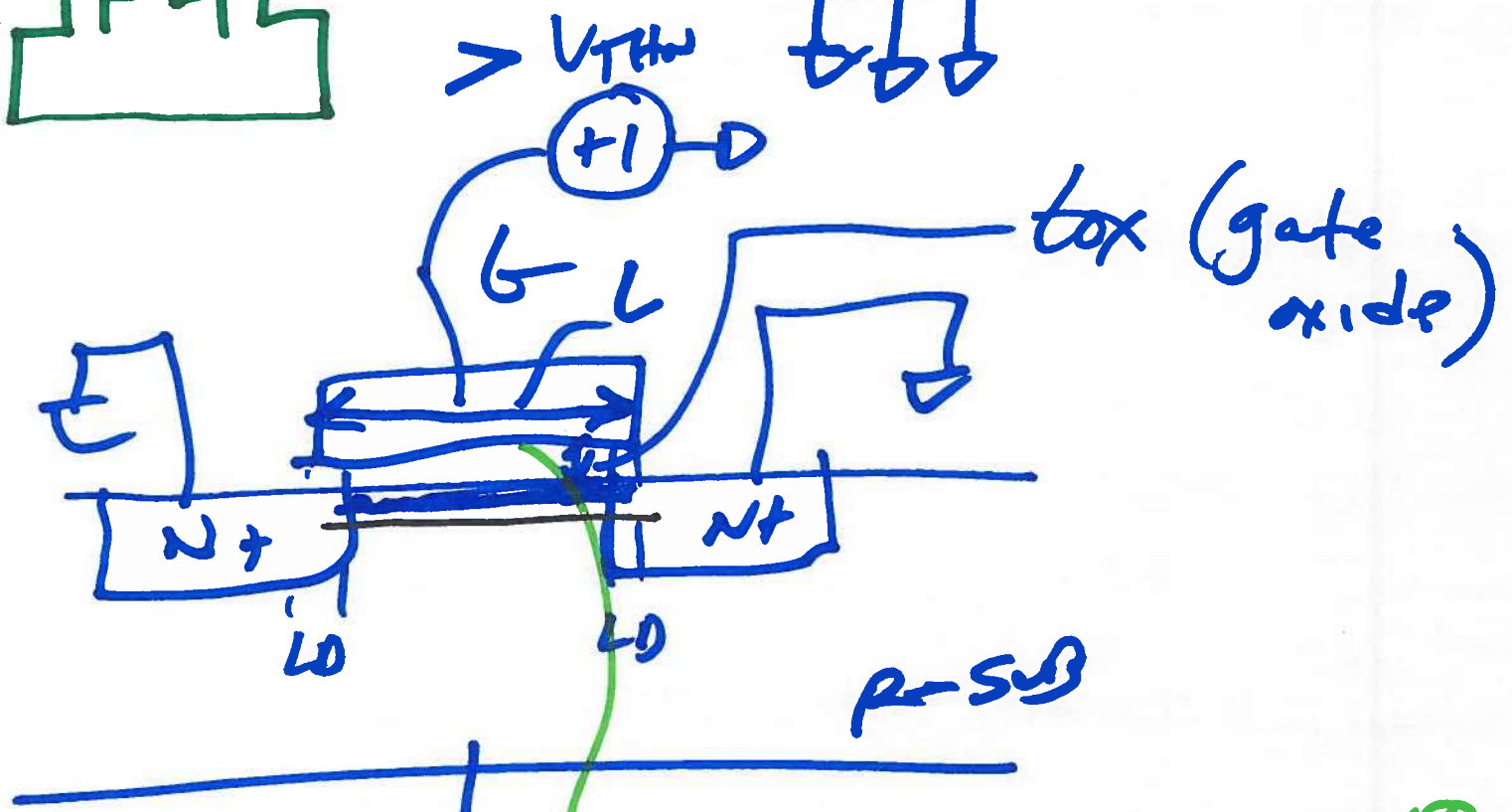

$$\epsilon_{ox} = 3.9 \cdot 8.85 \times 10^{-18} \frac{F}{\mu m}$$

ϵ_0