

EE 421 / ECG 621


Digital IC Design

Lecture 134

OCT. 17, 2018


$$-\frac{R_E}{R_{IN}}$$

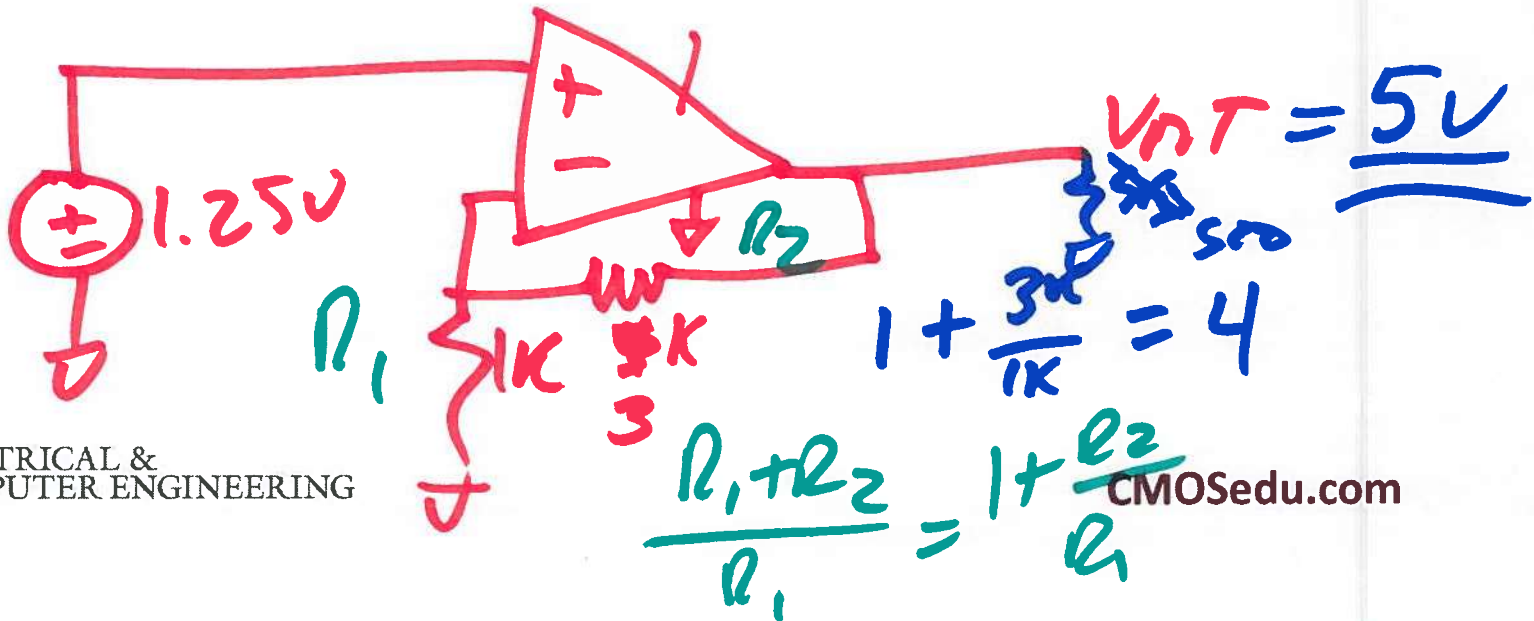BOOST Linear Power SUPPLY 6-7 Switching Power supply (SPS)



1)

Power Management IC
PMIC

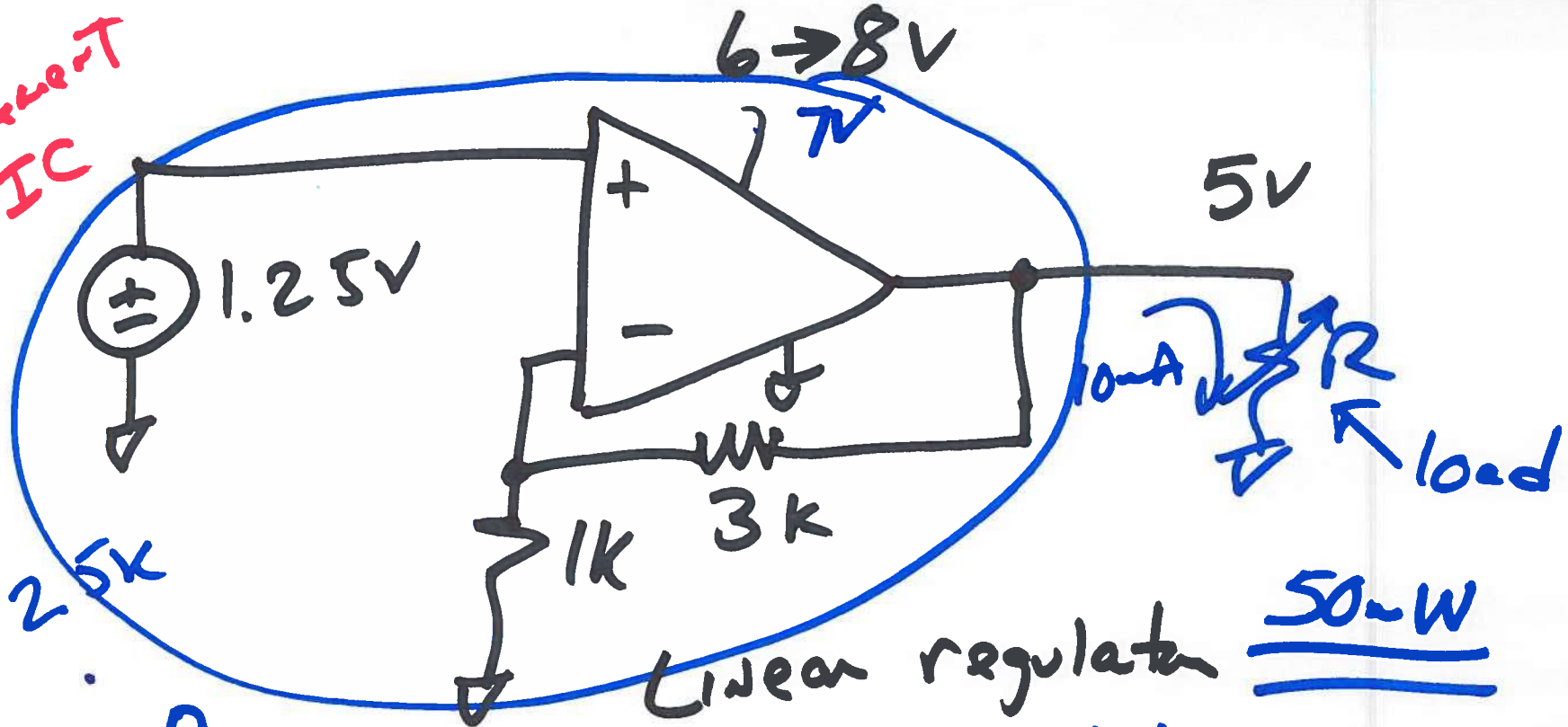

$$\frac{5}{2 \times 1k} = 2.5k$$


$$\frac{5}{50 \times 10^{-3}} = 100$$

Linear regulator (power supply) 50mW


AA
1,000 mA·hr

$$1.5 \cdot \text{hr} = 1.5 \cdot 3600$$

5400 J

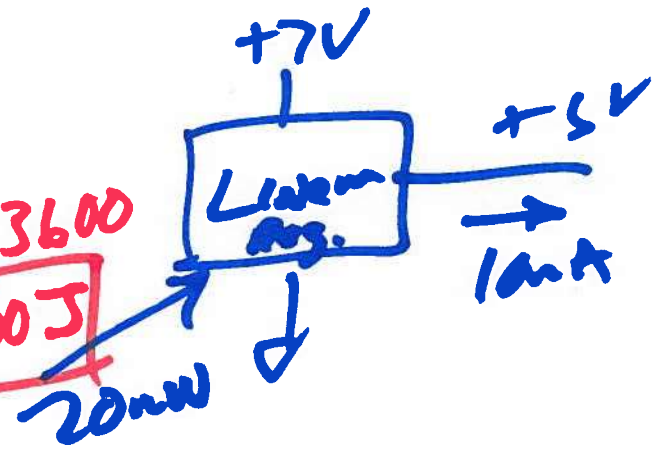

2)

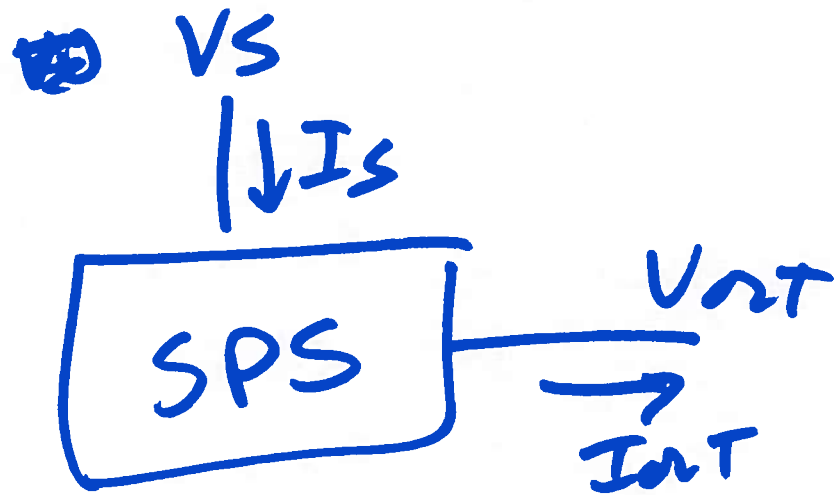

ideally



$$V_S I_S = V_{out} \cdot I_{out}$$


Reality

$$V_S \cdot I_S \cdot \eta = V_{out} I_{out}$$

$\eta > 90\%$

3)

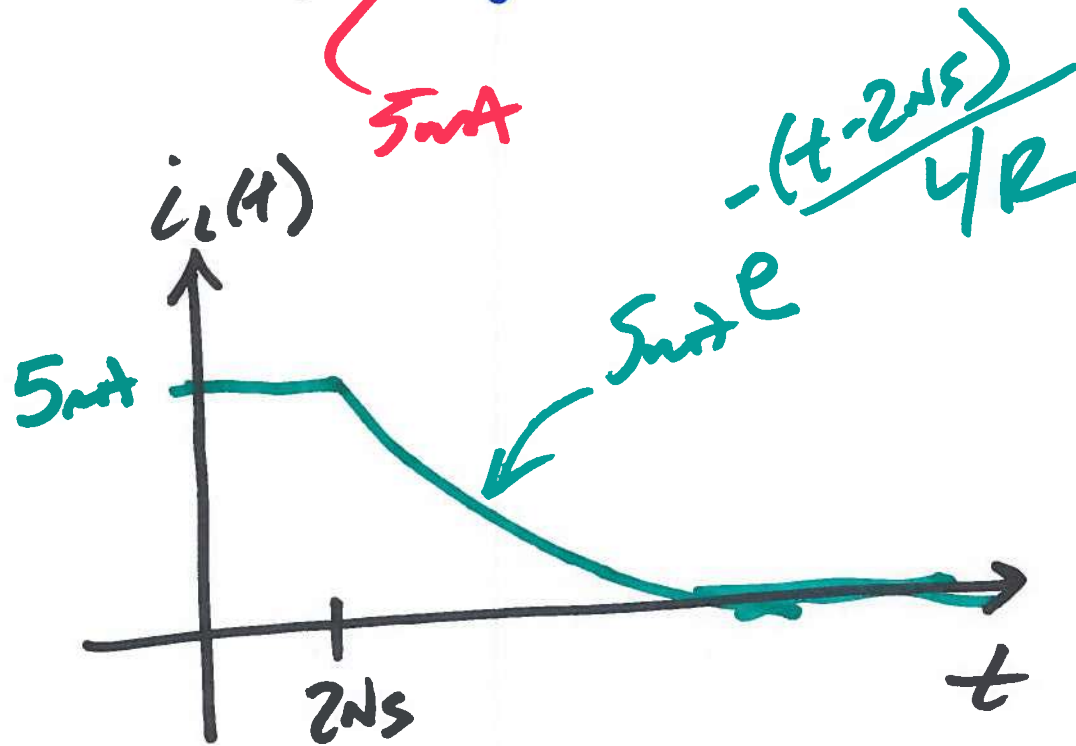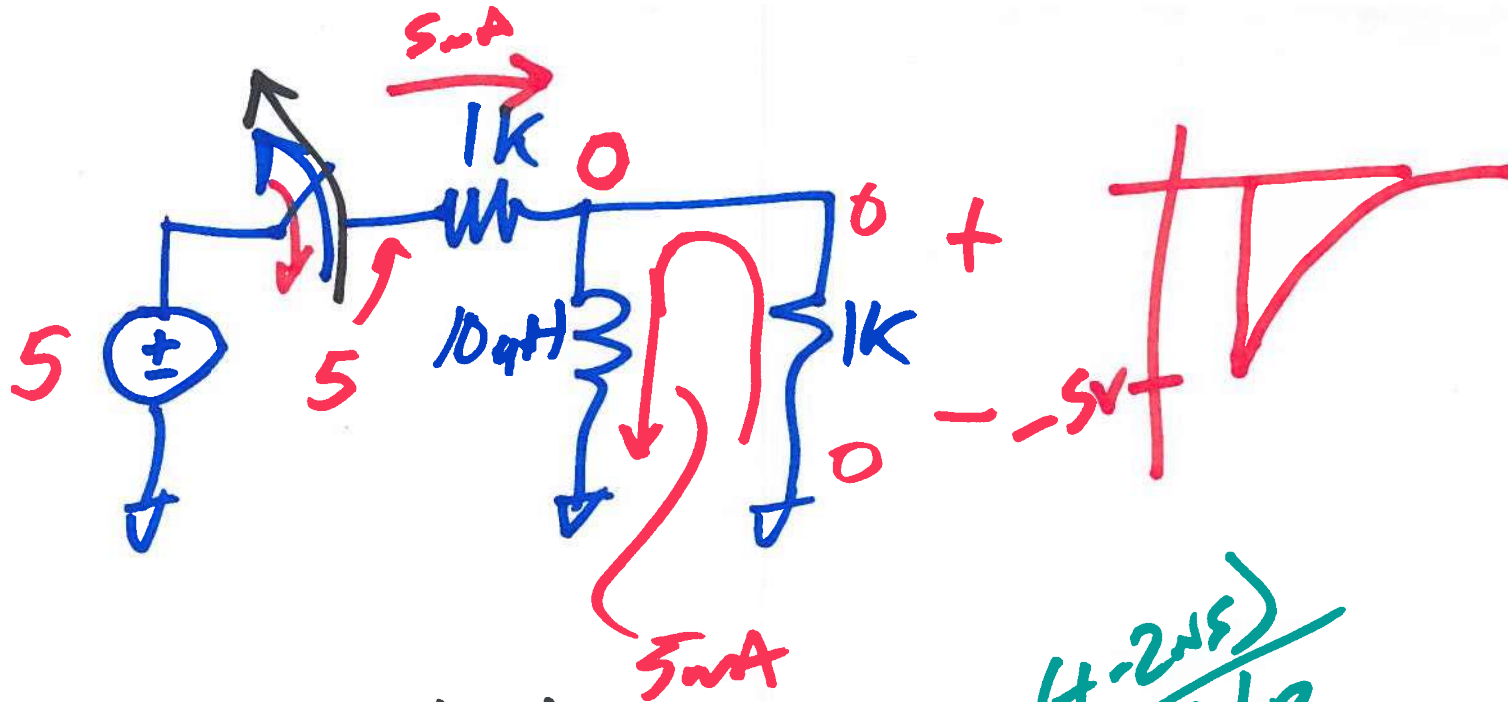

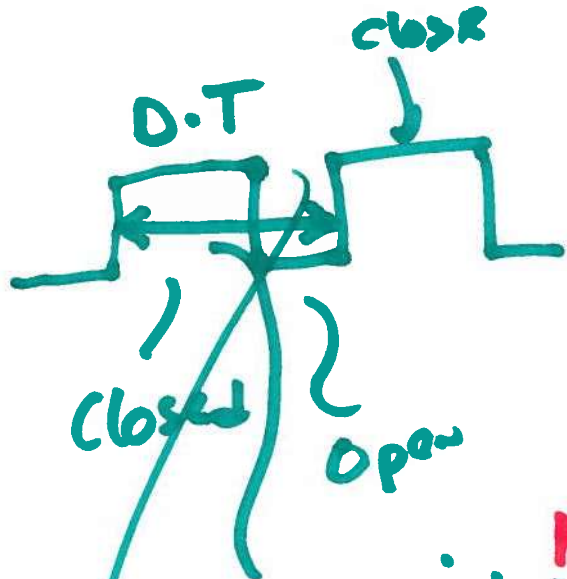


$T = \text{period}$

$$f = \frac{1}{T}$$

$(1-D)T$

$$0 < D < 1$$

duty cycle

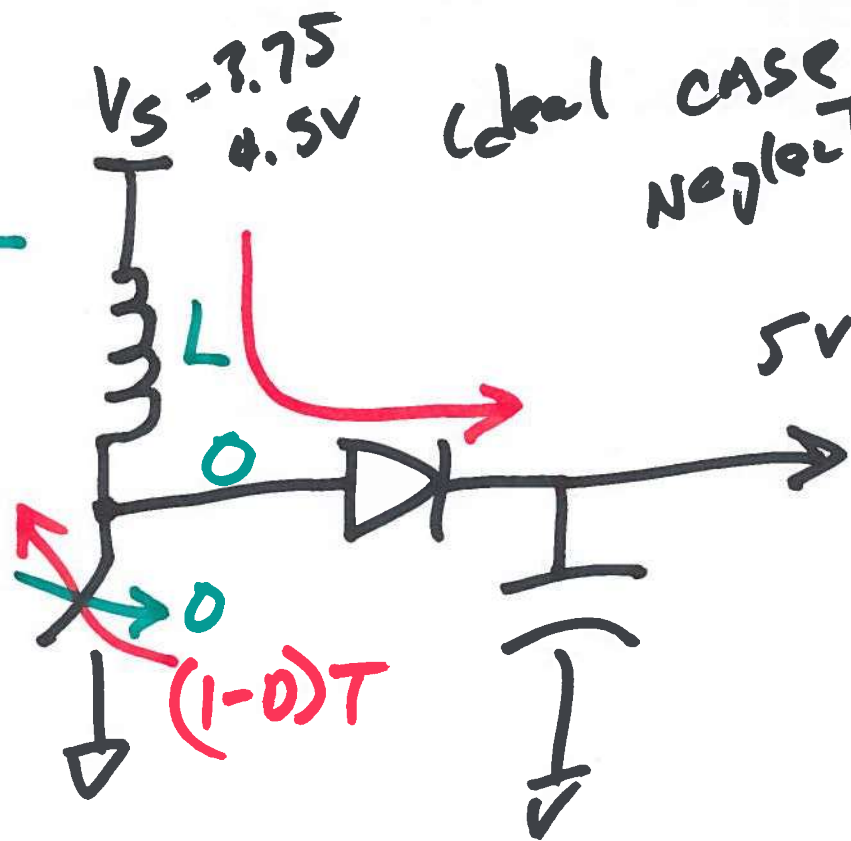

ideal case
neglect diode drop

V_{out}




Boost

$$V_{out} > V_s$$

$$L \frac{dI}{dt} = V = V_s - 0$$

$$V_s = L \cdot \frac{\Delta I}{D \cdot T}$$
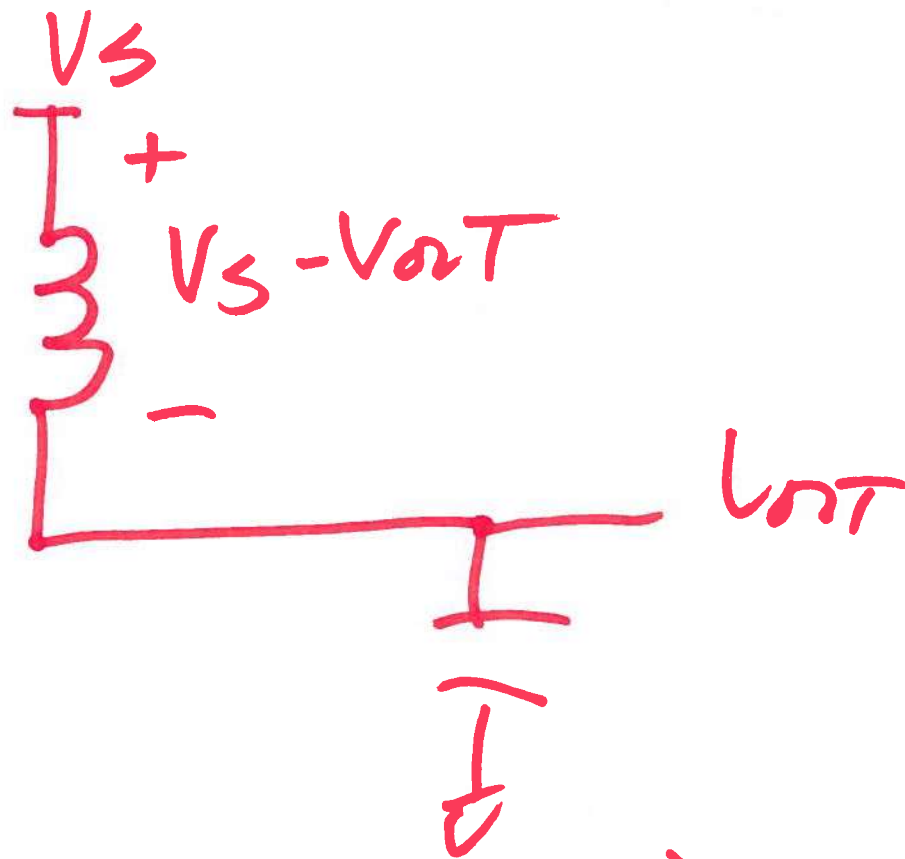
$$\Delta I = \frac{V_s}{L} \cdot D \cdot T = \frac{V_s}{L \cdot f} \cdot D$$



$$V = L \frac{di}{dt}$$


$$\frac{\Delta I}{\Delta T} \Delta T = \frac{(V_s - V_{out}) \cdot (1-D)T}{L}$$

$$0 = \frac{V_s}{L} \cdot DT + \frac{V_s - V_{out} \cdot (1-D)T}{L}$$

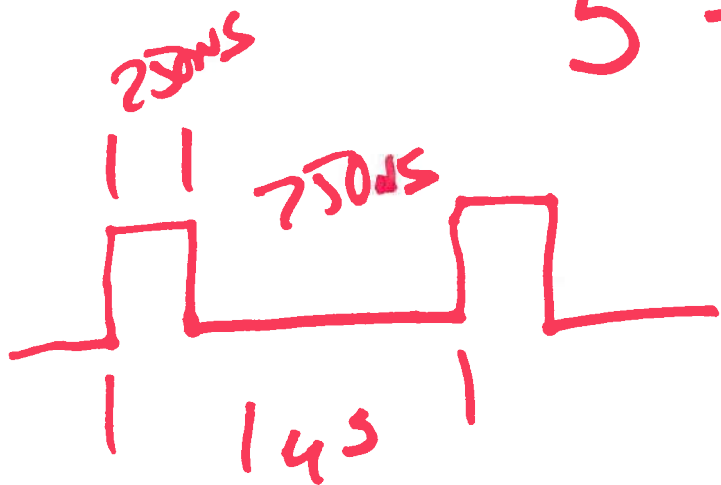6)

$$V_{out} = \frac{V_s}{1-D} \quad (\text{Boost})$$

$$5 = \frac{3.75}{1-D} = \frac{3.75}{.75} = 5$$



$$1-D = \frac{3.75}{5}$$


$$D = \frac{3.75}{5}$$


$$3.75 = 5 - 5D$$

$$1.25 = 5D$$

$$D = \frac{1.25}{5} = .25$$


b)

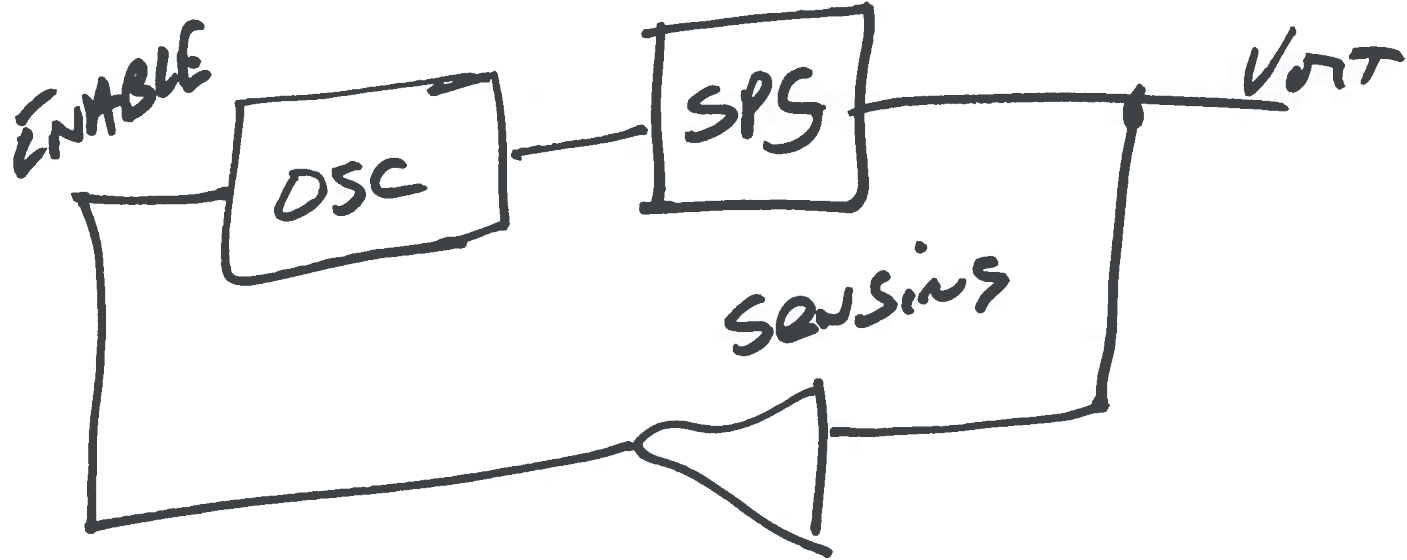

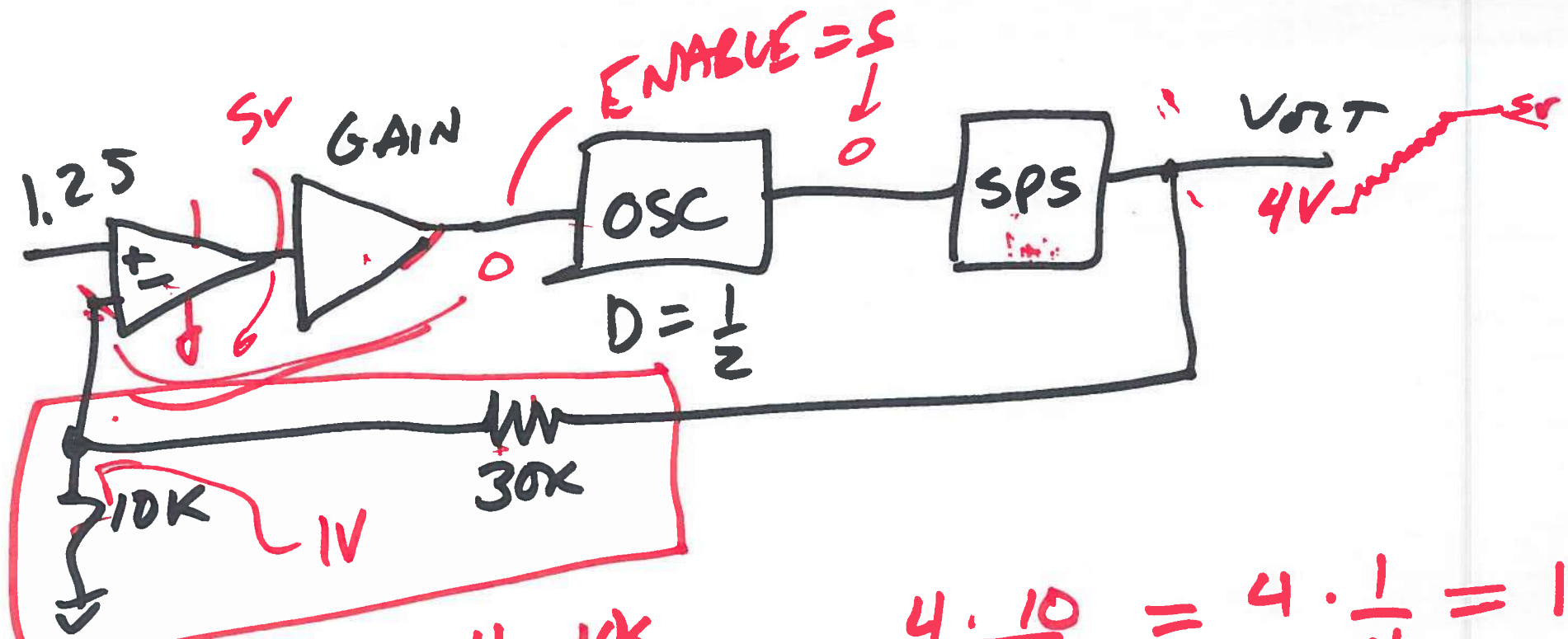

$$H = \frac{1}{4}$$
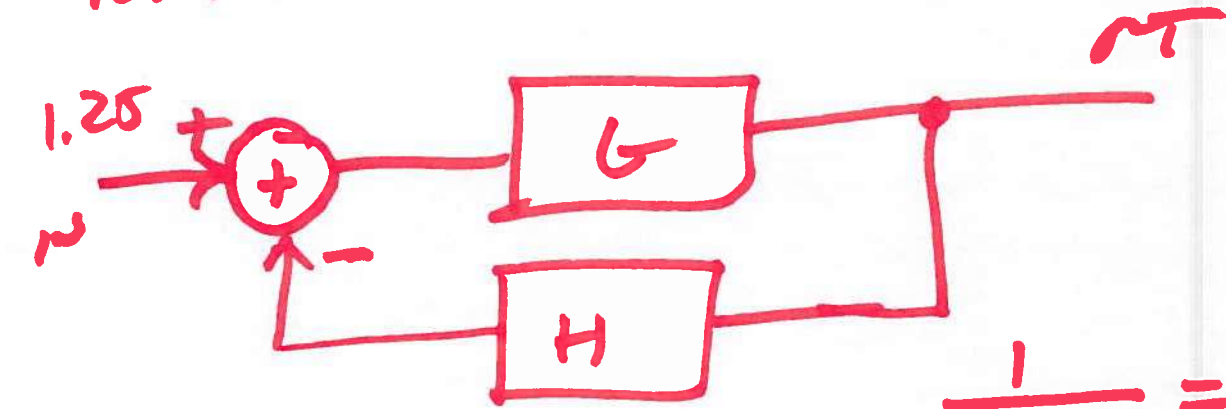
$$4 \cdot \frac{10K}{10K + 30K} = 4 \cdot \frac{10}{40} = 4 \cdot \frac{1}{4} = 1V$$



$$\frac{OUT}{IN} = \frac{G}{1 + GH} = \frac{1}{\frac{1}{4} + 4} = 4$$

8)