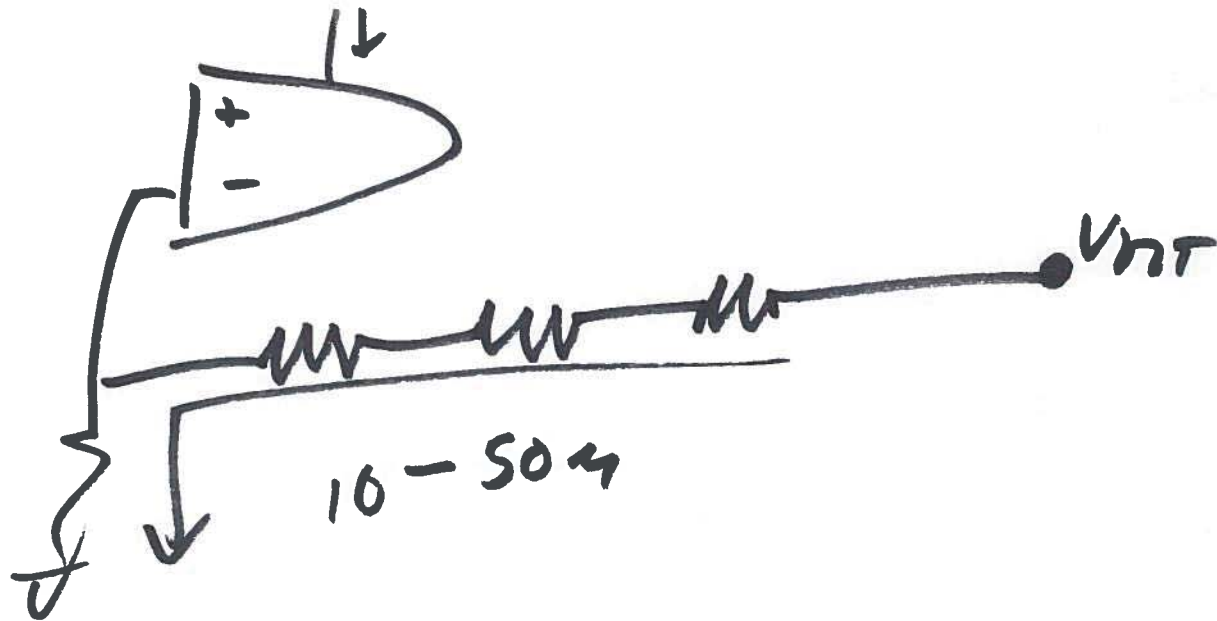



EE 421 / ECG 621

Lecture 25

11/28/2018


Digital IC Design



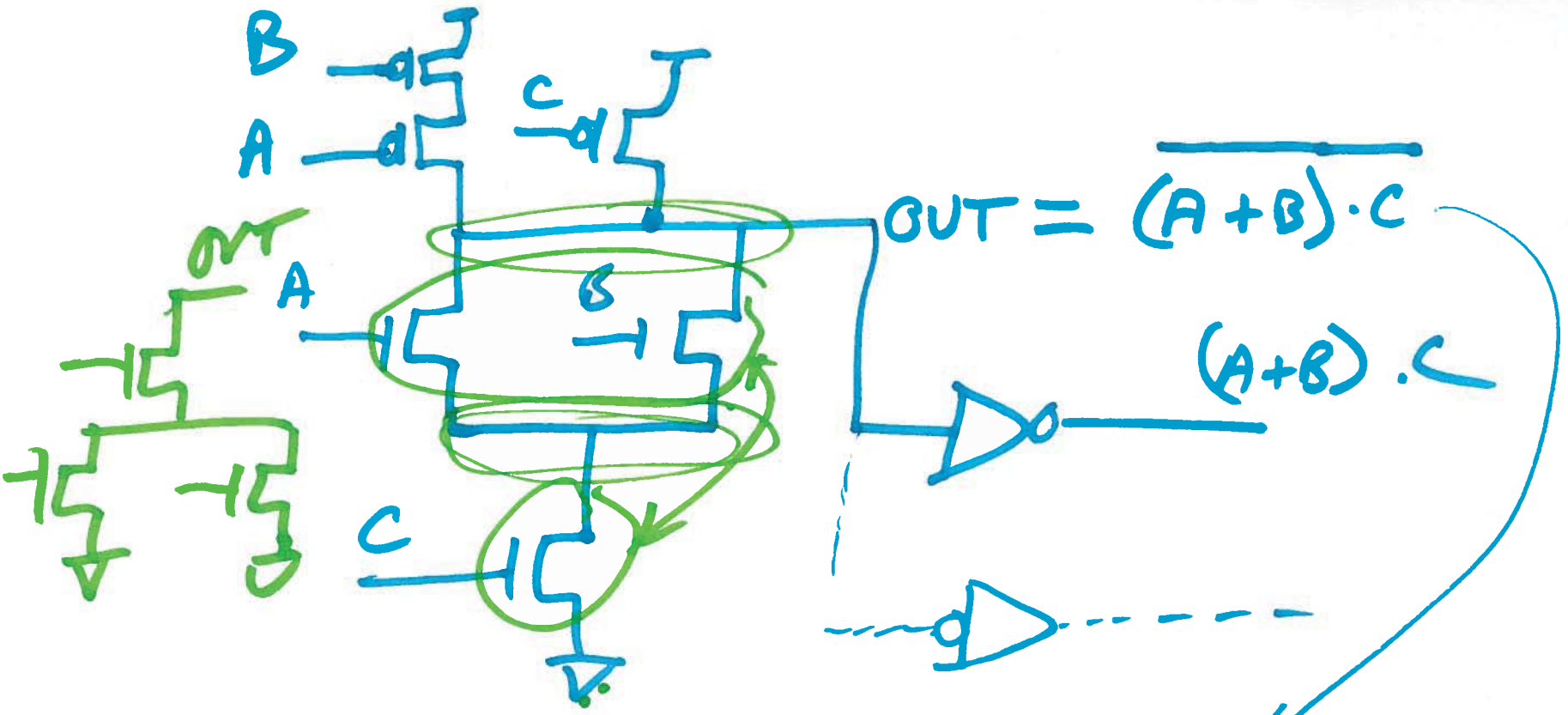


$$\bar{A} \cdot \bar{B} + \bar{C}$$

REVIEW  
XOR  
XNOR

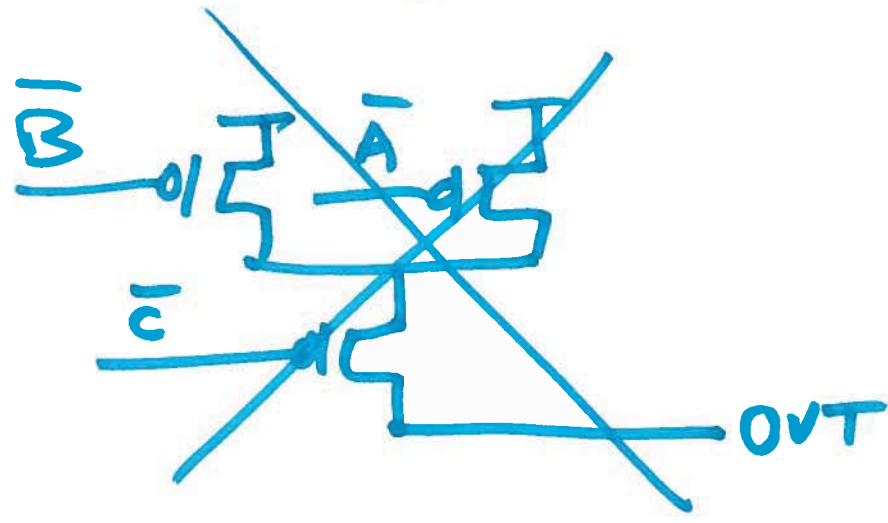

2)

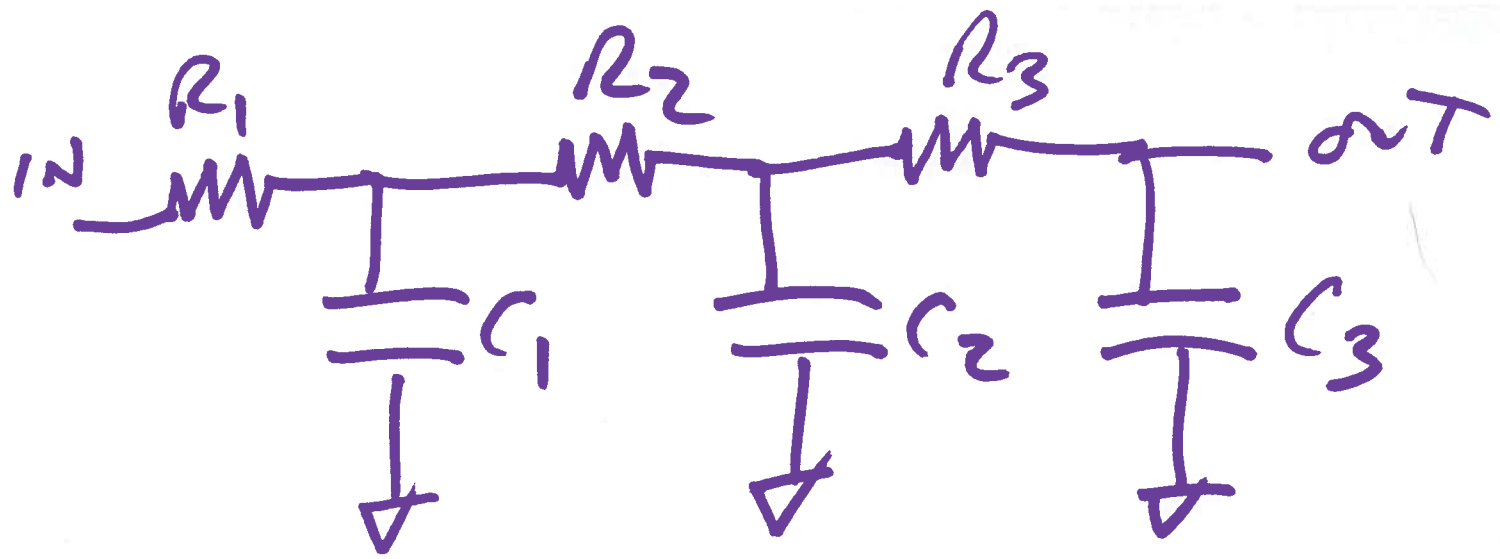

$$t_d = 0.7 \left( R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 \right)$$

3)

